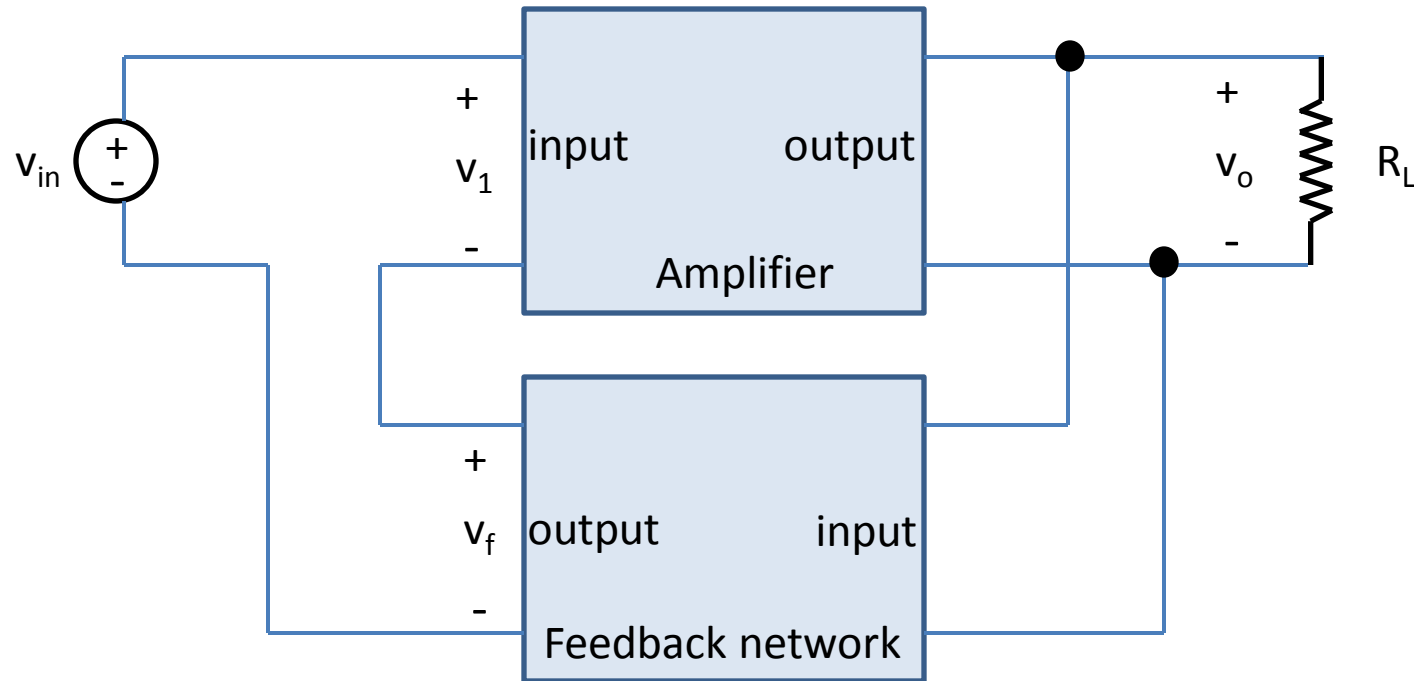


Op-Amp Circuits: Feedback

S. Lodha


References: L. Bobrow's book and Prof. M. B. Patil's slides

What is feedback?



- Output of circuit/system returned back to input
- Four possible connections
 - Above is an example of *series-parallel* feedback
 - Output of feedback in *series* with input of amp, input of feedback in *parallel* with output of amp
 - Most beneficial for voltage amplification applications

Example of series-parallel feedback

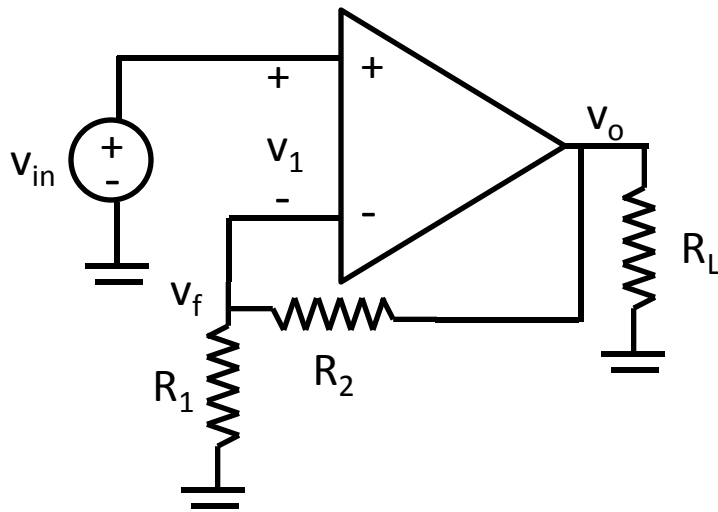


$$v_1 = v_{in} - v_f$$

$$A_F = \frac{v_o}{v_{in}} = 1 + \frac{R_2}{R_1}$$

$$B = \frac{v_f}{v_o} = \frac{R_1}{R_1 + R_2} = \frac{1}{A_F}$$


For Ideal Op-Amp

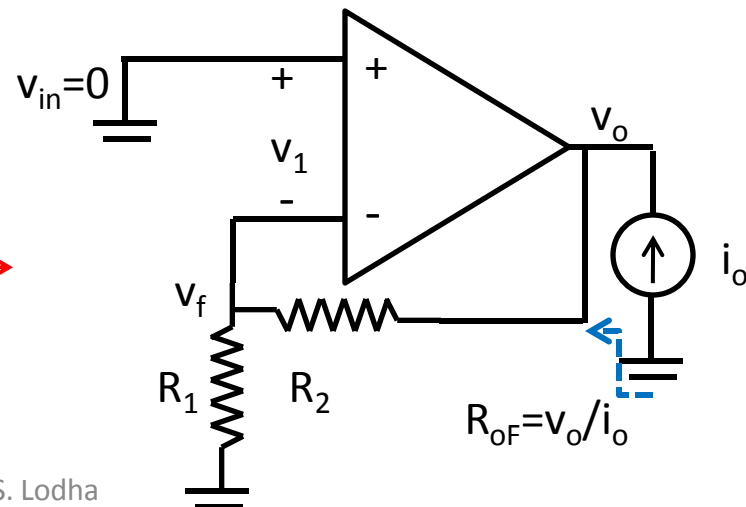- Infinite gain
- Infinite Input Resistance
- Zero Output Resistance



Feedback with non-ideal Op Amp

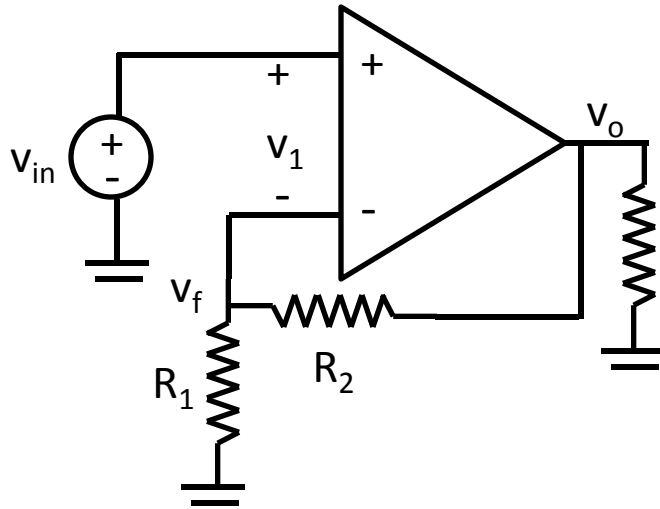Assume A is finite, but $R_{in}=\infty$ and $R_o=0$



$$v_f = Bv_o$$

$$v_o = A(v_{in} - v_f) = Av_{in} - ABv_o$$

$$A_F = \frac{v_o}{v_{in}} = \frac{A}{1 + AB}$$

$$A_F = \frac{A}{1 + AB} \approx \frac{A}{AB} = \frac{1}{B} = 1 + \frac{R_2}{R_1}$$

For large A

Trade-off gain with increase in stability!


$$A=200000, R_1=1 \text{ k}\Omega, R_2=100 \text{ k}\Omega \rightarrow A_F=100.959$$

$$\text{Suppose } A \text{ changes by 10\% to } 220,000 \rightarrow A_F=100.964$$

Only 0.005% change!

Feedback effect on input R

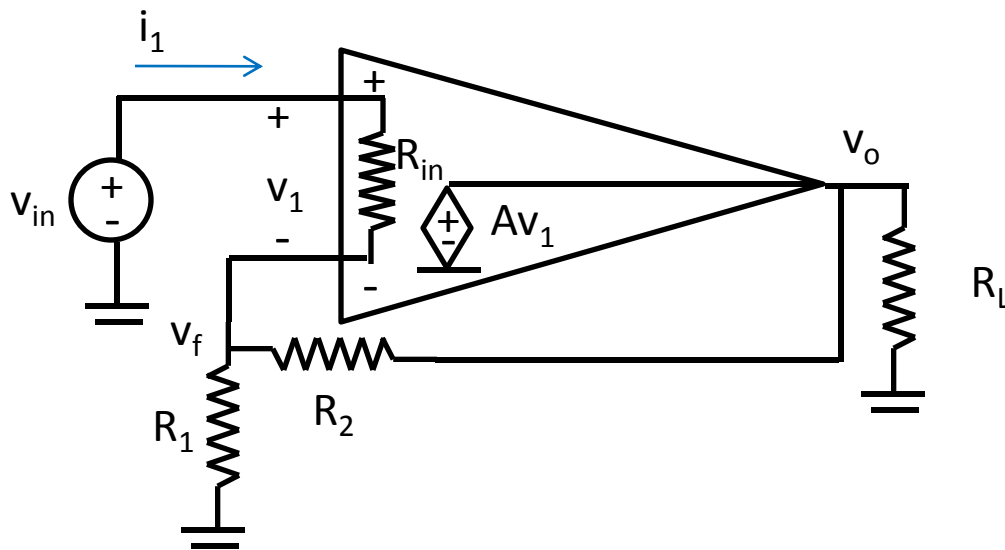Assume A and R_{in} are both finite, but $R_o = 0$



$$R_{iF} = \frac{v_{in}}{i_1} = \frac{v_{in}}{v_1} R_{in} = \frac{v_{in}}{v_o} A R_{in}$$

$$R_{in} \gg R_1$$


$$\frac{v_o}{v_{in}} = \frac{A}{1 + AB}$$

$$R_{iF} = (1 + AB) R_{in}$$

Negative feedback can be used to increase the input resistance of an amplifier.

Feedback effect on output R

Assume A , R_{in} and R_o are all finite

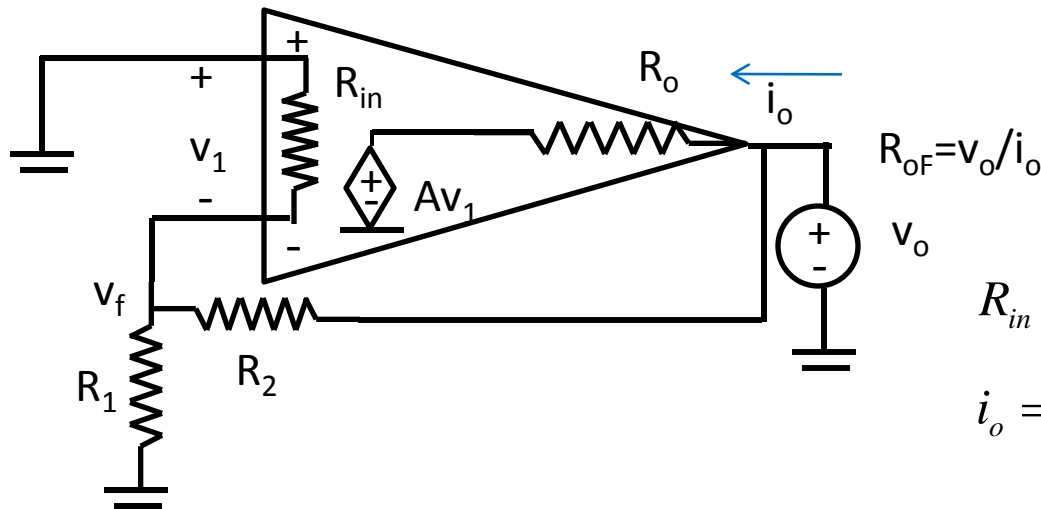

$$R_{in} \gg R_1$$

$$i_o = \frac{1+AB}{R_o} v_o + \frac{1}{R_1+R_2} v_o$$


$$\Rightarrow \frac{1}{R_{oF}} = \frac{i_o}{v_o} = \frac{1+AB}{R_o} + \frac{1}{R_1+R_2}$$

$$\Rightarrow R_{oF} = \frac{R_o}{1+AB} \parallel (R_1+R_2) \approx \frac{R_o}{1+AB}$$

Negative feedback can be used to decrease the output resistance of an amplifier.

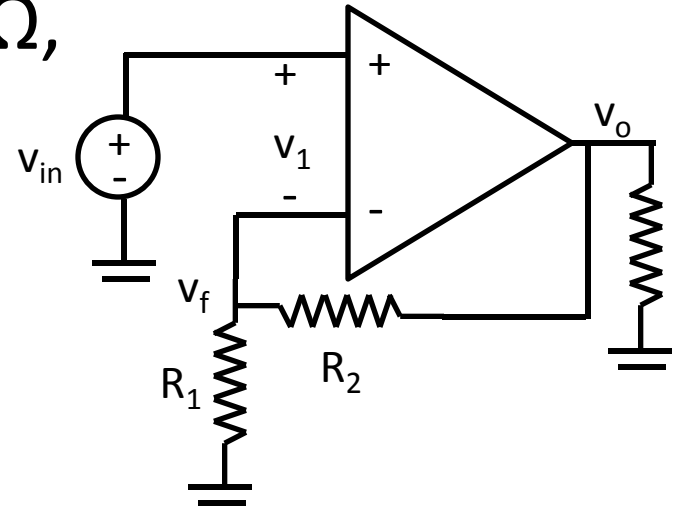Example

- $A=200000$, $R_{in}=2\text{ M}\Omega$, $R_o=75\text{ }\Omega$,
 $R_1=1\text{ k}\Omega$, $R_2=100\text{ k}\Omega$
 - $B=R_1/R_1+R_2=0.0099$
 - $R_{iF}=(1+AB)R_{in}=3960\text{ M}\Omega$
 - $R_{oF}=R_o/1+AB=0.038\text{ }\Omega$



Frequency Response

$$\mathbf{A} = \frac{A}{1 + j\omega / \omega_H}$$

A is called the “open-loop” gain (frequency dependent), A is the dc gain

$$\mathbf{A}_F = \frac{\mathbf{A}}{1 + \mathbf{A}B} = \frac{\left[\frac{A}{1 + j\omega / \omega_H} \right]}{1 + \left[\frac{A}{1 + j\omega / \omega_H} \right] B}$$

For the example, $A_F = A / (1 + AB)$

$$\mathbf{A}_F = \frac{A}{1 + AB} \frac{1}{1 + j \left[\frac{\omega}{(1 + AB)\omega_H} \right]} = \frac{A_F}{1 + j\omega / \omega_{HF}}$$

$$\omega_{HF} = (1 + AB)\omega_H \quad \text{Upper cut-off frequency}$$

- Lower cut-off frequency is 0
- Internal transistor capacitances determine upper cut-off frequency
 - Acts like a low-pass filter
- With feedback, upper-cut off frequency multiplied by $(1 + AB)$
 - Large increase in bandwidth


Gain-Bandwidth Product

$$f_T = Af_H \quad \text{Product of dc gain with upper cut-off frequency in Hz}$$

$$f_{HF} = A_F f_{HF} = \frac{A}{1+AB} (1+AB) f_H = Af_H = f_T$$

- Addition of feedback does not change the gain-bandwidth product
 - Feedback amplifier and op-amp have the same product
 - What you lose in gain is made up in bandwidth

Feedback: Inverting Amplifier

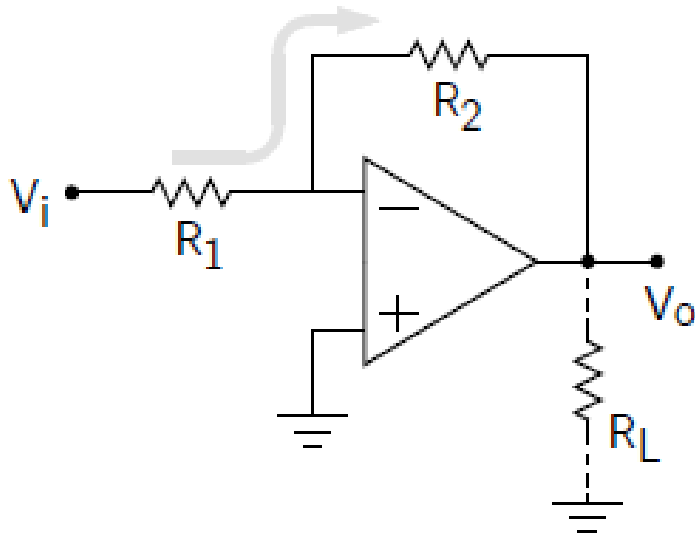


$$V_o = A_V (V_+ - V_-) \quad \text{Eq. 1}$$

$$V_- = V_i \frac{R_2}{R_1 + R_2} + V_o \frac{R_1}{R_1 + R_2} \quad \text{Eq. 2}$$

$$V_i \uparrow \rightarrow \boxed{V_- \uparrow} \rightarrow V_o \downarrow \rightarrow \boxed{V_- \downarrow}$$

Eq. 2 Eq. 1 Eq. 2

Stable equilibrium is reached

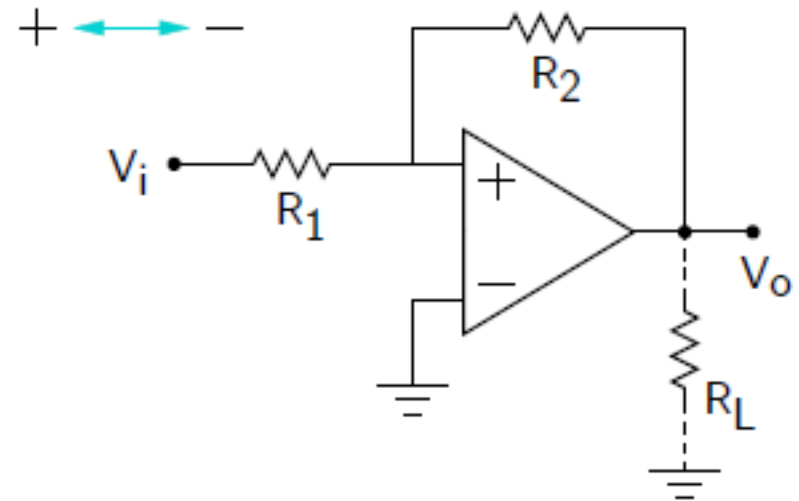


$$V_+ = V_i \frac{R_2}{R_1 + R_2} + V_o \frac{R_1}{R_1 + R_2} \quad \text{Eq. 3}$$

$$V_i \uparrow \rightarrow \boxed{V_+ \uparrow} \rightarrow V_o \uparrow \rightarrow \boxed{V_+ \uparrow}$$


Eq. 3 Eq. 1 Eq. 3

V_o rises (or falls) indefinitely till saturation \rightarrow positive feedback

Feedback: Non-Inverting Amplifier

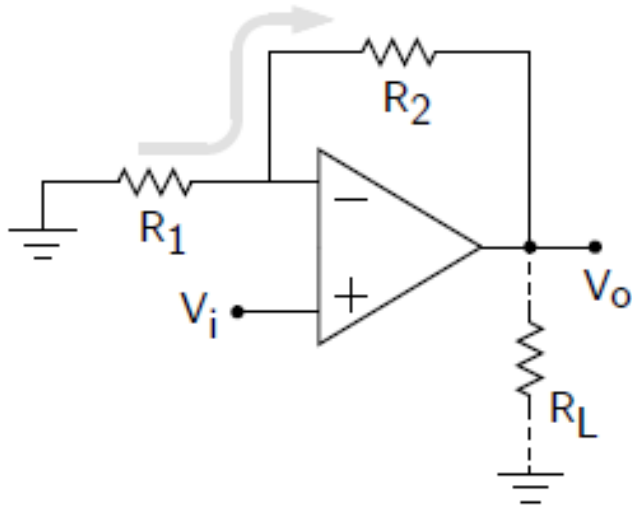

+ ↔ -

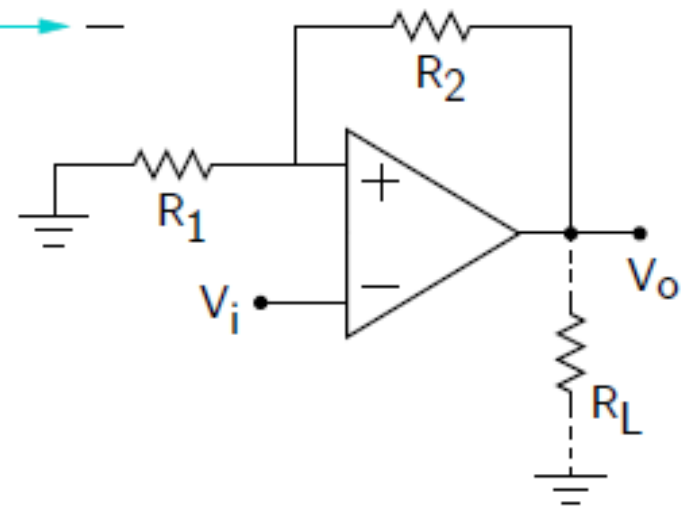

$$V_o = A_v (V_+ - V_-) \quad \text{Eq. 1}$$

$$V_- = V_o \frac{R_1}{R_1 + R_2} \quad \text{Eq. 2}$$

$$V_i \uparrow \rightarrow \boxed{V_o \uparrow} \rightarrow V_- \uparrow \rightarrow \boxed{V_o \downarrow}$$

Eq. 1 Eq. 2 Eq. 1

Stable equilibrium is reached


$$V_+ = V_o \frac{R_1}{R_1 + R_2} \quad \text{Eq. 3}$$

$$V_i \uparrow \rightarrow \boxed{V_o \downarrow} \rightarrow V_+ \downarrow \rightarrow \boxed{V_o \downarrow}$$

Eq. 1 Eq. 3 Eq. 1



V_o rises (or falls) indefinitely till saturation → positive feedback

Feedback

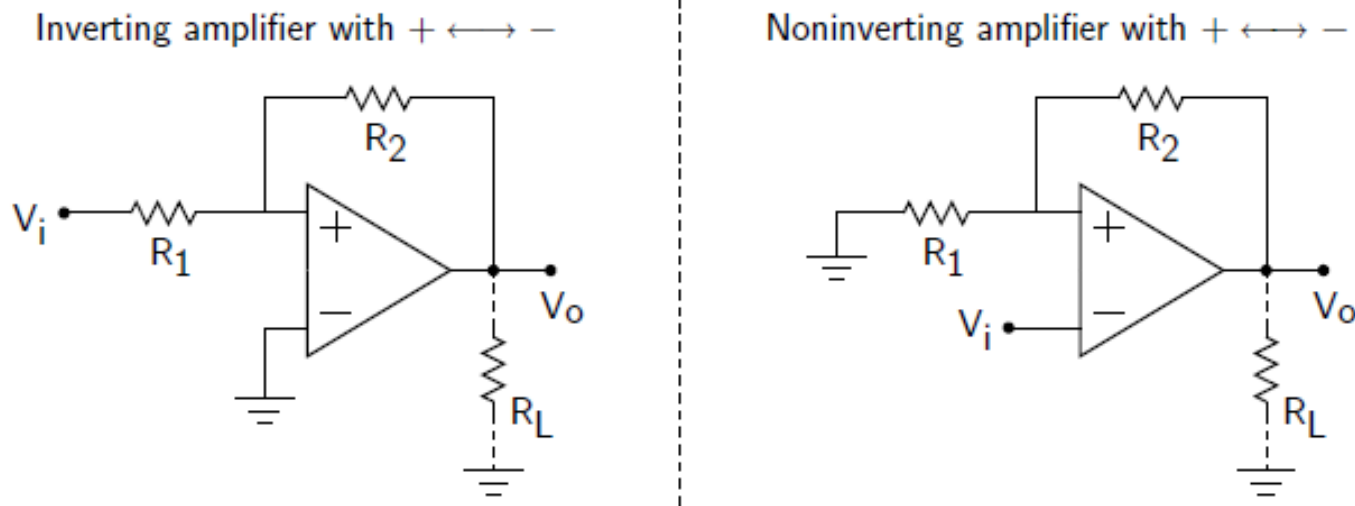

- Both circuits exhibit positive feedback
- Output is limited by saturation, i.e. $V_o = \pm V_{\text{sat}}$

Inverting Schmitt Trigger

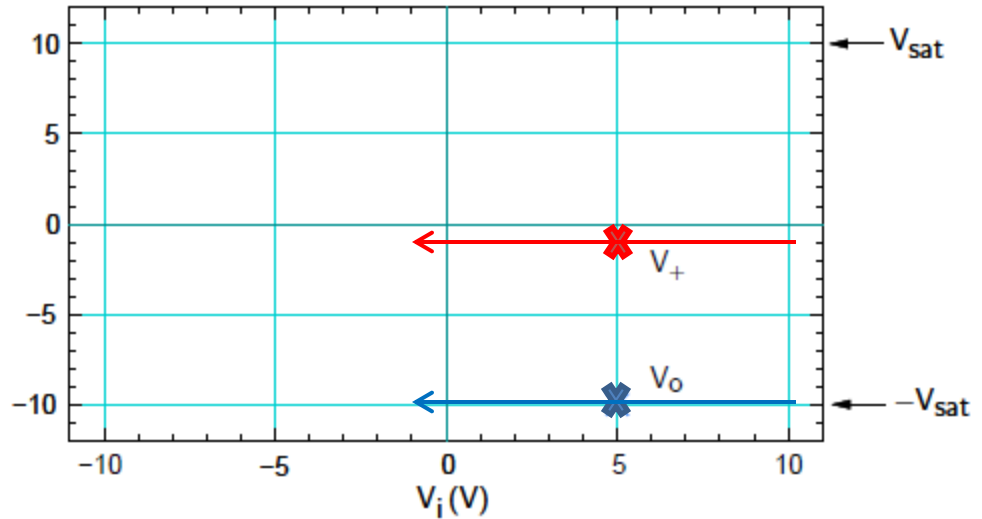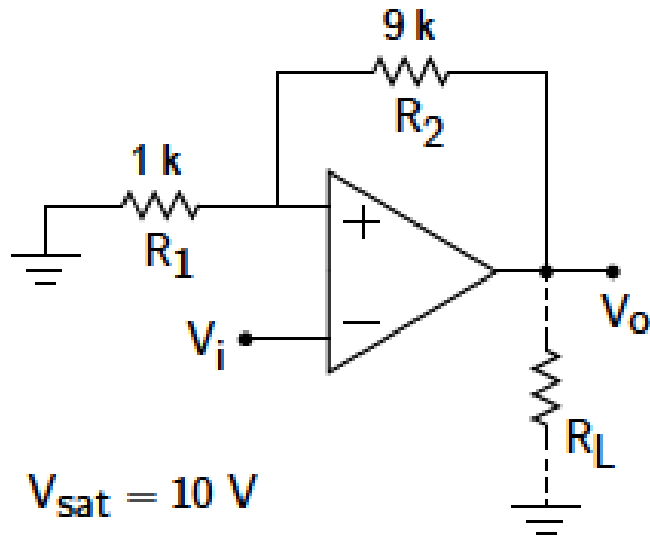

V_o is either $+10\text{V}$ ($V_+ > V_-$) or -10V ($V_+ < V_-$) because of positive feedback



Case 1

$V_i = 5\text{V}$, Assume $V_o = 10\text{V}$, $V_+ = 1\text{V} \rightarrow V_+ - V_- = 1 - 5 = -4\text{ V} \rightarrow V_o = -10\text{V}$ Inconsistent!

Case 2

$V_i = 5\text{V}$, Assume $V_o = -10\text{V}$, $V_+ = -1\text{V} \rightarrow V_+ - V_- = -1 - 5 = -6\text{ V} \rightarrow V_o = -10\text{V}$ consistent!

Inverting Schmitt Trigger

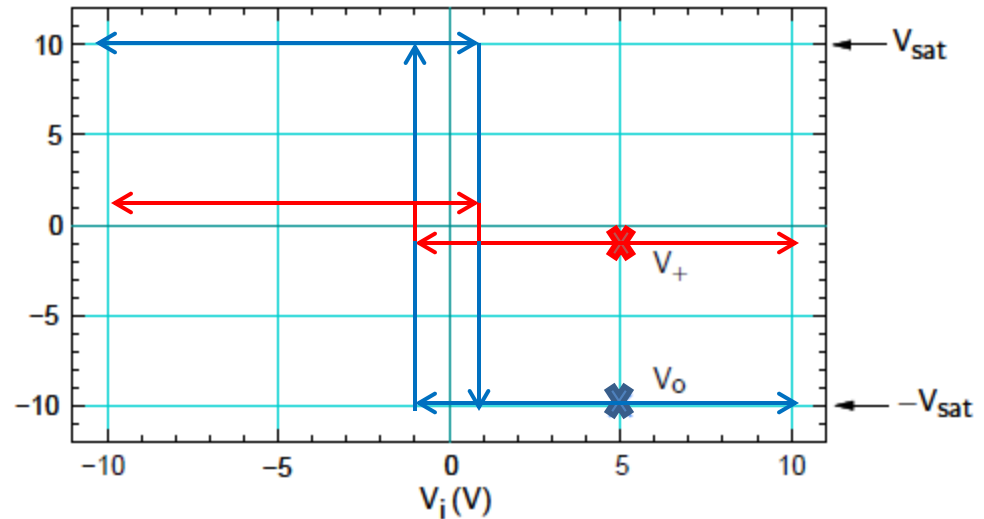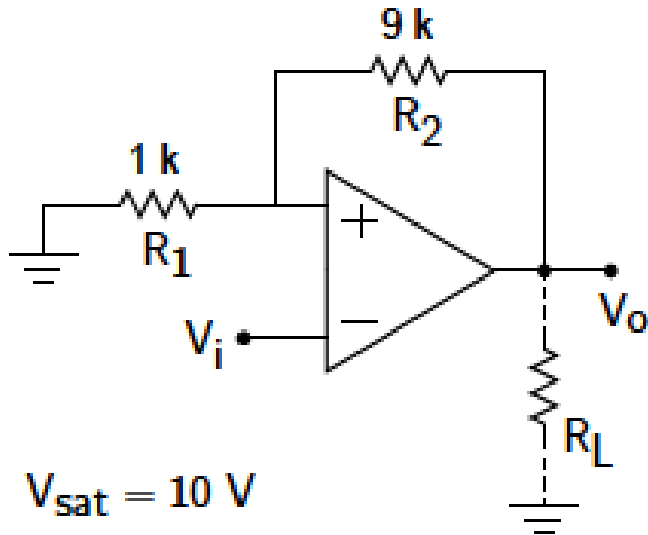



For decreasing values of V_i , $V_o = -10\text{V}$ and $V_+ = -1\text{V}$ till V_i goes below -1V

When $V_i = V_- < V_+ = -1\text{V}$ $V_o = +V_{sat} = 10\text{V}$ V_+ becomes $+1\text{V}$

Decreasing V_i further does not change V_o , since $V_+ - V_- = 1 - V_i > 0$



Coming back (increasing V_i) threshold voltage for flipping is $+1\text{V}$.

Inverting Schmitt trigger

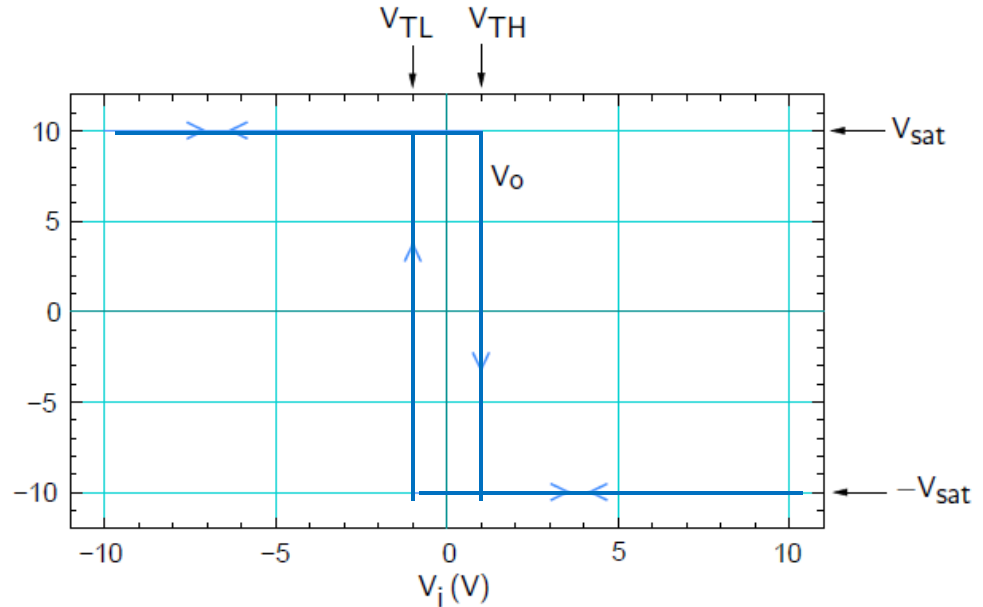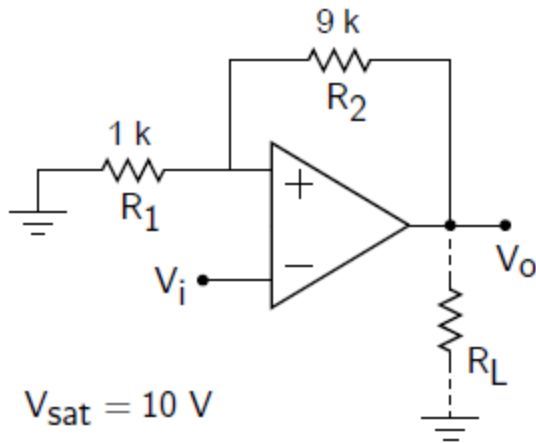

- The threshold (tripping) voltages V_{TL} and V_{TH} are $\pm \left(\frac{R_1}{R_1 + R_2} \right) V_{\text{sat}}$
- Tripping point depends on position on V_o axis \rightarrow MEMORY!
- $\Delta V_T = V_{\text{TH}} - V_{\text{TL}}$ is called hysteresis width

Non-inverting Schmitt Trigger

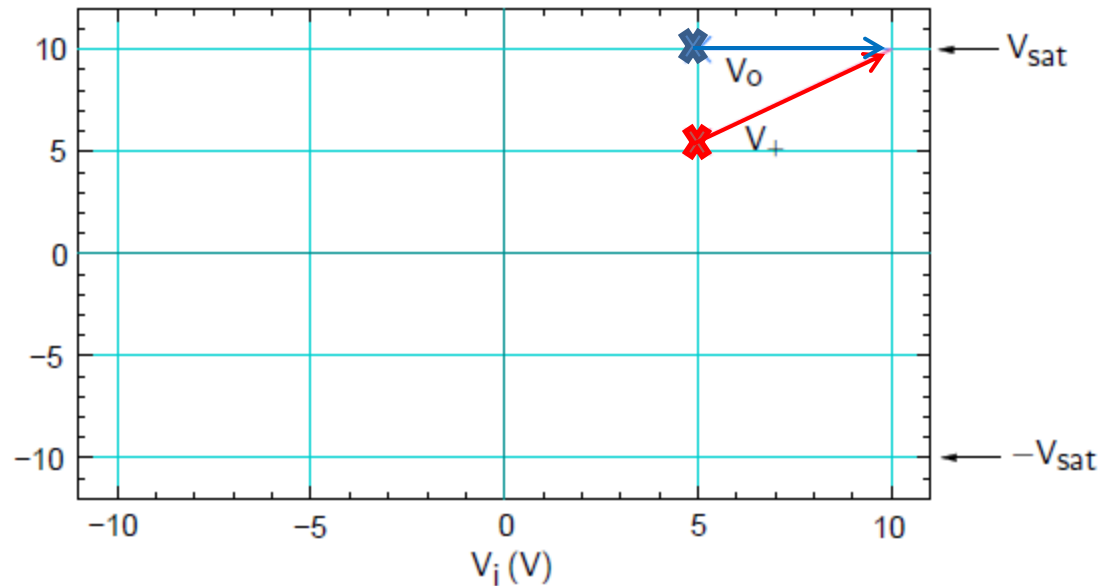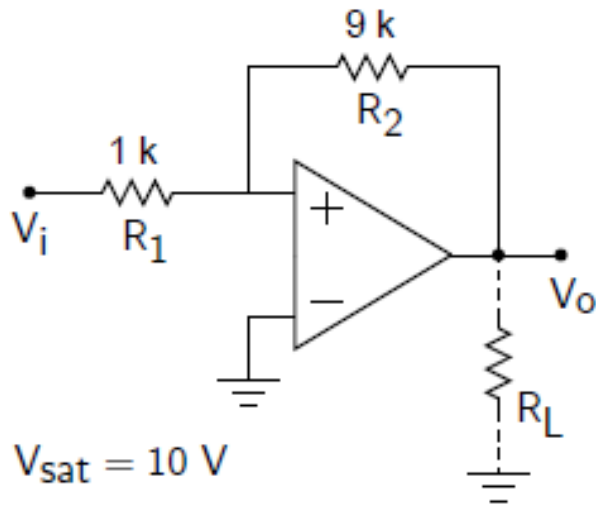

V_o is either $+10V$ ($V_+ > V_-$) or $-10V$ ($V_+ < V_-$) because of positive feedback



Case 1

$V_i = 5V$, Assume $V_o = -10V$, $V_+ = (R_2/R_1 + R_2)V_i + V_o(R_1/R_1 + R_2) = 3.5V \rightarrow V_+ - V_- = 3.5 - 0 = 3.5V \rightarrow V_o = -10V$ Inconsistent!

Case 2

$V_i = 5V$, Assume $V_o = +10V$, $V_+ = 5.5V \rightarrow V_+ - V_- = 5.5 - 0 = 5.5V \rightarrow V_o = +10V$ consistent!

Non-inverting Schmitt Trigger

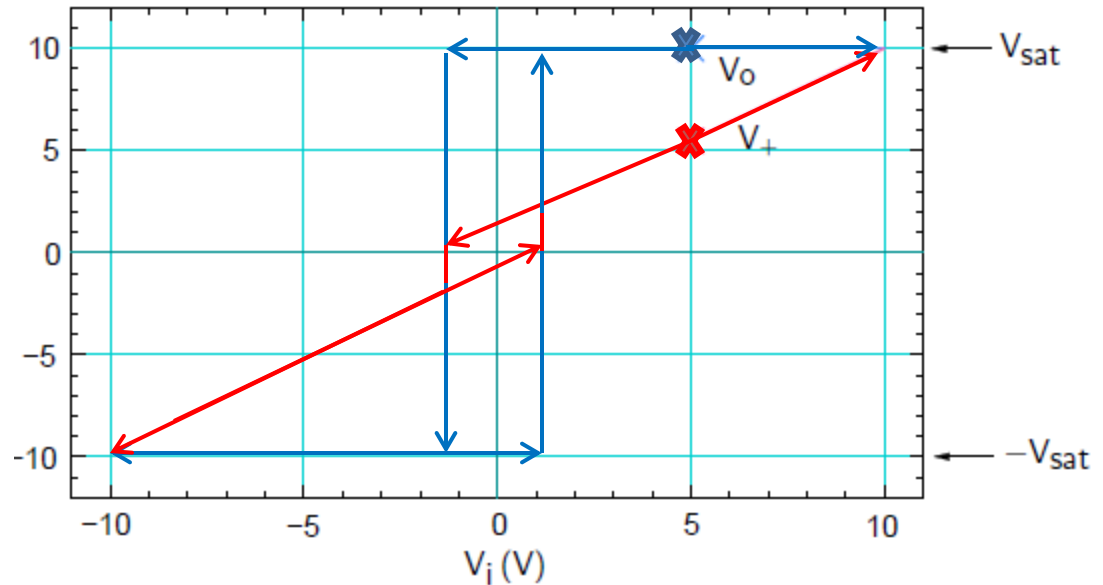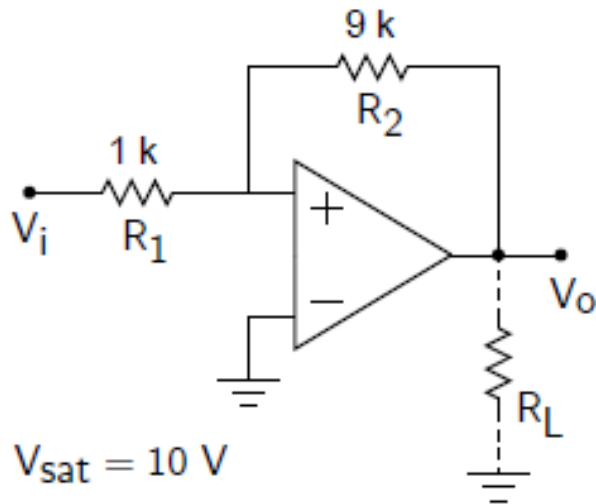

$$V_+ = \frac{R_2}{R_1 + R_2} V_i + \frac{R_1}{R_1 + R_2} V_o = \frac{9}{10} V_i + \frac{1}{10} V_{sat}$$

As V_i decreases and till $V_+ > 0$ $V_o = V_{sat}$



For $V_+ = 0V$, $V_i = -(R_1/R_2)V_{sat} = -1.11 V$, $V_o = -V_{sat}$

$$V_+ = \frac{R_2}{R_1 + R_2} V_i + \frac{R_1}{R_1 + R_2} V_o = \frac{9}{10} V_i - \frac{1}{10} V_{sat}$$

Further reduction of V_i does not change $V_o = -V_{sat}$, since $V_+ < 0$




V_o again flips to $+V_{sat}$ when $V_+ = 0V$, when $V_i = 1.11V$

Non-inverting Schmitt Trigger


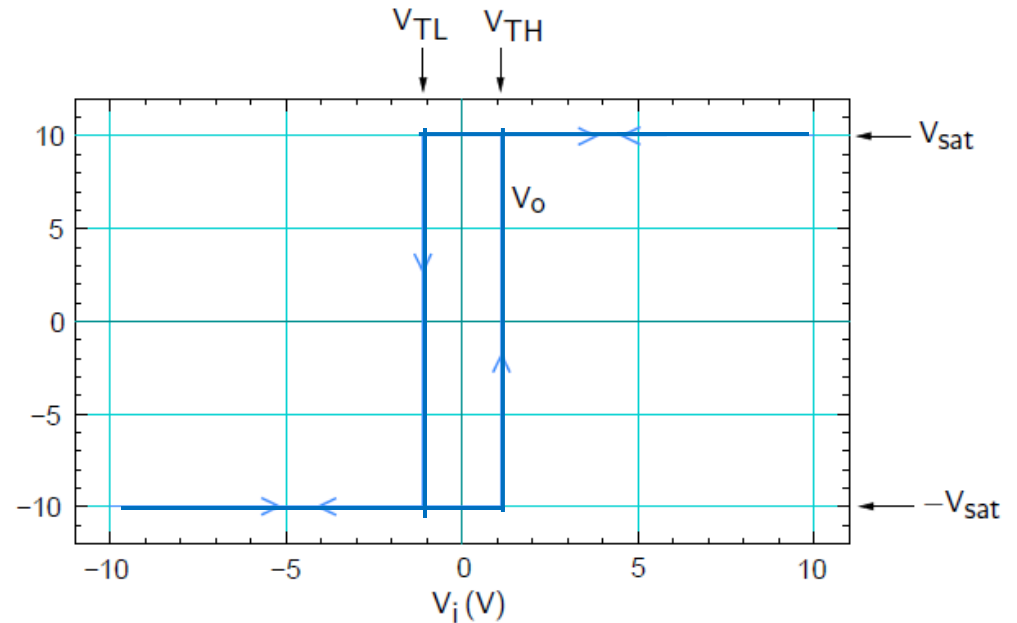
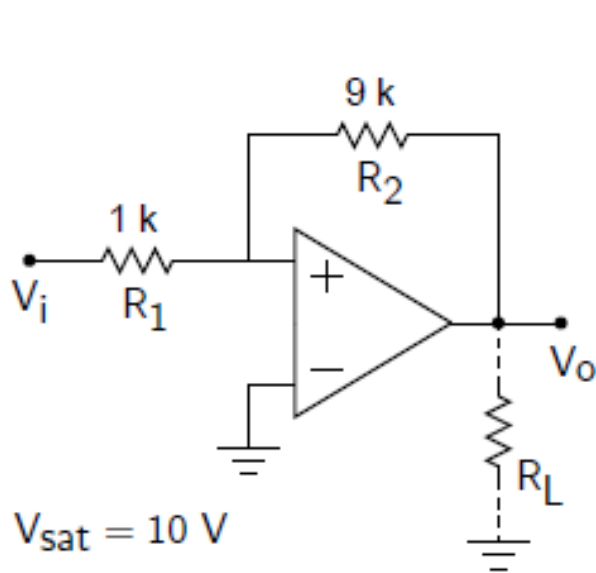


- The threshold (tripping) voltages V_{TL} and V_{TH} are $\pm \left(\frac{R_1}{R_2} \right) V_{sat}$
- Tripping point depends on position on V_o axis \rightarrow MEMORY!
- $\Delta V_T = V_{TH} - V_{TL}$ is called hysteresis width

Schmitt Triggers

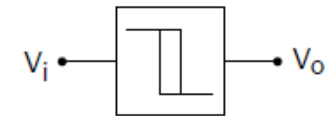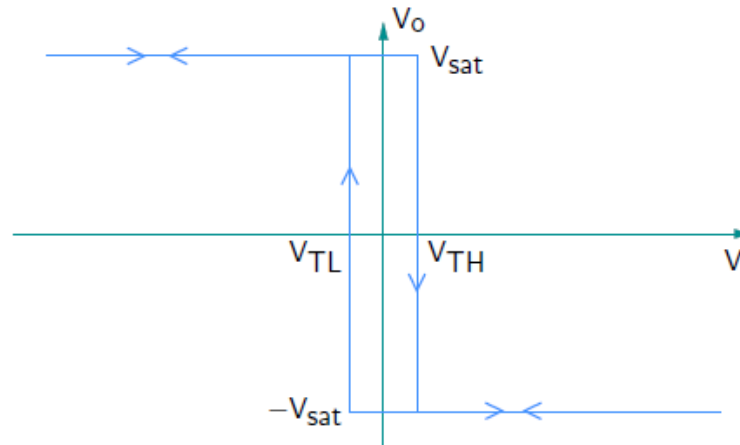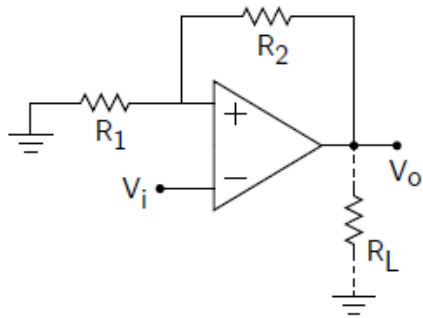


Inverting

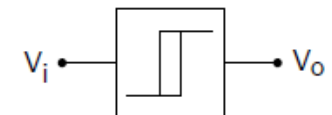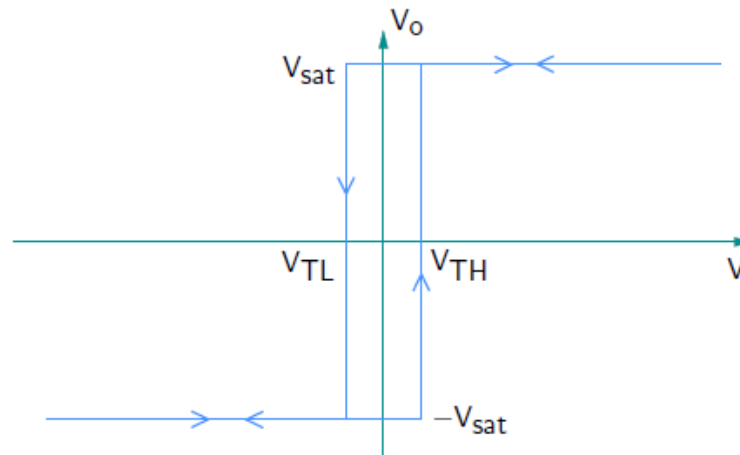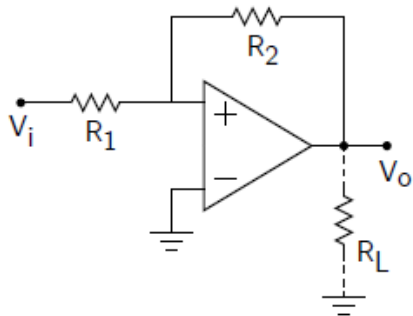



Noninverting

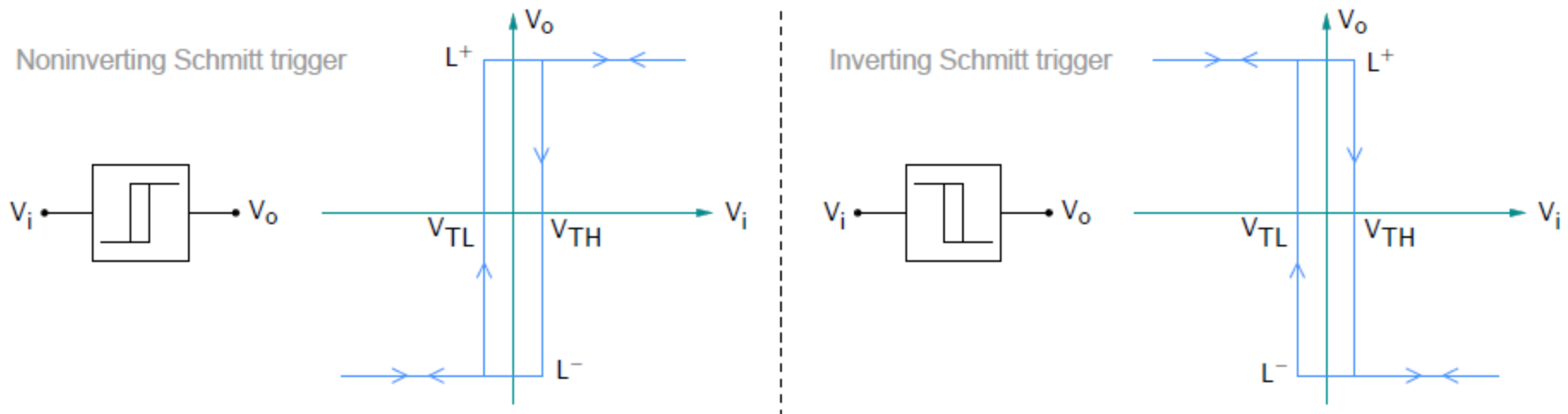Schmitt Trigger: Application → Astable multivibrator



- With a suitable RC circuit, Schmitt trigger can be made to freely oscillate between L^+ and L^-
 - Called an “astable multivibrator” (oscillator, wave-form generator)
- Produces oscillations where the frequency is controlled by component values ($f_{\max} \sim 10$ kHz)
- Other vibrator circuits
 - Monoshot (Timer)
 - Bistable (Flip-flop)

Astable MV

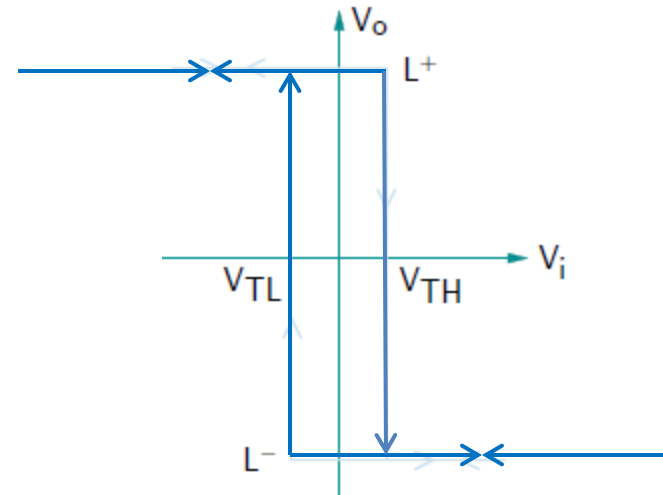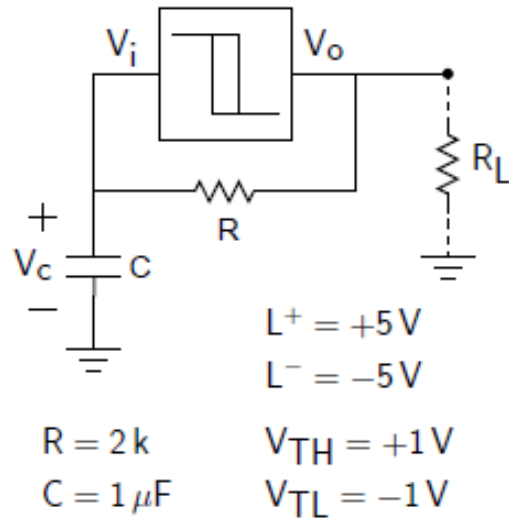


At $t=0$, $V_o=L^+$ and $V_c=0$

Capacitor starts charging towards L^+
 As $V_c (=V_i)$ crosses V_{TH} , V_o flips to L^-


Capacitor starts discharging towards L^-
 As $V_c (=V_i)$ crosses V_{TL} , V_o flips to L^+

Circuit oscillates on its own.

Also called a “relaxation oscillator”.

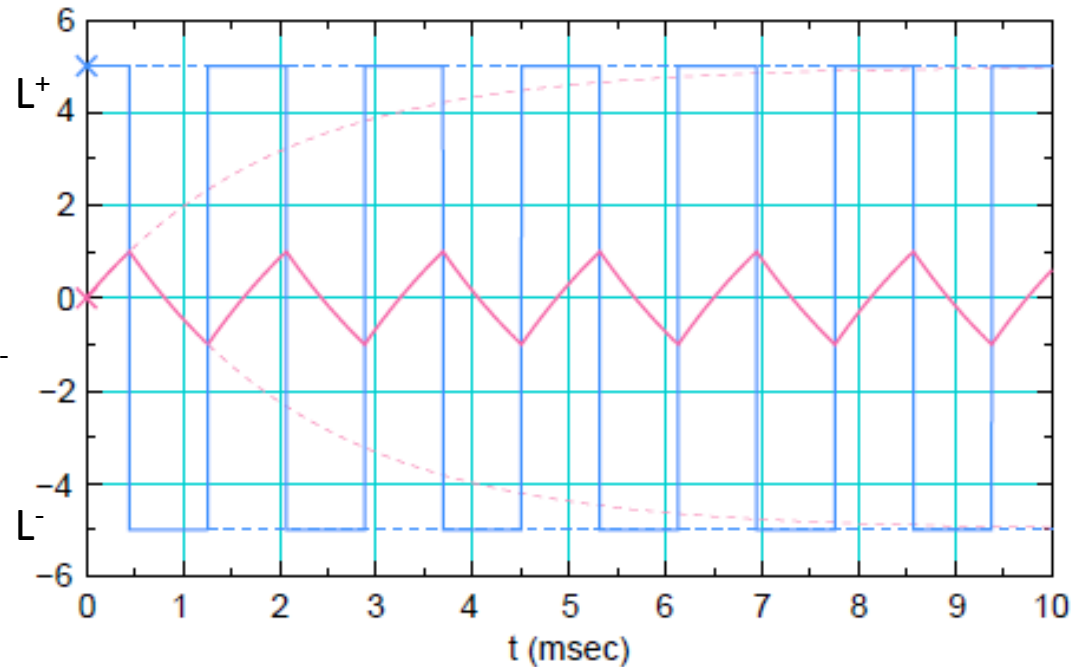

What is T ($=1/f$)?

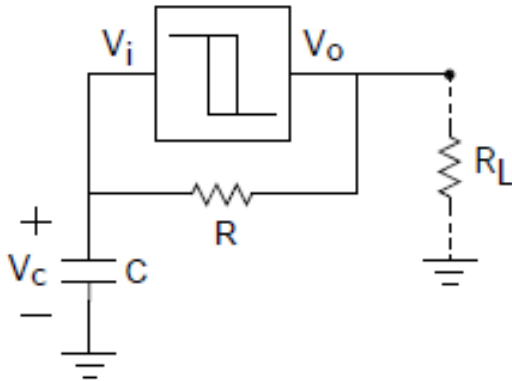


$$V_c(t) = A_1 e^{-t/\tau} + B_1$$

$$V_c(0) = V_{TL}, V_c(\infty) = L^+$$

Find A_1 and B_1

$$V_{TH} = A_1 e^{-t_1/\tau} + B_1$$

Find t_1

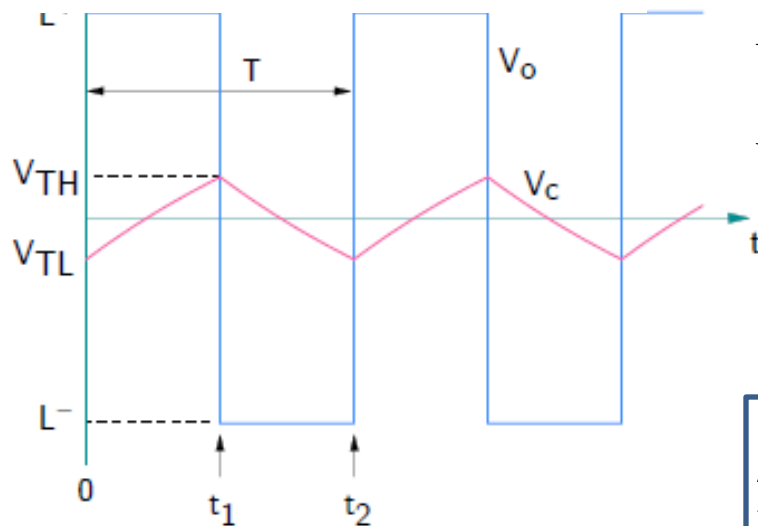

$$V_c(t) = A_2 e^{-(t-t_1)/\tau} + B_2$$

$$V_c(t_1) = V_{TH}, V_c(\infty) = L^+$$

Find A_2 and B_2



$$V_{TL} = A_2 e^{-(t_2-t_1)/\tau} + B_2$$

Find t_2

$$L^+ = L, L^- = -L, V_{TH} = V_T, V_{TL} = -V_T$$

$$T = 2RC \ln \left(\frac{L + V_T}{L - V_T} \right)$$

Astable MV

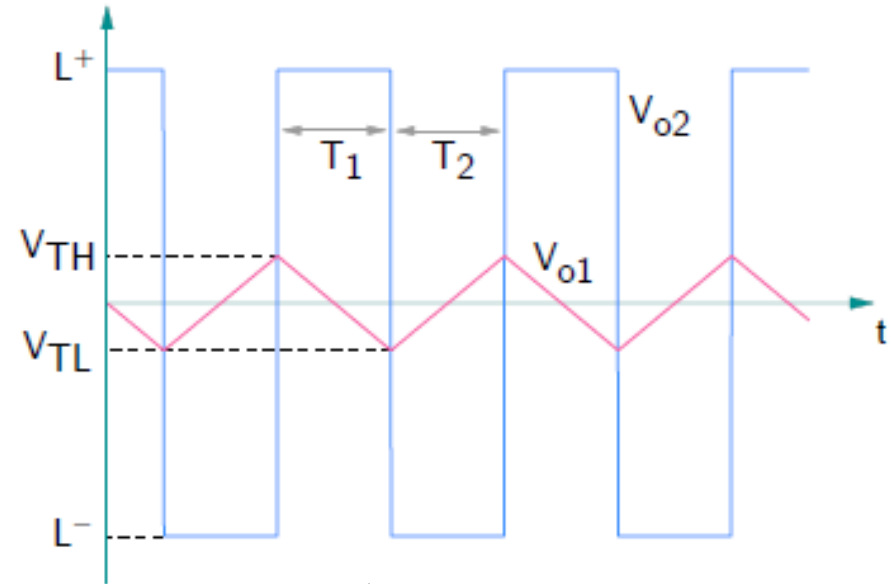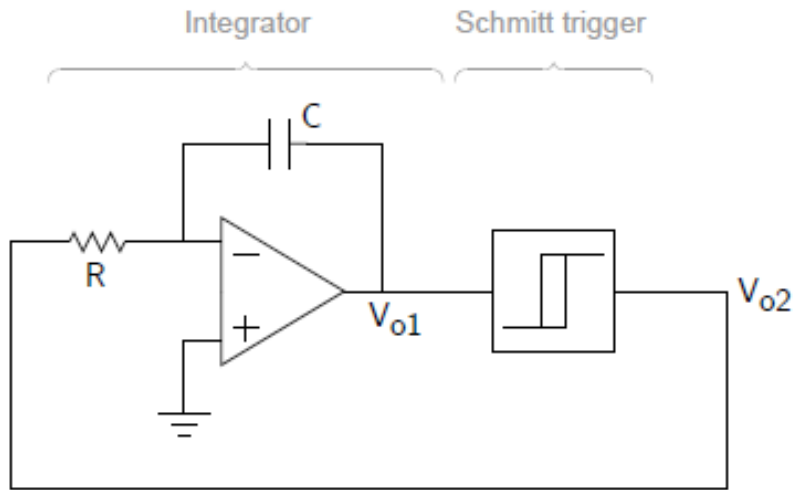

- Plot V_{o2} and V_{o1} vs t
- Find the time period

$$V_{o1} = -\frac{1}{RC} \int V_{o2} dt$$


$V_{o2} = L^+ \rightarrow V_{o1}$ Decreases linearly

$V_{o2} = L^- \rightarrow V_{o1}$ Increases linearly

$$T_1 = \frac{V_{TH} - V_{TL}}{L^+ / RC} = RC \frac{V_{TH} - V_{TL}}{L^+}$$



$$T_2 = \frac{V_{TH} - V_{TL}}{-L^- / RC} = RC \frac{V_{TH} - V_{TL}}{-L^-}$$

Vibrator Circuit: Examples

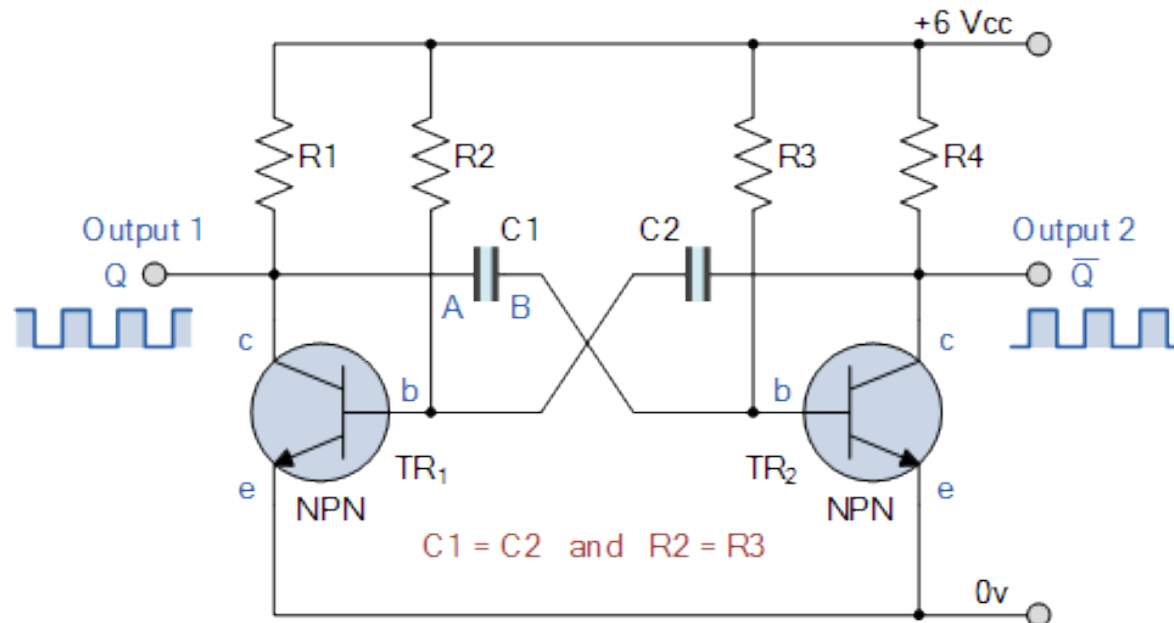



- Astable multivibrator
 - No stable state
 - Keeps oscillating

Vibrator Circuit: Examples

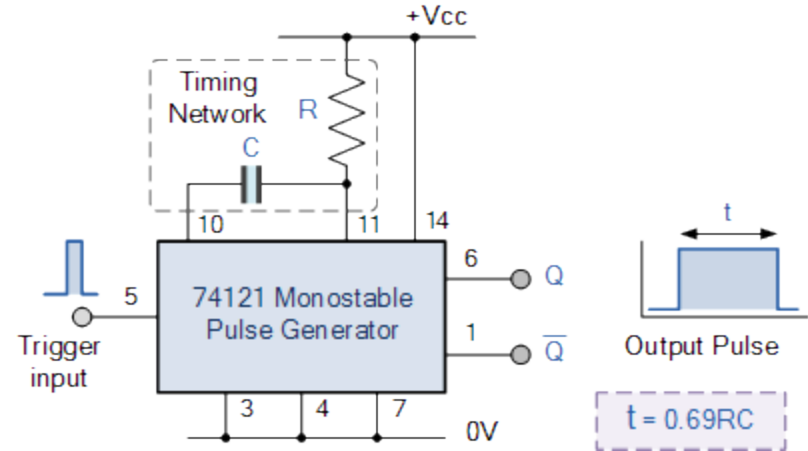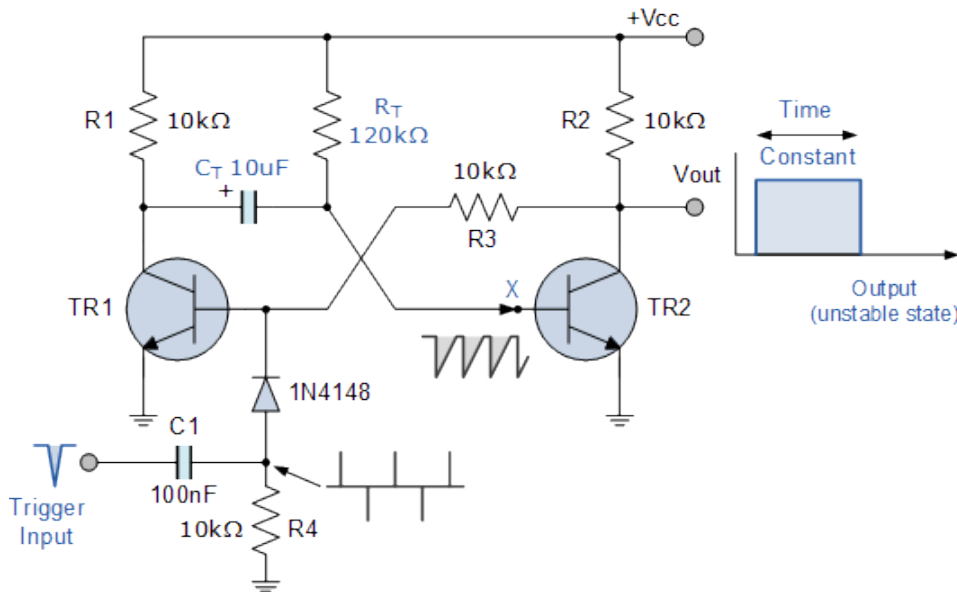


- Monostable multivibrator
 - No stable state
 - Produce a pulse with a trigger input

Vibrator Circuit: Examples

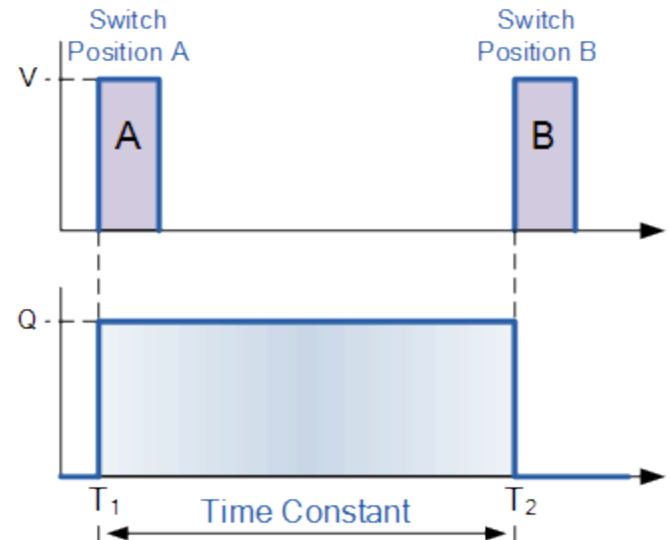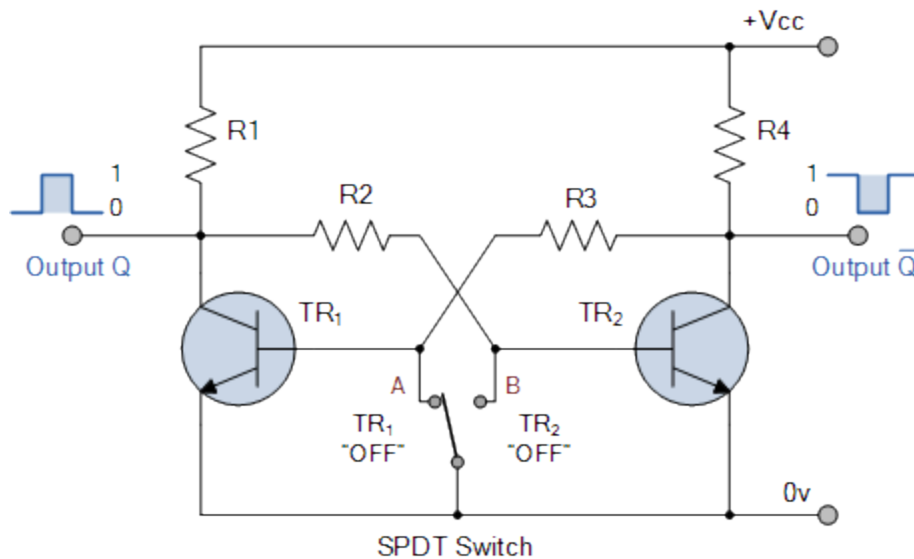

- Bistable multivibrator
 - Two stable states
 - Trigger/switch needed to move from one to another state

Comparators


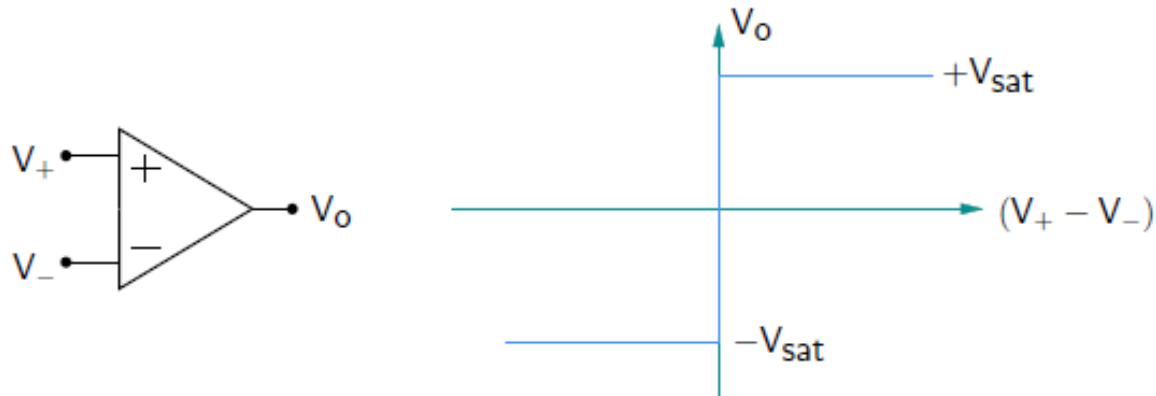


$$V_+ > V_- \Rightarrow V_o = V_{sat}$$

$$V_+ < V_- \Rightarrow V_o = -V_{sat}$$

- Width of the linear region ~ 0.1 mV can be neglected
 - High gain in linear region
- “Compare” V_+ with V_-




Comparator

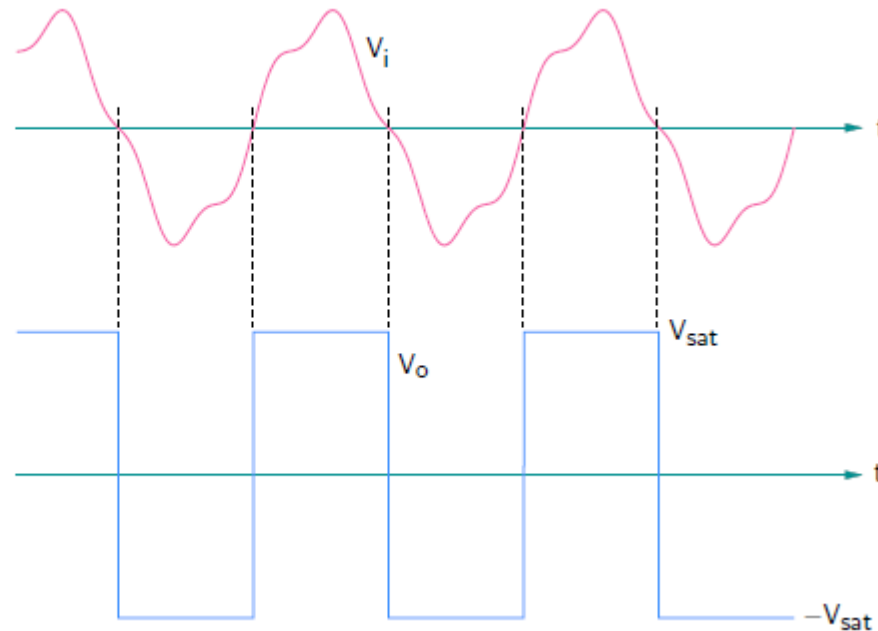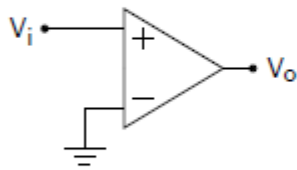


- An analog signal can be converted into digital signal (high/low) for further processing by digital circuits
- Also called a level detector if the reference voltage is not zero
- Zero-crossing detector if reference voltage is zero (above)

Schmitt Trigger based Comparator

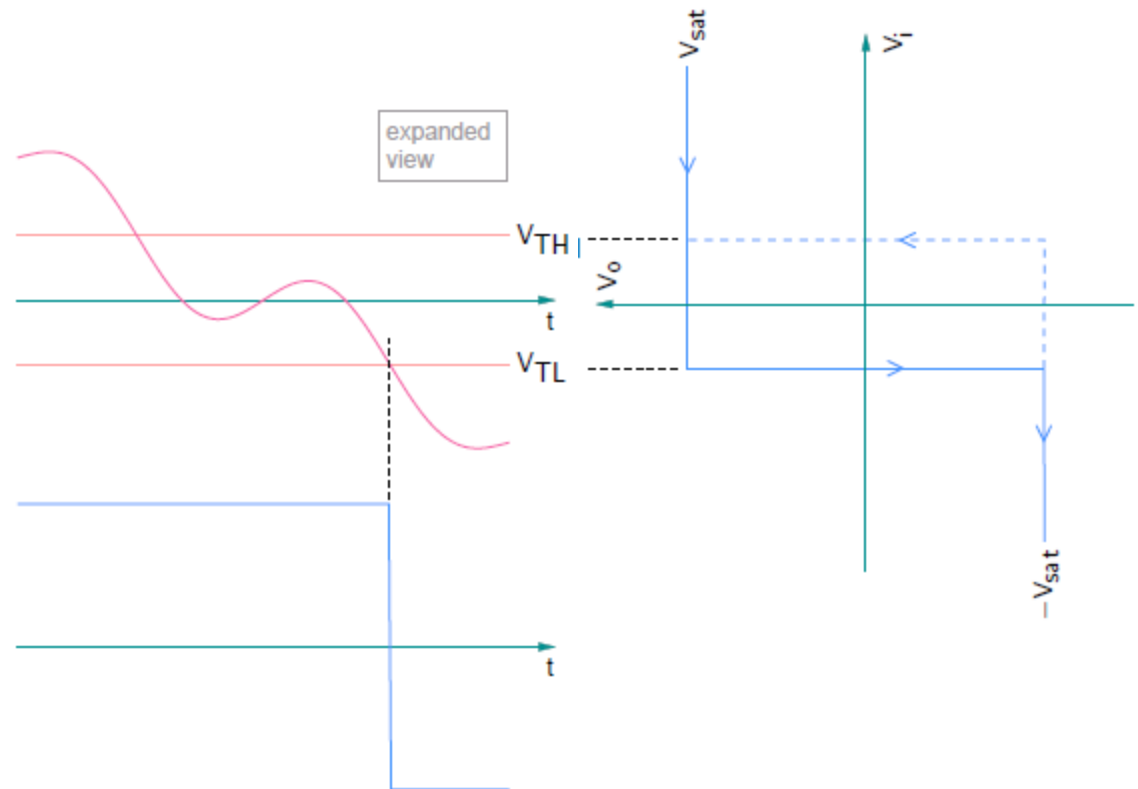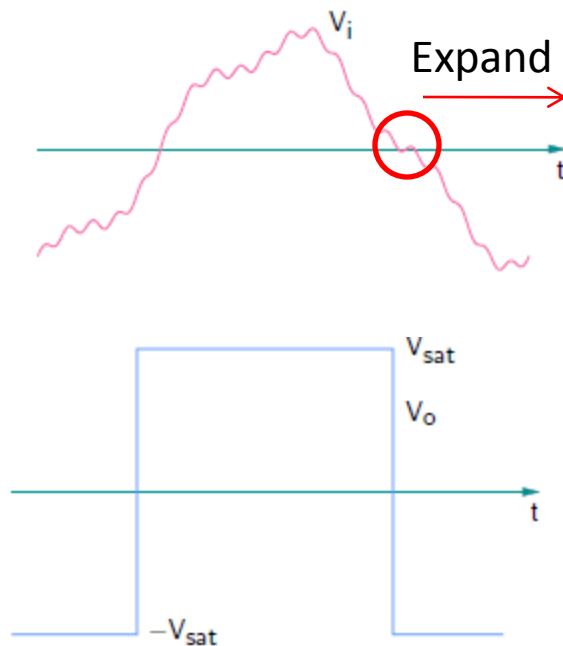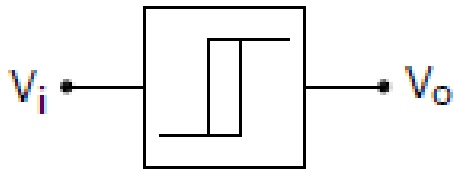- Output flips at V_{TH} and V_{TL} crossing, not zero
- Input signal noise will not affect output



Sinusoidal (Linear) Oscillators

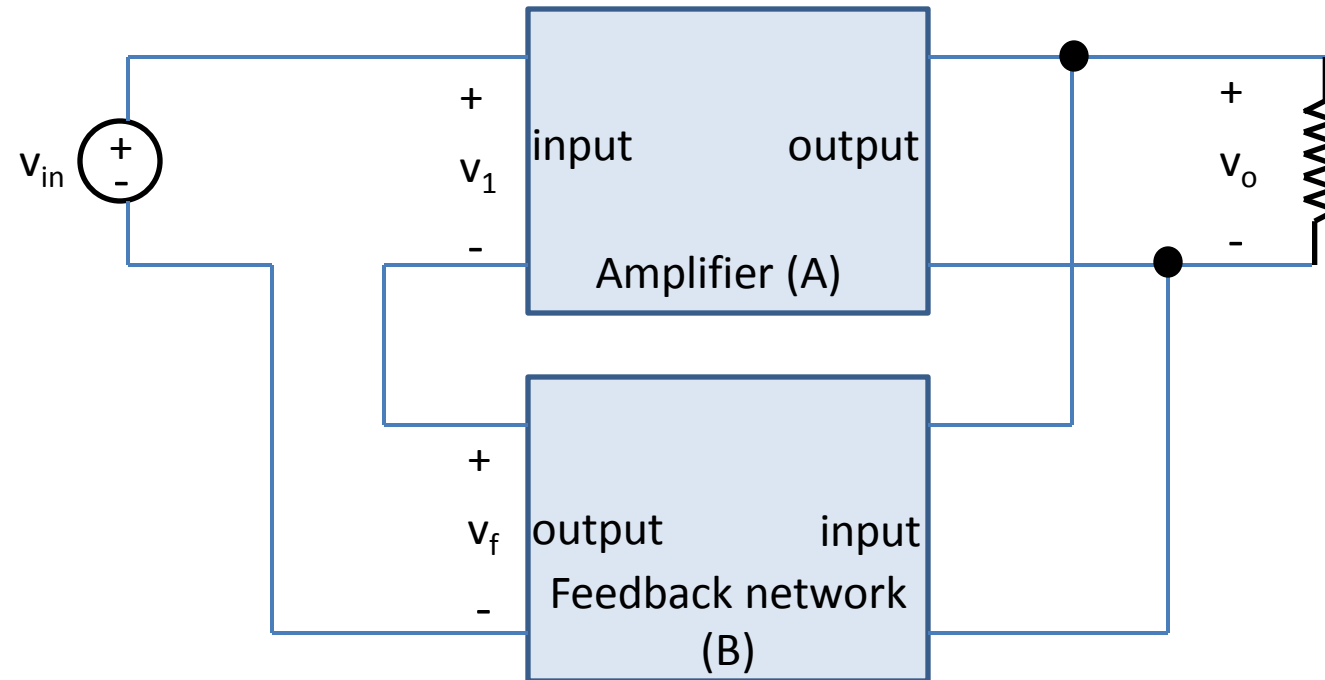

$$v_{in} = v_1 + v_f$$

$$v_o = Av_1$$

$$v_f = Bv_o$$

$$\Rightarrow v_{in} = \frac{v_o}{A} + Bv_o$$

$$\Rightarrow A_F = \frac{v_o}{v_{in}} = \frac{A}{1 + AB}$$

If $AB > 0$, $A_F < A \rightarrow$ negative (degenerative) feedback

If $A_F > A \rightarrow$ positive (regenerative) feedback

Barkhausen Condition (Oscillation)

$v_{in} = v_o = v_f = 0$ Initial Condition


$v_o = A(v_{in} - v_f) = Av_{in}$ Apply v_{in}

$v_f = Bv_o = BAv_{in}$ Apply v_{in}

$v_{in} = 0$ Make input zero

$v_1 = -v_f = -BAv_{in}$

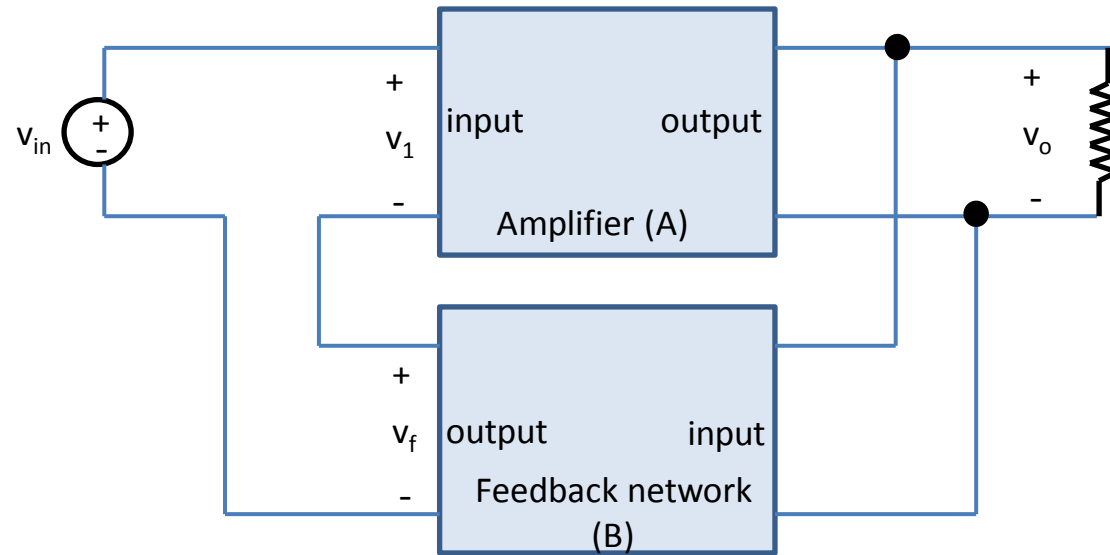
$BA = -1 \Rightarrow v_1 = v_{in}$ Original input



- Feedback network allows maintaining original input voltage and same output voltage
- Non-zero output without external input \rightarrow oscillator
- Loop gain \rightarrow product of individual gains around loop without external input
- Condition for oscillation \rightarrow $-AB=1$ (Barkhausen condition)
 - Unity loop gain
 - $A_F \rightarrow$ infinite (non-zero output with no input)

$$\frac{v_o}{v_1} \times \frac{v_f}{v_o} \times \frac{v_1}{v_f} = A \times B \times -1 = -AB$$

Sinusoidal (Linear) Oscillators

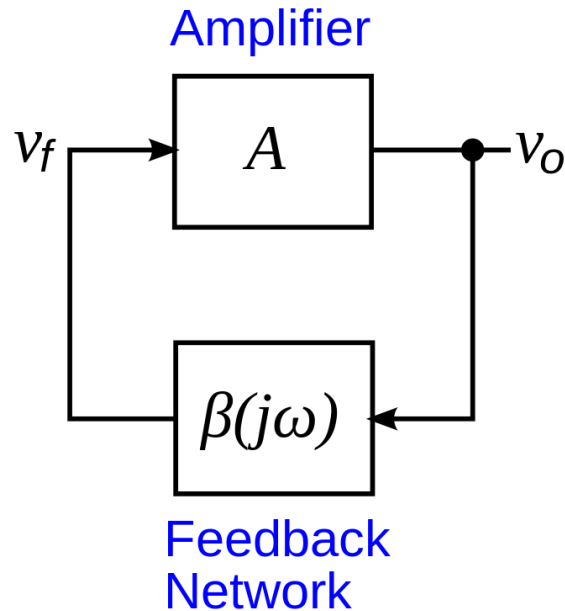


- In general, Barkhausen condition for loop gain βA states that the oscillator will sustain steady-state oscillations only for those frequencies for which:

$$|\beta A| = 1$$


$$\angle \beta A = 2\pi n, n = 0, 1, 2, \dots$$

Sinusoidal Oscillators

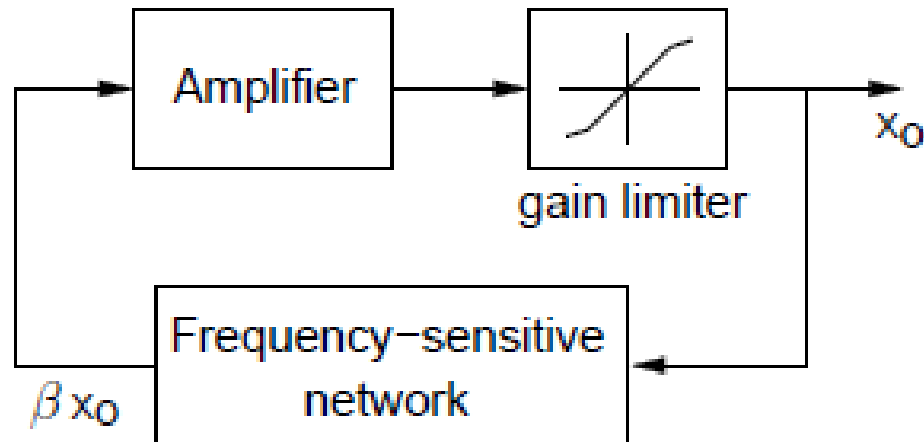


- Gain limiting circuit needed to limit amplitude of oscillations
 - Op-Amps (+/- V_{sat})
 - Diode resistor networks
- Upto ~ 100 kHz, op-amps and RC feedback networks are ok
- For high frequencies, gain and slew rate limitations
 - Transistor amplifiers, LC feedback

Wein-bridge Oscillator


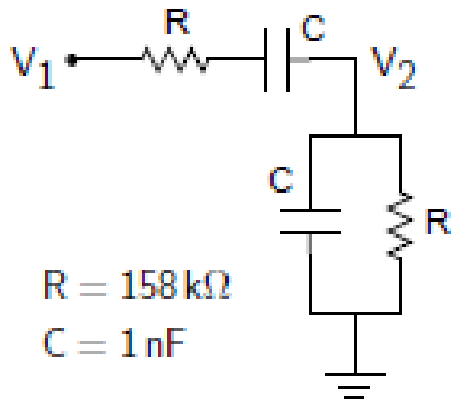

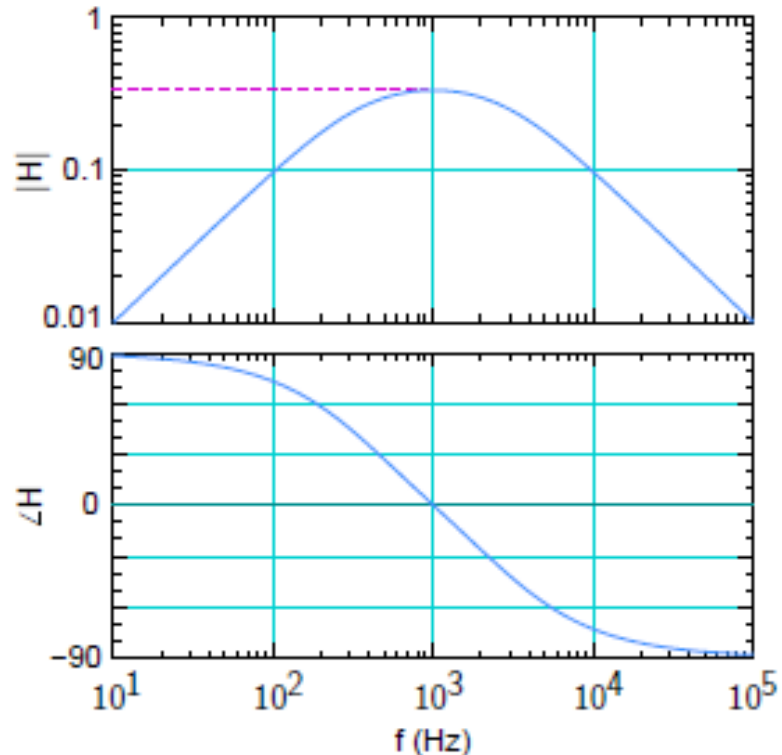
$$H(j\omega) = \frac{V_2(j\omega)}{V_1(j\omega)} = \frac{j\omega RC}{-(\omega RC)^2 + 3j\omega RC + 1}$$



- The condition that $\angle \beta A = 2\pi n, n = 0, 1, 2, \dots$ is satisfied at only one frequency $\omega_o = 1/RC$, i.e. $f_o = 1 \text{ kHz}$
- For this frequency, $\beta(j\omega_o) = H(j\omega_o) = 1/3$

Wein-bridge Oscillator

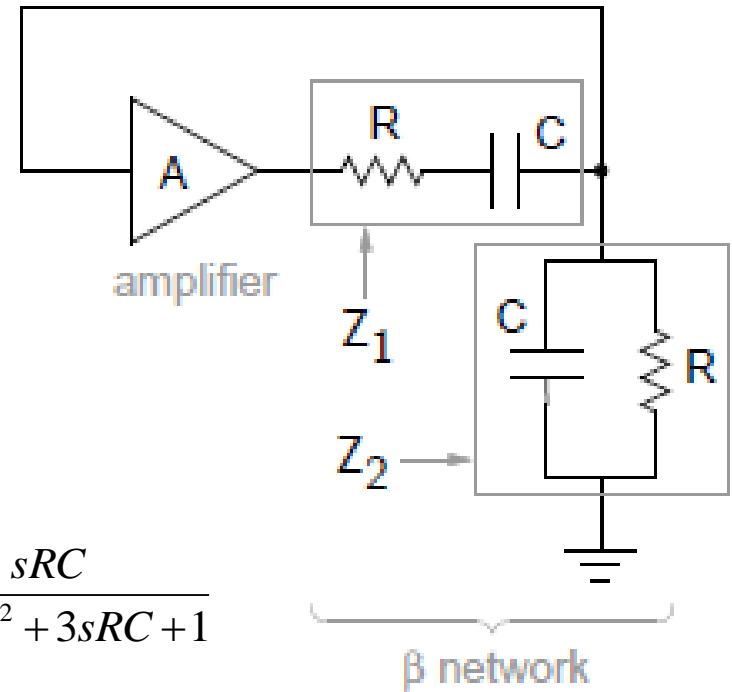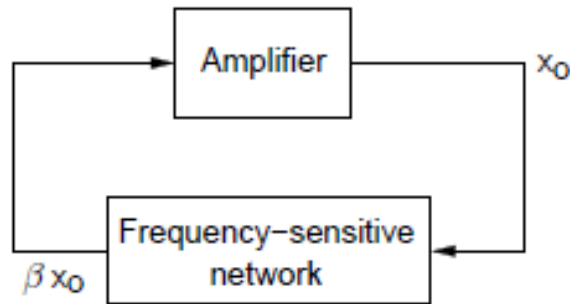

Assuming $R_{in} = \infty$ for the amplifier (β -network not loaded by amplifier)


$$A(s)\beta(s) = A \frac{Z_2}{Z_1 + Z_2} = A \frac{R \parallel (1/sC)}{R + (1/sC) + R \parallel (1/sC)} = A \frac{sRC}{(sRC)^2 + 3sRC + 1}$$

For $|A\beta| = 1$ (and with A equal to a real positive number)


$$\frac{j\omega RC}{-(\omega RC)^2 + 3j\omega RC + 1} \quad \text{Must be real and equal to } 1/A$$

$$\Rightarrow \omega_o = 1/RC, |\beta(j\omega_o)| = \frac{1}{3} \Rightarrow A = 3$$


Wein-bridge Oscillator

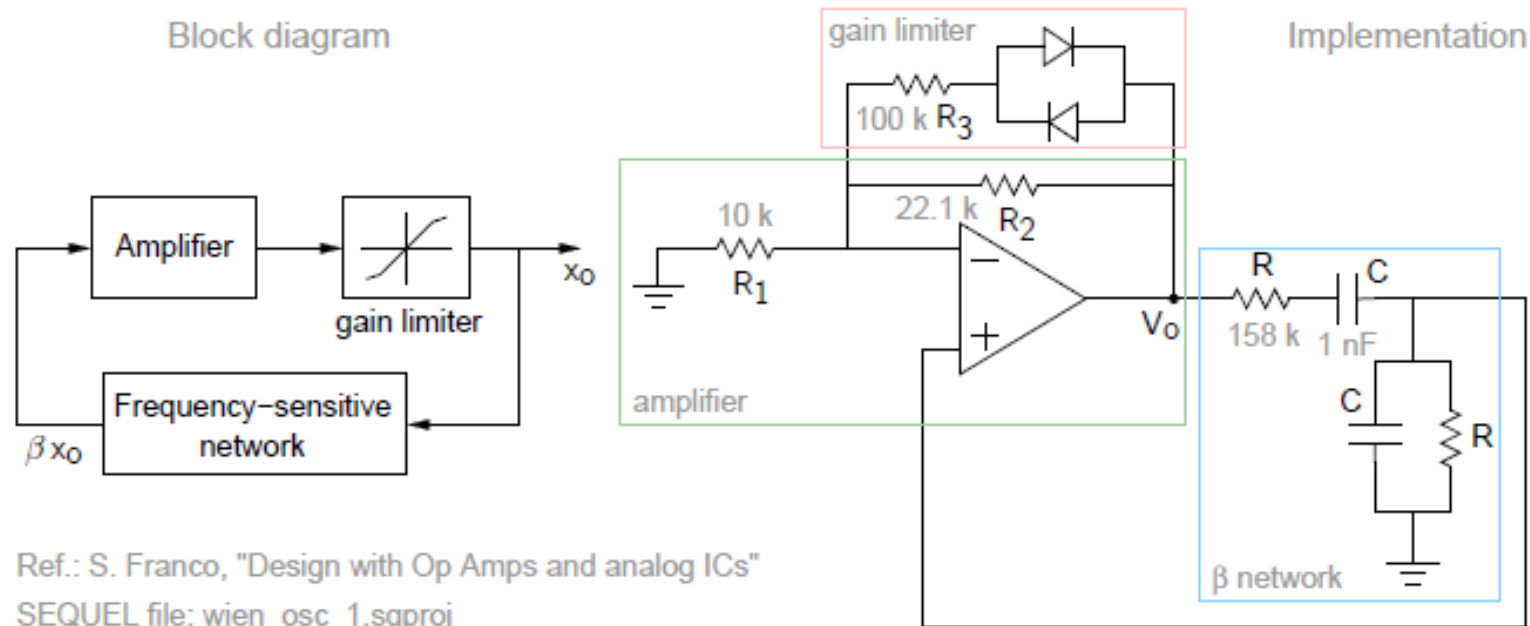

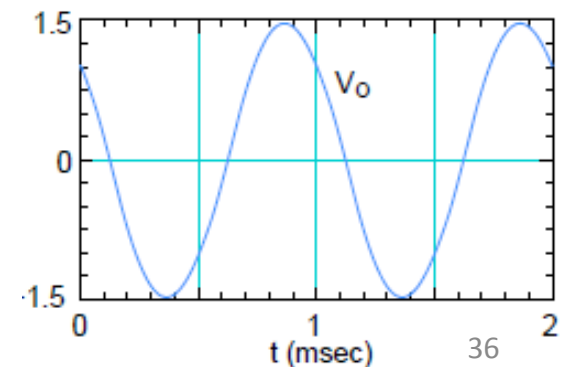- Frequency $\omega_0 = 1/RC$, i.e. $f_0 = 1\text{kHz}$
- For amplifier gain $A=3$, $1+R_2/R_1=3 \rightarrow R_2=2R_1$
- For limiting gain, diodes are used. When one of the two conducts, $R_2 \rightarrow R_2 \parallel R_3$ and gain reduces



Phase-shift oscillator

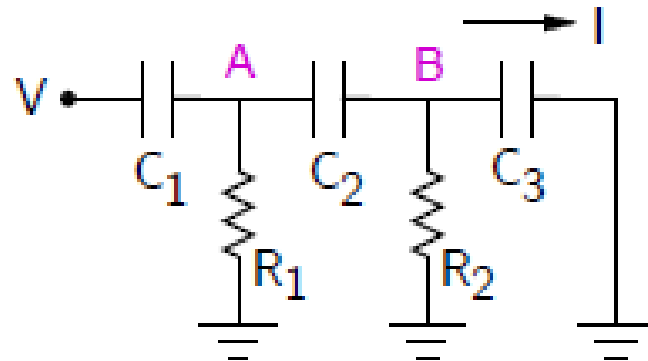

$$R_1 = R_2 = R, C_1 = C_2 = C_3 = C$$


$$sC(V_A - V) + GV_A + sC(V_A - V_B) = 0 \quad (1)$$

$$sC(V_B - V_A) + GV_B + sCV_B = 0 \quad (2)$$

Solving (1) and (2)

$$I = \frac{1}{R} \frac{(sRC)^3}{3(sRC)^2 + 4sRC + 1} V$$

Phase-shift oscillator

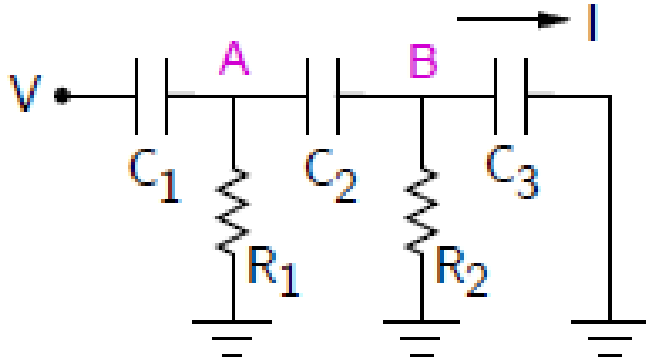


$$\beta(j\omega) = \frac{I(j\omega)}{V(j\omega)} = \frac{1}{R} \frac{(j\omega RC)^3}{3(j\omega RC)^2 + 4j\omega RC + 1}$$

For $\beta(j\omega)$ to be a real number, denominator should be purely imaginary

$$-3(\omega RC)^2 + 1 = 0 \Rightarrow \omega \equiv \omega_o = \frac{1}{\sqrt{3}} \frac{1}{RC}$$

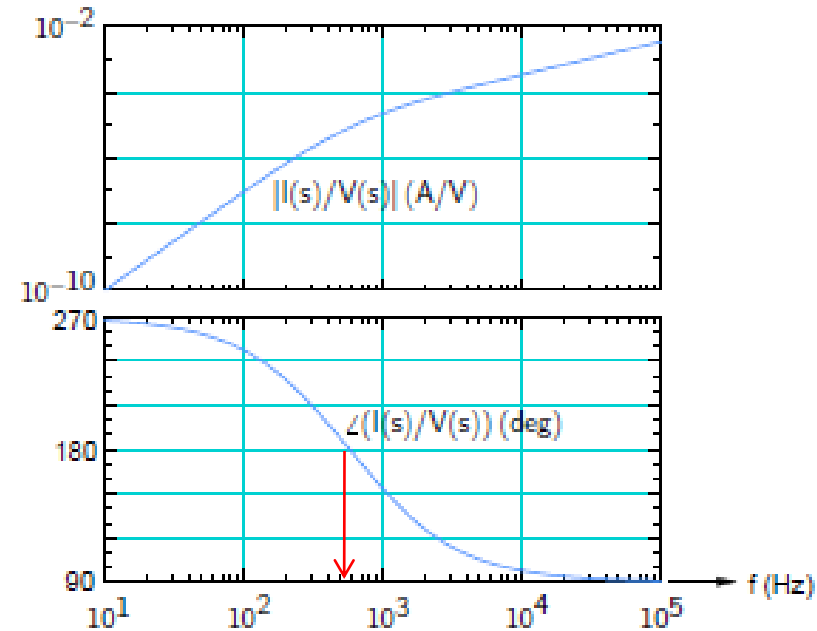
$$\beta(j\omega_o) = \frac{1}{R} \frac{(j/\sqrt{3})^3}{4j/\sqrt{3}} = -\frac{1}{12R}$$



$$R_1=R_2=R=10k, C_1=C_2=C_3=C=16nF$$

Phase angle=180 deg= π at ω_o

Phase-shift oscillator

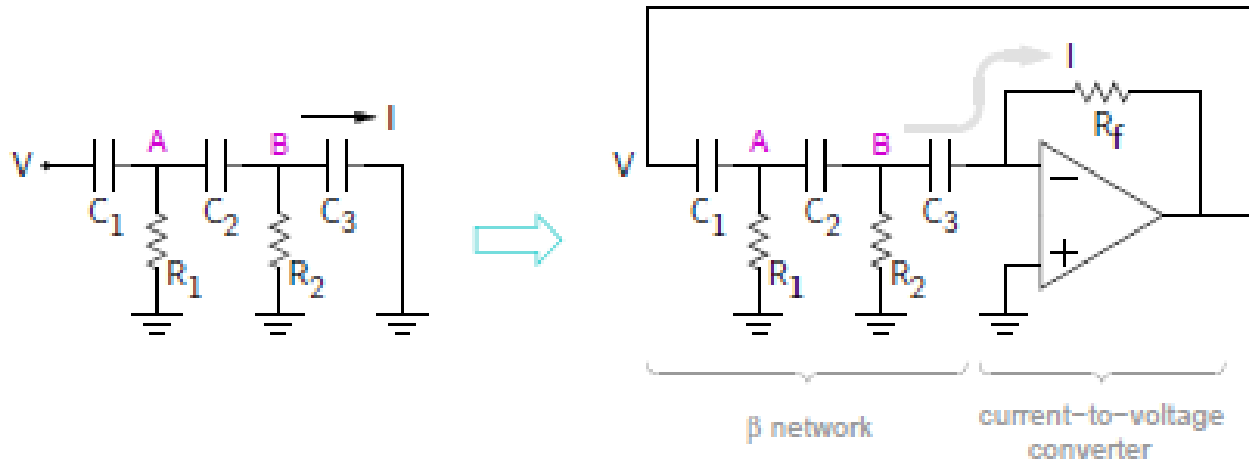

Note that virtual ground of the op-amp provides the ground of the β -network on the left

$$A\beta(j\omega) = \ominus R_f \frac{I(j\omega)}{V(j\omega)} = -\frac{R_f}{R} \frac{(j\omega RC)^3}{3(j\omega RC)^2 + 4j\omega RC + 1}$$


Phase angle = 180 deg = π , $\angle \beta A = \pi + \pi = 2\pi$

For the circuit to oscillate at ω_o (phase is 2π)


$$|A\beta(j\omega_o)| = 1 \Rightarrow R_f \times \frac{1}{12R} = 1 \Rightarrow R_f = 12R$$

Phase-shift oscillator


Block Diagram

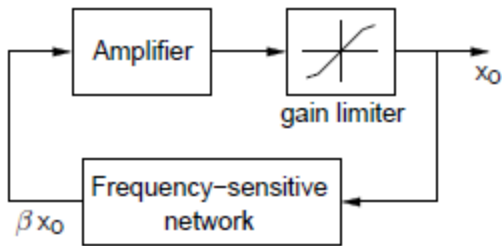

Implementation

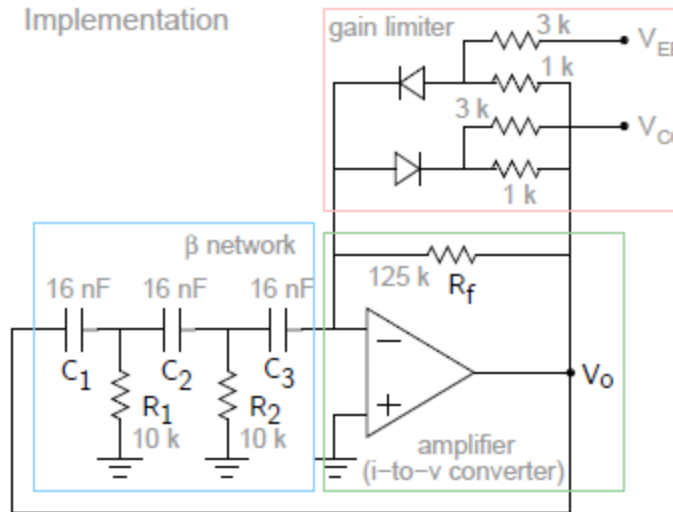

Output

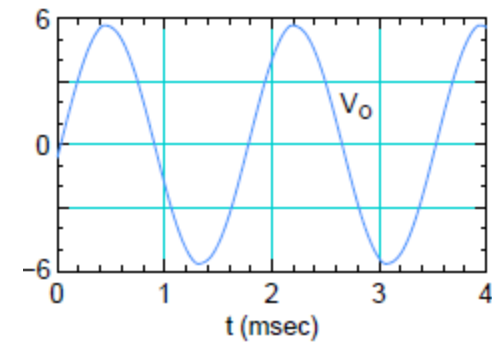

$$\omega_o = \frac{1}{\sqrt{3}} \frac{1}{RC} \Rightarrow f_o = 574 \text{ Hz}$$