

# EE101: MOSFET and CMOS Digital Logic

S. Lodha

# Digital Technologies

- Information en-coded in logic values = {0, 1}
- A logic value, 0 or 1, is called as Binary DigiT or **BIT**.
- Physical states representing bits in digital technologies:

Technology	State Representing Bit	
	0	1
Relay logic	Circuit open	Circuit closed
CMOS logic	0-1.5V	3.5-5V
Transistor-transistor logic	0-0.8V	2-5V
Fiber optics	Light off	Light on
Dynamic memory	Capacitor discharged	Capacitor charged
Nonvolatile, erasable memory	Electrons trapped	Electrons released
Bipolar read-only memory	Fuse blown	Fuse intact
Magnetic tape or disk	Flux direction N	Flux direction S
Read-only compact disc	No pit	Pit

# CMOS Digital Logic

- CMOS: Complementary MOS
- Information can be encoded using:
  - Current, Voltage, Phase, Frequency
- CMOS Digital systems use two **voltage levels** for encoding bits.
  - **LOW**: A signal close to the GND
  - **HIGH**: A signal close to the VCC


 


Fig. 1-1 An Example of Voltage Ranges for Binary Signals

 
# Basic building block for CMOS Digital Logic



- **MOS**FET: “Metal-oxide-semiconductor field effect transistor”
 
# MOSFET operation


Flow of current from “source” to “drain” is controlled by the gate voltage through a “field effect”.



- Gate voltage “modulates” the conductivity of the region below the gate → “channel”

# MOSFET as a 2-port device


MOSFET circuit symbol

 

current vs. voltage (IV)  
characteristics

$$I_D(V_G, V_S, V_D)$$





common source

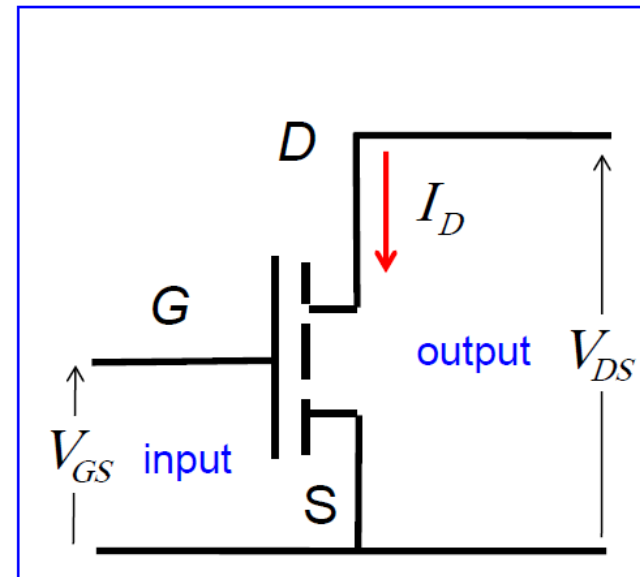

$I_D(V_{GS})$  at a fixed  $V_{DS}$  transfer


$I_D(V_{DS})$  at a fixed  $V_{GS}$  output
  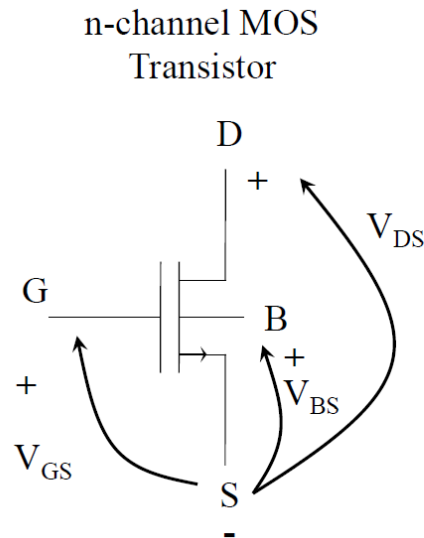 
# N and p-channel MOSFETs: Qualitative Description



- G=Gate, D=Drain, S=Source, B=Body (substrate)

 
# MOSFET IV Characteristics (1): Resistor



- “Linear” characteristics



 
# MOSFET IV Characteristics (2): Ideal Current Source




- Ideal current Source: “Saturation” Characteristics
 
# MOSFET IV Characteristics (2): Real current source




- Real Current Source: “Saturation” Characteristics

# Combined Characteristics

 


# Combined Characteristics

 


# Output and Transfer Characteristics


output characteristics

 


# Physical MOSFET

 

# I-V Characteristics: Details

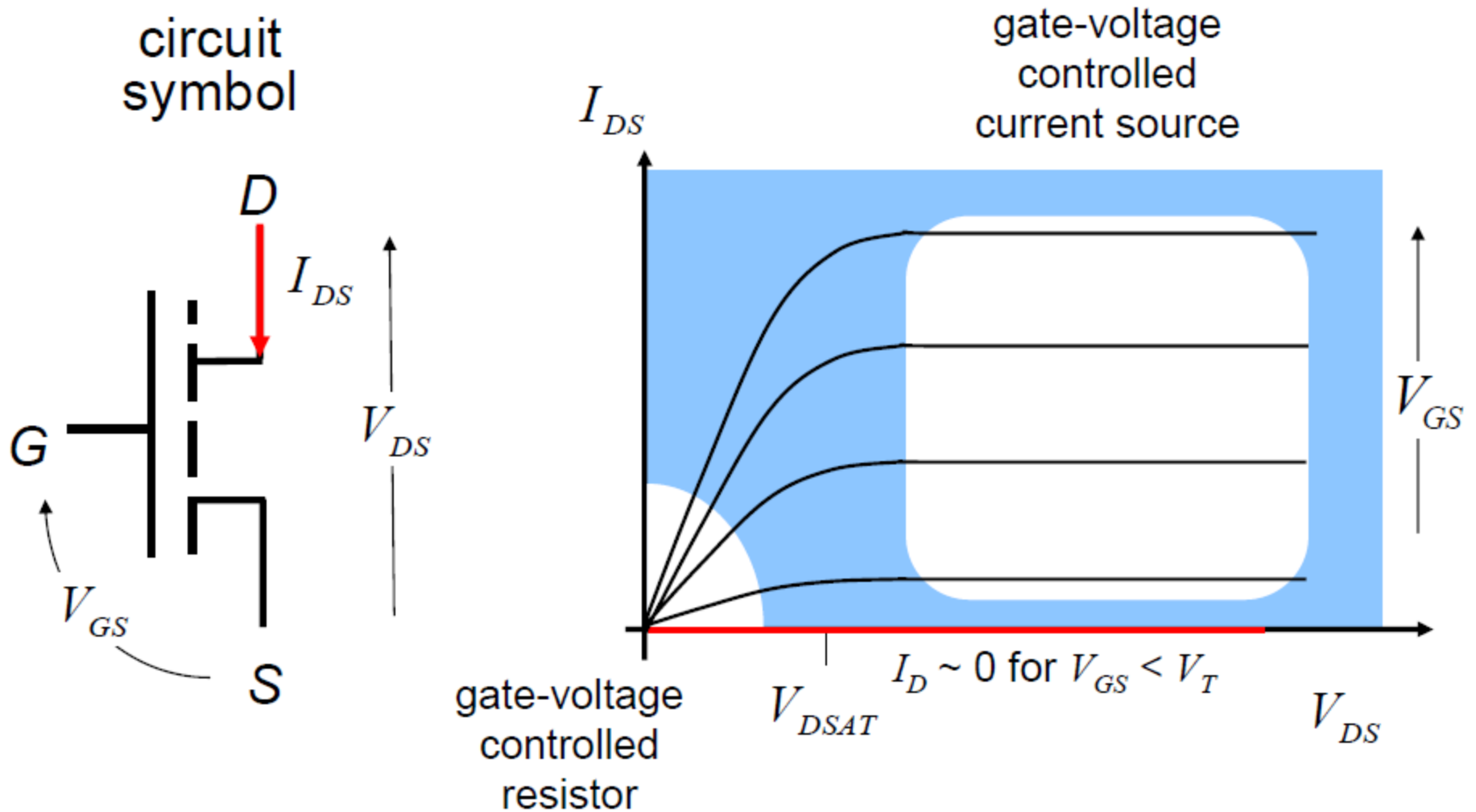


# MOSFET I-V: Low $V_{DS}$

 

$$I_D = W Q_i(x) v_x(x)$$

$$I_D = W C_{ox} (V_{GS} - V_T) \mu_{eff} \mathcal{E}_x$$


$$\mathcal{E}_x = \frac{V_{DS}}{L}$$

 


$$I_D = \frac{W}{L} \mu_{eff} C_{ox} (V_{GS} - V_T) V_{DS}$$



# MOSFET I-V: Pinch-off at high $V_{DS}$

 


# MOSFET I-V: High $V_{DS}$

 

$$I_D = W Q_i(x) v_x(x) = W Q_i(0) v_x(0)$$


$$I_D = W C_{ox} (V_{GS} - V_T) \mu_{eff} \mathcal{E}_x(0)$$
 
$$\mathcal{E}_x(0) \approx \frac{V_{GS} - V_T}{L}$$




$$I_D = \frac{W}{2L} \mu_{eff} C_{ox} (V_{GS} - V_T)^2$$
 
# MOSFET Device Metrics: Output Characteristics




# MOSFET Device Metrics: Transfer Characteristics

transfer characteristics:

 

# MOSFET Device Metrics: Transfer Characteristics

transfer characteristics:

 

# Some facts

The number of transistors manufactured in 1997 exceeded the number of ants on the planet.

The cost of an IC “fab” is more than \$3B, but the cost of a transistor has dropped by more than a factor of one million over the past 30 years.

If the definition of a nanodevice is one that has two dimensions less than 100 nm, then the silicon transistor is the most successful nanodevice currently in production.

(channel length 22 nm and gate oxide thickness,  $< 2$  nm)

# Logic Gates

- Gates are basic digital devices.
  - A gate takes one or more inputs and produces an output.
  - Inputs are either 0 or 1.
    - Although they may have very different values of voltage.
  - Output is either 0 or 1.
  - A logic gate's operation is fully described by a **truth table**.



X	Y	X AND Y
0	0	0
0	1	0
1	0	0
1	1	1



X	Y	X OR Y
0	0	0
0	1	1
1	0	1
1	1	1



X	NOT X
0	1
1	0


# Logic Family

- A **logic family** is a collection of different integrated-circuit chips that have similar input, output, and internal circuit characteristics, but that perform different logic functions.
- Logic gates are made from transistors.
  - **TTL (Transistor-Transistor Logic)** family gates are made from bipolar transistors.
  - **CMOS (Complementary Metal Oxide Semiconductor)** family logic gates are made from MOS transistors.



 
# MOS Transistors – N-type MOSFET

- OFF (open circuit) : when gate is logical zero
- ON (short circuit) : when gate is logical one
- Passes a good logical zero
- Degrades a logical one


 
# MOS Transistors – P-type MOSFET

- OFF (open circuit) : when gate is logical one
- ON (short circuit) : when gate is logical zero
- Passes a good logical one
- Degrades a logical zero




# CMOS Inverter Technology


- Complementary MOS, or CMOS, needs both PMOS and NMOS devices for the logic gates to be realized
- The concept of CMOS was introduced in 1963 by Wanlass and Sah, but it did not become common until the 1980's as NMOS microprocessors were dissipating as much as 50 W and alternative design technique was needed
- CMOS dominates digital IC design today
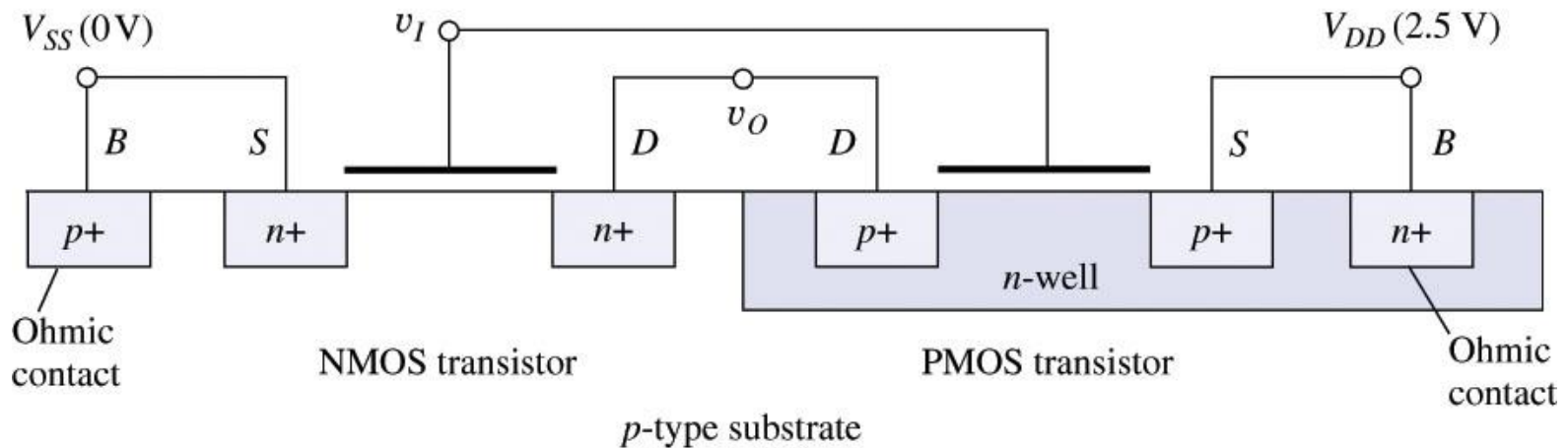
# CMOS Inverter Technology

- The CMOS inverter consists of a PMOS device stacked on top of an NMOS device, but they need to be fabricated on the same wafer
- To accomplish this, the technique of “n-well” implantation is needed as shown in this cross-section of a CMOS inverter



# CMOS Inverter

 

- (a) Circuit schematic for a CMOS inverter
- (b) Simplified operation model with a high input applied
- (c) Simplified operation model with a low input applied


# CMOS Inverter Operation

- When  $v_i$  is pulled high (to  $V_{DD}$ ), the PMOS transistor is turned off, while the NMOS device is turned on pulling the output down to  $V_{SS}$
- When  $v_i$  is pulled low (to  $V_{SS}$ ), the NMOS transistor is turned off, while the PMOS device is turned on pulling the output up to  $V_{DD}$

# Key Properties


- Full rail-to-rail swing → high noise margins
  - Logic levels not dependent upon the relative device sizes → Transistors can be minimum size → ratio less
- Always a path to VDD or GND in steady state → low output impedance (output resistance in  $k\Omega$  range) → large fan-out.
- Extremely high input resistance (gate of MOS transistor is near perfect insulator) → nearly zero steady-state input current
- **No direct path steady-state between power and ground**
  - **no static power dissipation**
- Propagation delay function of load capacitance and resistance of transistors

# Generalized CMOS Logic Gates

 






# Inverter

 


$V_{IN}$	$Q1$	$Q2$	$V_{OUT}$
0.0 (L)	off	on	5.0 (H)
5.0 (H)	on	off	0.0 (L)

 

# Inverter

  

# NAND – Not AND

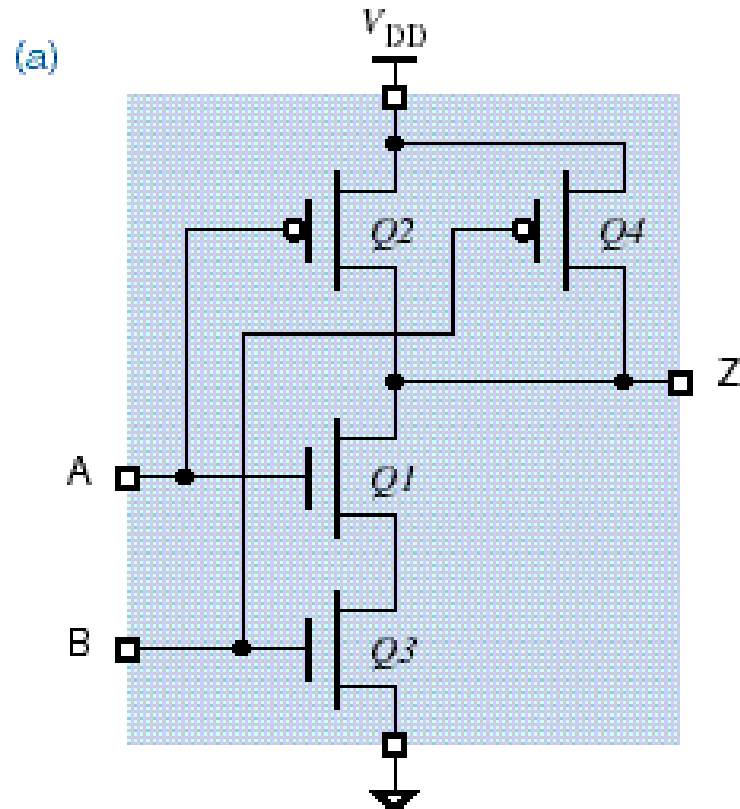


Copyright © 2000 by Prentice Hall, Inc.  
Digital Design Principles and Practices, 3/e




(b)

A	B	$Q1$	$Q2$	$Q3$	$Q4$	Z
L	L	off	on	off	on	H
L	H	off	on	on	off	H
H	L	on	off	off	on	H
H	H	on	off	on	off	L


(c)

 

# NAND

   


# NOR – Not OR

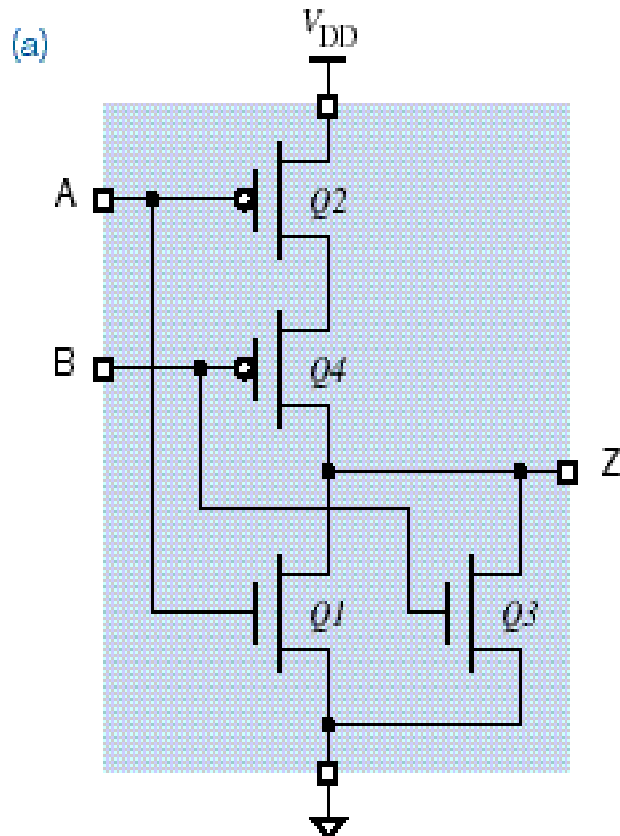

(b)


A	B	$Q1$	$Q2$	$Q3$	$Q4$	Z
L	L	off	on	off	on	H
L	H	off	on	on	off	L
H	L	on	off	off	on	L
H	H	on	off	on	off	L

(c)

 

Copyright © 2000 by Prentice Hall, Inc.  
Digital Design Principles and Practices, 3/e


# Non-inverting Buffer

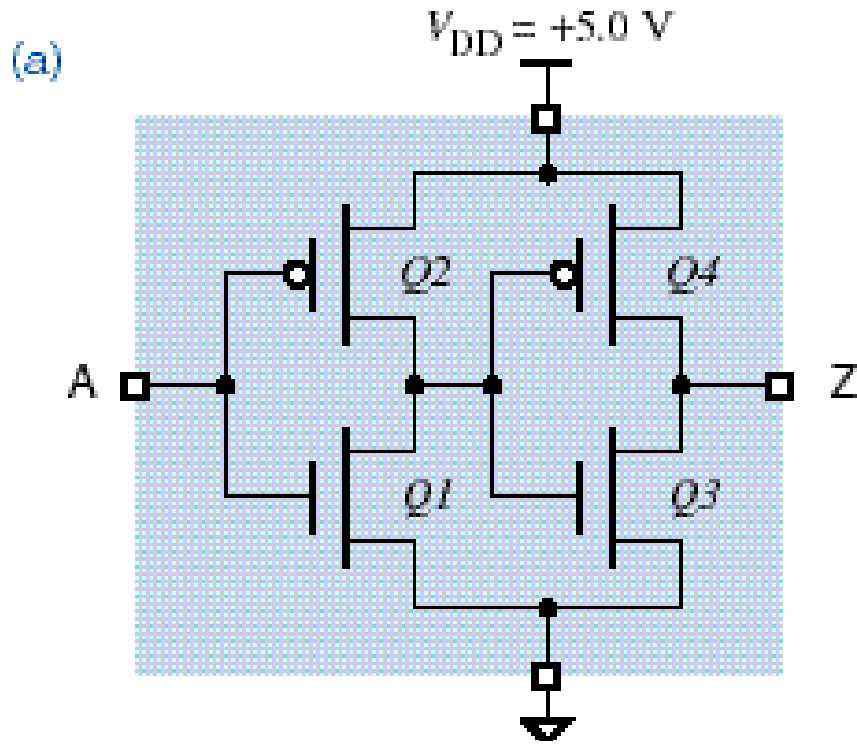


Copyright © 2000 by Prentice Hall, Inc.  
Digital Design Principles and Practices, 3/e

(b)

$A$	$Q1$	$Q2$	$Q3$	$Q4$	$Z$
L	off	on	on	off	L
H	on	off	off	on	H

 


# AND Gate

 

(b)

A	B	Q1	Q2	Q3	Q4	Q5	Q6	Z
L	L	off	on	off	on	on	off	L
L	H	off	on	on	off	on	off	L
H	L	on	off	off	on	on	off	L
H	H	on	off	on	off	off	on	H


(c)

 

Copyright © 2000 by Prentice Hall, Inc.  
Digital Design Principles and Practices, 3/e

# OR Gate


(a)

 

(b)

A	B	$Q1$	$Q2$	$Q3$	$Q4$	$Q5$	$Q6$	Z
L	L	off	on	off	on	on	off	L
L	H	off	on	on	off	on	off	H
H	L	on	off	off	on	on	off	H
H	H	on	off	on	off	off	on	H

(c)

 




# Key CMOS Electrical Characteristics

- Logic voltage levels
- DC noise margin
- Speed
- Power consumption
- Fan-in
- Fan-out

# Key CMOS Electrical Characteristics

- Logic voltage levels
- DC noise margin
- Speed
- Power consumption
- Fan-in
- Fan-out

# CMOS Inverter

 


- No power consumption while idle in any logic state
  - No static power dissipation

Basic Operation:

- $V_{IN} = 0 \Rightarrow V_{OUT} = V_{DD}$   
 $V_{GSn} = 0 < V_{Tn} \Rightarrow$  **NMOS OFF**  
 $V_{SGp} = V_{DD} > -V_{Tp} \Rightarrow$  **PMOS ON**
- $V_{IN} = V_{DD} \Rightarrow V_{OUT} = 0$   
 $V_{GSn} = V_{DD} > V_{Tn} \Rightarrow$  **NMOS ON**  
 $V_{SGp} = 0 < -V_{Tp} \Rightarrow$  **PMOS OFF**

Output characteristics of both transistors:

# CMOS Static Characteristics

 

Note:



$$V_{IN} = V_{GSn} = V_{DD} - V_{SGp} \Rightarrow V_{SGp} = V_{DD} - V_{IN}$$

$$V_{OUT} = V_{DSn} = V_{DD} - V_{SDp} \Rightarrow V_{SDp} = V_{DD} - V_{OUT}$$

$$I_{Dn} = -I_{Dp}$$


Combine into single diagram of  $I_D$  vs.  $V_{OUT}$  with  $V_{IN}$  as parameter

# CMOS Inverter Static Characteristics

  

- Rail-to-Rail logic: logic levels are “0” and “ $V_{DD}$ ”
- High  $|A_v|$  around threshold  $\rightarrow$  high noise margins

# CMOS Inverter: Noise Margins

 

- Calculate  $V_M$
- Calculate  $A_v(V_M)$
- Calculate  $NM_H$  and  $NM_L$

# CMOS Inverter: $V_M$

Calculate  $V_M$  ( $V_M = V_{IN} = V_{OUT}$ )

At  $V_M$  both transistors are saturated:

$$I_{Dn} = \frac{W_n}{2L_n} \mu_n C_{ox} (V_M - V_{Tn})^2$$

$$-I_{Dp} = \frac{W_p}{2L_p} \mu_p C_{ox} (V_{DD} - V_M + V_{Tp})^2$$

# CMOS Inverter: $V_M$

Define:

$$k_n = \frac{W_n}{L_n} \mu_n C_{ox}; \quad k_p = \frac{W_p}{L_p} \mu_p C_{ox}$$

Since :

$$I_{Dn} = -I_{Dp}$$

Then:

$$\frac{1}{2} k_n (V_M - V_{Tn})^2 = \frac{1}{2} k_p (V_{DD} - V_M + V_{Tp})^2$$

Solve for  $V_M$ :

$$V_M = \frac{V_{Tn} + \sqrt{\frac{k_p}{k_n}} (V_{DD} + V_{Tp})}{1 + \sqrt{\frac{k_p}{k_n}}}$$

Usually,  $V_{Tn}$  and  $V_{Tp}$  fixed and  $V_{Tn} = -V_{Tp}$   
 $\Rightarrow V_M$  engineered through  $k_p/k_n$  ratio.



- **Symmetric case:**  $k_n = k_p$

$$V_M = \frac{V_{DD}}{2}$$

This implies:

$$\frac{k_p}{k_n} = 1 = \frac{\frac{W_p}{L_p} \mu_p C_{ox}}{\frac{W_n}{L_n} \mu_n C_{ox}} \approx \frac{\frac{W_p}{L_p} \mu_p}{\frac{W_n}{L_n} 2\mu_p} \Rightarrow \frac{W_p}{L_p} \approx 2 \frac{W_n}{L_n}$$

Since usually  $L_p \approx L_n = L_{min} \Rightarrow W_p \approx 2W_n$

- **Asymmetric case:**  $k_n \gg k_p$ , or  $\frac{W_n}{L_n} \gg \frac{W_p}{L_p}$

$$V_M \approx V_{Tn}$$

NMOS turns on as soon as  $V_{IN}$  goes above  $V_{Tn}$ .

- **Asymmetric case:**  $k_n \ll k_p$ , or  $\frac{W_n}{L_n} \ll \frac{W_p}{L_p}$

$$V_M \approx V_{DD} + V_{Tp}$$



PMOS turns on as soon as  $V_{IN}$  goes below  $V_{DD} + V_{Tp}$ .

## CMOS Inverter: $V_M$

- Sizing of the transistors can be used to tune  $V_M$

# CMOS Inverter: $A_v$


## Small Signal Model

 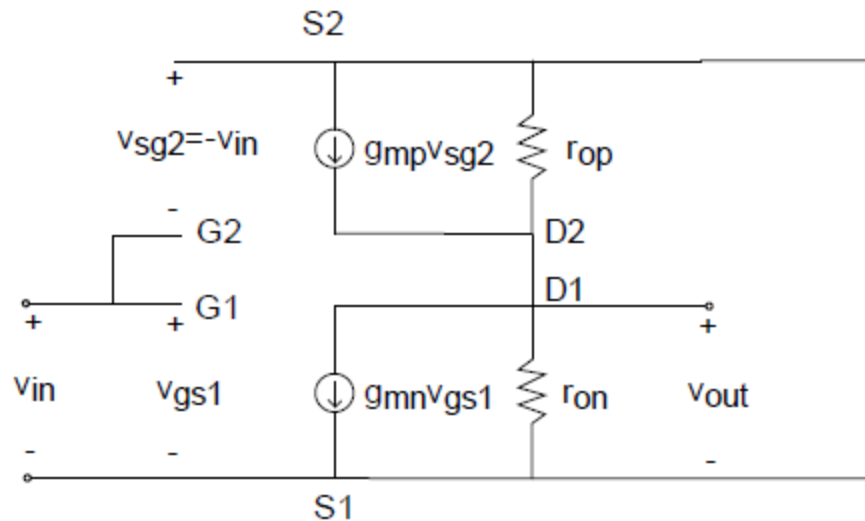

- $A_v$  can be quite large

$$A_v = - (g_{mn} + g_{mp}) (r_{on} \parallel r_{op})$$

# CMOS Inverter: Noise Margins

 

- Noise-margin low,  $NM_L$ :

$$V_{IL} = V_M - \frac{V_{DD} - V_M}{|A_v|}$$

$$NM_L = V_{IL} - V_{OL} = V_{IL} = V_M - \frac{V_{DD} - V_M}{|A_v|}$$

- Noise-margin high,  $NM_H$ :

$$V_{IH} = V_M \left( 1 + \frac{1}{|A_v|} \right)$$

$$NM_H = V_{OH} - V_{IH} = V_{DD} - V_M \left( 1 + \frac{1}{|A_v|} \right)$$


- High  $A_v$  gives high noise margins

Inverter propagation delay: time delay between input and output signals; figure of merit of logic speed.

Typical propagation delays:  $< 100$  ps.

□ Complex logic system has 10-50 propagation delays per clock cycle.

 **Estimation of  $t_p$ : use square-wave at input**







Average propagation delay:

$$t_p = \frac{1}{2}(t_{PHL} + t_{PLH})$$

## CMOS Inverter: Speed (Propagation Delay)

- More the delay less is the speed
    
# CMOS Inverter: Propagation Delay → High to Low



- Discharging of Load Capacitance

During early phases of discharge, NMOS is saturated and PMOS is cut-off.

Time to discharge *half* of charge stored in  $C_L$ :

□

$$t_{pHL} \approx \frac{\frac{1}{2} \text{ charge on } C_L \text{ @ } t = 0^-}{\text{NMOS discharge current}}$$

# CMOS Inverter: Propagation Delay → High to Low

Charge in  $C_L$  at  $t=0^-$ :

$$Q_L(t = 0^-) = C_L V_{DD}$$

Discharge Current (NMOS in saturation):



$$I_{Dn} = \frac{W_n}{2L_n} \mu_n C_{ox} (V_{DD} - V_{Tn})^2$$

Then:

$$t_{PHL} \approx \frac{C_L V_{DD}}{\frac{W_n}{L_n} \mu_n C_{ox} (V_{DD} - V_{Tn})^2}$$


- High  $V_{DD}$  reduces  $t_{PHL}$
- Higher current ( $I$ ) reduces  $t_{pHL}$

## Graphical Interpretation

  

# CMOS Inverter: Propagation Delay → Low to High

- Charging of load capacitance

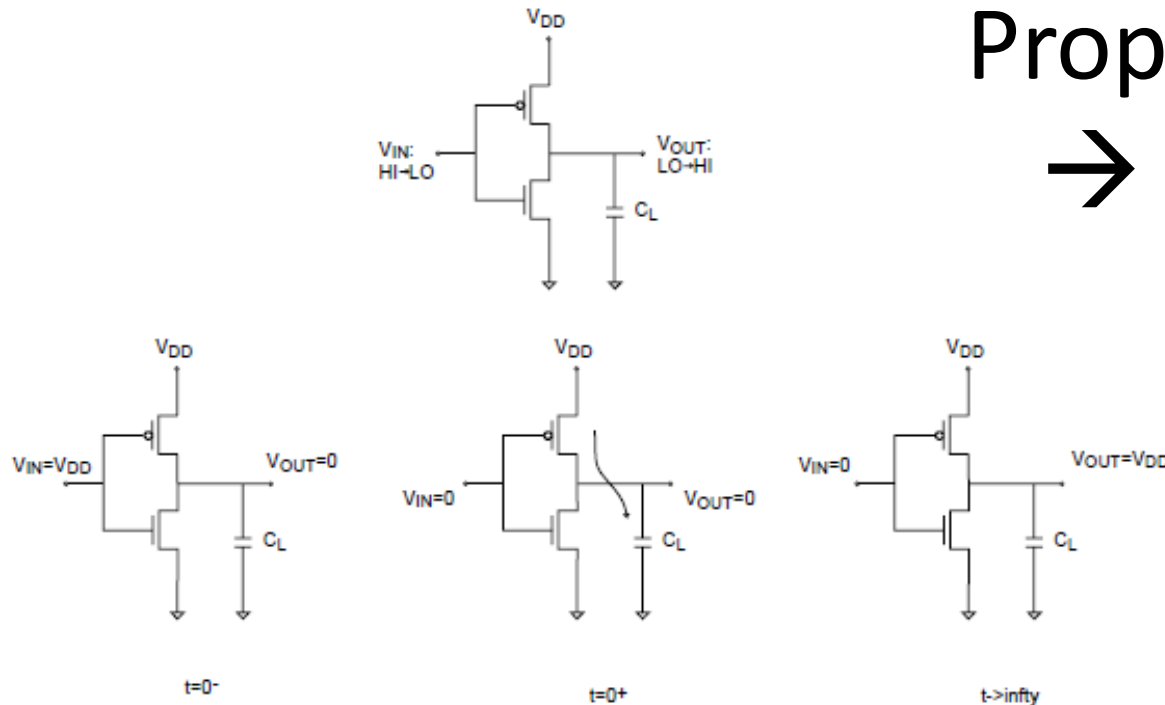

During early phases of discharge, PMOS is saturated and NMOS is cut-off.

Time to charge to *half* of final charge on  $C_L$ :

□

$$t_{PLH} \approx \frac{\frac{1}{2} \text{ charge on } C_L @ t = \infty}{\text{PMOS charge current}}$$

# CMOS Inverter:

## Propagation Delay → Low to High

Charge in  $C_L$  at  $t=\infty$ :

$$Q_L(t = \infty) = C_L V_{DD}$$

Charge Current (PMOS in saturation):

$$-I_{Dp} = \frac{W_p}{2L_p} \mu_p C_{ox} (V_{DD} + V_{Tp})^2$$

Then:

$$t_{PLH} \approx \frac{C_L V_{DD}}{\frac{W_p}{L_p} \mu_p C_{ox} (V_{DD} + V_{Tp})^2}$$

### Key dependencies of propagation delay:

- $V_{DD} \uparrow \Rightarrow t_p \downarrow$ 
  - Reason:  $V_{DD} \uparrow \Rightarrow Q(C_L) \uparrow$ , but  $I_D$  goes as square  $\uparrow$
  - Trade-off:  $V_{DD} \uparrow \Rightarrow$  more power consumed.
- $L \downarrow \Rightarrow t_p \downarrow$ 
  - Reason:  $L \downarrow \Rightarrow I_D \uparrow$
  - Trade-off: manufacturing cost!

- Scaling  $L$  can help reduce delay
  - New CMOS technologies
- Increasing  $V_{DD} \rightarrow$  higher power!



# Power Dissipation

- Energy from power supply needed to charge up the capacitor:

$$E_{charge} = \int V_{DD} i(t) dt = V_{DD} Q = V_{DD}^2 C_L$$

- Energy stored in capacitor:

$$E_{store} = 1/2 C_L V_{DD}^2$$

- Energy lost in p-channel MOSFET during charging:

$$E_{diss} = E_{charge} - E_{store} = 1/2 C_L V_{DD}^2$$

- During discharge the n-channel MOSFET dissipates an identical amount of energy.
- If the charge/discharge cycle is repeated  $f$  times/second, where  $f$  is the clock frequency, the **dynamic power dissipation** is:

$$P = 2E_{diss} * f = C_L V_{DD}^2 f$$

In practice many gates do not change state every clock cycle which lowers the power dissipation.

- Note
  - $V_{DD}$  dependence
  - $f$ -dependence
- Reduction of  $C_L$  is a win-win for both speed and power