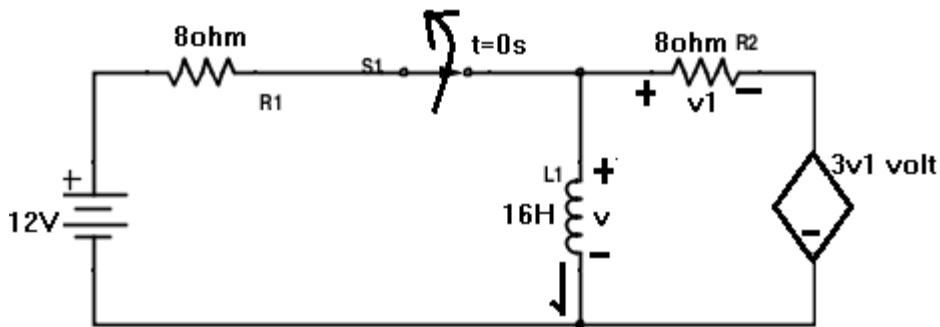


- 1) **1)** For the circuit shown in Figure below the switch opens at time  $t = 0$  s. Write a differential equation in  $i(t)$  for  $t \geq 0$  s. Find  $i(t)$  and  $V(t)$  for all time .




### Solution

**At  $t=0$  or just before switch is open:** Inductor acts as short circuit so no current flows through the 8 ohms resistor branch and  $3V_1$  branch.

$$i(0) = 12/8 = 1.5 \text{ amps}$$

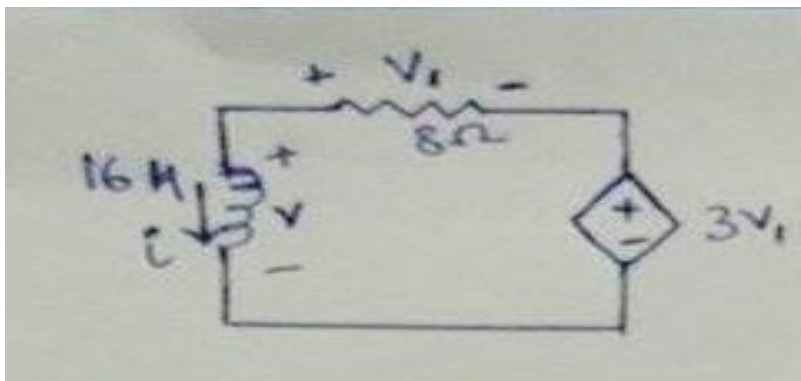**After  $t \geq 0$  :**  $V_s = 0$ , so circuit looks like:



By KVL in this loop :

$$-3V_1 + V - V_1 = 0$$

$$V = 4V_1$$

$$V_1 = 8i$$

$$\text{So, } V = -32i$$

$$L \frac{di}{dt} = -32i$$

$$\int \frac{di}{i} = \int -2dt + \ln C$$

$$i = Ce^{-2t}$$

$$\text{At } t=0, i(0) = 1.5 \text{ amps}$$

$$\text{So, } i = 1.5e^{-2t} \text{ amp}$$

Hence,

$$\text{When } t < 0 \quad i = 1.5 \text{ amp}$$

$$t \geq 0 \quad i = 1.5e^{-2t} \text{ amp}$$

for voltage


$$\text{when } t < 0 \quad V = 0 \text{ volts}$$

$$t \geq 0 \quad V = 16 \frac{d}{dt} [1.5e^{-2t}]$$

$$V = (-) * 16 * 1.5 * 2e^{-2t}$$

$$V = -48e^{-2t} \text{ volts}$$

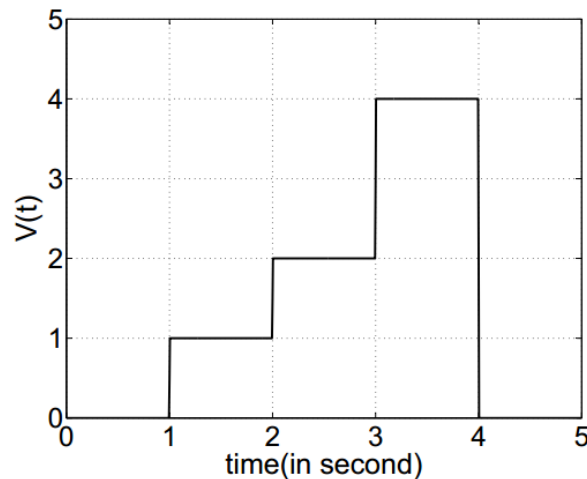2) The staircase input voltage wave form shown in Fig. (a) is applied across a series LR circuit consisting of  $R=1\Omega$  and  $L=1H$ . Find the current through the circuit.



**Sol:-** The given waveform is the summation of four unit step function

$$V(t) = u(t-1) + u(t-2) + 2u(t-3) - 4u(t-4)$$

$$= V_a + V_b + V_c + V_d$$

For RL ckt. Current  $i_L$  for  $u(t)$  is given by

$$i(t) = I_0 \left(1 - e^{-\frac{t}{\tau}}\right) u(t) \quad \text{where} \quad \tau = \frac{L}{R} = 1$$

$$I_0 = \frac{V}{R}$$

**for  $V_a$**   $I_0=1$  A  $i_{La}(t) = (1 - e^{-(t-1)})u(t-1)$

**for  $V_b$**   $I_0=1$  A  $i_{Lb}(t) = (1 - e^{-(t-2)})u(t-2)$

**for  $V_c$**   $I_0=2$  A  $i_{Lc}(t) = 2(1 - e^{-(t-3)})u(t-3)$


**for  $V_d$**   $I_0=-4$  A  $i_{Ld}(t) = -4(1 - e^{-(t-4)})u(t-4)$

So, the total current due to this complete wave form would be

$$i_L(t) = i_{La}(t) + i_{Lb}(t) + i_{Lc}(t) + i_{Ld}(t)$$

## TUTORIAL 2

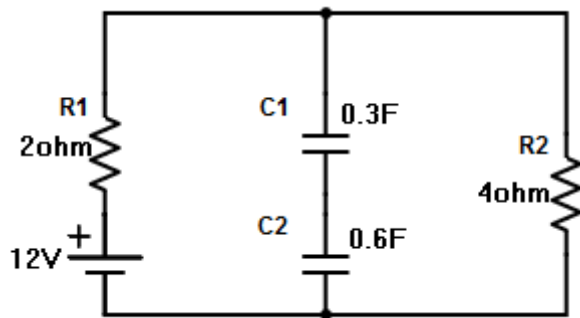3) **Q1)** Given  $V_{C1}(0^-) = 6$  and  $V_{C2}(0^-) = 24$ , Find  $V_o$ :



**Solution:**

**At  $t \geq 0$**

$$V_o(0^-) = V_{C1}(0^-) + V_{C2}(0^-)$$

$$V_o(0^-) = 24 + 6 = 30 \text{ volts}$$

$$V_o(0^-) = V_o(0^+) = 30 \text{ volts}$$




$$V_o = (\text{Initial value} - \text{Final value})e^{\frac{-t}{\tau}} + (\text{Final value})$$

$$= [V_o(0^+) - V_o(0^-)]e^{\frac{-t}{\tau}} + [V_o(+\infty)] \quad (1)$$

**Final value at  $t = +\infty$**

$$V_o(+\infty_o) = \frac{12 * 4}{4 + 2} = 8 \text{ volts}$$

**Time constant ( $\tau$ )**

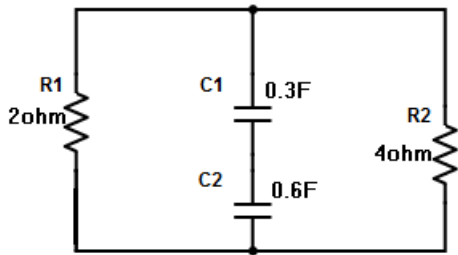

$$C_{eq} = \frac{0.6 * 0.3}{0.3 + 0.6} = 0.2F$$


$$R_{eq} = \frac{2 * 4}{2 + 4} = \frac{4}{3} \text{ ohms}$$

$$\tau = R_{eq} C_{eq} = 0.266 \text{ seconds}$$


**Hence, by (1)**

$$V_o = (22) e^{\frac{-t}{0.266}} + 8$$

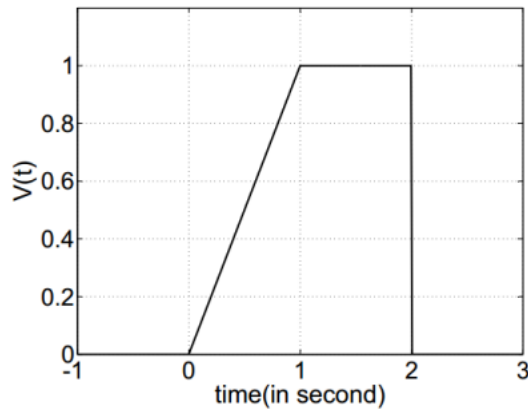4) The input voltage wave form shown in Fig. (a) is applied across a RC circuit shown in Fig. (b). Find the output voltage across the capacitor C. Plot  $i_c(t)$ ,  $v_c(t)$ .



(a)

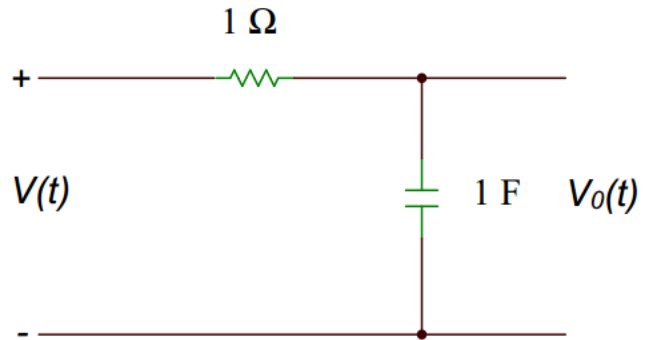

(b)

**Sol:-**  $V(t) = t$  for  $0 < t \leq 1$  Region 1  
 $= 1$  for  $1 < t \leq 2$  Region 2  
 $= 0$  otherwise Region 3

As  $t < 0$   $V(t) = 0$ , so for  $t < 0$  ckt. was in steady state so  $V_c(0_-) = 0 = V_c(0_+)$

For Region 1  $V(t) = t$ .

using KVL  $V_R + V_C = V(t)$

$$\text{or, } Ri + \frac{1}{C} \int i dt = V(t)$$

$$\frac{di}{dt} + i = \frac{dV}{dt} \quad \text{as } R=1\Omega \text{ and } C=1F$$

$$\frac{di}{dt} + i = \frac{dV}{dt} \quad \text{as } V(t)=t \text{ so } \frac{dV}{dt} = 1$$

So, the sol.  $i = 1 + K_1 e^{-t}$   $K_1 = \text{const.}$

at  $t=0$   $i(0)=0$  so,  $0 = 1 + K_1$  so,  $K_1 = -1$

so,  $i(t) = 1 - e^{-t}$  .....(1)

as,  $V_c = \frac{1}{C} \int i dt$  so,  $V_c = t + e^{-t} + K_2$

as,  $V_c(0)=0$  so,  $K_2 = -1$ . So,  $V_c(t) = t - 1 + e^{-t}$  .....(2) Reg. 1

For Region 2 using KVL  $V_R + V_L = V(t)$

$$Ri + \frac{1}{C} \int i dt = V(t)$$

$$\frac{di}{dt} + i = \frac{dV}{dt}$$

$$\frac{di}{dt} + i = 0 \quad \text{as } V(t)=1 \quad \text{so} \quad \frac{dV}{dt} = 0$$

So,  $i = K_3 e^{-t}$

For this region at  $t=1$   $i(1) = (1 - e^{-1}) = K_3 e^{-1}$  or,  $K_3 = (e - 1)$

So,  $i = (e - 1)e^{-t}$  .....(3)

as,  $V_c = \frac{1}{C} \int i dt$  so,  $V_c = -(e - 1)e^{-t} + K_4$

at  $t=1$   $V_c(1) = e^{-1}$

so,  $e^{-1} = -(e - 1)e^{-1} + K_4$  or,  $e^{-1} = -1 + e^{-1} + K_4$

so,  $K_4=1$ .  $V_c(t) = 1 + e^{-t} - e^{-(t-1)}$  .....(4) for Reg. 2



For Region 3 as  $V(t)=0$  for this region so  $V_c(t) = V_0 e^{-t}$

so  $V_c(2-) = V_c(2+) = 1 + e^{-2} - e^{-1}$

so, at  $t=2$   $(1 + e^{-2} - e^{-1}) = V_0 e^{-2}$  so,  $V_0 = e^2 - e^1 + 1$

$$V_c(t) = (e^2 + 1 - e)e^{-t}$$

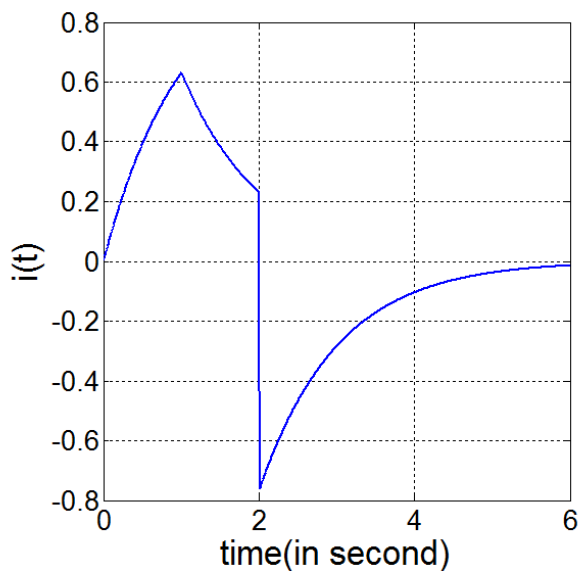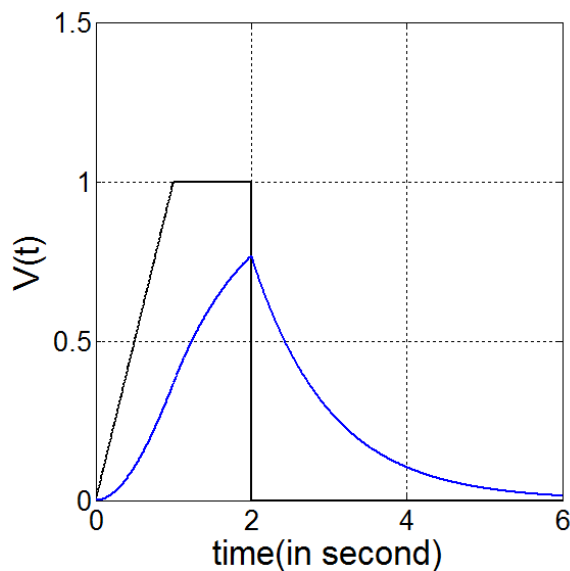or,  $V_c(t) = (e^{-t} - e^{-(t-1)} + e^{-(t-2)})$



4) The given signal can be written as

$$\begin{aligned} V(t) &= t u(t) - (t-1)u(t-1) - u(t-2) \\ &= V_a + V_b + V_c \end{aligned}$$

For  $V_a$  for CR ckt we know

$$\frac{dV_C}{dt} + \frac{V_C}{RC} = \frac{V}{RC}$$

As here  $R=1\Omega$  and  $C=1\text{ F}$  so  $RC=1$ .

So eq. becomes  $\frac{dV_C}{dt} + V_C = V$

As we know the sol. of  $\frac{dx}{dt} + ax(t) = f(t)$

is  $x(t) = e^{-at} \int e^{at} f(t) dt + Ae^{-at}$

so here  $V_{ca}(t)$  will be  $V_{ca}(t) = (t-1) + Ae^{-t}$

at  $t=0$   $V_c(0)=0$  so  $A=1$  So  $V_{ca}(t) = t - 1 + e^{-t}$ ,

For  $V_b$   $V_b = -(t-1)u(t-1) = -t'u(t')$  where  $t' = t-1$

we know the response for  $t u(t)$

so, the response for  $-t'u(t') = -[t' - 1 + e^{-t'}]$

now, put  $t' = t-1$ ; so,  $V_{bc} = -[(t-1) - 1 + e^{-(t-1)}]$   
 $= -t + 2 - e^{-(t-1)}$

For  $V_c$  for  $V u(t)$  we know  $V_C(t) = V \left(1 - e^{-\frac{t}{RC}}\right)$


so here for  $-u(t-2)$   $V_{Cc}(t) = -(1 - e^{-(t-2)})$

So, the final solution for  $V_c(t)$  will be

$$V_c = V_{ca}(t)u(t) + V_{cb}(t)u(t-1) + V_{cc}(t)u(t-2)$$




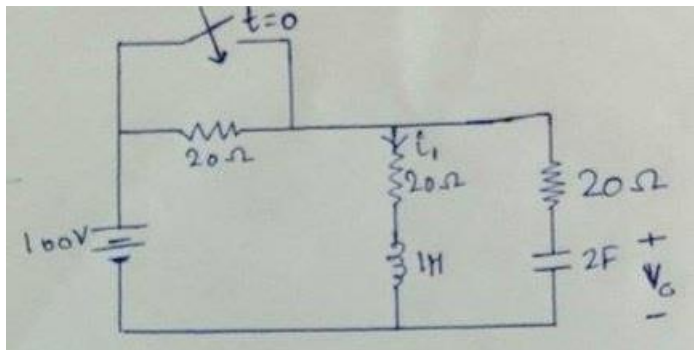5) **FIND**  $\frac{di_1}{dt}(0^+)$ ,  $\frac{dv_c}{dt}(0^+)$ ,  $i_1(0^+)$ ,  $v_c(\infty)$  in the below figure



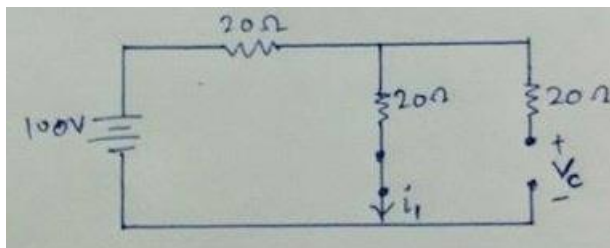**Solutions:**

**At  $t=0^-$ :** Inductor is short circuited and capacitor is open circuited




$$i_1(0^-) = \frac{100}{40} = 2.5 \text{ A} = i_1(0^+)$$

$$V_c(0^-) = 100 - 50 = 50 \text{ Volts} = V_c(0^+)$$

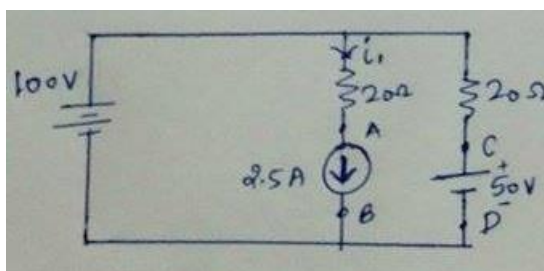**At  $t=0^+$**

Replace inductor by a current source of value  $i_1(0^+)=2.5 \text{ A}$  and capacitor by voltage source of value  $V_c(0^+)$



$$V_{20 \text{ ohm}} = 50 \text{ volts}$$

$$i_{20\ ohm} = \frac{50}{20} = 2.5A$$

$$50 = V_L = L \frac{di}{dt} = 1 \frac{di}{dt}$$

$$50 = \frac{di}{dt}(0^+) \text{ A/sec}$$


Also,

$$i_c = C \frac{dv_c}{dt}$$

$$2.5 = i_c = 2 * \frac{dv_c}{dt}$$

$$\frac{dv_c}{dt}(0^+) = 1.25 \text{ volts/sec}$$

**At  $t = +\infty$**

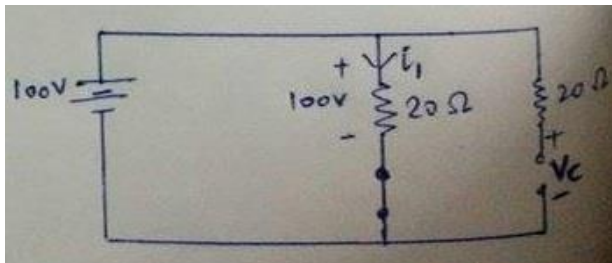


$$i_1 = \frac{100}{20} = 5A$$


$$i_1(+\infty) = 5A$$

$$v_c(+\infty) = 100 \text{ volts}$$

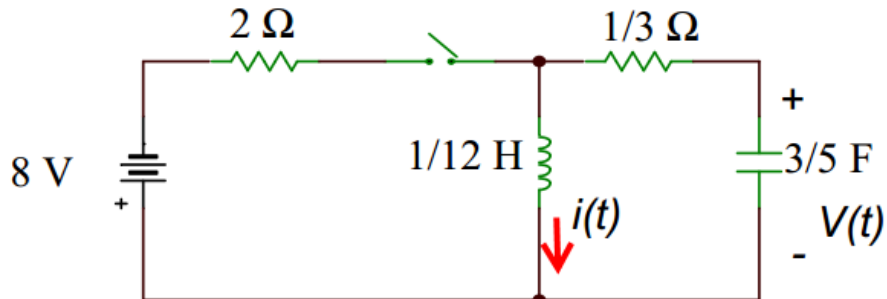6) For the circuit shown in the Fig.6 , the switch opens at time  $t = 0$ . Find  $V(t)$  and  $i(t)$  for all time.




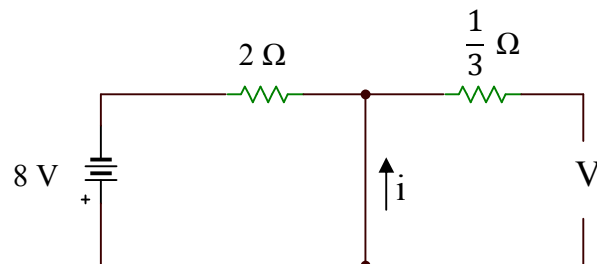**Sol:-** for  $t < 0$  ckt. was in steady state so inductor was short and capacitor was open and the ckt. looks like



so  $i = 4A$  and  $V = 0V$

for  $t > 0$  the ckt. looks like

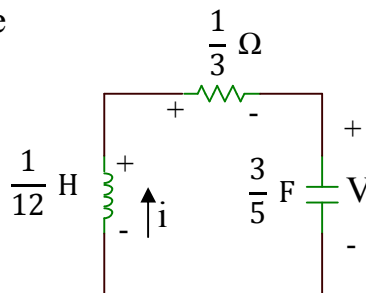

$$\text{so, } L \frac{di}{dt} + Ri + V = 0 \quad \text{or} \quad \frac{1}{12} \frac{di}{dt} + \frac{1}{3} i + V = 0 \quad \dots\dots\dots(1)$$

$$\text{as, } i = C \frac{dV_C}{dt} \quad \text{or} \quad i = \frac{3}{5} \frac{dV_C}{dt} \quad \text{so eq. (1) becomes}$$

$$\frac{1}{20} \frac{d^2V}{dt^2} + \frac{1}{5} \frac{dV}{dt} + V = 0 \quad \text{or} \quad \frac{d^2V}{dt^2} + 4 \frac{dV}{dt} + 20V = 0$$

$$\text{so, } \alpha = 2 \quad \text{and} \quad \omega_n^2 = 20 \quad \text{so, roots are } s = -\alpha \pm \sqrt{\alpha^2 - \omega_n^2} = -2 \pm 4j$$

$$V_C(t) = e^{-2t}(A_1 \cos 4t + A_2 \sin 4t)$$

at  $t=0$   $V_C(0) = 0$ ;     so,  $A_1 = 0$ .      $V_C(t) = A_2 e^{-2t} \sin 4t$


again  $i_C = C \frac{dV_C}{dt} = \frac{3}{5} A_2 [-2e^{-2t} \sin 4t + 4e^{-2t} \cos 4t]$

at  $t=0$   $i_C(0) = i_L(0+) = i_L(0-) = 4$      so  $\frac{3}{5} A_2 4 = 4$      or  $A_2 = \frac{5}{3}$


so,  $V_C(t) = \frac{5}{3} e^{-2t} \sin 4t$

then  $i_C(t) = C \frac{dV_C}{dt} = \frac{3}{5} \frac{5}{3} [-2e^{-2t} \sin 4t + 4e^{-2t} \cos 4t]$   
 $= e^{-2t} [4 \cos 4t - 2 \sin 4t]$

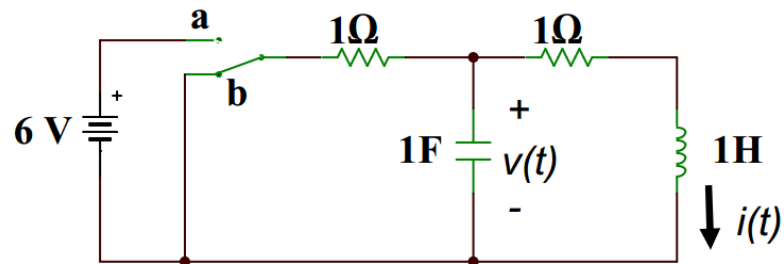7) For the circuit shown in fig. switch was moved from position *a* to position *b* at time  $t=0$ ; Find  $i(t)$  and  $v(t)$  for  $t>0$ .




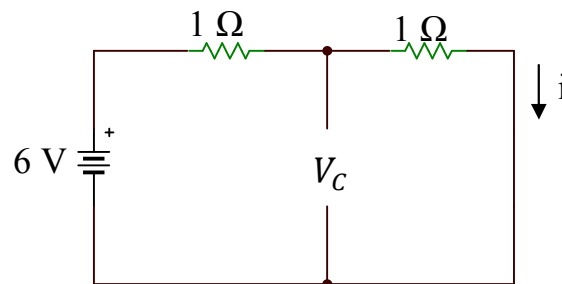**Sol:-** for  $t<0$  ckt. was in steady state and it looks like



$$\text{so } V_C = 3V = V_C(0^-) \text{ and } i = 3A = i_L(0^-)$$

for  $t>0$  ckt. looks like

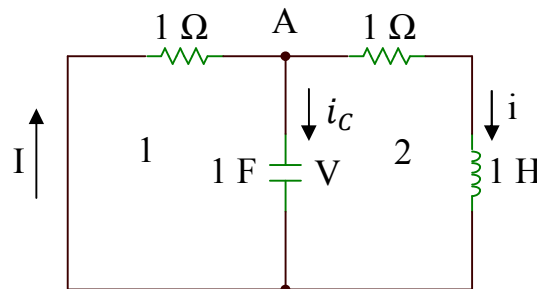

$$\text{KVL in loop 2 gives } V = Ri + L \frac{di}{dt} \quad \text{or } V = i + \frac{di}{dt} \quad \dots\dots\dots(1)$$

$$\text{applying KCL at node A we get } I = i_C + i$$

$$\text{or, } \frac{0-V}{1} = C \frac{dV}{dt} + i \quad \text{or } -V = \frac{dV}{dt} + i$$

$$\text{putting V from eq. (1)} \quad -i - \frac{di}{dt} = \frac{di}{dt} + \frac{d^2i}{dt^2} + i \quad \text{or } \frac{d^2i}{dt^2} + 2\frac{di}{dt} + 2i = 0$$

$$\text{so } \alpha = 1 \text{ and } \omega_n^2 = 2 \quad \text{so, roots are } s = -\alpha \pm \sqrt{\alpha^2 - \omega_n^2} \\ = -1 \pm j$$

so, sol. of current  $i(t)$  is  $i(t) = e^{-t}(A_1 \cos t + A_2 \sin t)$   
 at  $t=0$ ,  $i(0)=3$ , so  $A_1 = 3$  then  $i(t) = e^{-t}(3 \cos t + A_2 \sin t)$

from eq. (1) we  $V(t) = i + \frac{di}{dt}$


$$= e^{-t}(3 \cos t + A_2 \sin t) - e^{-t}(3 \cos t + A_2 \sin t) + e^{-t}(A_2 \cos t - 3 \sin t)$$

$$= e^{-t}(A_2 \cos t - 3 \sin t)$$

at  $t=0$   $V(0)=3$  so  $A_2=3$

so, *current*  $i(t) = 3e^{-t}(\cos t + \sin t)$   
*voltage*  $v(t) = 3e^{-t}(\cos t - \sin t)$

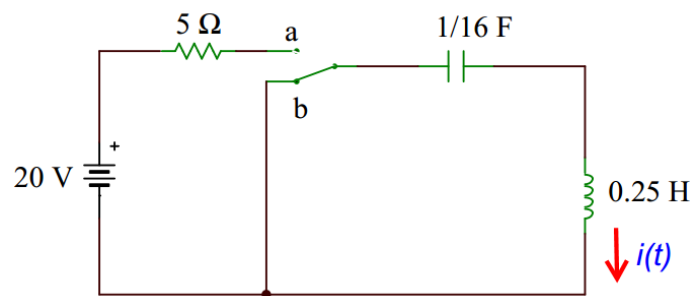8) For the circuit shown in fig. switch was moved from position *a* to position *b* at time  $t=0$ ; Find  $i(t)$  for  $t>0$ .



**Sol:-** for  $t<0$  ckt. was in steady state

so,  $i(0^-) = 0 \text{ A}$  and  $V_C(0^-) = 20 \text{ V}$

for  $t>0$  ckt. looks like as shown in the problem figure

so,  $V_C + V_L = 0$  or,  $CV_C + LV_L = 0$

$$C \frac{dV_C}{dt} + L \frac{dV_L}{dt} = 0 \quad \text{or,} \quad i + C \frac{d}{dt} \left( L \frac{di}{dt} \right) = 0$$

$$\text{or,} \quad \frac{d^2 i}{dt^2} = -\frac{1}{LC} i = -64i \quad \text{so,} \quad i(t) = A_1 \cos 8t + A_2 \sin 8t$$

$$i(0^+) = i_L(0^-) = 0 \quad \text{so,} \quad A_1 = 0 \quad \text{so,} \quad i(t) = A_2 \sin 8t \quad \dots\dots\dots(1)$$

$$\text{at } t = 0^+ \quad \text{so,} \quad V_C(0^+) + V_L(0^+) = 0; \quad \text{so,} \quad V_L(0^+) = -V_C(0^+) = -20$$

$$\text{so,} \quad V_L(0^+) = L \left. \frac{di}{dt} \right|_{t=0^+} = -20; \quad \text{so,} \quad \left. \frac{di}{dt} \right|_{t=0^+} = -80$$

$$\text{so, from eq. (1)} \quad \frac{di}{dt} = 8A_2 \cos 8t$$

$$\text{at } t=0^+ \quad -80=8A_2 \quad A_2=-10 \quad \text{so, current } i(t)=-10\sin 8t$$