


Tutorial 6

Part-1

Note: All Diodes have a forward drop of 0.7V.

1) Given that aluminum wires can tolerate current densities upto 1 MA/cm^2 , find the maximum values of the current through and the voltage across the wire for a 500 μm long, 3 μm wide and 1 μm thick aluminium. (Resistivity of Aluminium is $2.7 \times 10^{-8} \text{ ohm-meter}$).

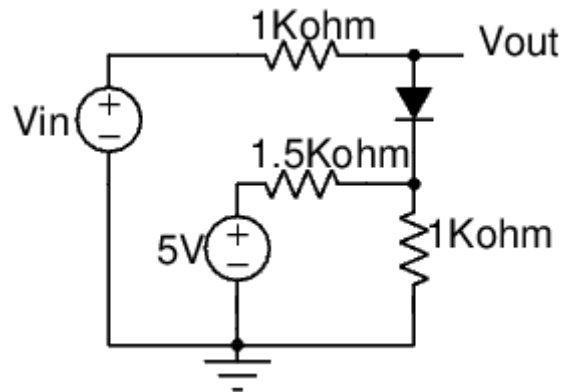2) For the circuit shown, measure V_{out} for a) $V_{in} = 1\text{V}$ b) $V_{in} = 3\text{V}$




3) In the circuit diagram, the zener diode has $V_Z = 5\text{V}$.


a) Measure V_{RL} , I_Z and I_{RL} for $R_L = 60 \text{ ohms}$.

b) Measure V_{RL} , I_Z and I_{RL} for $R_L = 120 \text{ ohms}$.

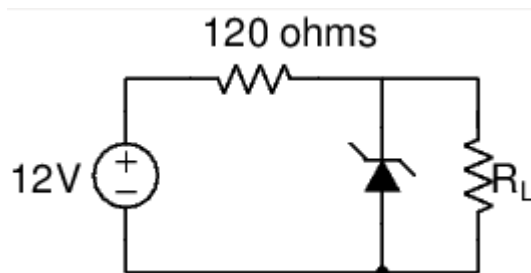
c) Given the maximum power rating of zener is 150mW. Find a range of value for R_L for which the zener diode is operational.



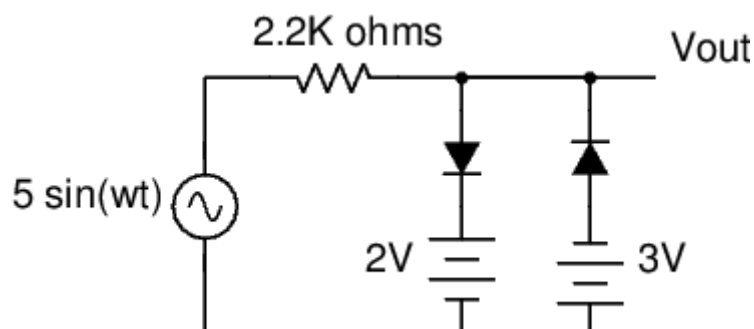4) Plot the output voltage and the diode currents for the network with an input of $5 \sin(\omega t)$.




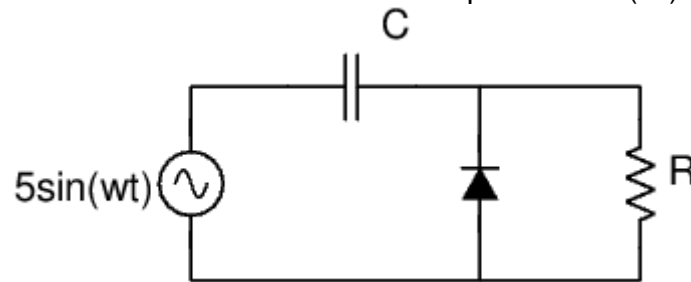5) Plot the output waveform for the network with an input of $5\sin(\omega t)$ at steady state.



Part-2 (NGSpice)

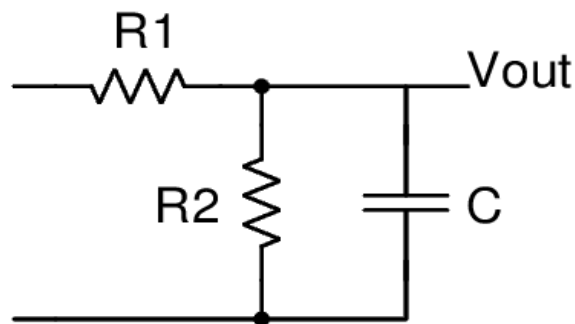1) For the circuit shown below $R1 = R2 = 10\text{Kohms}$ and $C = 1\mu\text{F}$. Perform the following.




a) With a step input of 5V, measure the time needed to charge the output to 99% of the final value using NGSpice ?

b) Obtain the time constant of the circuit theoretically. How does the time obtained in part a compare with $5 \times \text{time constant}$?


c) Find the cut-off frequency of the circuit using ac analysis in NGSpice ?

d) How does this cut-off frequency relate with the time constant that was calculated in part b?

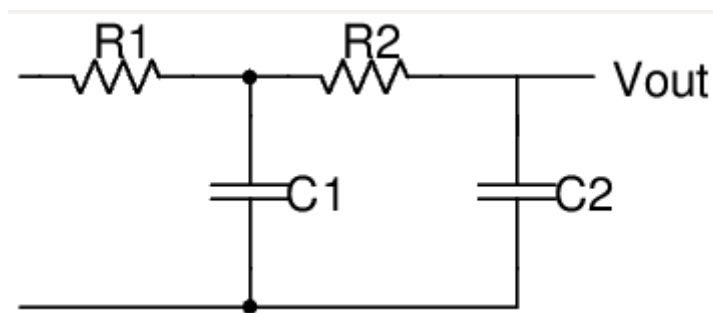2) For the circuit shown below, with $R1 = R2 = 10\text{Kohms}$ and $C1 = C2 = 1\mu\text{F}$. Repeat part a, b, c and d of problem 1 for this circuit.




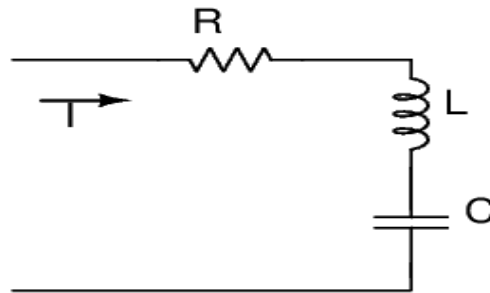3) A series RLC circuit is shown in the figure below with $R=10\text{k}\Omega$, $L=25\text{mH}$ and $C=1\mu\text{F}$.



- Find the resonant frequency of the circuit by simulation in NGSpice.
- Find the Bandwidth of the network from simulation. Hence obtain the Quality factor from the information available.
- Apply a sinusoidal input with 0.5V amplitude and resonant frequency as the input frequency to the circuit. Measure the voltage across capacitor and inductor at steady state and compare the voltage with the Quality-factor that was obtained in part b.

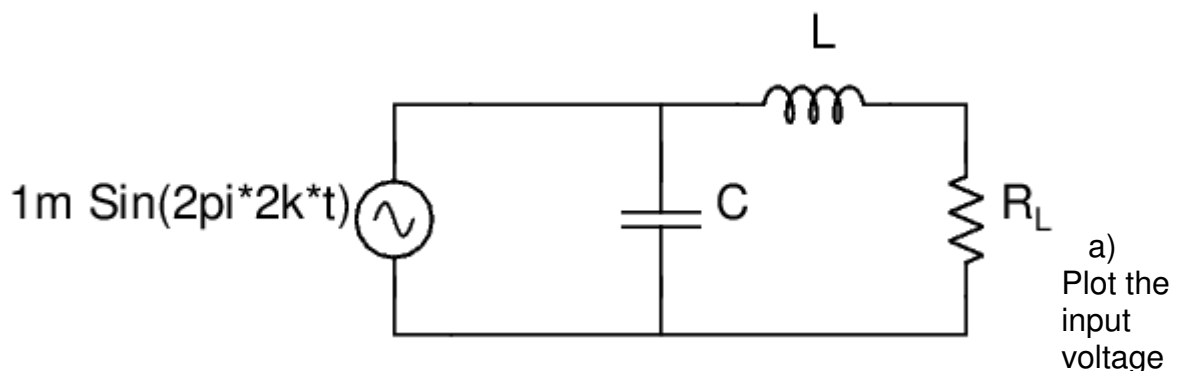4) Apply an input sinusoid of 1mV amplitude and 2kHz frequency to the circuit shown below. The values of $C=25.62\text{mF}$, $L=6.89\text{mH}$ and load $R_L = 50\Omega$.



and input current of the circuit in NGSpice. Is the impedance looking in real or complex ? How does it relate to the load resistance R_L ? (Impedance matching).

- Plot the voltage across and current through the load in NGSpice. How much of the input power is being delivered to the load R_L ?

5) Generate the following waveform in NGSpice and apply this as an input to a series RC circuit with $R=1\text{Kohms}$ and $C=1\mu\text{F}$. Plot the output voltage across capacitor.

