

BJT Amplifiers (Analog Circuits)

EE 101

S. Lodha

Reference material: L. Bobrow's Book




Nobel Prize in Physics 2014



Isamu Akasaki, Hiroshi Amano and Shuji Nakamura

**EFFICIENT BLUE LIGHT-EMITTING DIODES LEADING
TO BRIGHT AND ENERGY-SAVING WHITE LIGHT SOURCES**


Blue LED

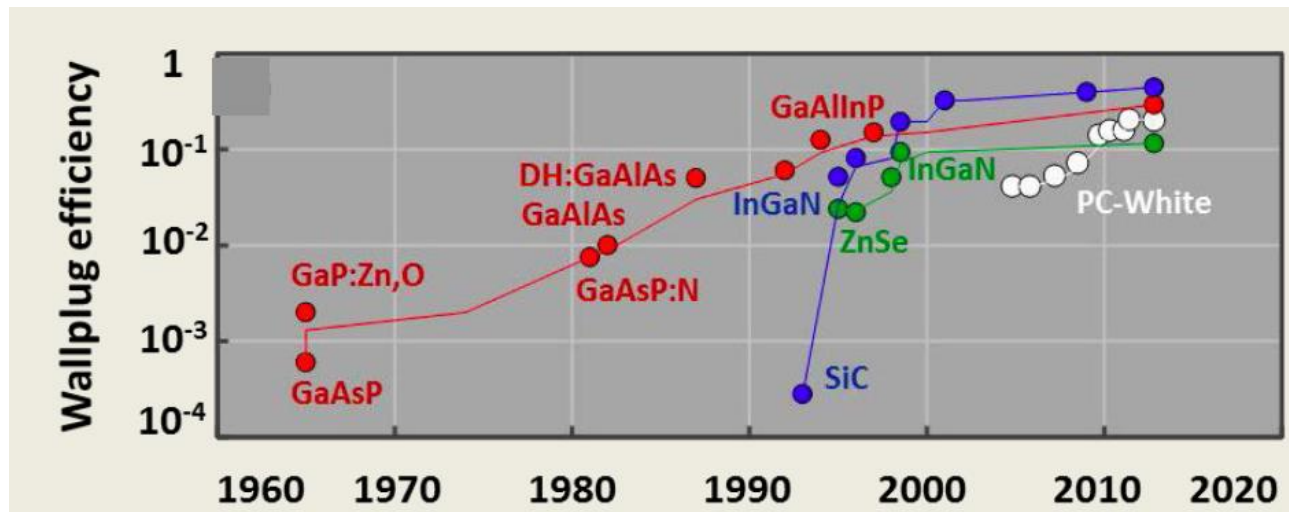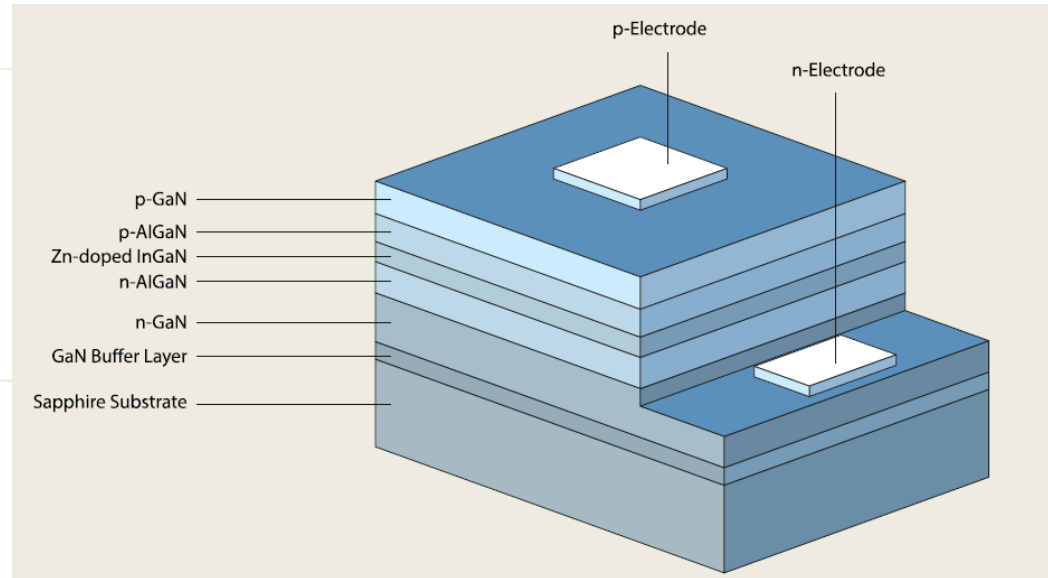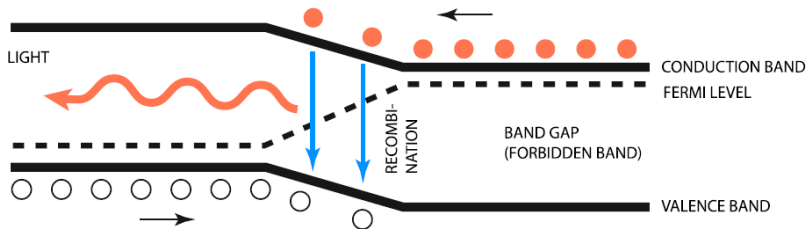

Impact

- Transformed entire lighting industry
 - 20-30% of electricity is used for lighting
 - Standard bulb → 16 lm/W (4% efficiency)
 - LED → 300 lm/W (50% efficiency)
 - 100,000 hour lifetime
- Other applications
 - Displays in electronics
 - Sensors etc.

BJT Amplifier: Collector Characteristics

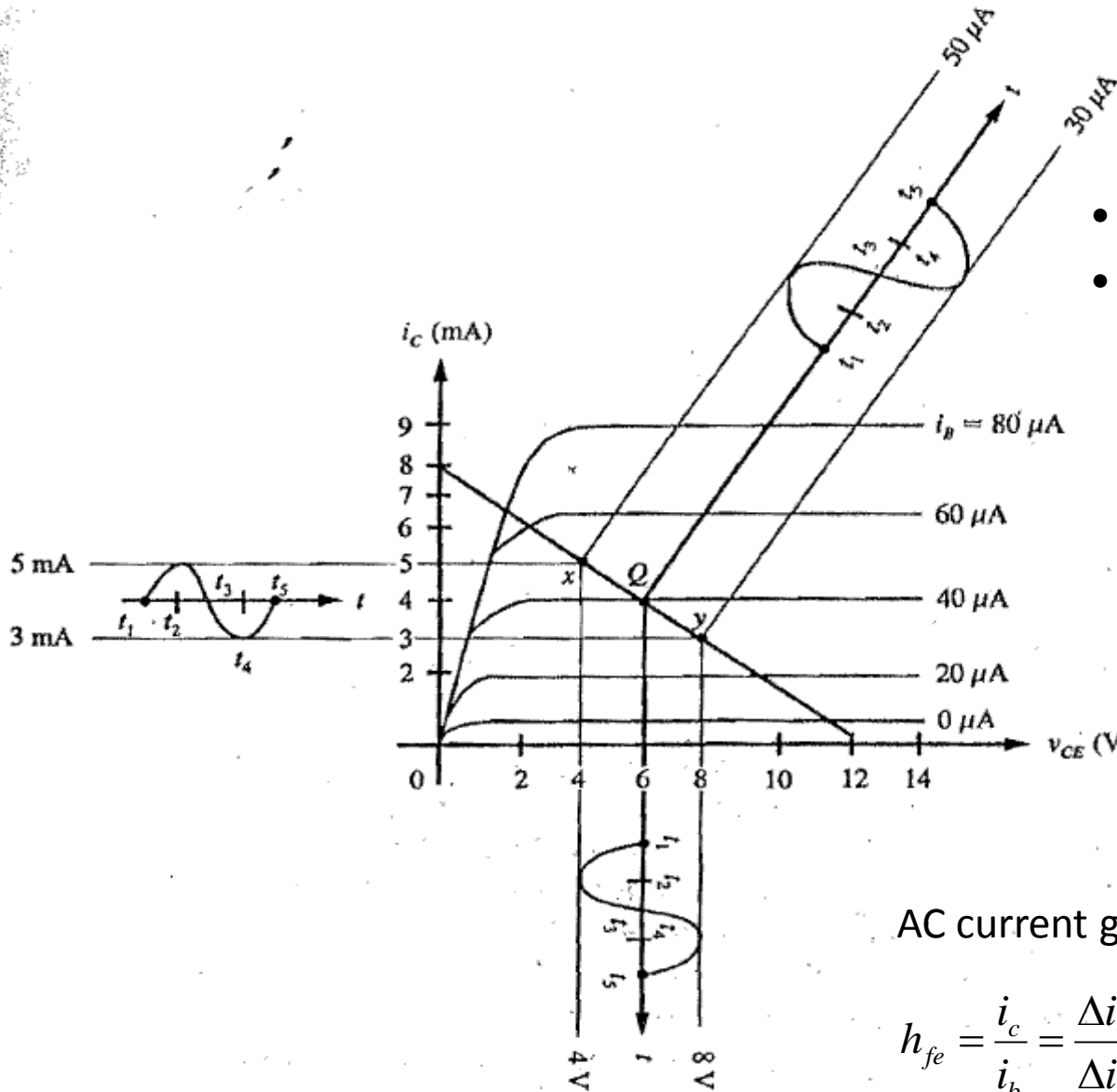

- Active region operation
- $Q \rightarrow$ quiescent operating point

$$i_C = I_{CQ} + i_c = 4 + \sin \omega t \text{ mA}$$

$$i_B = I_{BQ} + i_b = 40 + 10 \sin \omega t \mu A$$


$$v_{CE} = V_{CE} + v_{ce} = 6 - 2 \sin \omega t \text{ V}$$

AC current gain $h_{fe} = \beta_{ac}$

$$h_{fe} = \frac{i_c}{i_b} = \frac{\Delta i_C}{\Delta i_B} = \frac{i_{Cx} - i_{Cy}}{i_{Bx} - i_{By}} = \frac{(5 - 3) \times 10^{-3}}{(50 - 30) \times 10^{-6}} = 100$$

DC biasing of BJT: Fixed Bias


Example 1

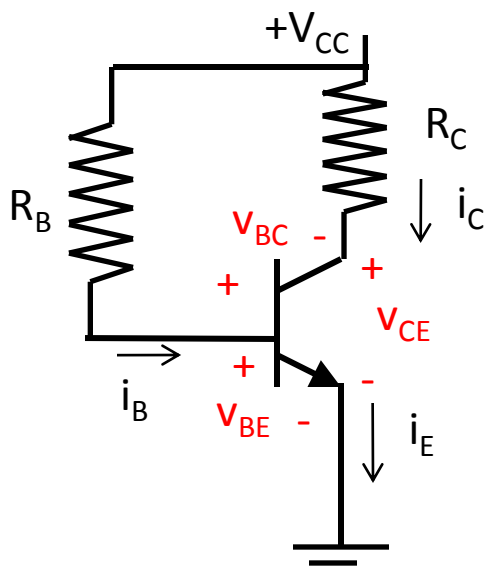

$$i_B = \frac{V_{CC} - v_{BE}}{R_B} \quad i_C = h_{FE} i_B$$

$$v_{CE} = -R_C h_{FE} i_B + V_{CC}$$

Example 2 (Voltage divider bias)

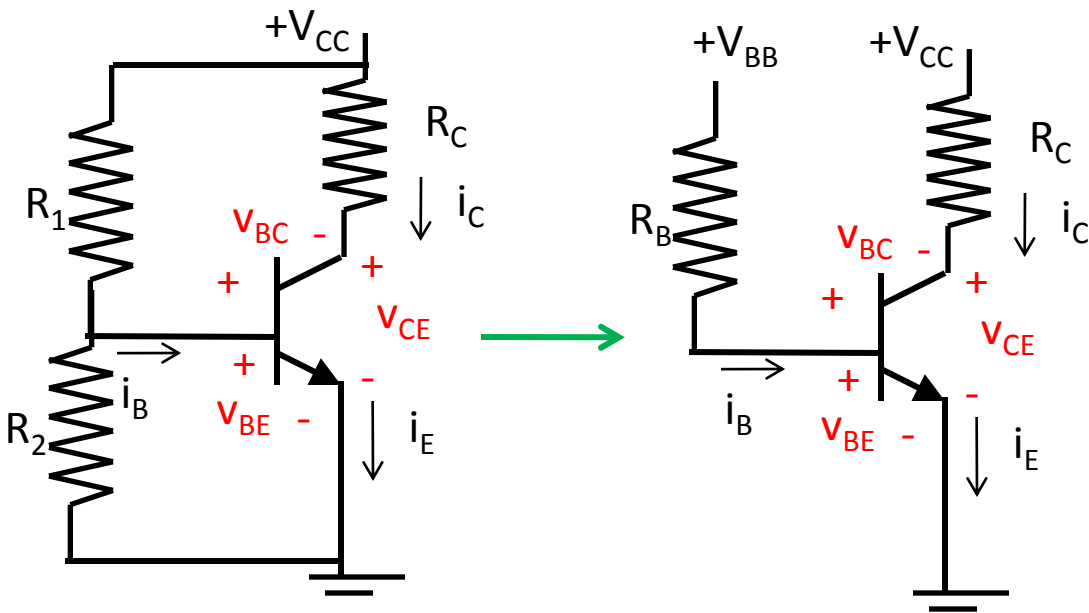


Thevenin
Equivalent

$$R_B = R_1 \parallel R_2$$

$$V_{BB} = V_{CC} (R_2 / R_1 + R_2)$$

- In fixed bias, variations (temperature, transistor-to-transistor) in h_{FE} can affect Q point
 - h_{FE} increases, i_C increases


DC biasing of BJT: Self-Bias

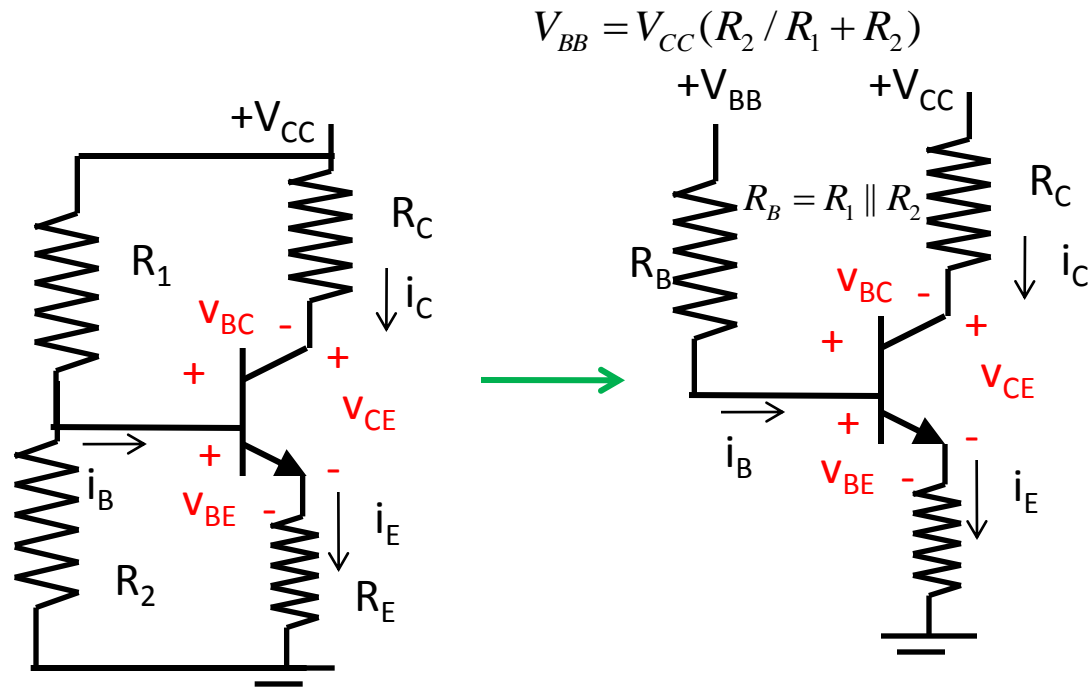

$$V_{BB} = R_B i_B + v_{BE} + R_E (i_B + i_C) \Rightarrow i_B = \frac{V_{BB} - v_{BE}}{R_B + (1 + h_{FE}) R_E}$$





- If h_{FE} increases $\rightarrow i_C$ tends to increase but i_B decreases and tends to decrease i_C
- **More stable** Q point, also called self-biasing circuit

How to add ac signal to DC bias?

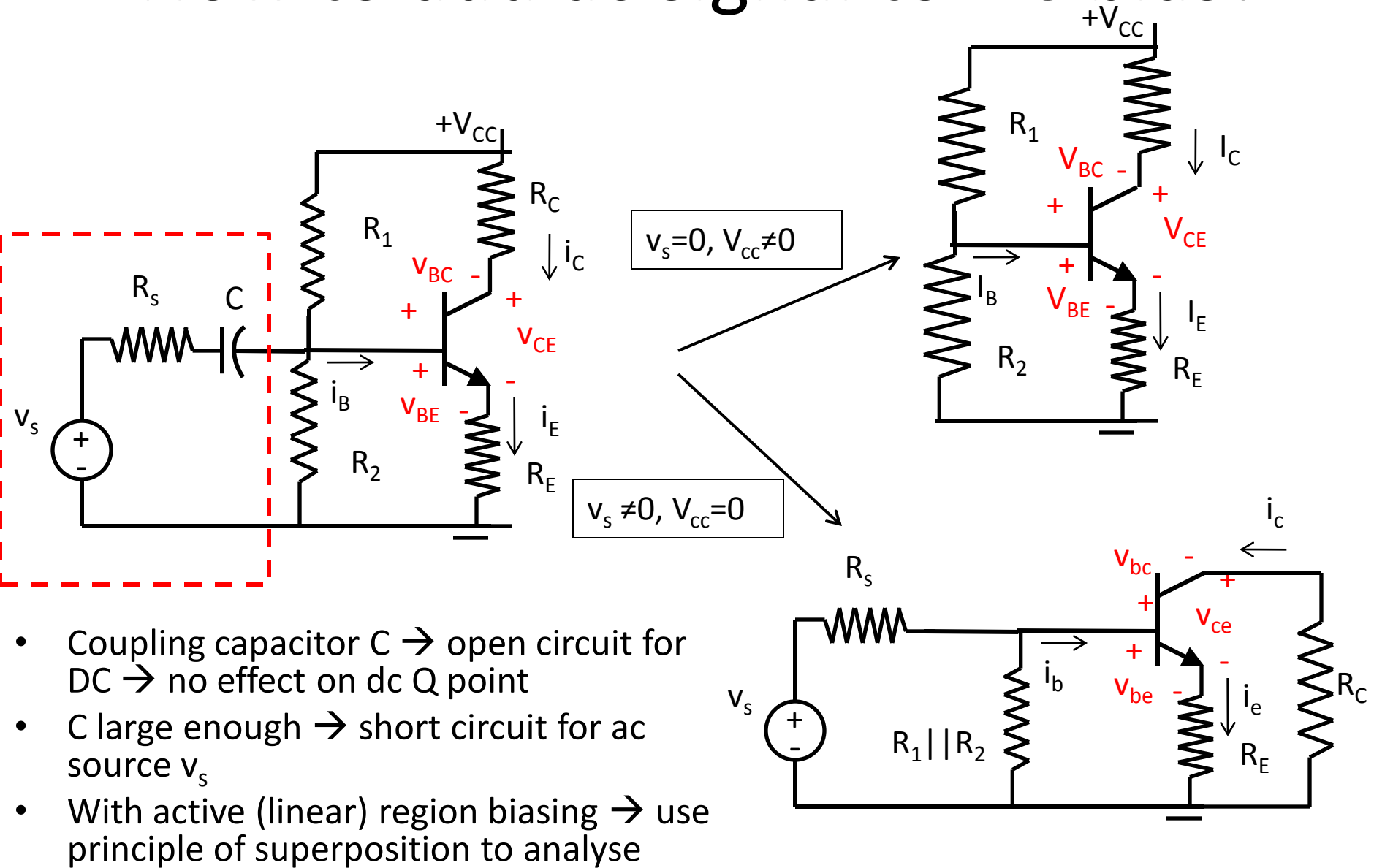


Small signal ac models

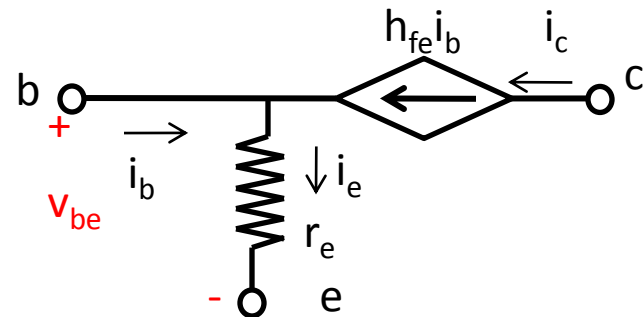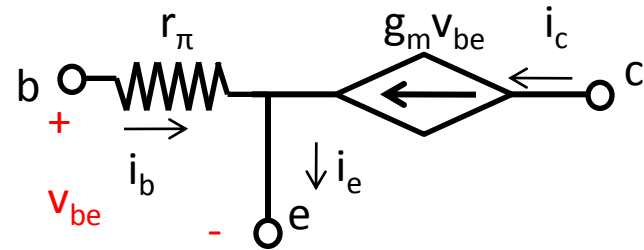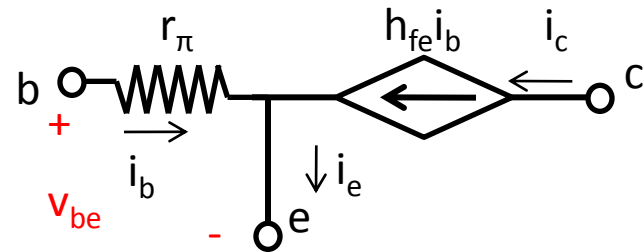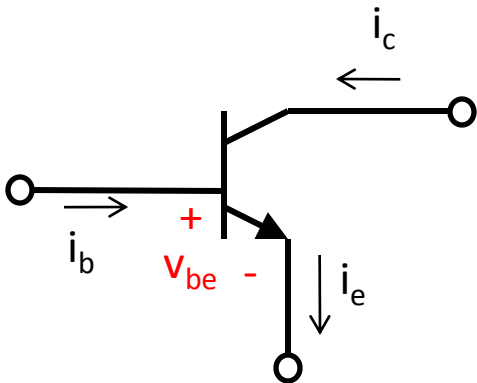- Ac signal is small such that
 - transistor operates in active mode
 - Non-linear effects/distortions can be ignored
 - o/p characteristics are linear and parallel



Small signal model

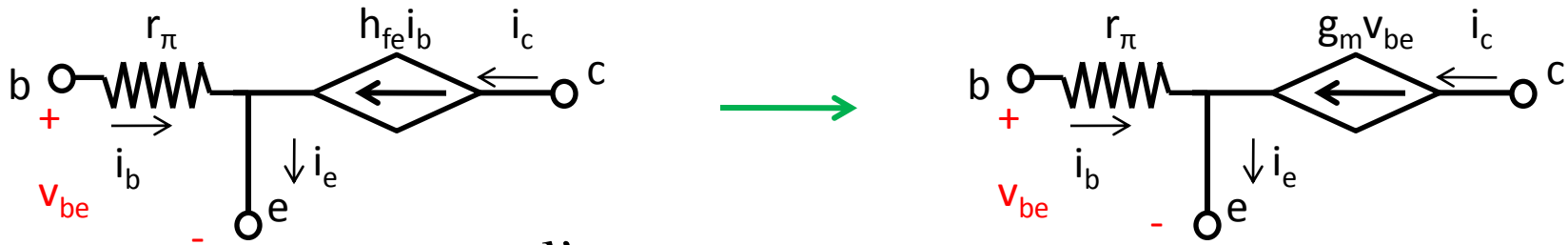


$$i_b = \frac{v_{be}}{r_\pi}$$

Ac base resistance = r_π

$$h_{fe} i_b = h_{fe} \frac{v_{be}}{r_\pi} = g_m v_{be}$$

Transconductance $g_m = h_{fe}/r_\pi$

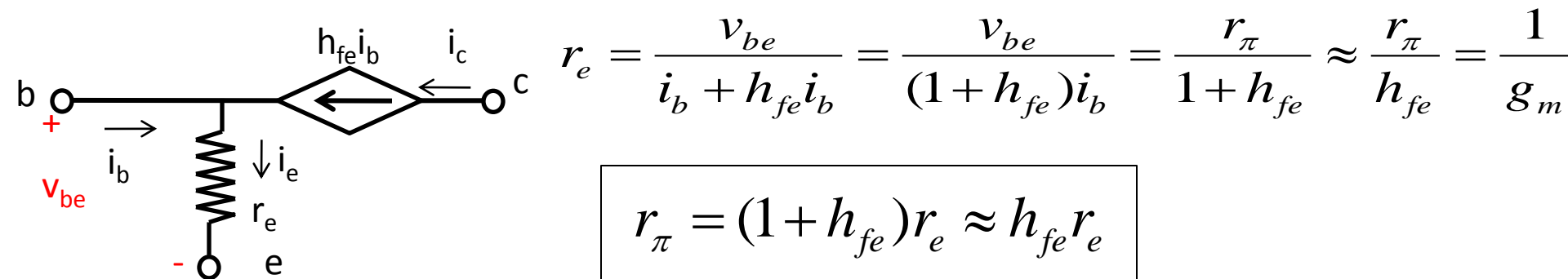

$$r_e = \frac{v_{be}}{i_b + h_{fe} i_b} = \frac{v_{be}}{(1 + h_{fe}) i_b} = \frac{r_\pi}{1 + h_{fe}} \approx \frac{r_\pi}{h_{fe}} = \frac{1}{g_m}$$

$$r_\pi = (1 + h_{fe}) r_e \approx h_{fe} r_e$$

g_m, r_π, r_e

For npn transistor in active mode

$$i_C = I_S (e^{v_{BE}/V_T} - 1) \approx I_S e^{v_{BE}/V_T}$$

$$di_C = d[I_S (e^{v_{BE}/V_T} - 1)] = \frac{1}{V_T} (I_S e^{v_{BE}/V_T}) dv_{BE} \approx \frac{i_C}{V_T} dv_{BE}$$

$$g_m = \frac{i_c}{v_{be}} = \frac{di_C}{dv_{BE}} = \frac{i_C}{V_T}$$

Biased at $i_C = I_{CQ}$,


$$g_m = \frac{I_{CQ}}{V_T}$$

$$r_e = \frac{1}{g_m} = \frac{V_T}{I_{CQ}}$$

$$r_\pi = h_{fe} r_e = \frac{h_{fe} V_T}{I_{CQ}}$$

At room temperature,
 $V_T = kT/q = 0.026 \text{ V}$

CE Amplifier: AC gain

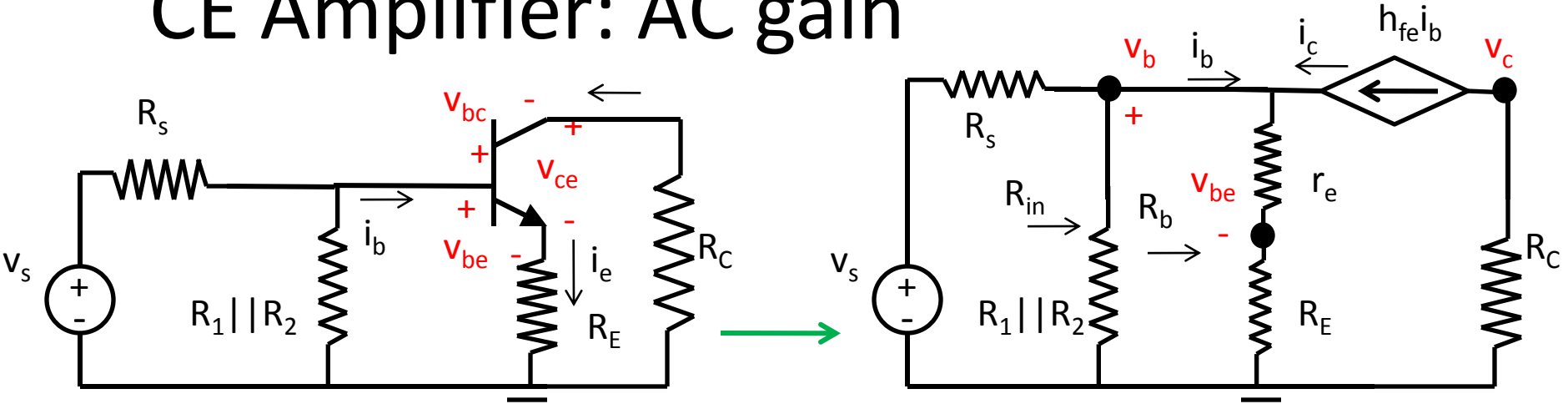

$$v_b = r_e (i_b + h_{fe} i_b) + R_E (i_b + h_{fe} i_b)$$

$$\Rightarrow R_b = \frac{v_b}{i_b} = (1 + h_{fe})(r_e + R_E) \approx h_{fe}(r_e + R_E)$$

R_b is the resistance between base and reference looking into the transistor

$$R_{in} = (R_1 \parallel R_2) \parallel R_b$$


R_{in} is the resistance between base and reference looking into the amplifier \rightarrow ac input resistance

$$A_v = \frac{v_c}{v_b} = \frac{-R_C h_{fe} i_b}{R_b i_b} = \frac{-R_C h_{fe}}{(1 + h_{fe})(r_e + R_E)} \approx \frac{-R_C}{r_e + R_E}$$

ac voltage gain A_v , v_c is 180 degrees out of phase w.r.t. v_b

- r_e is determined by Q point
- R_E can be decreased to increase gain, but will compromise stability

CE Amplifier: Bypass capacitor

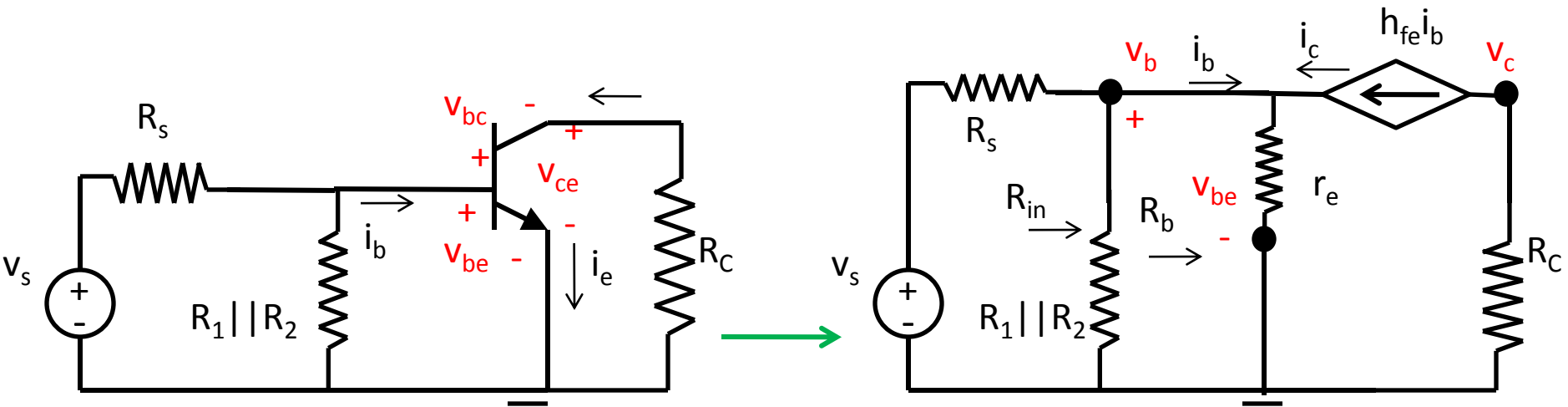

A bypass capacitor added in parallel to R_E with negligible impedance w.r.t R_E

-Does not affect dc conditions (open circuit, r_e unchanged)



-Short circuit for ac

$$A_v = \frac{v_c}{v_b} = \frac{-R_C h_{fe}}{(1 + h_{fe}) r_e} \approx \frac{-R_C}{r_e}$$

$$A_{vs} = \frac{v_c}{v_s} = \frac{v_c}{v_b} \frac{v_b}{v_s} = \frac{R_{in}}{R_{in} + R_s} A_v$$

ac voltage gain A_{vs} from source to output

CE Amplifier with load

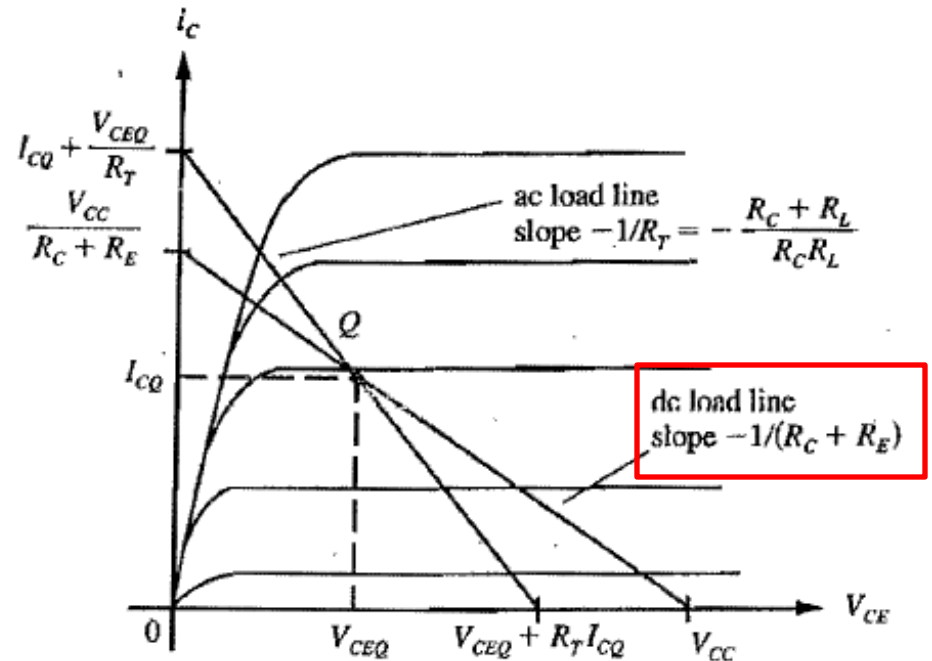
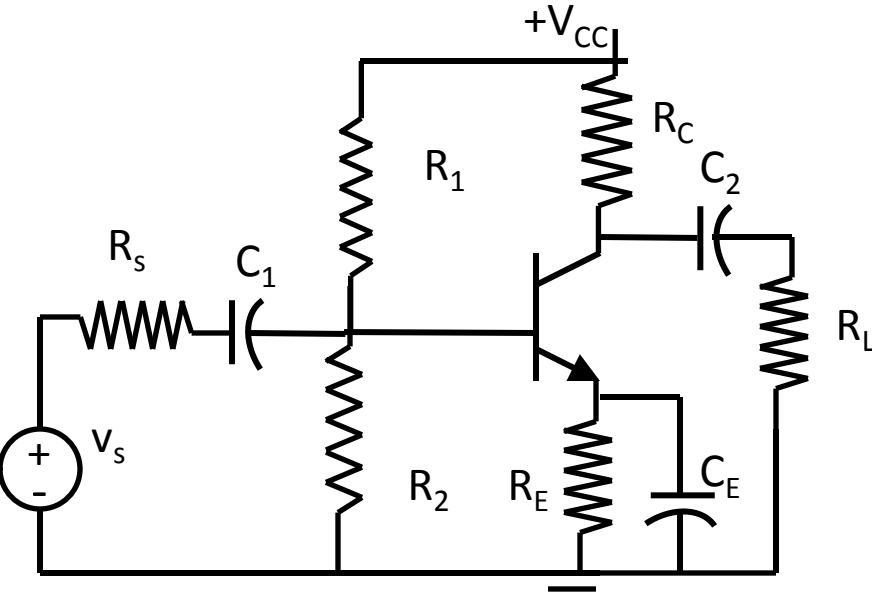


$$V_{CC} = R_C i_C + v_{CE} + R_E (i_B + i_C) \approx R_C i_C + v_{CE} + R_E i_C$$

$$\Rightarrow i_C = -\frac{1}{R_C + R_E} v_{CE} + \frac{V_{CC}}{R_C + R_E}$$

DC load line

AC load line

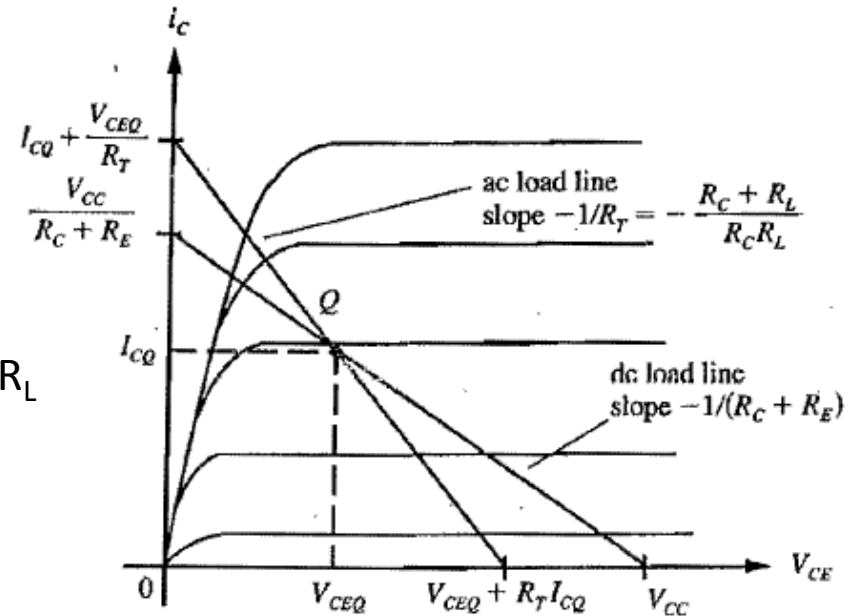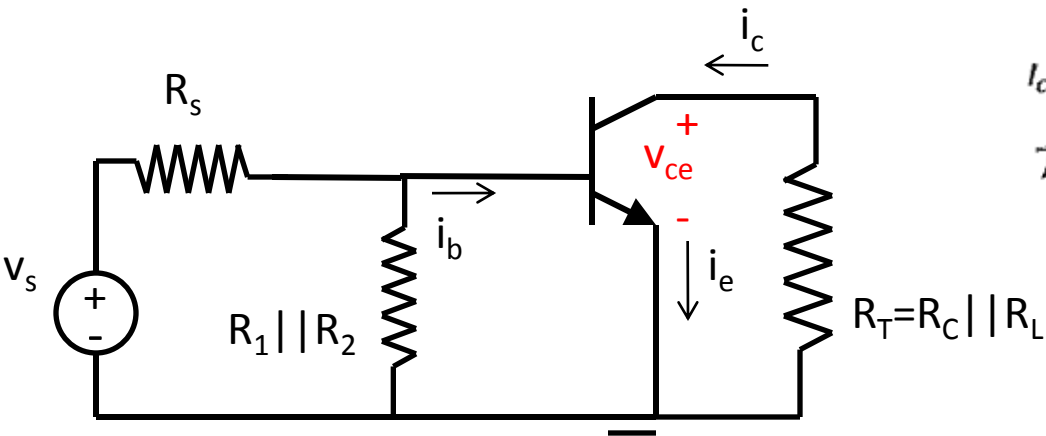

$$v_{CE} = V_{CEQ} + v_{ce}$$


$$i_C = I_{CQ} + i_c \Rightarrow i_c = i_C - I_{CQ}$$

$$v_{ce} = -R_T i_c$$

$$v_{CE} = V_{CEQ} - R_T (i_C - I_{CQ}) \Rightarrow i_C = -\frac{1}{R_T} v_{CE} + (I_{CQ} + \frac{V_{CEQ}}{R_T})$$

AC load line

Current gain

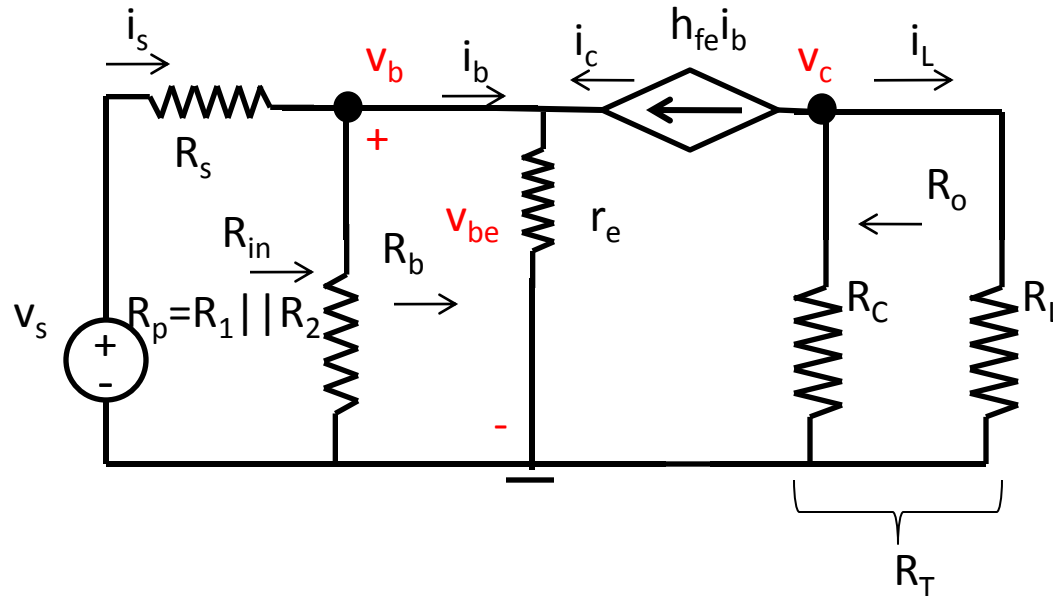


$$R_b = (1 + h_{fe})r_e \approx h_{fe}r_e \quad R_{in} = (R_1 \parallel R_2) \parallel R_b$$

$$A_v = -\frac{h_{fe}R_T}{(1 + h_{fe})r_e} \approx -\frac{R_T}{r_e} \quad A_i = \frac{i_L}{i_b} = \frac{-h_{fe}R_C}{R_C + R_L}$$

AC current gain

$$A_{is} = \frac{i_L}{i_s} = \frac{i_L}{i_b} \frac{i_b}{i_s} = \frac{A_i R_p}{R_p + R_b}$$


Output Resistance: R_o

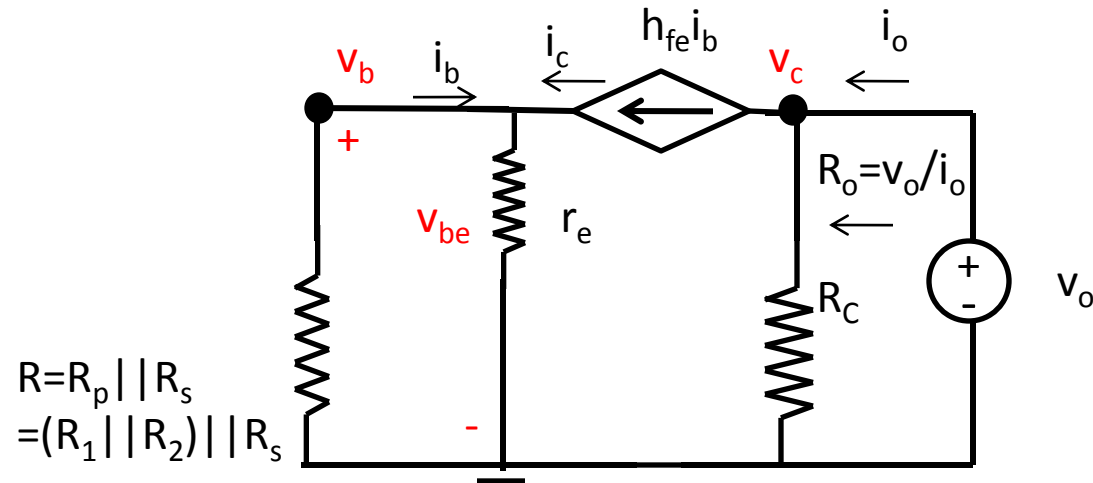


$$i_b + h_{fe}i_b = \frac{v_b}{r_e} \Rightarrow i_b = \frac{v_b}{(1 + h_{fe})r_e} = \frac{-Ri_b}{(1 + h_{fe})r_e} \Rightarrow i_b = 0$$

$$i_o = h_{fe}i_b + \frac{v_o}{R_C} = \frac{v_o}{R_o} \Rightarrow \boxed{R_o = R_C}$$

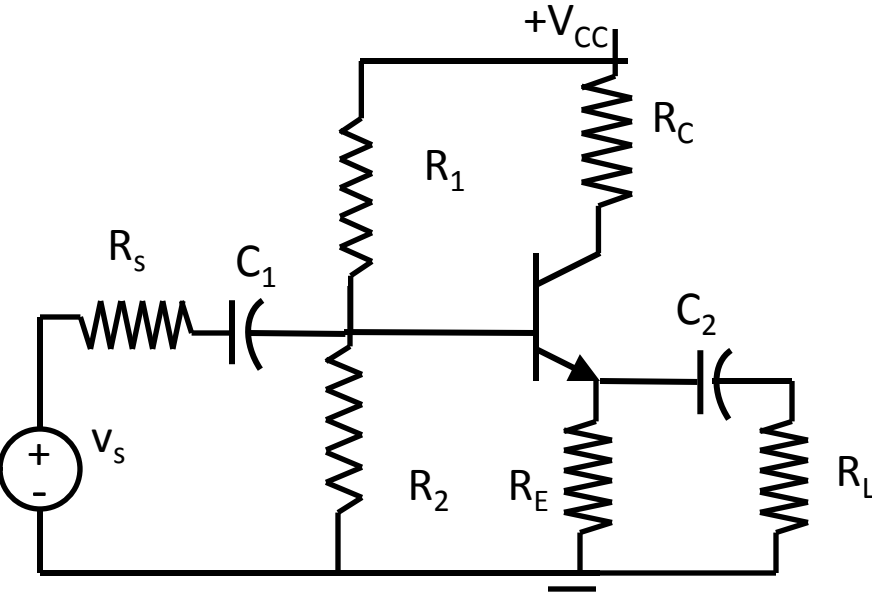Example: Emitter Follower (common collector amplifier)



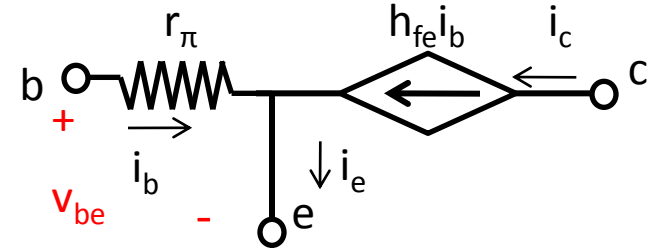For $R_T = R_E \parallel R_L$, and using,



Show that,

$$1. \quad A_v = \frac{v_e}{v_b} \approx \frac{R_T}{r_e + R_T} \quad \text{If } R_T \gg r_e, A_v = 1, v_e = v_b, \text{ emitter "follows" base voltage with unity gain}$$

$$2. \quad R_{in} = R_p \parallel R_b \quad \text{For large } h_{fe}, R_T, R_1 \text{ and } R_2, R_{in} \text{ can be made large}$$


$$R_b = \frac{v_b}{i_b} = r_{\pi} + (1 + h_{fe}) R_T \approx r_{\pi} + h_{fe} R_T$$

$$3. \quad R_o = R_E \parallel \left(\frac{r_{\pi} + R}{1 + h_{fe}} \right) \quad \text{For large } h_{fe}, R_{out} \text{ can be made small}$$

$$R = R_s \parallel (R_1 \parallel R_2)$$

Buffer or
isolation
amplifier

Accurate Hybrid (h) parameter model

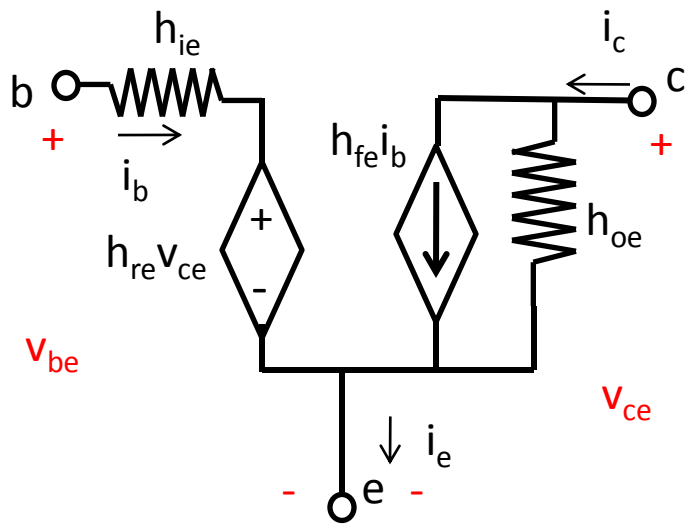

$$h_{ie} = \left. \frac{v_{be}}{i_b} \right|_{v_{ce}=0}$$

Short circuit input resistance

$$h_{re} = \left. \frac{v_{be}}{v_{ce}} \right|_{i_b=0}$$

open circuit reverse voltage gain

$$h_{oe} = \left. \frac{i_c}{v_{ce}} \right|_{i_b=0}$$


Open circuit output conductance

$$h_{fe} = \left. \frac{i_c}{i_b} \right|_{v_{ce}=0}$$

short circuit forward current gain


Typical values, $h_{ie}=1.5\text{k}\Omega$, $h_{re}=10^{-4}$, $h_{fe}=100$, $h_{oe}=10^{-5} \Omega^{-1}$

Frequency response

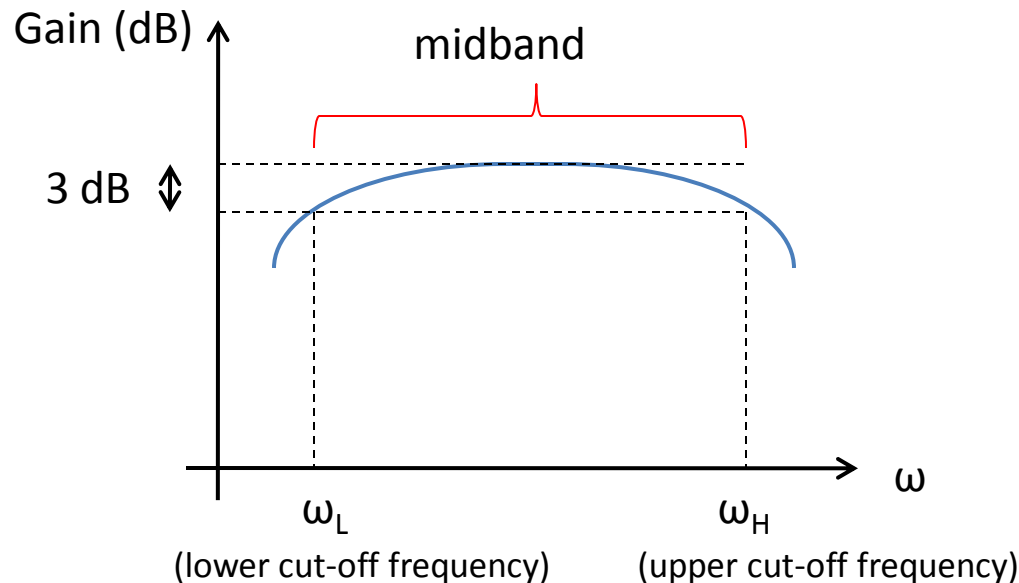

- So far we have ignored capacitive effects, in general gain is frequency dependent
- $\omega_L \rightarrow$ coupling and bypass capacitors
- $\omega_H \rightarrow$ determined by internal capacitances of the BJT

Recall: High pass filters

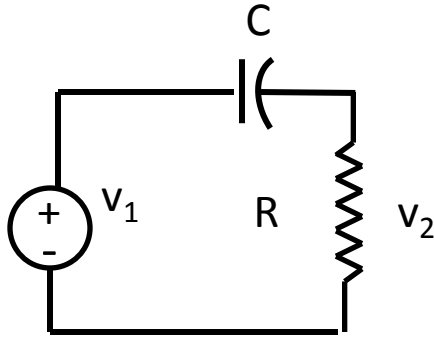


$$V_2 = \frac{j\omega RC}{1 + j\omega RC} V_1$$

$$\text{ang}(V_2) = 90^\circ - \tan^{-1}(\omega RC) + \text{ang}(V_1)$$

$$0 < \tan^{-1}(\omega RC) < 90^\circ \Rightarrow \text{ang}(V_2) > \text{ang}(V_1)$$


V_2 leads $V_1 \rightarrow$ lead network

High pass filter, $\omega_c = 1/RC$

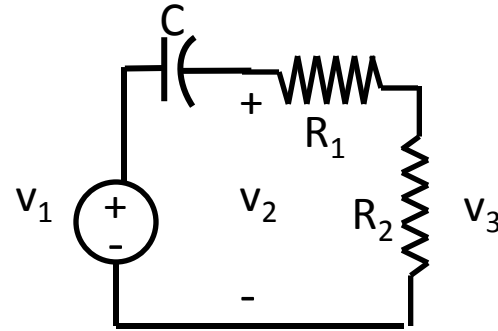

V_3 leads $V_1 \rightarrow$ also lead network
High pass filter, $\omega_c = 1/(R_1 + R_2)C$

Recall: Low pass filter

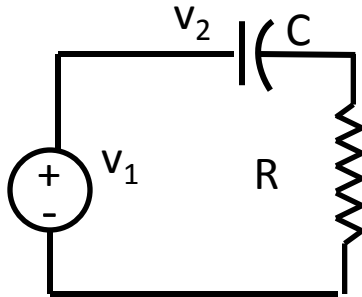


$$V_2 = \frac{1}{1 + j\omega RC} V_1$$

$$\text{ang}(V_2) = \text{ang}(V_1) - \tan^{-1}(\omega RC)$$

$$0 < \tan^{-1}(\omega RC) < 90^\circ \Rightarrow \text{ang}(V_2) < \text{ang}(V_1)$$

V_2 lags $V_1 \rightarrow$ lag network
Low pass filter, $\omega_c = 1/RC$

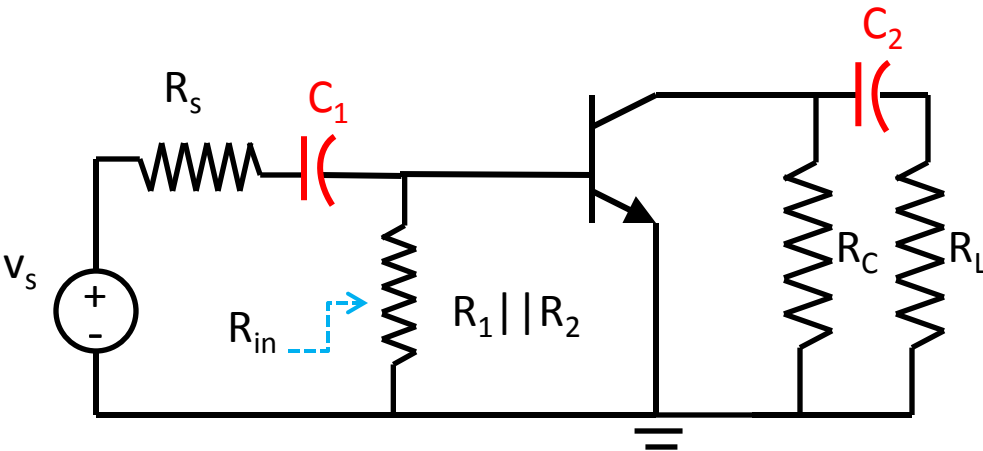
CE amplifier: Effect of coupling capacitor C_1



Ignoring, C_2


$$\omega_1 = \frac{1}{(R_s + R_{in})C_1}$$
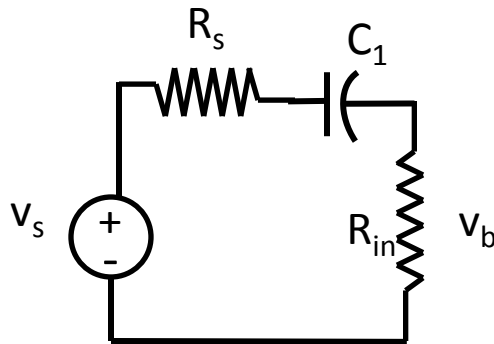
$$R_{in} = (R_1 \parallel R_2) \parallel R_b \quad R_b = (1 + h_{fe})(r_e)$$



Base-equivalent lead network

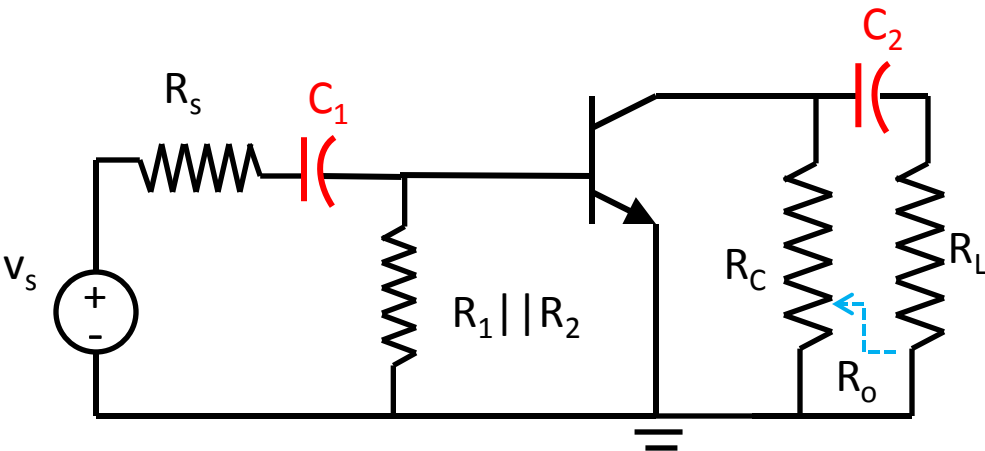
CE amplifier: Effect of coupling capacitor C_2



Ignoring, C_1


$$\omega_2 = \frac{1}{(R_o + R_L)C_2}$$

$$R_o = R_C$$

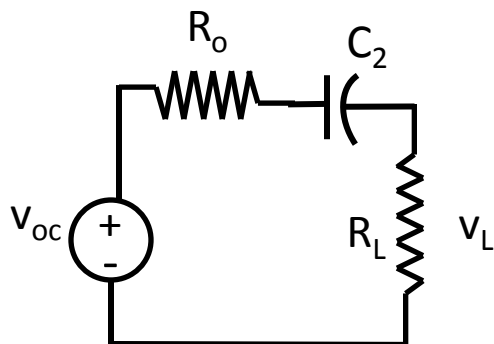

Collector-equivalent lead network

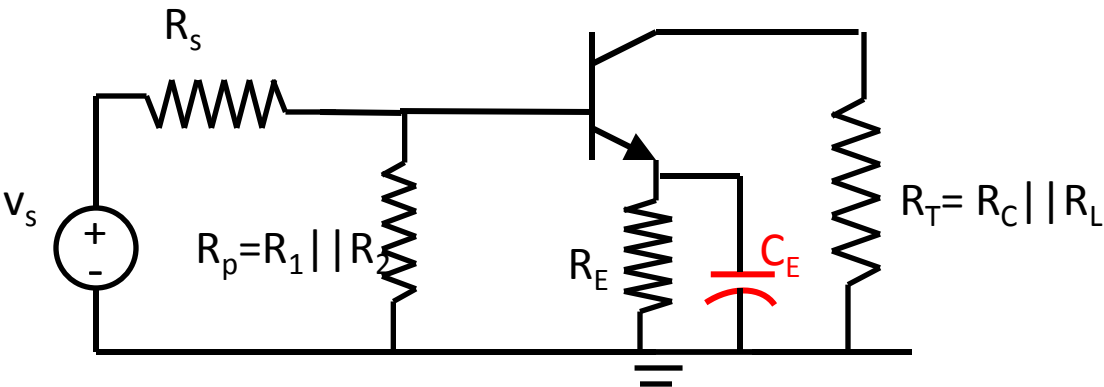
CE amplifier: Effect of bypass capacitor C_E



KCL at v_b

$$\frac{v_b}{R} + \frac{v_b - v_o}{r_e} = h_{fe} i_b = \frac{h_{fe}(v_b - v_o)}{(1 + h_{fe})r_e}$$
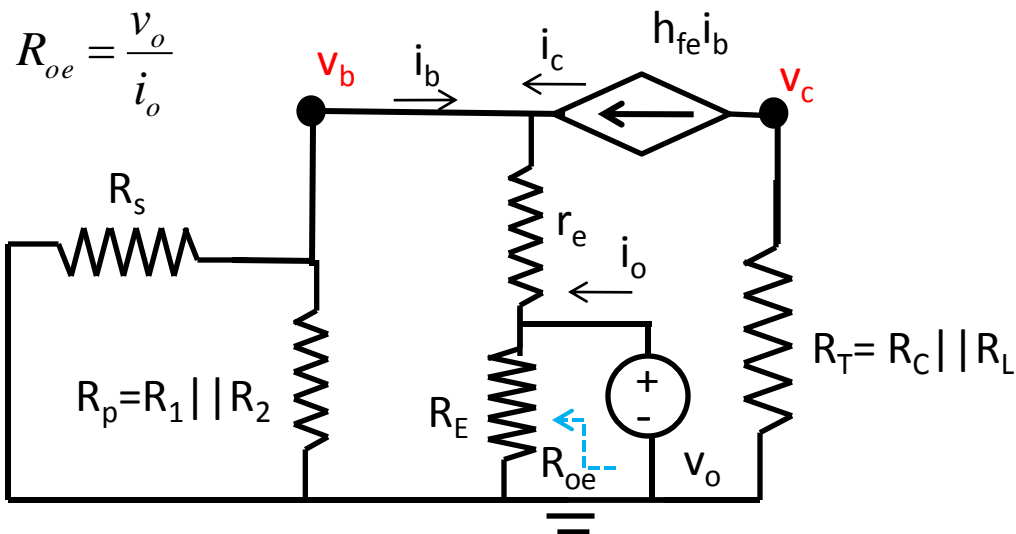
$$\Rightarrow v_b = \frac{R/(1 + h_{fe})}{r_e + R/(1 + h_{fe})} v_o$$



Circuit to determine R_{oe} in series with C_E


Substituting this for v_b in,

$$i_o = \frac{v_o}{R_E} + \frac{v_o - v_b}{r_e}$$

$$R_{oe} = \frac{v_o}{i_o} = R_E \parallel \left(r_e + \frac{R}{1 + h_{fe}} \right)$$


$$\omega_3 = \frac{1}{R_{oe} C_E}$$

Frequency response

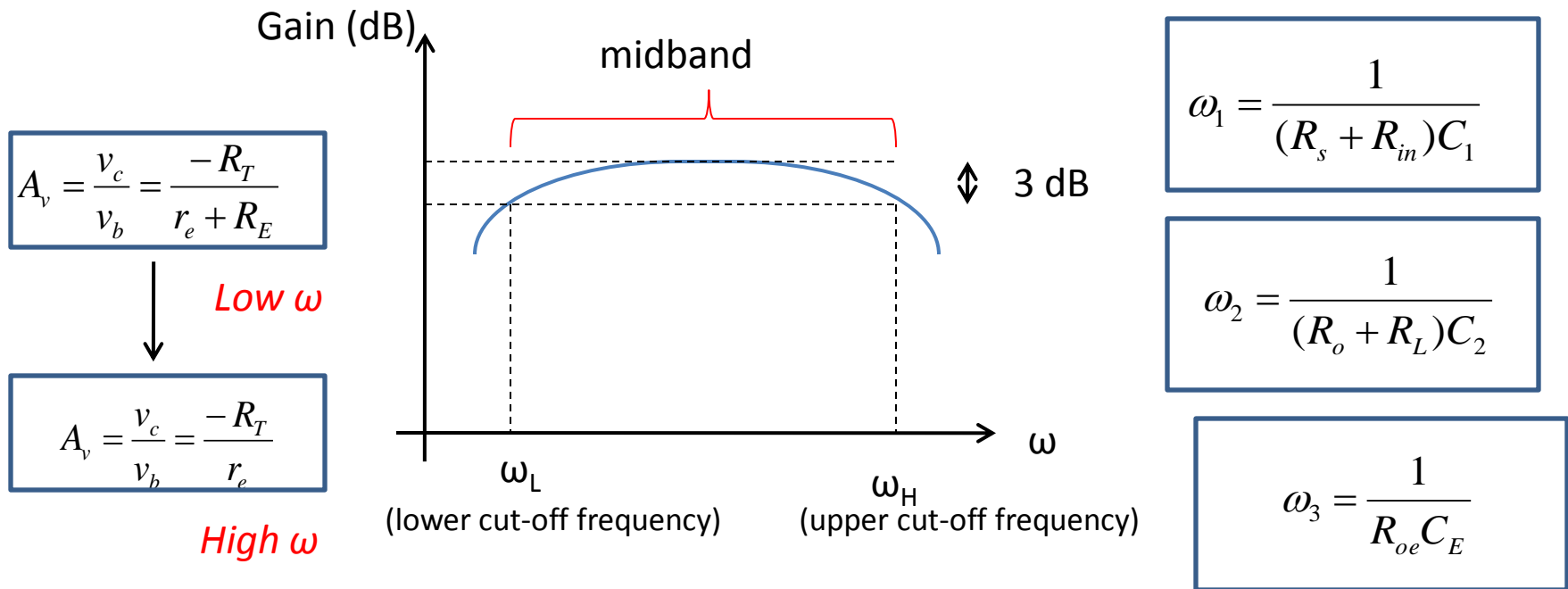

- The lower cut-off frequency is determined by which has the higher value amongst $\omega_1, \omega_2, \omega_3$
- Generally ω_3 is the largest of all three
 - At high ω , C_E behaves as a short circuit and gain increases
 - At low ω , C_E acts less and less as a short circuit and gain decreases

Miller's theorem

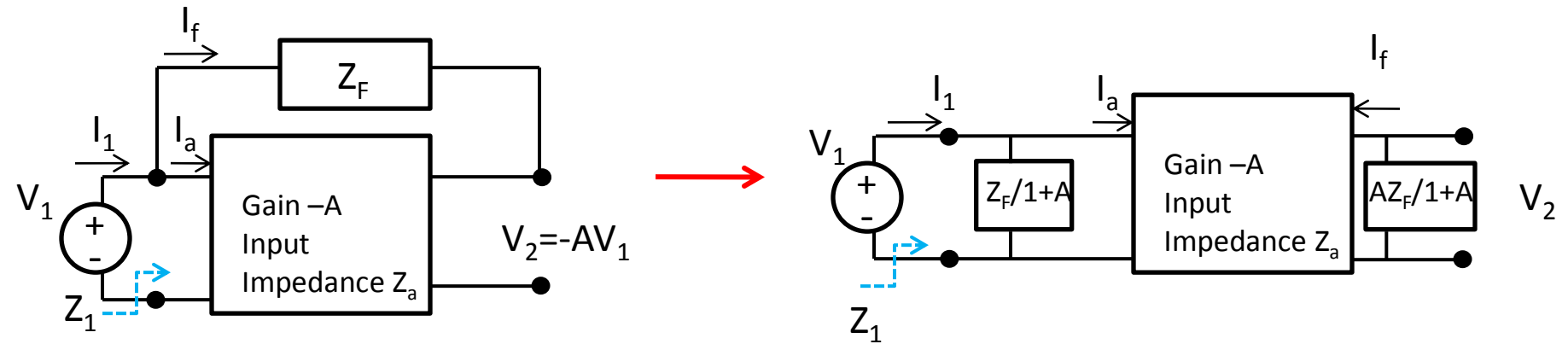

$$I_1 = I_a + I_f = \frac{V_1}{Z_a} + \frac{V_1 - V_2}{Z_F} = \frac{V_1}{Z_a} + \frac{(1+A)V_1}{Z_F}$$



$$\Rightarrow \frac{I_1}{V_1} = \frac{1}{Z_a} + \frac{(1+A)}{Z_F}$$

$$\Rightarrow Z_1 = Z_a \parallel \frac{Z_F}{1+A}$$

$$I_f = \frac{V_1 - V_2}{Z_F} = \frac{(-V_2 / A) - V_2}{Z_F} = \frac{V_2}{AZ_F / (1+A)}$$


Miller's theorem \rightarrow reflects feedback impedance across to input and output

High frequency Response

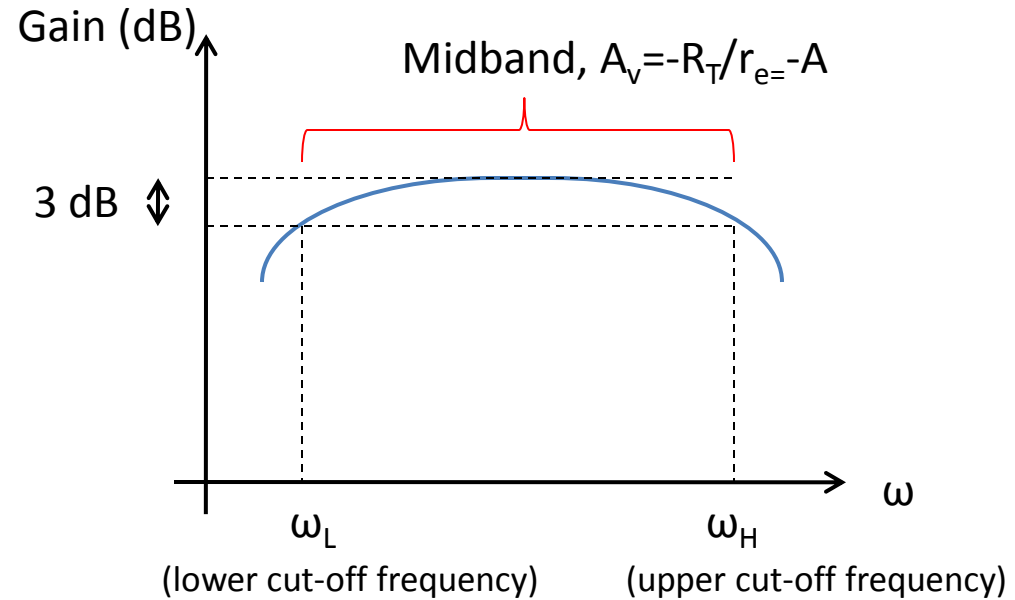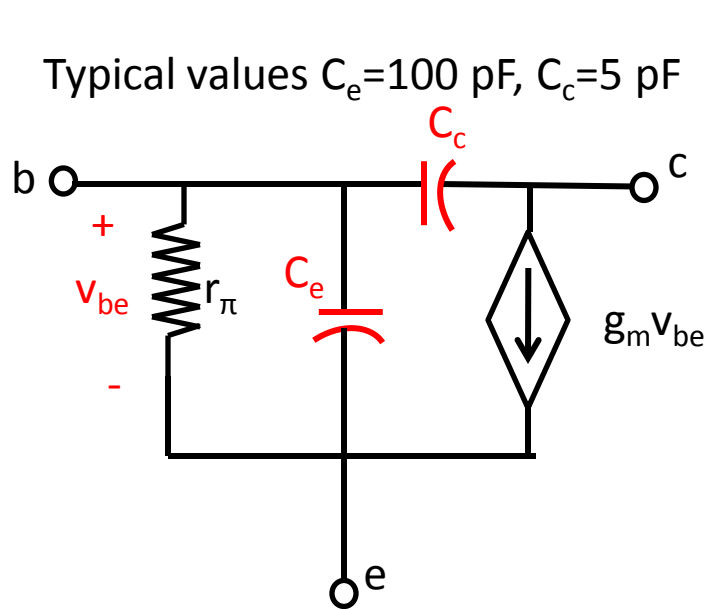

- At low ω , C_1 , C_2 and C_E need to be accounted for
- At mid ω , C_1 , C_2 and C_E are short circuits and C_c and C_e are open, $A_v = -R_T/r_e$
- At high ω , C_e and C_c need to be accounted for

High frequency response

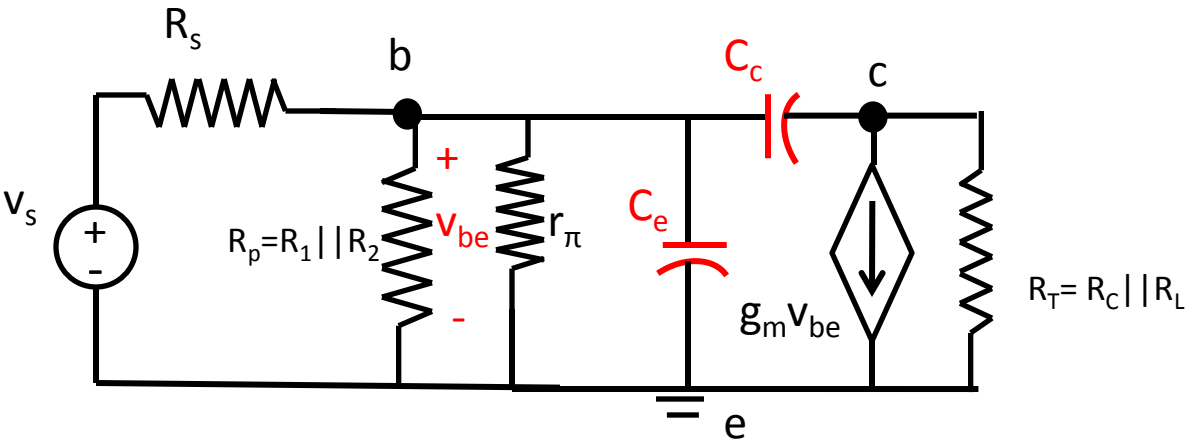


$$\frac{Z_F}{1+A} = \frac{1}{j\omega C_c (1+A)}$$

Input



$$\frac{AZ_F}{1+A} = \frac{1}{j\omega C_c (1+A)/A}$$

Output

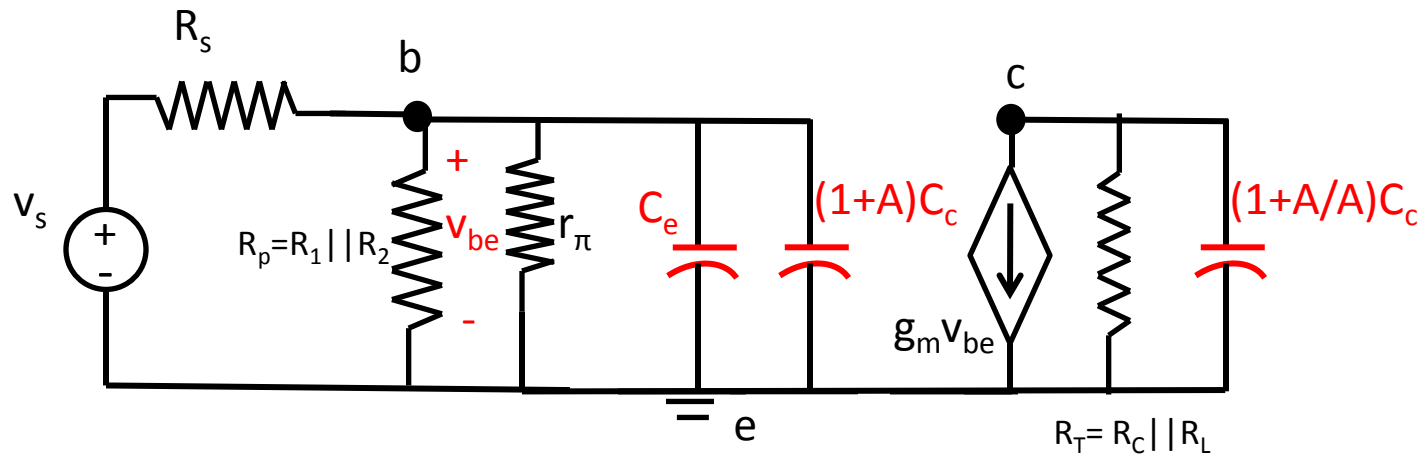

- C_c can be reflected using Miller's theorem

High frequency response

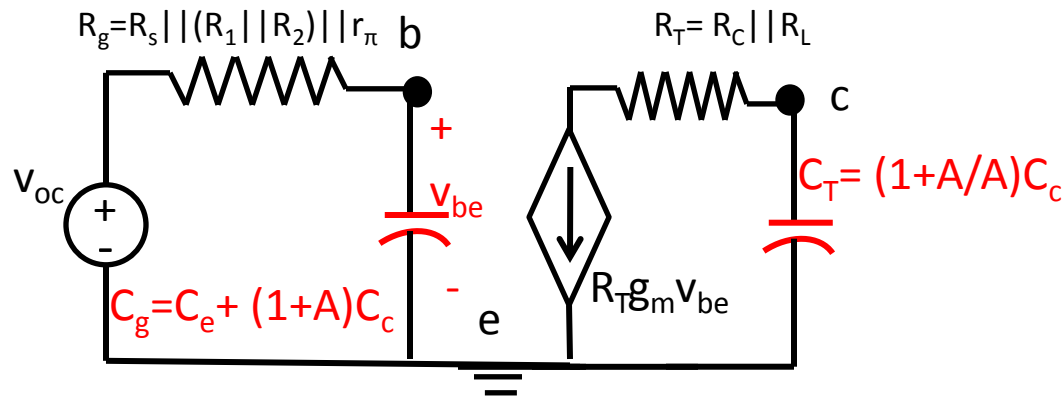
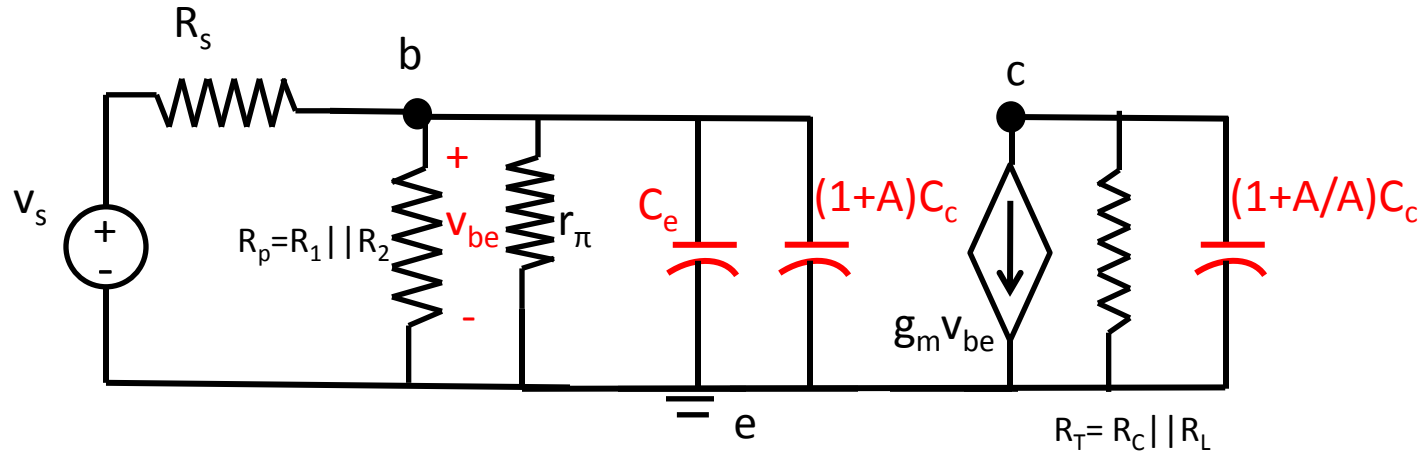


$$\omega_g = \frac{1}{R_g C_g}$$

$$\omega_T = \frac{1}{R_T C_T}$$

- Base and collector “lag” networks
- Upper cut-off frequency is the lower of the two $\rightarrow \omega_g, \omega_T$

Amplifier Power Analysis

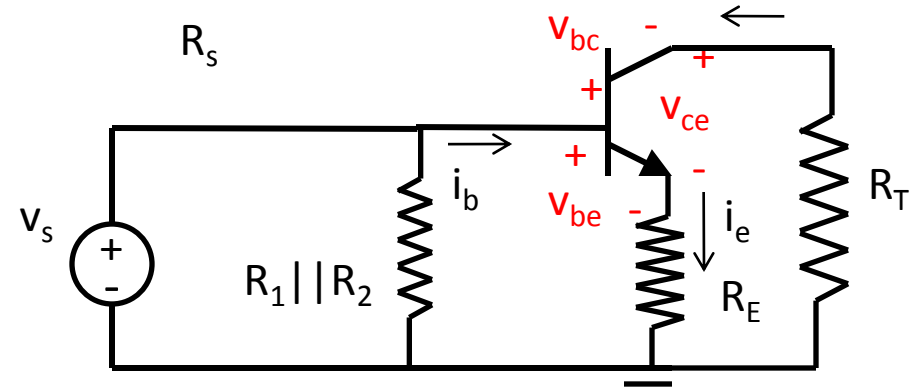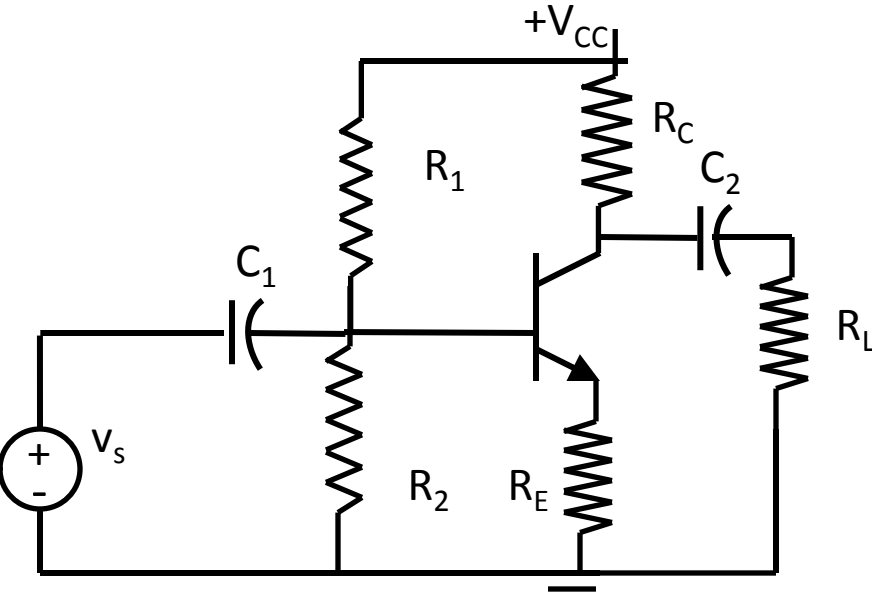

$$v_{CE} = V_{CEQ} + v_{ce}$$


$$v_{ce} = -(R_T + R_E)i_c$$

$$i_c = I_{CQ} + i_c \Rightarrow i_c = i_c - I_{CQ}$$

$$v_{CE} = V_{CEQ} - (R_T + R_E)(i_c - I_{CQ}) \Rightarrow i_c = -\frac{1}{R_T + R_E} v_{CE} + \left(I_{CQ} + \frac{V_{CEQ}}{R_T + R_E} \right)$$

AC load line

Amplifier AC Load Line

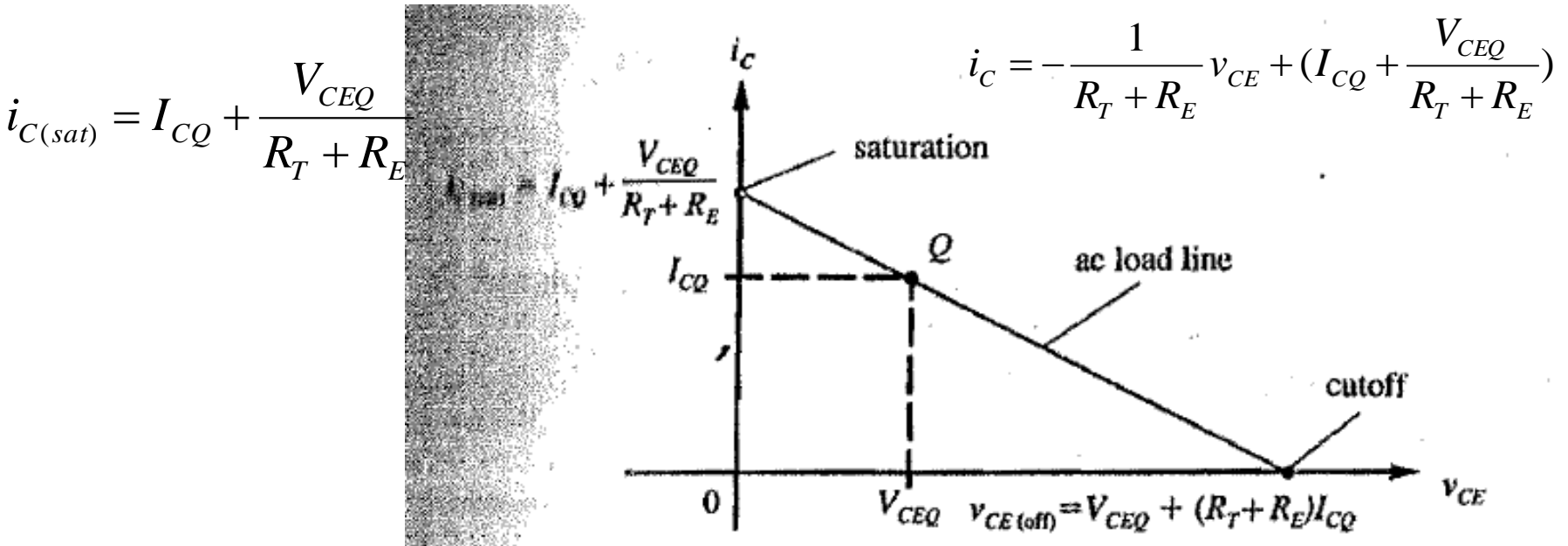

Assume $i_C(off)=0A$, $v_{CE}(sat)=0V$

$$i_{C(sat)} = I_{CQ} + \frac{V_{CEQ}}{R_T + R_E}$$


$$v_{CE(off)} = V_{CEQ} + (R_T + R_E)I_{CQ}$$

For largest possible ac signal, Q-point should be at the center of load line

$$i_{C(sat)} = I_{CQ} + \frac{V_{CEQ}}{R_T + R_E} = 2I_{CQ} \Rightarrow \boxed{\frac{V_{CEQ}}{I_{CQ}} = R_T + R_E}$$

Amplifier Power

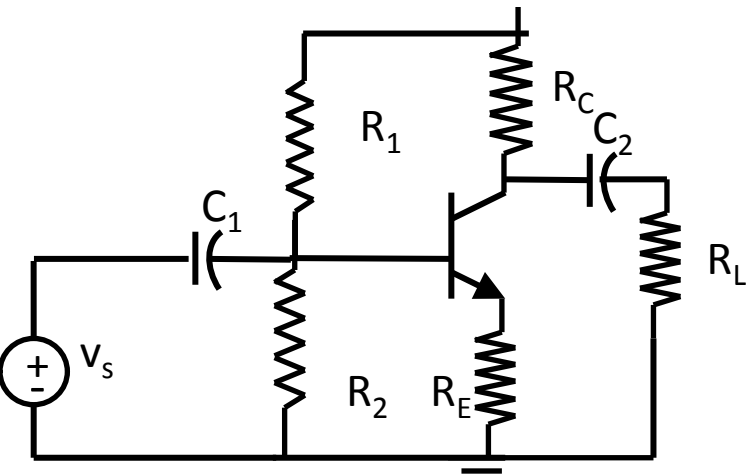Q-point at the center of load line gives maximum sinusoidal collector current amplitude I_{CQ}



Average ac power absorbed by R_T $P_T = R_T \left(\frac{I_{CQ}}{\sqrt{2}} \right)^2 = \frac{1}{2} I_{CQ}^2 R_T$

Average ac power absorbed by R_E $P_E = R_E \left(\frac{I_{CQ}}{\sqrt{2}} \right)^2 = \frac{1}{2} I_{CQ}^2 R_E$

Total ac output power

$$P_o = P_T + P_E = \frac{1}{2} I_{CQ}^2 (R_T + R_E)$$

Maximum output power

$$P_o = \frac{1}{2} I_{CQ} V_{CEQ}$$

Efficiency of the amplifier (output signal power/dc power)
(max efficiency = $\frac{1}{4}$)

$$\eta = \frac{P_o}{P_{dc}} = \frac{P_o}{V_{cc} I_{CQ}}$$

Instantaneous power dissipation of the BJT
(max at center of load line)

$$p = v_{CE} i_C$$

Quiescent power dissipation of the BJT (no ac signal)
(max at center of load line)

$$P_{DQ} = V_{CEQ} I_{CQ}$$