

Soln ① Let the BJT operates in saturation region.

$$\text{Then } V_{CE,\text{sat}} = 0.2V$$

$$\therefore I_C = \frac{V_{CC} - 0.2}{R_C}$$

$$= \frac{4.8}{1.5} \text{ mA} = 3.2 \text{ mA}$$

$$\begin{aligned} \text{# } I_B &= \frac{V_{BB} - V_{BE,\text{sat}}}{R_B} \quad [\text{Don't apply}] \\ &= \frac{6 - 0.8}{240} \\ &= 21.5 \mu\text{A} . \end{aligned}$$

$$\therefore \beta I_B = 2.58 \text{ mA} .$$

For BJT to work in saturation region  
 $I_C < \beta I_B$

So our assumption is incorrect &  
transistor is in Active region.

Again solve for active region consider:

$$\begin{aligned} I_B &= \frac{6 - 0.4}{240} \\ &= 19.6 \mu\text{A} . \end{aligned}$$

$$\begin{aligned} I_C &= \frac{19.6 \mu\text{A}}{\beta} \\ &= \frac{19.6 \mu\text{A}}{50} \\ &= 2.35 \text{ mA} . \end{aligned}$$

$$V_{CE} = I_C R_C = 10V$$

$$\text{or } V_{CE} = 2.46V$$

When  $R_C = 3k\Omega$ .

$$\text{then, } I_{C\text{sat}} = \frac{4.8}{3} = 1.6 \text{ mA}$$

Saturation current = 1.6 mA.

$$+ I_{B\text{sat}} = 21.5 \mu A$$

$$\beta I_{B\text{sat}} = 2.58 \text{ mA}$$

$$\therefore \beta I_B > I_{C\text{sat}}$$

$\therefore$  BJT is in saturation region.

saturation of BJT is at  $V_{CE} = 0.2V$ .  
P沟道饱和时， $V_{CE} = 0.2V$

$$[0 \rightarrow 1] \text{ and }$$

in holeholes and holes  $V_{CE} = 0.2V$  is  
not enough to agree with

$$V_{CE} \geq 3V$$

$$2.0 \geq \frac{0.2V}{0.2} \text{ mA}$$

$$V_{CE} \geq 0.2V$$

$$V_{CE} = 3V$$

$$\text{SOLN. ②} \quad \begin{cases} V_{OH} = 5V \\ V_{OL} = 0.2V \end{cases} \quad \begin{cases} V_{IL} = ? \\ V_{IH} = ? \end{cases}$$
$$V_{IL} = \frac{0.2V}{2k\Omega} \times 50\Omega = 5V$$

$$V_{IL} = V_{OH} - V_{IH}$$

$$V_{IL} \leq V_{IL} - V_{OL}$$

Considering negligible current through base, find  $V_B$ . (apply  $V_{BL}$ ).

$$\text{i.e. } V_B = \frac{(V_{in} \times 50) + (-5 \times 20)}{50 + 20}$$

$$\Rightarrow V_B = \frac{50V_{in} - 100}{70} - 0$$

$V_{IL}$  is the maximum i/p voltage which will be considered as a low i/p. [Logic 0].

$\therefore V_{IL}$  should be calculated at the range of BJT gets on.  
i.e.  $V_{BE} \leq 0.5V$ .

$$\Rightarrow \frac{50V_{in} - 100}{70} \leq 0.5$$

$$\Rightarrow V_{in} \leq 2.5V$$

$$\therefore V_{IL} = 2.5V$$

$V_{IH}$  is the minimum input voltage which is to be considered as ~~to~~ ~~for~~ high input [Logic 1]. Transistor should first enter the saturation region.

$$\text{i.e. } I_C \leq \beta I_B - ②$$

Now,

$$I_B = \left[ \frac{V_{in} - V_B}{20} \right] - \left[ \frac{V_B + 5}{50} \right]$$

$$= \frac{V_{in} - 0.8}{20} - \frac{5.8}{50} \quad [V_{BE, sat} = 0.8V]$$

By ②,

$$\frac{5 - 0.2}{2} \leq \frac{V_{in} - 0.8}{20} - \frac{5.8}{50}$$


$$\Rightarrow V_{in} \geq 3.6V$$

$$\therefore V_{IH} = 3.6V$$

$$\begin{aligned} \therefore Nm_L &= 2.4 - 0.2 + Nm_H - 3.6 \\ \Rightarrow Nm_L &= 2.5V \end{aligned} \Rightarrow \boxed{Nm_H = 1.4V}$$

$\overbrace{x-x-x}$

Q. 3

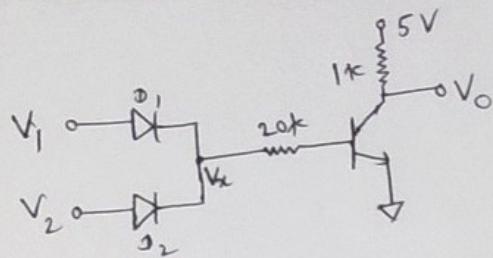

$V_1$	$V_2$	$V_0$
0	0	1
0	1	0
1	0	0
1	1	0

①  $h_{FE \min}$  for proper operatn.

(a) When  $V_1 = V_2 = \text{logic 0}$ , both  $D_1$  &  $D_2$  are off.  
∴  $V_x = 5V$ . [No dependency on  $\beta$ ].

When any one of  $V_1$  &  $V_2$  is logic 1 :-  
(5V)

$$V_x = 5 - 0.7 = 4.3V$$

For proper operatn BJT in this case should be in saturatn i.e.,  $V_o = \text{logic 0 (0.2V)}$

$$\text{i.e. } i_B \geq \frac{i_C}{\beta}$$

$$\Rightarrow \beta \geq \frac{4.8}{(4.3 - 0.8)} \quad \frac{4.8}{20}$$

$$\Rightarrow \boxed{\beta \geq 24.42}$$

$$\therefore \boxed{\beta_{\min} \approx 28}$$

(b)

$V_{IL}$

$$V_x < 0.5V$$

$$\Rightarrow V_i - 0.7 < 0.5$$

$$\Rightarrow V_i < 1.2V$$

$$\therefore \boxed{V_{IL} = 1.2V}$$

$$\text{Also, } V_{OL} = 0.2V \text{ & } V_{OH} = 5V$$

$$\therefore \boxed{NM_L = 1V, NM_H = 4.54V}$$

$V_{IH}$  (with  $\beta=100$ )

$$\beta \geq \frac{i_C}{i_B}$$

$$\Rightarrow 100 \geq \frac{4.8}{(V_i - 0.7 - 0.8)} \quad \frac{4.8}{20}$$

$$\Rightarrow \boxed{V_i \geq 2.46V}$$

$$\text{i.e. } \boxed{V_{IH} = 2.46V}$$

Sol 4 Given  $h_{FE} = 100$        $R_1 = R_2 = 400 \text{ k}\Omega$

$$R_E = R_S = 1 \text{ k}\Omega$$

$$R_L = 9 \text{ k}\Omega$$

$$V_{CC} = 20 \text{ V} \quad I_{CQ} = 3.09 \text{ mA}$$

$$\therefore r_e = \frac{0.026}{3.09 \times 10^3} = 8.414 \text{ }\Omega \quad r_c = \frac{0.026}{I_{CQ}}$$

$$R_T = R_E \parallel R_L = \frac{1 \times 9}{1+9} = 0.9 \text{ k}\Omega$$

$$\begin{aligned} r_\pi &= \beta r_c \\ &= 100 (8.414) \Omega \\ &= 841.4 \text{ }\Omega \end{aligned}$$

$$A_v = \frac{h_{FE} r_e R_T}{[r_{le} R_T + r_\pi]} = \frac{(100)(900)}{(100)(900) + 841.4} \approx 0.9907 \text{ (Ans)}$$

$$\begin{aligned} R_b &= r_\pi + h_{FE} R_T \\ &= (100)(900) + 841.4 \text{ }\Omega \\ &= 90.841 \text{ k}\Omega \end{aligned}$$

$$R_p = R_1 \parallel R_2 = \frac{400 \times 400}{400 + 400} = 200 \text{ k}\Omega$$

$$\therefore R_{in} = R_b \parallel R_p = \frac{90.841 \times 200}{290.841} \text{ k}\Omega \\ = 62.467 \text{ k}\Omega \text{ (Ans.)}$$

$$A_i = h_{FE} \cdot \frac{R_E}{R_E + R_L} = (100) \cdot \frac{L}{(L+9)} = 10 \text{ (Ans)}$$

$$R_o = R_E \parallel R'$$

$$R' = \frac{r_\pi + R}{1 + h_{fe}}$$

$$R' = \frac{841 + 0.995}{100}$$

$$= 0.01836 \text{ k}\Omega$$

$$= 18.36 \Omega \quad \cancel{\text{Ans}}$$

$$\therefore R_o = R_E \parallel R'$$

$$= \frac{18.36 \times 1000}{1018.36}$$

$$= 18.029 \Omega \text{ (Ans)}$$

$$R = R_S \parallel R_T$$

$$= \frac{1 \times 200}{200+1} \text{ k}\Omega$$

$$= 0.995 \text{ k}\Omega$$

$\square$  Input impedance  $Z_{in} = R_p \parallel (r_\pi + h_{fe} R_T)$

Output impedance  $Z_o = R_E \parallel \left( \frac{r_\pi + R_S \parallel R_p}{h_{fe}} \right)$

$$\cancel{\text{Ans}} \quad A_V = \frac{h_{fe} R_T}{h_{fe} R_T + r_\pi}$$


Now input impedance can be made higher by increasing  $h_{fe}$  and  $R_T$ .

Again output impedance can be decreased by increasing  $h_{fe}$ .

High input impedance and low output impedance means high value of  $h_{fe}$  and high value of  $R_T$  and at that condition  $A_V \approx 1$

$\therefore$  It works as unity gain amplifier

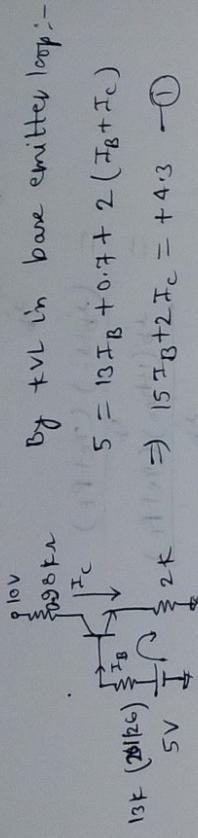Ques 5 DC equivalent circuit can be drawn as follows:-



By KVL in base emitter loop:-

$$5 = 13I_B + 0.7 + 2(I_B + I_C)$$

$$\Rightarrow 15I_B + 2I_C = +4.3 \quad \text{--- (1)}$$

By KVL in C-E loop:-

$$10 = 0.98I_C + 2(I_B + I_C) + V_{CE}$$

$$\Rightarrow 2.98I_C + 2I_B \pm V_{CE} = 10 - \text{--- (2)}$$

$$\text{Also, } I_C = \beta I_B$$

$$\Rightarrow I_C = 100I_B$$


$$\therefore \text{By (1), } \frac{15}{100}I_C + 2I_C = +4.3$$

$$\Rightarrow [I_C = 2 \text{ mA}]$$


$$(i) \because \theta_m = \frac{I_C}{V_T} = \frac{2}{26} = \frac{76.9 \text{ mA}}{\text{V}}$$

$$(ii) \because r_e = \frac{1}{\theta_m} = 13 \Omega.$$

A.C. equivalent circuit:-

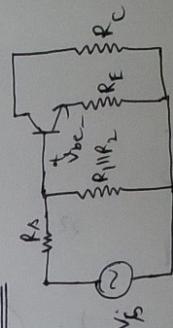

Small signal A.C. model:-

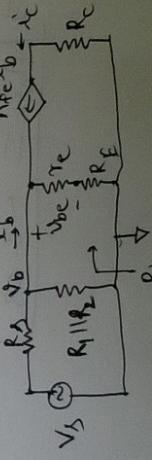

$$R_B = \frac{V_B}{i_B}$$

$$\text{Given } R_b = \frac{V_b}{i_b} \text{ and } i_b = \frac{(i_{b+e}) (r_{et} + R_E)}{i_b}$$

$$\text{①} \quad \Rightarrow \quad \frac{i_b}{i_b} = \frac{i_b (i_{b+e}) (r_{et} + R_E)}{i_b}$$

$$\Rightarrow R_b = (1 + h_{fe})(r_{et} + R_E) = 203.313 \text{ k}\Omega$$
  

$$\text{iii) } R_{in} = R_b || (R_1 || R_2)$$

$$= (203.313 || 2.3) \text{ k}\Omega$$

$$\Rightarrow R_{in} = 12.3 \text{ k}\Omega$$
  


$$\text{iv) } A_V = \frac{V_o}{V_b} = \frac{V_o}{\frac{V_o}{R_{in}} + r_{et} + R_E}$$


$$= \frac{-R_C (1 + h_{fe}) (r_{et} + R_E)}{R_C (1 + h_{fe}) (r_{et} + R_E)}$$

$$= \frac{-R_C h_{fe}}{R_C (1 + h_{fe}) (r_{et} + R_E)} = -\frac{h_{fe}}{1 + h_{fe}}$$


$$\text{v) } A_V \approx -\frac{R_C h_{fe}}{r_{et} + R_E}$$

$$\therefore A_V \approx -\frac{200}{203} = -98^\circ$$
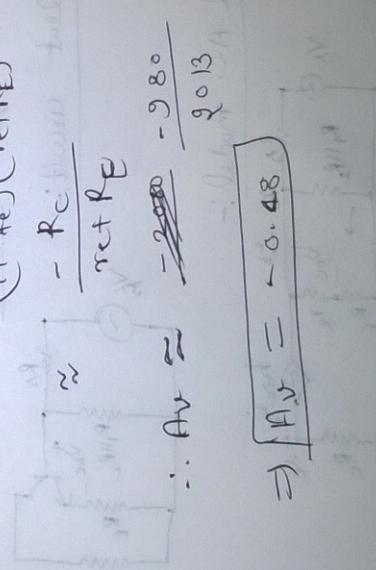
$$\Rightarrow A_V = -0.48$$

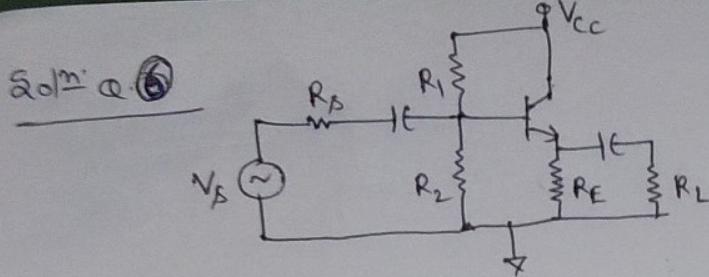


AC equivalent ckt. :-

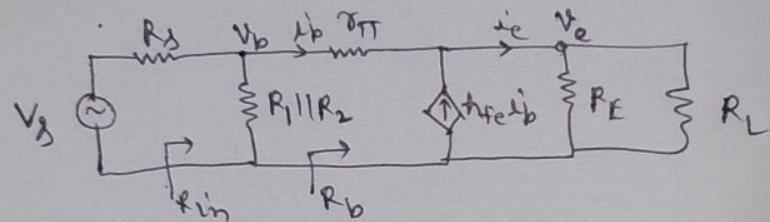

$$(a) \frac{V_e}{V_b} = ?$$

$$\therefore V_e = i_c \cdot (R_E || R_L)$$

$$\Rightarrow V_e = i_b (1 + h_{fe}) (R_E || R_L) \quad \textcircled{1}$$

~~$$\therefore \frac{V_b}{i_b} = V_e + r_\pi i_b$$~~

$$= i_b [(1 + h_{fe}) (R_E || R_L) + r_\pi]$$

$$\therefore Av = \frac{V_e}{V_b} = \frac{(1 + h_{fe}) (R_E || R_L)}{(1 + h_{fe}) (R_E || R_L) + r_\pi}$$


$$\approx \frac{R_E || R_L}{R_E || R_L + \frac{r_\pi}{h_{fe}}}$$

$$= \frac{R_E || R_L}{R_E || R_L + r_e} \quad \textcircled{2}$$

Ans

Finding  $r_e$   $r_e = \frac{1}{g_m} = \frac{V_T}{I_C}$  2

D.C equivalent ckt:-

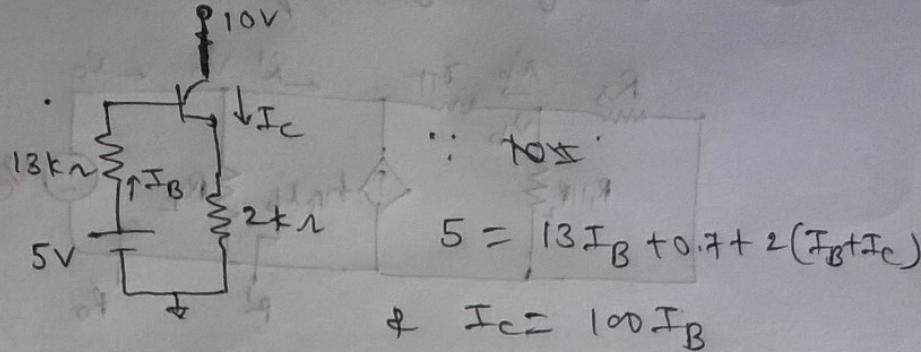

∴  $5 = 0.13I_C + 0.7 + 2 \times 1.13I_C$

$\therefore I_C = 1.8 \text{ mA}$

$\therefore r_e = 14.4 \Omega$

$\therefore \frac{V_E}{V_B} = \frac{1000}{1014.4} = 0.98$

(b)  $R_{in} = ?$   $R_{in} = (R_1 \parallel R_2) \parallel R_b$

$R_b = \left( \frac{V_b}{I_b} + r_e \right) = (r_e + h_{fe})$

$= (1 + h_{fe})(R_E \parallel R_L) + r_e$

$= 101 \times 1k + 1.44k$


$= 102.44k$

$\therefore R_{in} = 13 \parallel 102.44$

$= 11.53 \Omega$

$$(c) \underline{R_o = ?}$$

ckt for finding  $R_o$

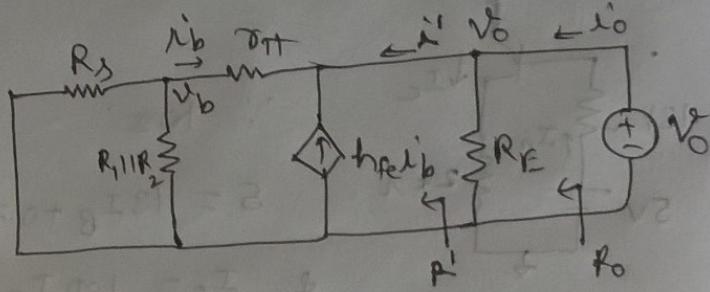

$$i_b = -V_b / (R_s || R_1 || R_2) \quad \text{--- (1)}$$

$$R_o = R_E || R' \quad \text{--- (2)}$$

$$\frac{i'}{i_b} = \frac{V_o}{i'} \quad \boxed{\mu \cdot M = 50}$$

$$\text{By KCL, } i' + i_b + h_{fe}i_b = 0$$

$$\Rightarrow i' = -(1 + h_{fe})i_b$$

$$= -(1 + h_{fe})V_b (R_s || R_1 || R_2)$$

$$\text{Hence } \frac{V_o}{i'} = \frac{V_o}{(1 + h_{fe})V_b (R_s || R_1 || R_2)} \quad \boxed{\text{By eq (1)}}$$

$$\frac{V_o}{i'} = V_b + i_b r_\pi$$

$$\Rightarrow V_o = V_b + V_b r_\pi / \underbrace{(R_s || R_1 || R_2)}_{R_X}$$

$$V_o = V_b \left[ 1 + \frac{r_\pi}{R_X} \right] \quad \text{--- (4)}$$

By (1) & (4),

$$i_b = \frac{-V_o R_X}{R_X + r_\pi} \times \frac{1}{R_X}$$

$$\Rightarrow i_b = \frac{-V_o}{R_x + r_\pi}$$

$$\therefore i_d = -(1+h_{fe}) \cdot \left( \frac{-V_o}{R_x + r_\pi} \right)$$

$$\therefore \cancel{R} =$$

$$\therefore R' = \frac{R_x + r_\pi}{1+h_{fe}}$$

~~negative feedback~~ ~~1 + h<sub>fe</sub> > 1~~

$$\beta_{rec} = 100$$

~~Now,  $r_\pi = 1.44 k\Omega$~~

$$h_{fe} = 100$$

$$R_x = 13 k\Omega || 1 k\Omega$$

(Assume  $R_s = 1 k\Omega$ )

$$\Rightarrow R_x = 9.28.5 \Omega$$


$$\therefore R' = 23.20 \Omega$$

$$\therefore R_o = R_E || R'$$

$$\Rightarrow R_o = 23.10 \Omega$$

$\leftarrow x - x -$

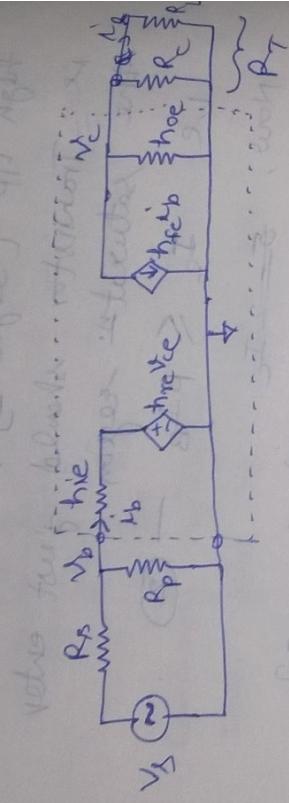Soln. ⑧ Ac equivalent becomes as shown below:-



$$\therefore i_{be} = \frac{V_b - V_{be}}{R_B + r_{hoe}}$$

$$\Rightarrow i_{ie} = \frac{V_b - 10^{-4}V_c}{1.3k}$$

$$R_T = R_B || R_L = 1k\Omega$$

$$r_{oe} = V_{hoe} = 100\Omega$$

$$\therefore V_c = -h_{fe} i_{eb} \cdot (R_T || R_L)$$

$$= -100 i_{eb} \cdot (100k || 1k)$$

$$= -99 \times 10^3 \Omega$$

$$\therefore V_c = -99 \times 10^3 \times \frac{V_b - 10^{-4}V_c}{100}$$

$$\Rightarrow \frac{V_c}{V_b} = -77.7 \quad [\text{By } c_v=0]$$

Without three & four :-

$$i_b = \frac{V_b}{1.3k} - \textcircled{2}$$
$$\therefore V_c = -h_{fe} i_b + V_T$$
$$= -100 \times 10^3 i_b - \textcircled{3}$$

$\therefore B_3 \textcircled{2} + \textcircled{3} ,$

$$-100 \times 10^3 i_b = V_c$$
$$\Rightarrow -100 \times 10^3 \times \frac{V_b}{13.00} = V_c$$
$$\Rightarrow \boxed{\frac{V_c}{V_b} = -76.9}$$

In this case answer is nearly same  
but calculation becomes easy.