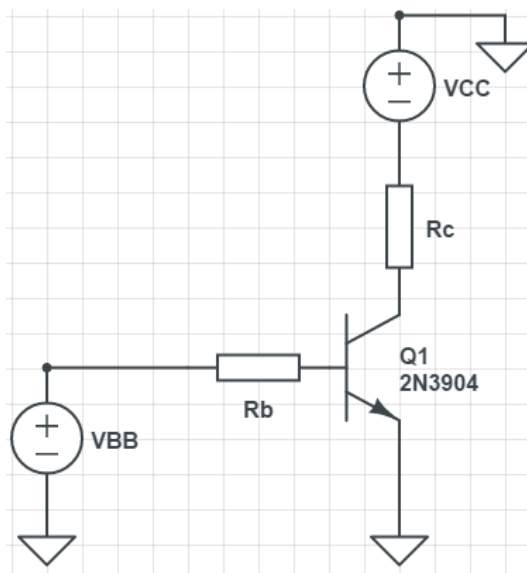



Tutorial 6
EE 101
BJT Circuits

Q1. For circuit 1 shown in the figure, suppose $R_B = 270K$, $R_C = 1.5K$, $V_{BB} = V_{CC} = 6V$, and $\beta = 120$. Find whether BJT operates in active region or saturation region? Find I_C , I_B , and V_{CE} . If the value of R_C is changed to $3K$, find whether BJT is in active or saturation region?



Circuit:1

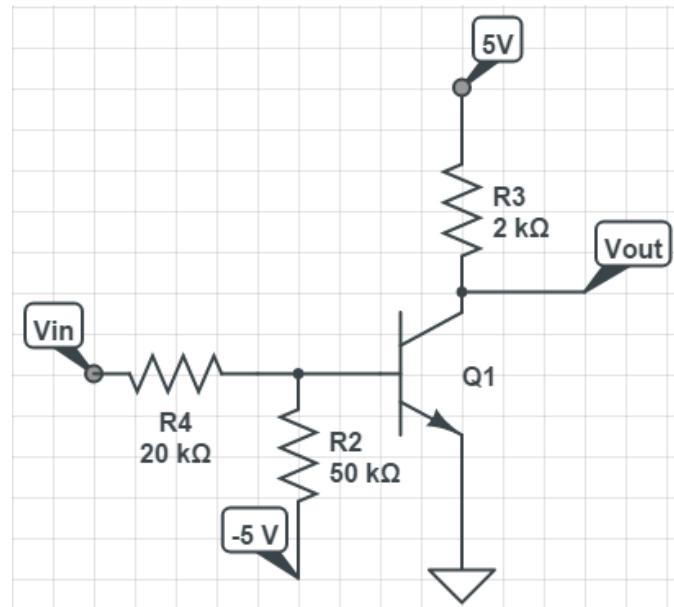
Q2. For the inverter circuit shown in figure 2, BJT has $\beta = 100$. Find noise margins NM_L and NM_H .



Circuit: 2

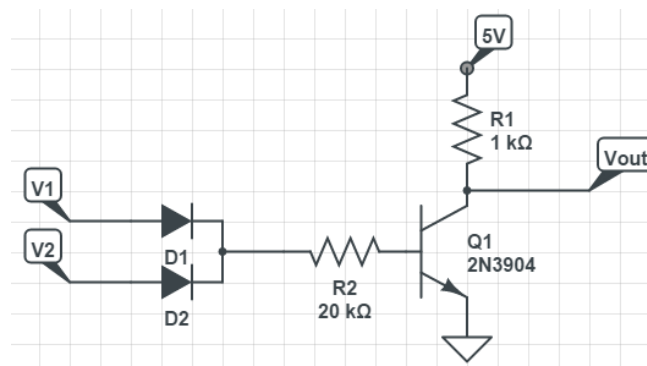
Q3. The DTL circuit shown in the circuit 3 is a NOR gate. Suppose that the voltage across a forward biased diode is 0.7V. If the low voltage is 0.2 V and high voltage is 5 V, find:

- The minimum value of β required for proper operation.
- Noise margin for the case when β is 100.




Circuit: 3

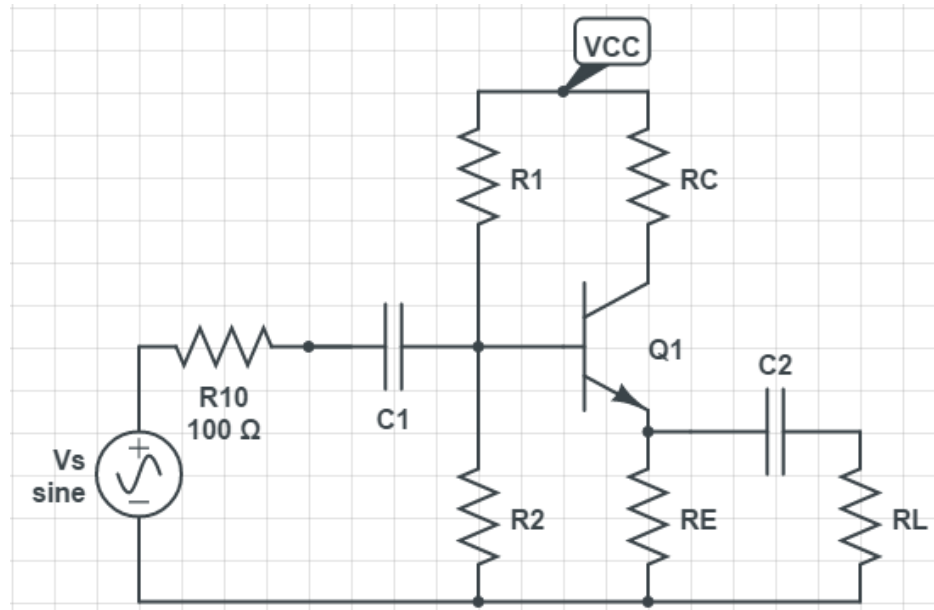Q4. For the amplifier below, $h_{fe}=h_{FE}=100$, $R_1=R_2=400\text{ k}\Omega$, $R_E=R_S=1\text{ k}\Omega$, $R_L=9\text{ k}\Omega$, and $V_{CC}=20\text{V}$. Given that $I_{CQ}=3.09\text{ mA}$, find (a) A_v , (b) R_{in} , (c) $A_i=i_L/i_b$, (d) R_o . Does this amplifier act as a unity gain amplifier with high input resistance and low output resistance?



Circuit: 4

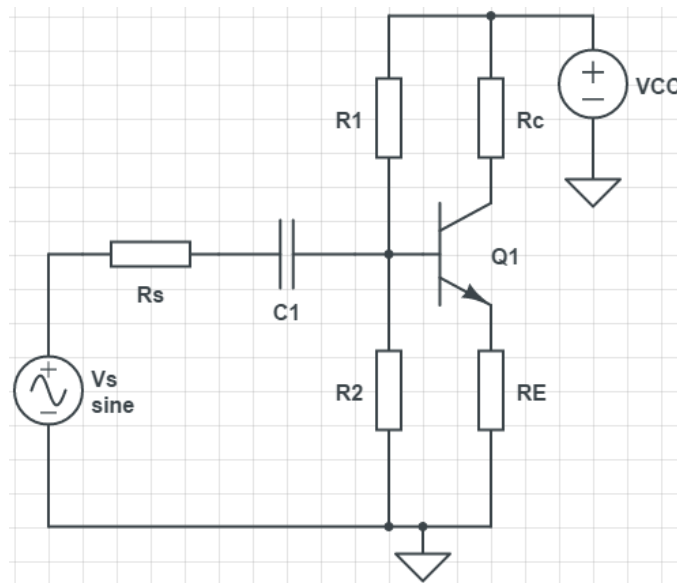Q5. For the circuit given in figure 5 suppose $h_{FE} = h_{fe} = 100$, $R_1 = R_2 = 26\text{K}$, $R_C = 980$, $R_E = 2\text{K}$ and $V_{CC} = 10\text{V}$. Find: g_m , r_e , R_{in} and A_v .



Circuit: 5

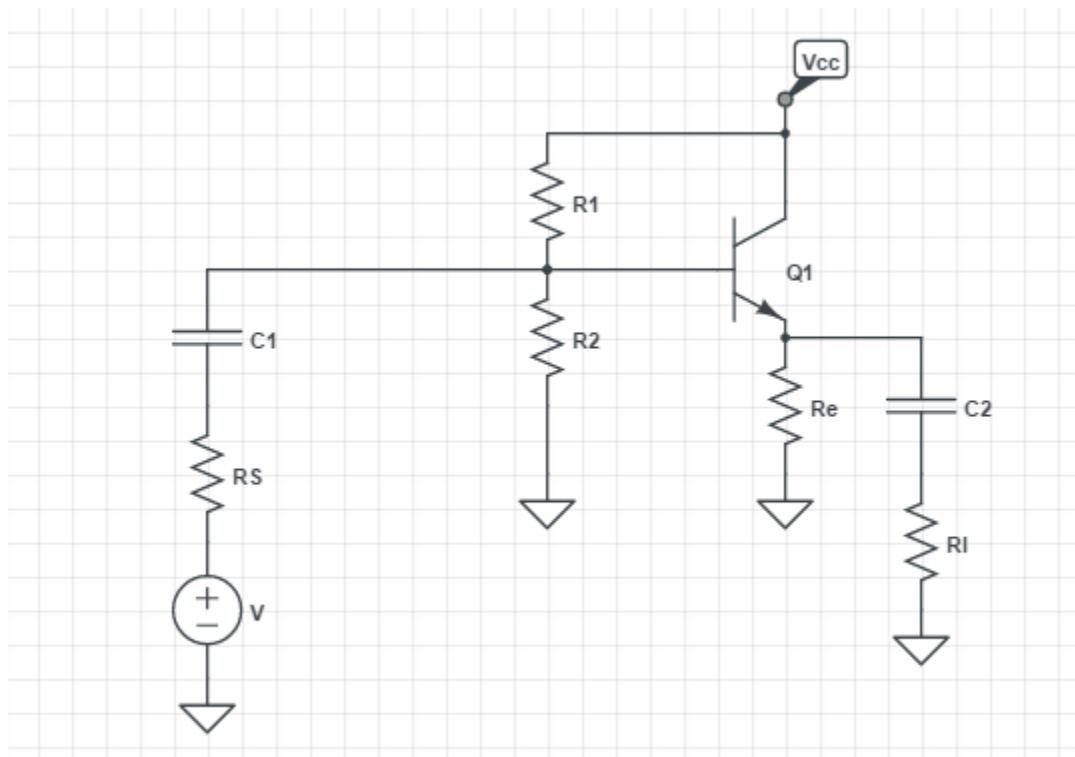


Fig.6

Problem 6. For the emitter follower circuit in figure 6 suppose that $h_{FE}=h_{fe}=100$, $R_1=R_2=26\text{k-ohm}$, $R_e=R_L=2\text{kohm}$, $R_s=1\text{k ohm}$ and $V_{cc}=10\text{V}$. Find (i) V_e/V_b , (ii) R_{in} and (iii) R_o


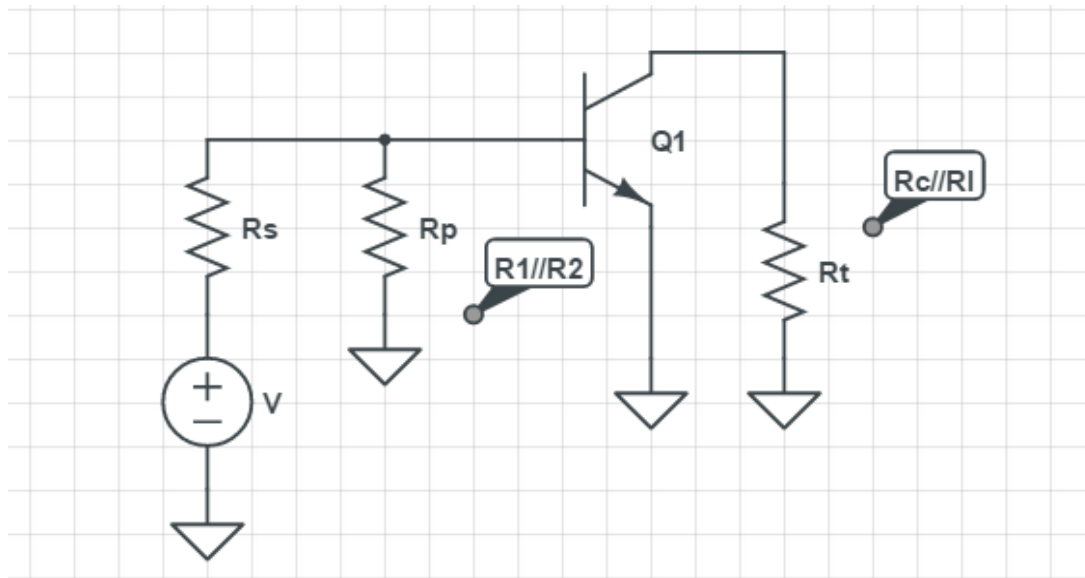


Fig.7

(a)

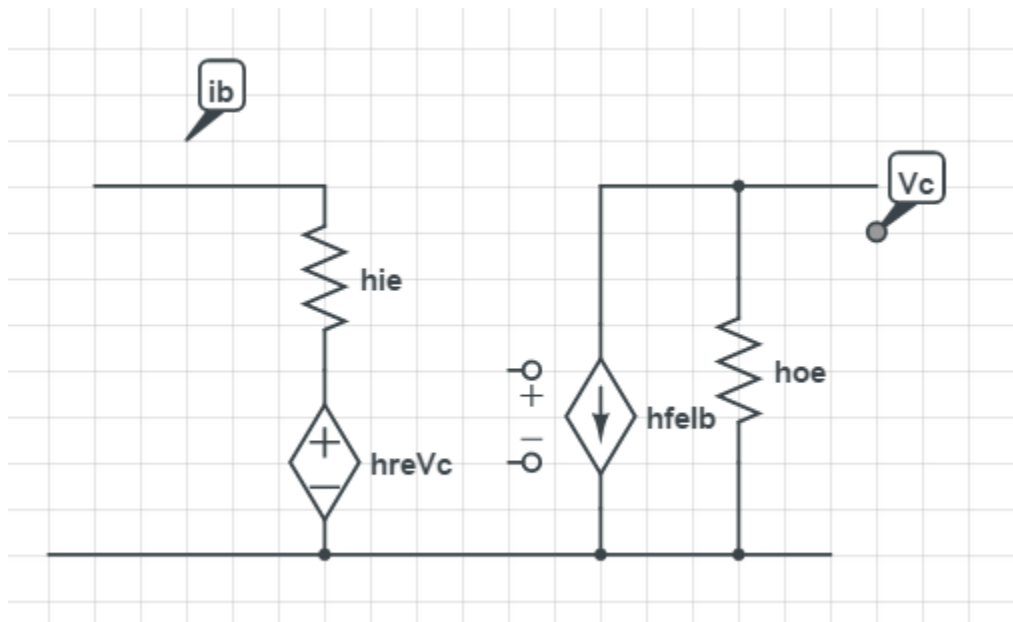

(b)

Problem7. Assume figure 7b to be the equivalent small signal model of the transistor in figure 7a. Calculate V_c/V_b for the circuit in the figure taking $R_c=R_L=2k$ ohm, $h_{ie}=1.3K$ ohm, $h_{re}=10^{-4}$, $h_{fe}=100$, $h_{oe}=10^{-5}$ mho. Now, repeat the calculation without h_{re} and h_{oe} . How does the answer differ.