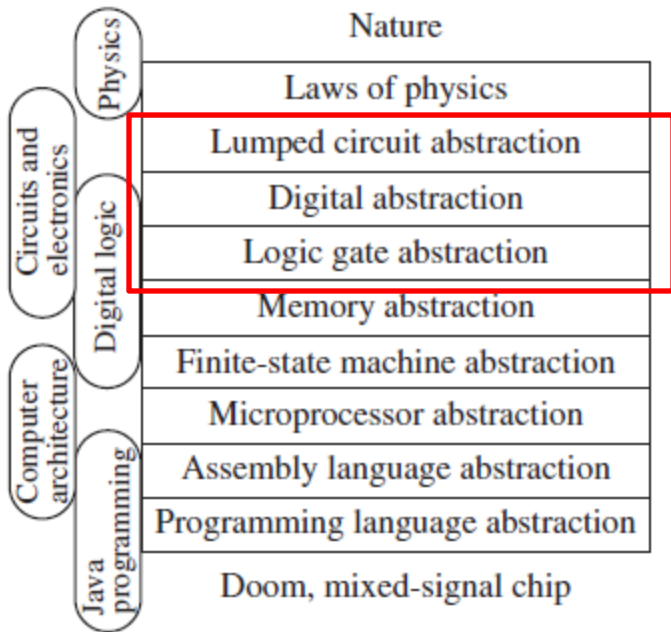


# EE101: Circuit elements and laws


S. Lodha

*References: 1) L. Bobrow, 2) Agarwal and Lang*

# Layers of Abstraction



**Example 1**

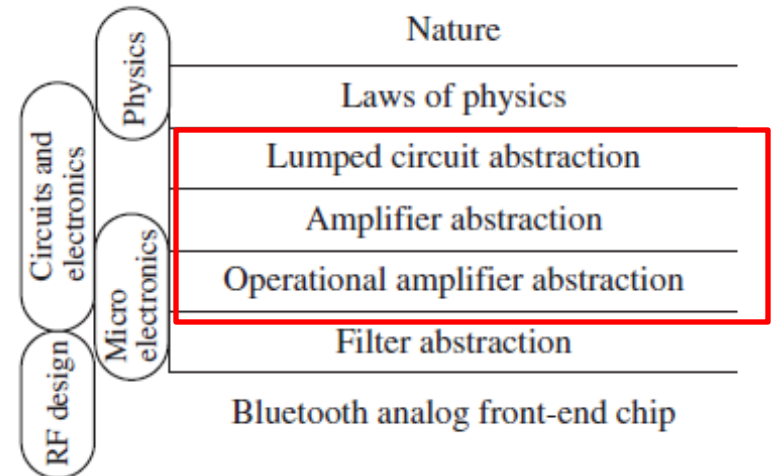

**Example 2**


- Multiple layers of abstraction to build modern complex systems

# Maxwell's laws

DIFFERENTIAL FORM	INTEGRAL FORM	POPULAR NAME
$\nabla \cdot \mathbf{E} = \frac{\rho}{\epsilon_0}$	$\oint \mathbf{E} \cdot d\mathbf{S} = \frac{q}{\epsilon_0}$	Gauss's law for electricity
$\nabla \cdot \mathbf{B} = 0$	$\oint \mathbf{B} \cdot d\mathbf{S} = 0$	Gauss's law for magnetism
$\nabla \times \mathbf{E} = -\frac{\partial \mathbf{B}}{\partial t}$	$\oint \mathbf{E} \cdot d\mathbf{l} = -\frac{\partial \Phi_B}{\partial t}$	Faraday's law of induction
$\nabla \times \mathbf{B} = \mu_0 \epsilon_0 \frac{\partial \mathbf{E}}{\partial t} + \mu_0 \mathbf{J}$	$\oint \mathbf{B} \cdot d\mathbf{l} = \mu_0 \epsilon_0 \frac{\partial \Phi_E}{\partial t} + \mu_0 i$	Ampere's law (extended)
$\nabla \cdot \mathbf{J} = -\frac{\partial \rho}{\partial t}$	$\oint \mathbf{J} \cdot d\mathbf{S} = -\frac{\partial q}{\partial t}$	Continuity equation

- Laws of physics describing natural phenomena
- Faraday's law and Continuity equation are critical to circuit analysis

# Lumped circuit element

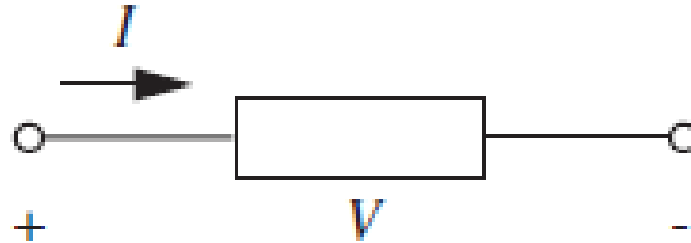

- ***Unique value*** of voltage from one terminal to another
- ***Unique value*** of current entering one terminal and exiting the other
- Elements in a circuit interact only through their terminal voltages and currents
  - No electric or magnetic field outside the elements that can cause interaction
  - Counter example?

# Lumped element



1. Rate of change of magnetic flux through any closed loop outside an element = 0 for all time

$$\oint \mathbf{E} \cdot d\mathbf{l} = -\frac{\partial \Phi_B}{\partial t} \quad \boxed{\frac{\partial \Phi_B}{\partial t} = 0}$$

2. No time varying charge within the element for all time

$$\oint \mathbf{J} \cdot d\mathbf{S} = -\frac{\partial q}{\partial t} \quad \boxed{\frac{\partial q}{\partial t} = 0}$$

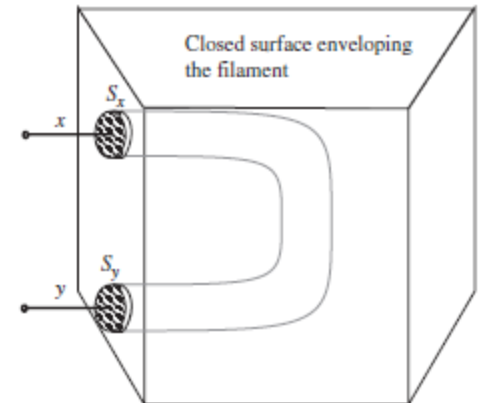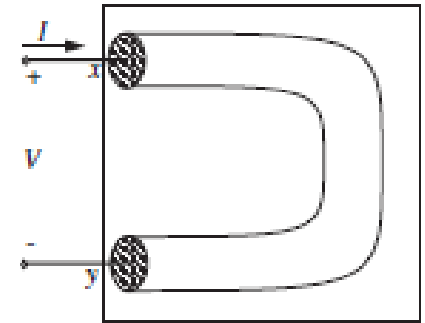3. Operate where signal timescales  $\gg$  propagation delay of EM waves  $\rightarrow$  instantaneous propagation of the signals (electromagnetic waves  $\rightarrow$  wavelength of the V and I signals is  $\gg$  size of the element)



# Lumped circuit

- Rate of change of magnetic flux linked with any portion of the circuit must be zero for all time

**Kirchoff's voltage law**

- Rate of change of the charge at any node (connection of two or more element terminals) must be zero

**Kirchoff's current law**

- Signal timescales must be much larger than the propagation delay of electromagnetic waves through the circuit

**Critical assumption → see next slide**

# Signal propagation

- Circuit must be smaller than the wavelength of the light at highest operating frequency of interest
  - e.g. 1 kHz, 1 MHz and 1 GHz circuits have to be smaller than 300 km, 300 m and 300 mm respectively
  - Else model wave phenomena accurately
  - Will a 5000-km power grid at 60 Hz or a 30 cm computer motherboard at 1 GHz satisfy this condition?


# Signal propagation

- Latest microprocessor (June 2015)
  - Intel Broadwell 14nm (i7, 37.5x37.5 mm, 3.3 GHz)
- Propagation speed of electromagnetic signals
  - In vacuum  $\rightarrow$  30 cm per ns
  - Approx  $\frac{1}{2}$  of that in microproc. ( $\epsilon=4$ )  $\rightarrow$  15 cm per ns
  - $\sim 1/4$  ns to propagate through 37.5mm ( $\sim 4$  cm)
  - 3.3 GHz  $\rightarrow$   $1/3.3$  ns for a clock cycle
  - Propagation delay is the same as one clock cycle!
  - Need distributed circuit models using waveguides, transmission lines etc.



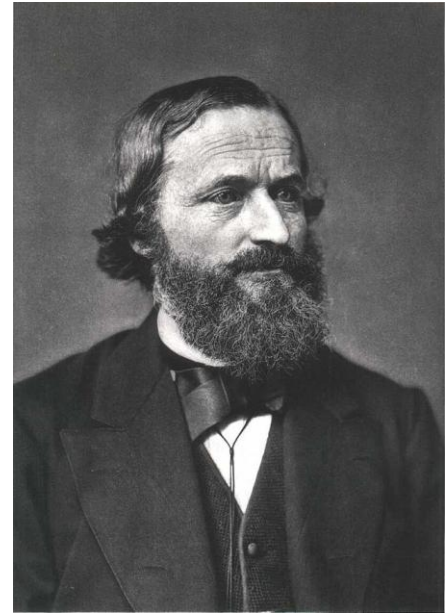
# Gustav Kirchhoff (1824- 1887)

- Kirchhoff's laws- 1845 (graduate student)
- Other contributions
  - Three laws in spectroscopy
  - Discovery of caesium and rubidium with Bunsen
  - Emission of black body radiation



# Kirchoff's laws

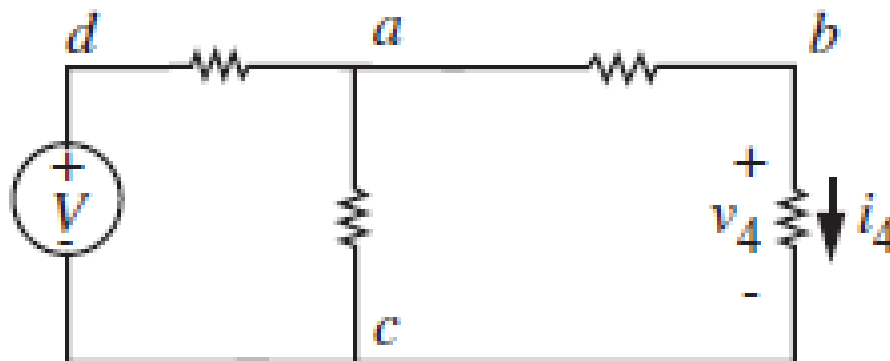

$$\oint \mathbf{E} \cdot d\mathbf{l} = -\frac{\partial \Phi_B}{\partial t}$$


$$\oint \mathbf{E} \cdot d\mathbf{l} = 0 \quad \text{For closed circuit loops}$$

$$\oint \mathbf{J} \cdot d\mathbf{S} = -\frac{\partial q}{\partial t}$$


$$\oint \mathbf{J} \cdot d\mathbf{S} = 0. \quad \text{For circuit nodes}$$

Reading: Appendix A.2 of A. Agarwal's book

# Kirchoff's laws

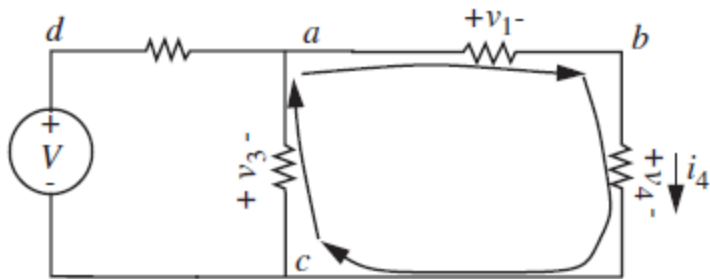
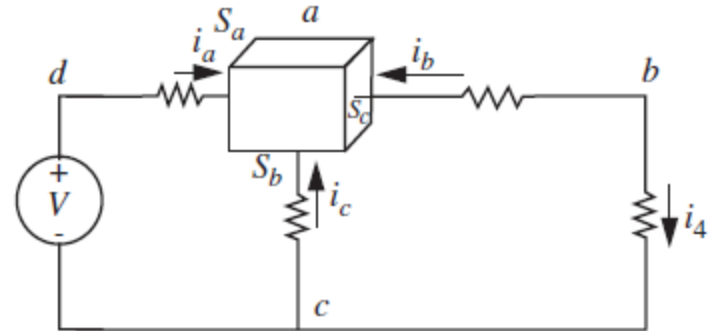
$$\int_a^b \mathbf{E} \cdot d\mathbf{l} + \int_b^c \mathbf{E} \cdot d\mathbf{l} + \int_c^a \mathbf{E} \cdot d\mathbf{l} = v_1 + v_2 + v_3 = 0.$$




$$\int_{S_a} \mathbf{J} \cdot d\mathbf{S} + \int_{S_b} \mathbf{J} \cdot d\mathbf{S} + \int_{S_c} \mathbf{J} \cdot d\mathbf{S} = -i_a - i_b - i_c = 0.$$

- Algebraic sum of voltages around any closed path in a network is zero.
- Algebraic sum of currents flowing into any node is zero.

# Kirchoff's Current Law (KCL)

- A connection of two or more elements is called a node (solid dot)
- KCL:
  - At any node of a circuit, at every instant of time, the sum of currents into the node is equal to the sum of currents out of the node
  - At any node of a circuit, the currents algebraically sum to zero

# Example

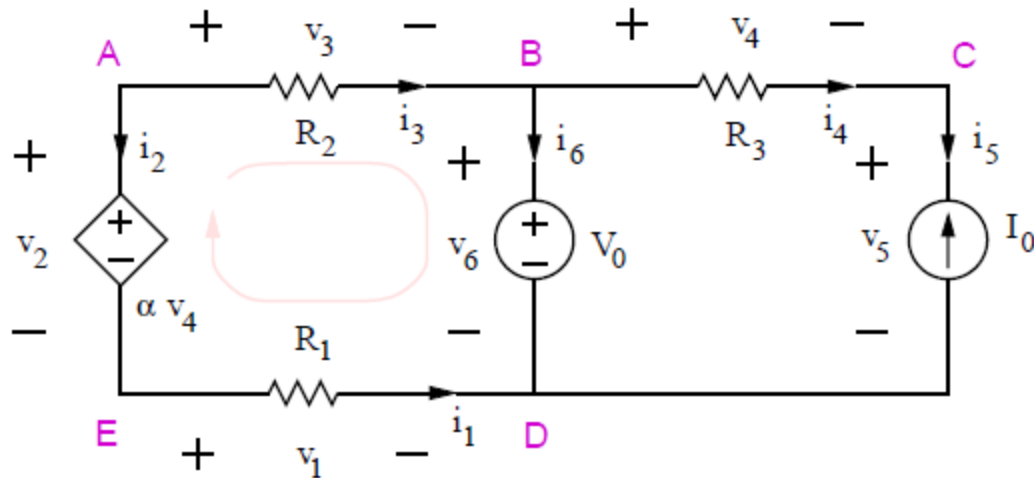


- At node B:  $-i_3 + i_6 + i_4 = 0$
- Convention: Current leaving a node is positive
- In general KCL is also applicable for any closed region of the circuit (conservation of charge)

# Kirchoff's Voltage Law (KVL)



- Loop: Starting at any node  $n$  in a circuit, we form a loop by traversing through elements (open circuits included) and returning to the starting node  $n$ , and never encountering any other node more than once.
- KVL:
  - In traversing any loop in any circuit, at every instant of time, the sum of the voltages having one polarity equals the sum of the voltages having the opposite polarity.
  - Around any loop in a circuit, the voltages algebraically sum to zero.

# Example

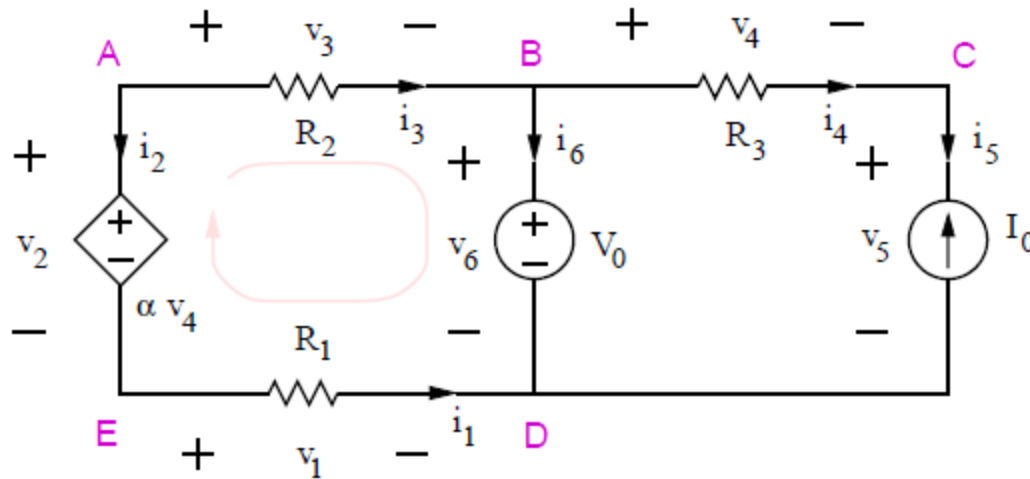


- For the loop:  $v_3 + v_6 - v_4 - v_2 = 0$
- Convention: Voltage drop is positive

# KCL examples

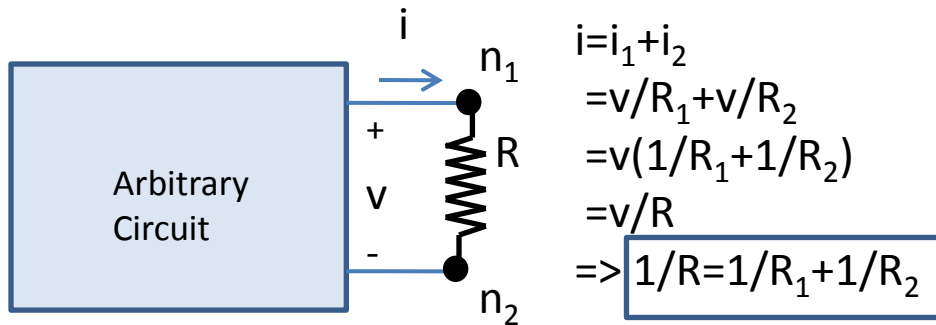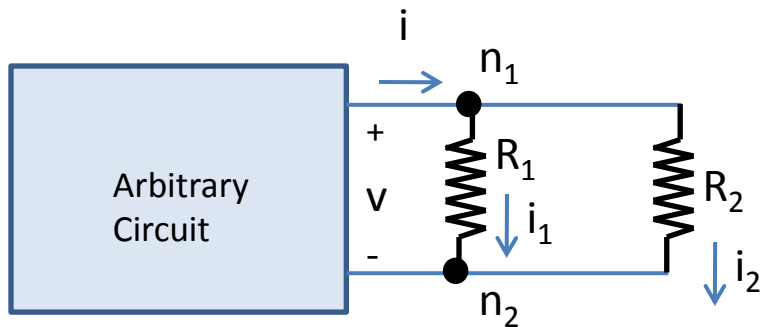

**Resistances in parallel**

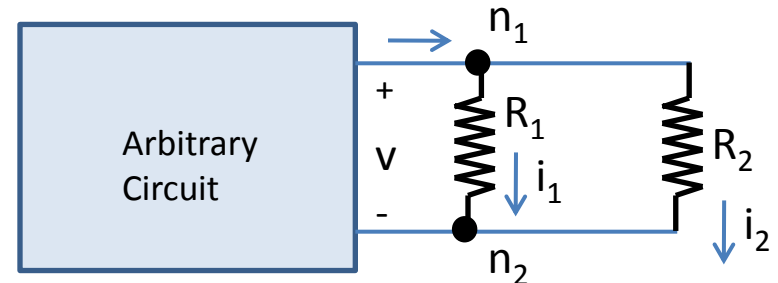

$$v = i[R_1 R_2 / (R_1 + R_2)]$$

$$i_1 = v/R_1 \text{ and } i_2 = v/R_2$$

Therefore,

$$i_1 = i (R_2 / (R_1 + R_2))$$



$$i_2 = i (R_1 / (R_1 + R_2))$$

**Current Division**


- Assume  $R_1 \gg R_2 \Rightarrow i_2 \gg i_1$
- Current takes the path of least resistance!



# KVL Examples

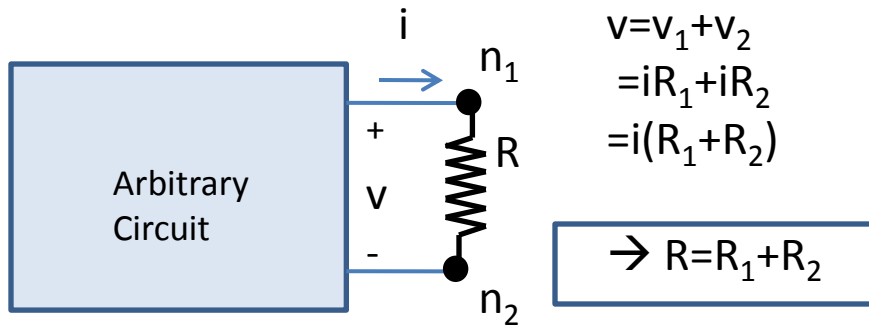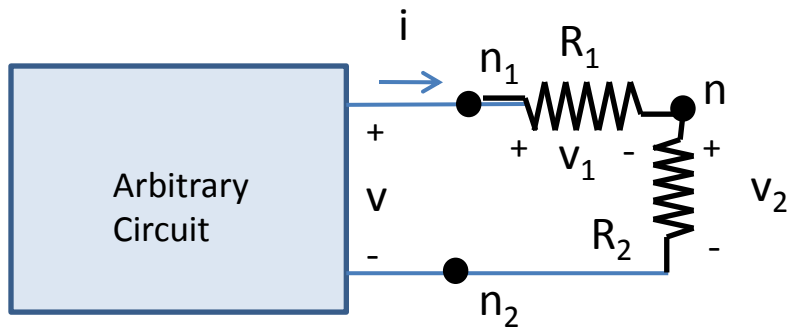

**Resistances in series**

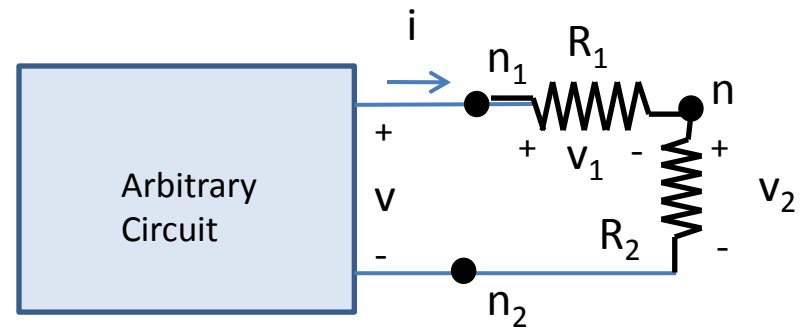

$$i = v / (R_1 + R_2)$$






$$v_1 = iR_1 = v(R_1 / (R_1 + R_2))$$

$$v_2 = iR_2 = v(R_2 / (R_1 + R_2))$$

**Voltage Division**







- Assume  $R_1 \gg R_2 \Rightarrow v_1 \gg v_2$
- Larger voltage drop across the larger resistor

# Circuit Elements

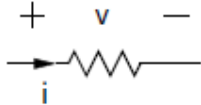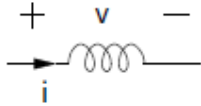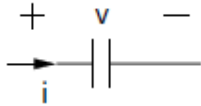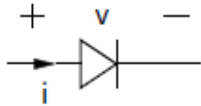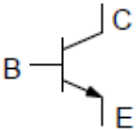Element	Symbol	Equation
Resistor		$v = R i$
Inductor		$v = L \frac{di}{dt}$
Capacitor		$i = C \frac{dv}{dt}$
Diode		to be discussed
BJT		to be discussed


- Some typical elements

# Ideal Current and Voltage Sources

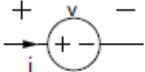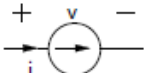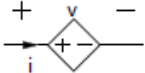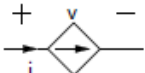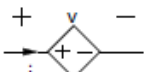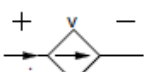
	Element	Symbol	Equation
Independent	Voltage source		$v(t) = v_s(t)$
	Current source		$i(t) = i_s(t)$
Dependent	VCVS		$v(t) = \alpha v_c(t)$
	VCCS		$i(t) = g v_c(t)$
	CCVS		$v(t) = r i_c(t)$
	CCCS		$i(t) = \beta i_c(t)$

- Note that these can be time dependent sources

# Voltage Source

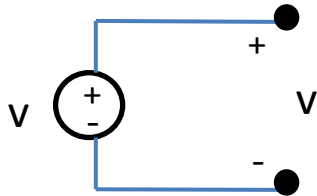


Ideal

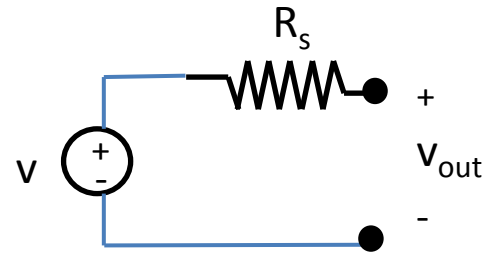


Non-ideal

- An ideal voltage source produces a voltage or potential difference of  $v$  volts across its terminals regardless of what is connected to it
  - Except for a short circuit ( $R=0$ )
  - Current flowing through it can take any value
- You cannot have two (or more) ideal voltage sources connected to the same pair of terminals

# Current Source

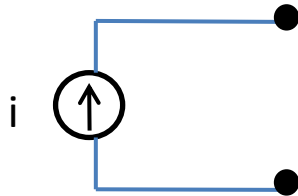

Ideal

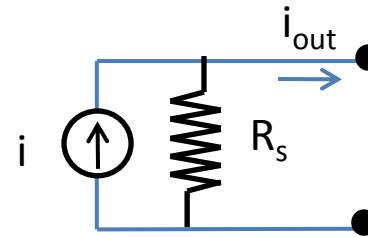

Non-ideal

- An ideal current source produces  $i$  amperes regardless of what is connected to it
  - Except for an open circuit ( $R=\infty$ )
  - It can take any voltage across its terminals
- You cannot have two (or more) ideal current sources in series