

Operational Amplifiers and Linear Op-Amp Circuits

S. Lodha


References: L. Bobrow's book and Prof. M. B. Patil's slides

Op-Amps

- Most basic Analog IC
 - Also called linear amplifier
- Why is it better than a BJT (ac) amplifier?
 - No need of coupling and bypass capacitors
 - Low frequency response can go to dc
 - Easy fabrication
 - Smaller in size and economical
- Versatile building block for large variety of electronic circuits
 - Oscillators, comparators, rectifiers, filters etc.
- Works with dc voltages also → applications in sensing, e.g. temperature, pressure etc.
- Nearly ideal characteristics → ckts work as per theoretical design


Op Amp 741

Internal Ckt

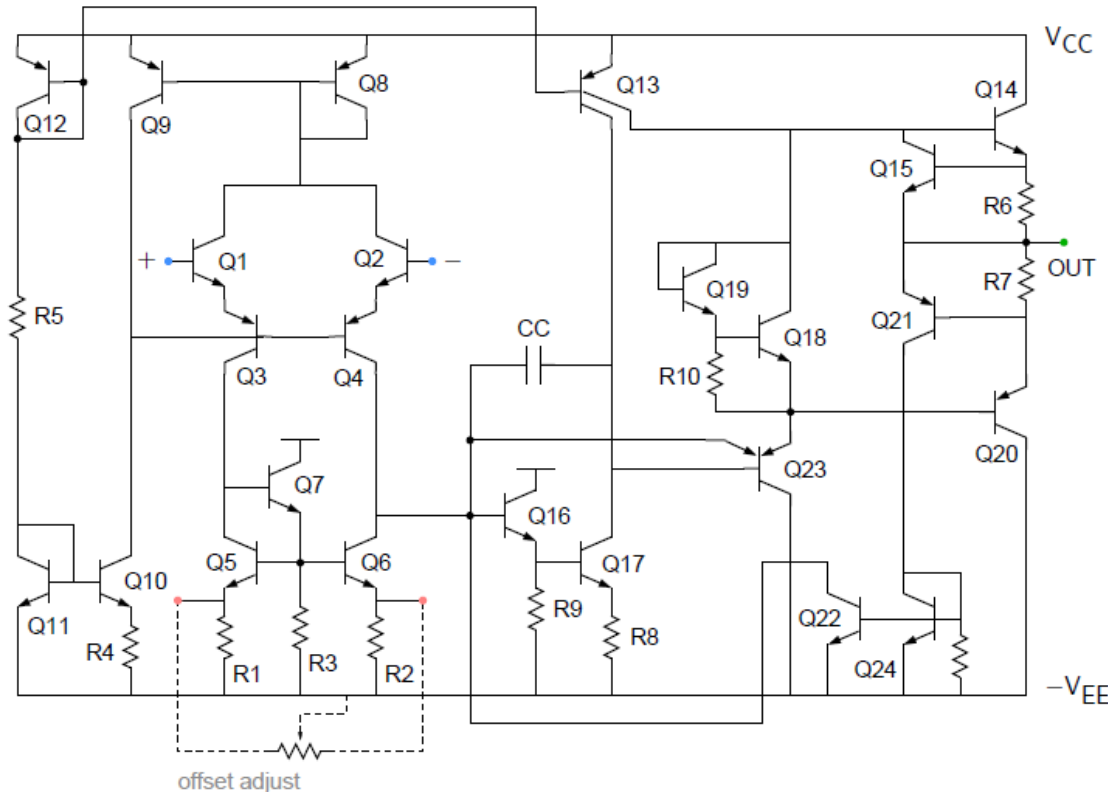


24 BJTs, 11 resistors and a capacitor

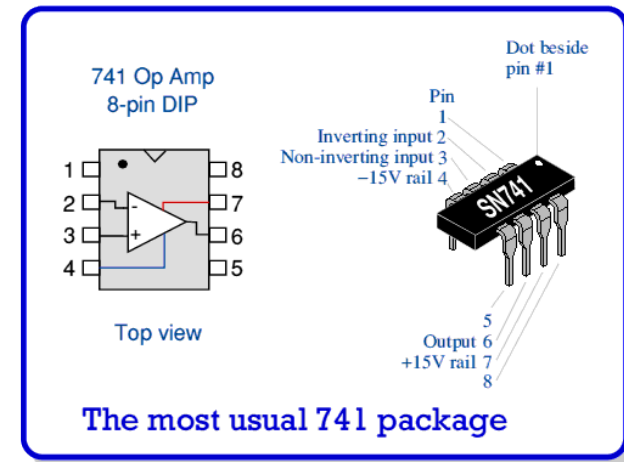
- The user need not worry about internal details
 - Easy to design circuits



Symbol

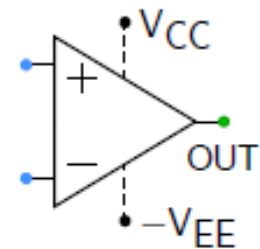


Equivalent Circuit

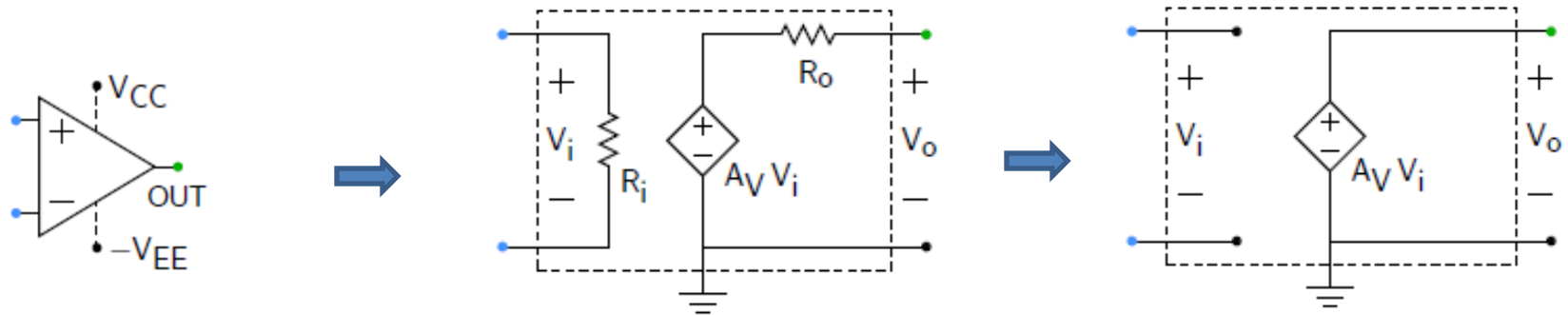

- Compared to external resistances, $R_i \rightarrow \infty$ and $R_o \rightarrow 0$
- V_{CC} and V_{EE} are supply voltages, typically ± 15 V
- Parameters



Parameter	Ideal Op-Amp	741
A_v	∞	10^5 (100 dB)
R_i	∞	2 M Ω
R_o	0	75 Ω

Op-Amp: Internal Blocks

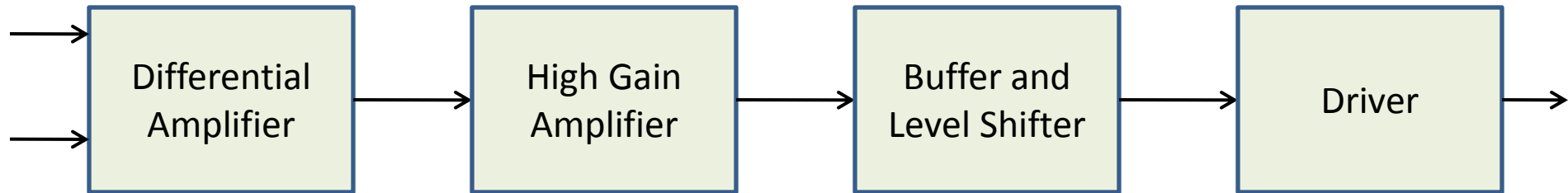


- Differential amplifier provides high R_{in}
- High gain amplifier provides additional gain
- Buffer is typically an emitter follower
- Driver is a large signal (power) amplifier with low output resistance

Modes of operation

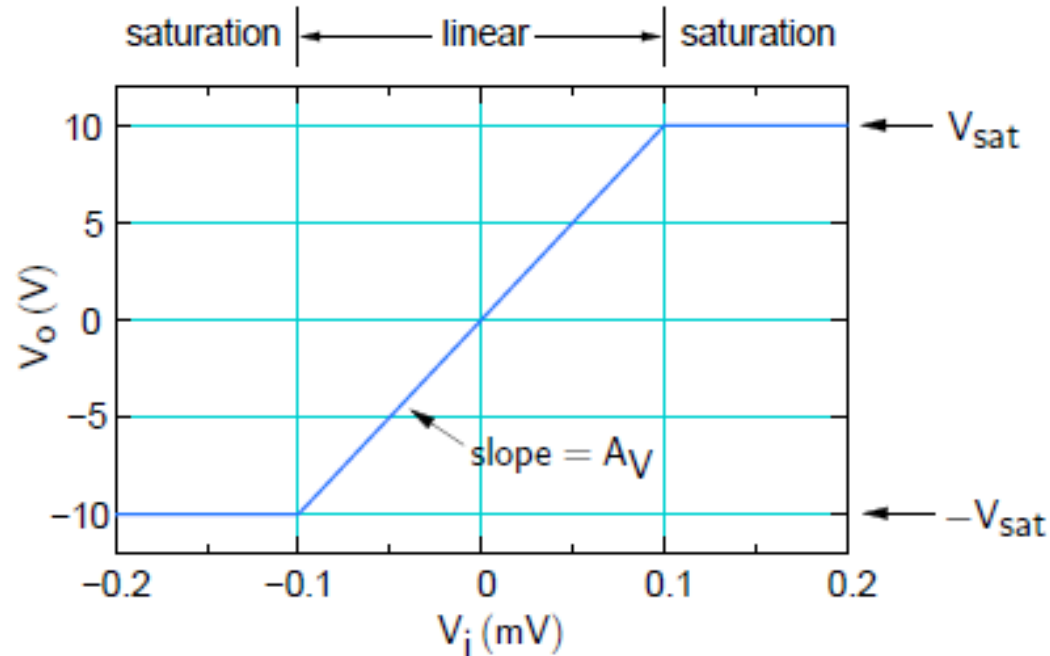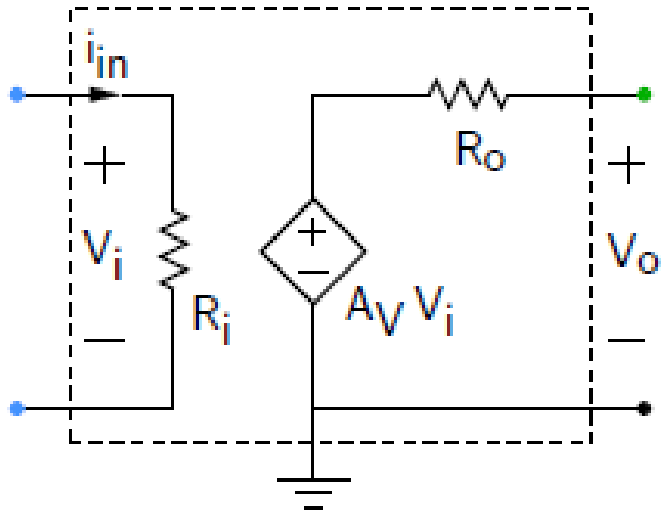

- Two modes \rightarrow linear and saturation
 - Depends on magnitude of input voltage and feedback
- Output is limited to $V_{sat} \sim V_{CC} - 1.5$ V
- In linear region
 - $V_i = V_+ - V_- = V_o / A_V \rightarrow 0$, hence $V_+ \sim V_-$ (V_+ and V_- are virtually the same)
 - $i_{in} \sim 0$

Linear Op-Amp Circuits: Example 1

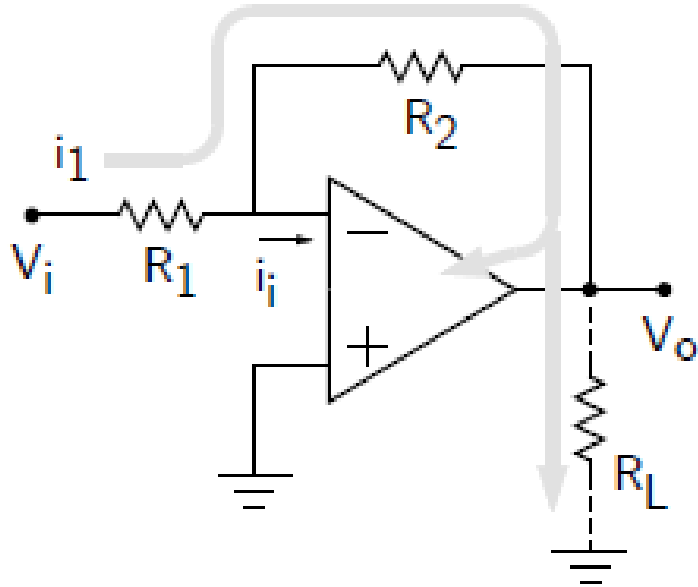







$$V_- \sim V_+ = 0V \Rightarrow i_1 = \frac{V_i}{R_1}$$

$$V_o = V_- - i_1 R_2 = 0 - \left(\frac{R_2}{R_1} \right) V_i = - \left(\frac{R_2}{R_1} \right) V_i$$

$$V_o = - \left(\frac{R_2}{R_1} \right) V_i$$


- Non inverting input is at real ground.
- Inverting input is at “virtual” ground.
- Inverting amplifier
- $-\left(\frac{R_2}{R_1}\right)$ is the “closed loop” gain. “Open loop” gain is the gain of the op amp ($\sim 10^5$)
- Effective input resistance is $V_i/i_1 = R_1$

Simulation Examples

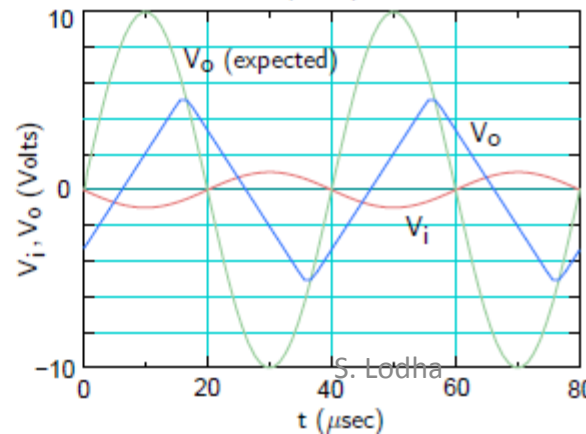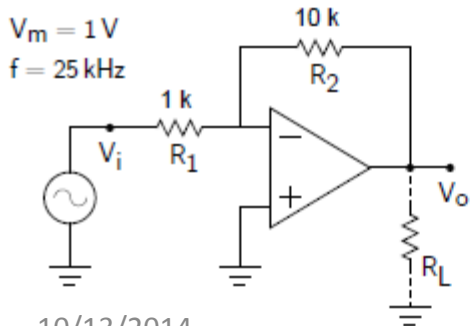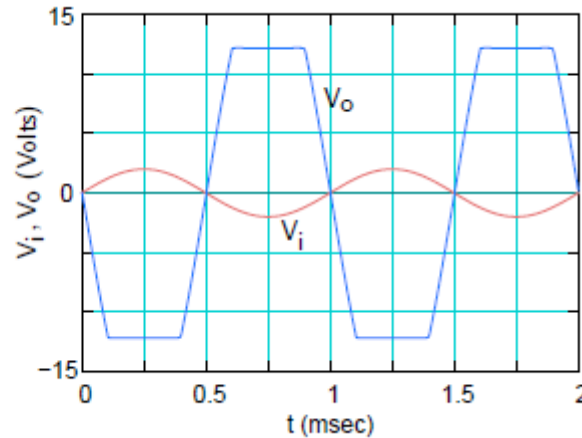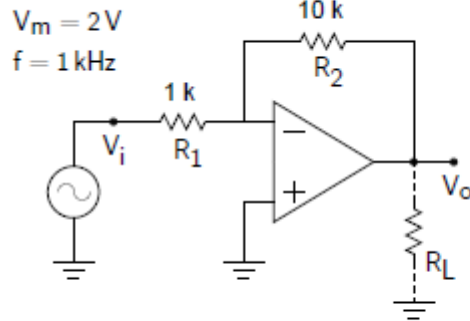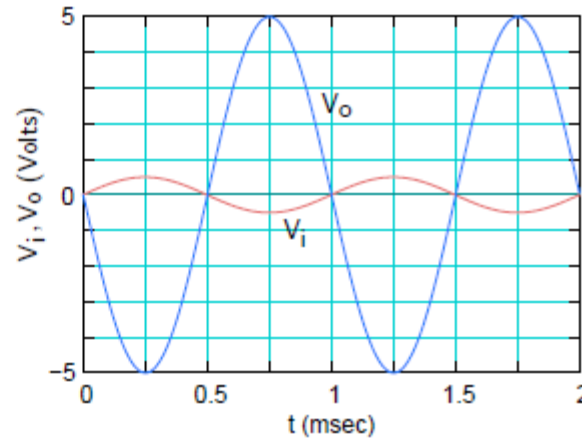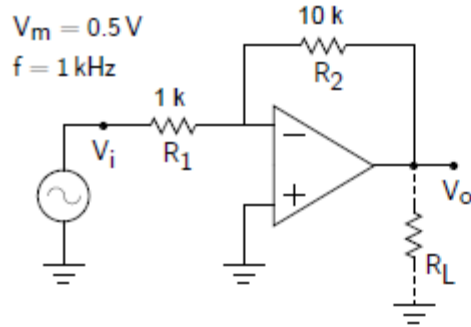

- Adjustable gain using R_2 and R_1
 - BJT $\rightarrow -g_m R_T$ depends on biasing
- Output voltage limited to $V_{\text{sat}} \sim V_{\text{CC}} - 1.5\text{ V}$
- Output rise/fall not able to keep up with high frequency signals
 - Slew rate of 741 is $0.5\text{ V}/\mu\text{sec}$

Linear Op-Amp circuits: Example 2

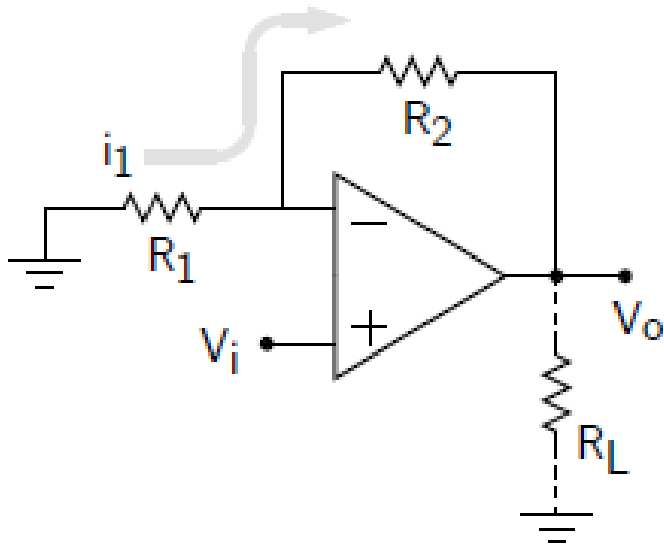





$$V_- \sim V_+ = V_i \Rightarrow i_1 = -\frac{V_i}{R_1}$$

$$V_o = V_i - i_1 R_2 = V_i - \left(-\frac{V_i}{R_1}\right) R_2 = \left(1 + \frac{R_2}{R_1}\right) V_i$$

$$V_o = \left(1 + \frac{R_2}{R_1}\right) V_i$$


- Non-inverting amplifier
- Swapping terminals will change the entire circuit (negative \rightarrow positive) feedback
- Effective input resistance is $R_i \rightarrow \infty$

Inverting or non-inverting?

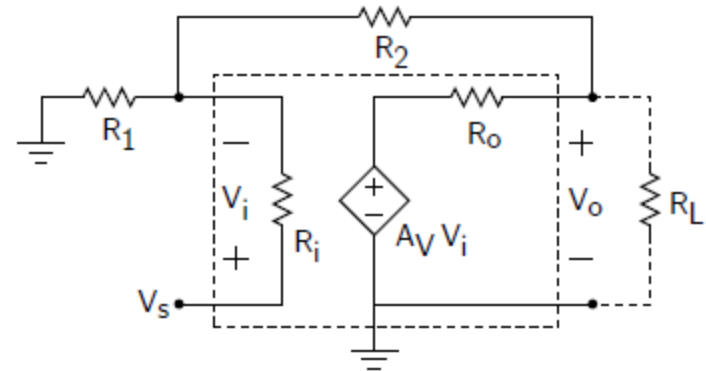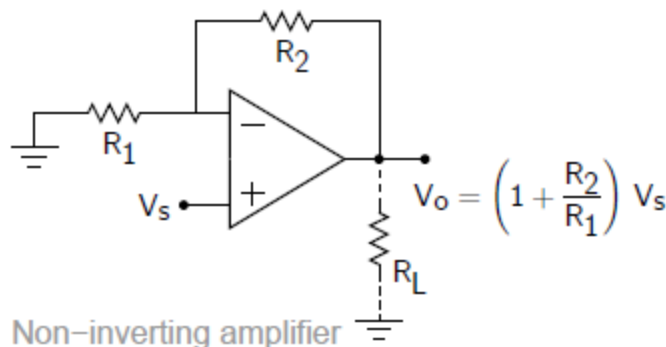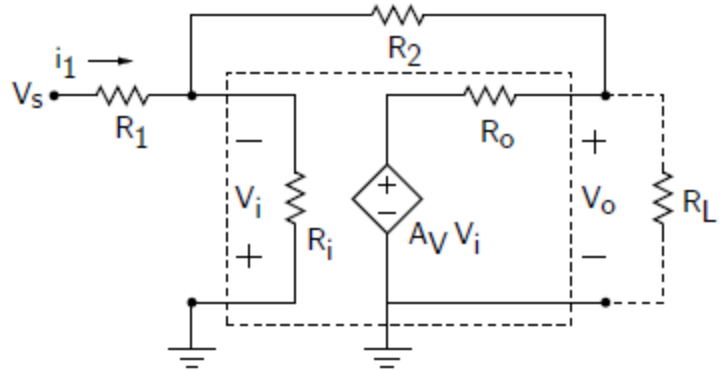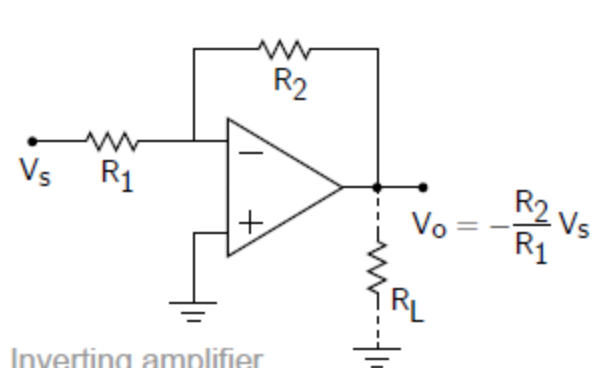

- For inverting amp, $R_{in} = V_s / i_1 = R_1$
- For non-inverting amp, $R_{in} \sim R_i$, which is a few $M\Omega$.
Hence if large R_{in} is needed, non-inverting is preferred


Linear Op-amp circuits: Example 3

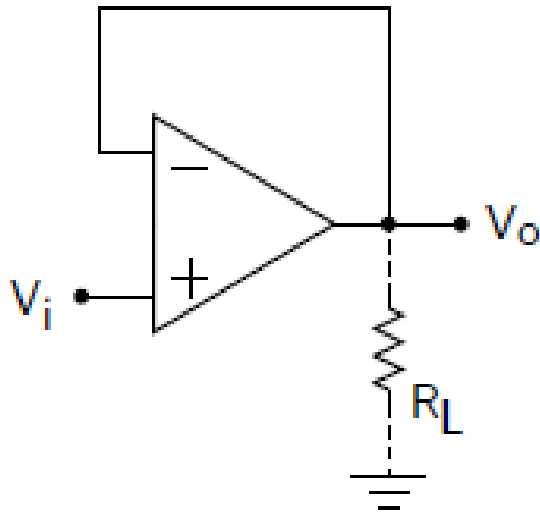

$$V_o = \left(1 + \frac{R_2}{R_1}\right) V_i = V_i$$

- Modified non-inverting amp, $R_1 = \infty$, $R_2 = 0$
- Unity-gain amplifier / voltage follower / buffer

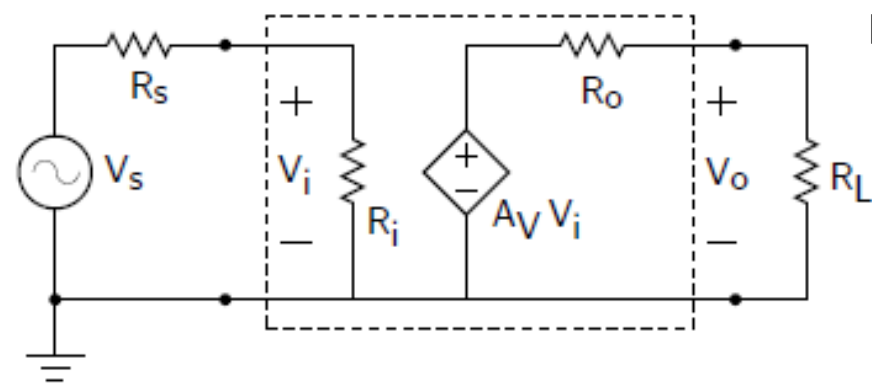Use of Buffer/voltage follower: Avoid Loading



Ideally $V_o = A_v V_s$

But

$$V_o = \frac{R_L}{R_o + R_L} A_v V_i = A_v \frac{R_L}{R_o + R_L} \frac{R_i}{R_i + R_s} V_s$$


Requires

$$R_i \rightarrow \infty$$

$$R_o \rightarrow 0$$


- Buffer/voltage follower provides both $R_i \rightarrow \infty$
 $R_o \rightarrow 0$

R_{in} and R_o of Buffer

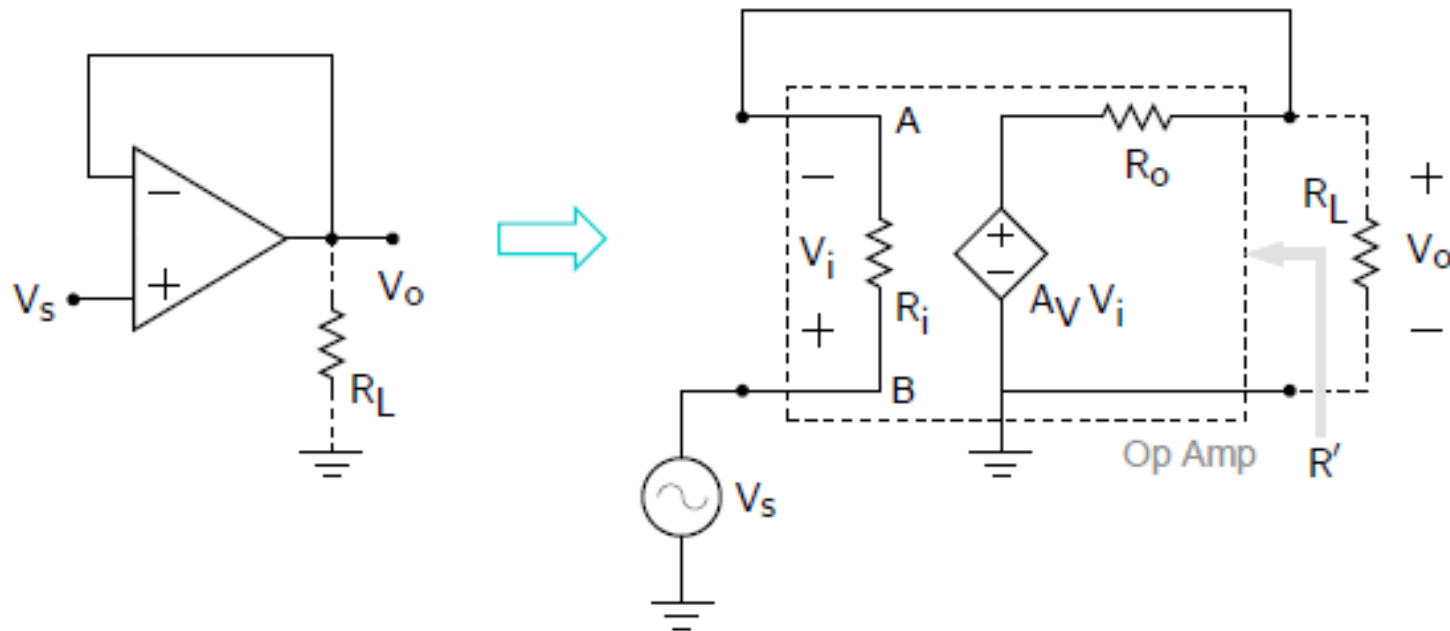

- Current from V_s is small \rightarrow **High input resistance** due to high input resistance of the amplifier
- Output resistance is $R' = R_o \rightarrow$ **low** because the output resistance of the amplifier is low

Use of buffer

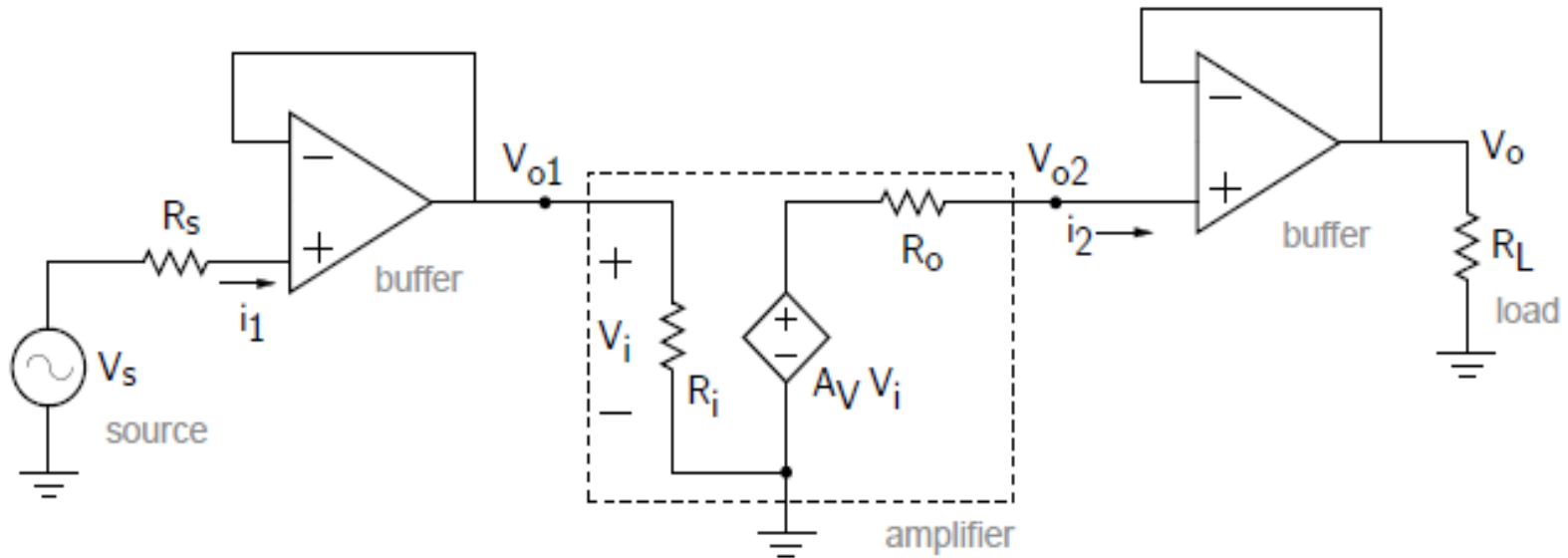


$$i_1 \approx 0, V_{o1} = V_s$$

$$i_2 \approx 0, V_{o2} = A_v V_s$$

$$V_o = V_{o2} = A_v V_s$$

Irrespective of R_s and R_L

Linear Op-Amp circuits: Example 4

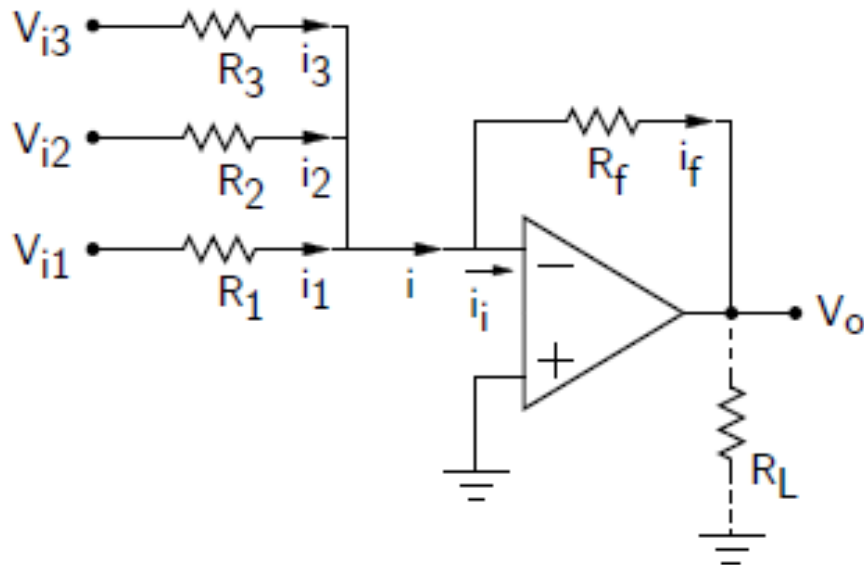


$$V_o = -\left(\frac{R_f}{R_1}V_{i1} + \frac{R_f}{R_2}V_{i2} + \frac{R_f}{R_3}V_{i3}\right) = -\frac{R_f}{R}(V_{i1} + V_{i2} + V_{i3})$$


$$R_1 = R_2 = R_3 = R = 1\text{k}\Omega$$

$$R_f = 2\text{k}\Omega$$

“Summer” if $R_1 = R_2 = R_3$

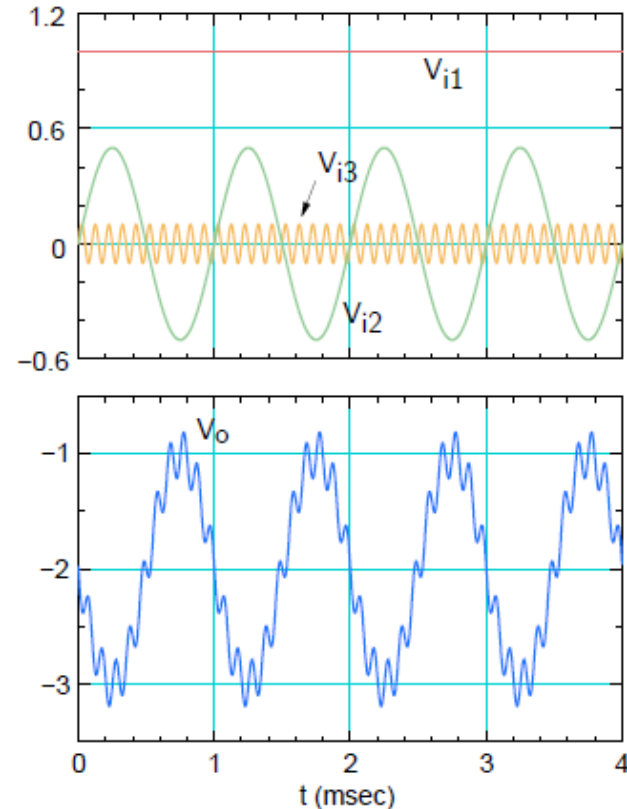

Difference Amplifier

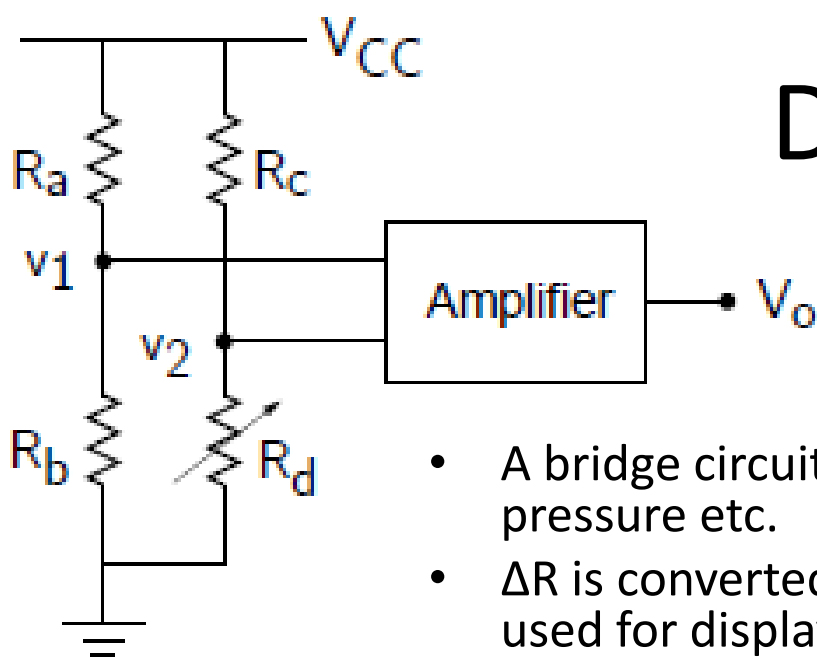

- A bridge circuit for sensing changes in temperature, pressure etc.
- ΔR is converted to a signal voltage by bridge, amplified and used for display/control

$$R_a = R_b = R_c = R$$

$$R_d = R + \Delta R \quad \leftarrow \text{Varies with quantity to be measured}$$

$$v_1 = \frac{R}{R+R} V_{cc} = \frac{1}{2} V_{cc}$$

$$v_2 = \frac{(R + \Delta R)}{R + (R + \Delta R)} V_{cc} = \frac{1}{2} \frac{1+x}{1+x/2} V_{cc} \approx \frac{1}{2} (1+x) \left(1 - \frac{x}{2}\right) V_{cc} = \frac{1}{2} \left(1 + \frac{x}{2}\right) V_{cc}$$


$$x = \frac{\Delta R}{R}$$

Example: $V_{cc}=15V$, $R=1k$, $\Delta R=0.01k$

$v_1=7.5V$

$v_2=7.5+0.0375 V$

Common and differential mode

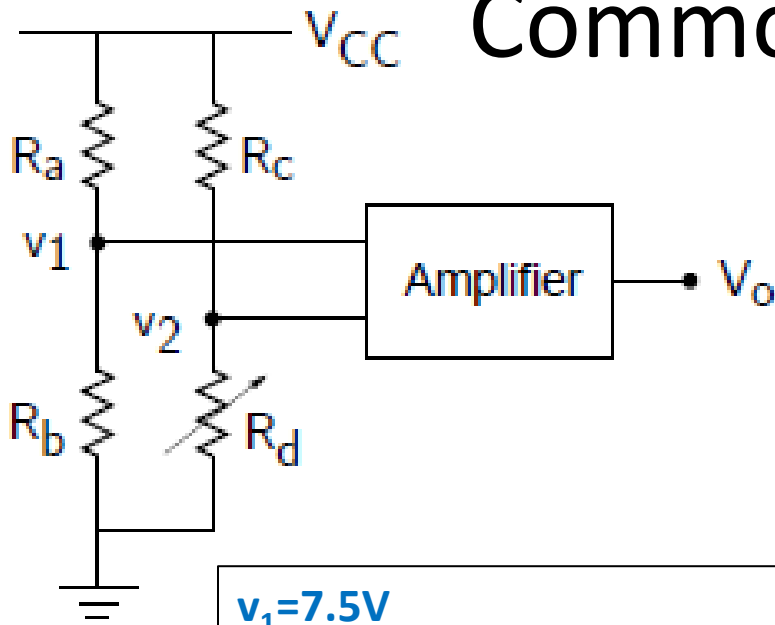

$$v_1 = \frac{1}{2} V_{CC}$$

$$v_2 = \frac{1}{2} \left(1 + \frac{x}{2}\right) V_{CC}$$

$$x = \frac{\Delta R}{R}$$

$$v_1 = 7.5V$$

$$v_2 = 7.5 + 0.0375V$$

Amplifier should only amplify 0.0375V → signal from ΔR

Define:

$$v_c = \frac{1}{2} (v_1 + v_2)$$

Common-mode voltage

$$v_d = (v_2 - v_1)$$

Differential-mode voltage


$$v_1 = v_c - \frac{v_d}{2}$$

$$v_2 = v_c + \frac{v_d}{2}$$

In example,

$$v_c \sim 7.5V, v_d \sim 0.0375V$$

Common-mode rejection

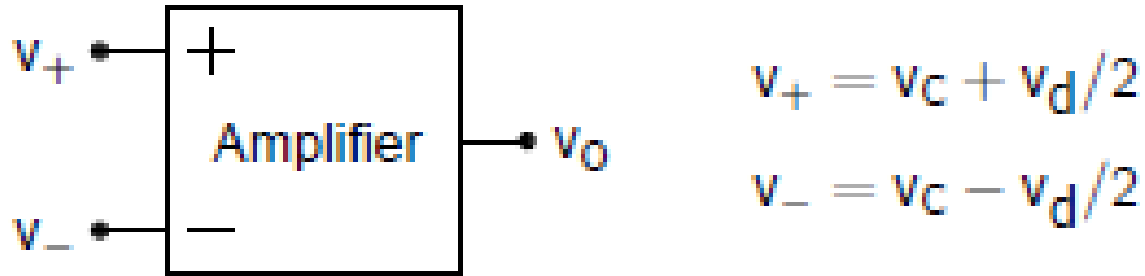

Ideally,

$$v_o = A_d (v_+ - v_-) = A_d v_d \quad A_d = \text{Differential gain}$$

In practice

$$v_o = A_d v_d + A_c v_c \quad A_c = \text{Common-mode gain}$$


Ability to reject
common-mode
signal

$$CMRR = \frac{A_d}{A_c}$$

Common **M**ode **R**ejection **R**atio

For the 741 Op Amp, CMRR=90dB (~30,000)

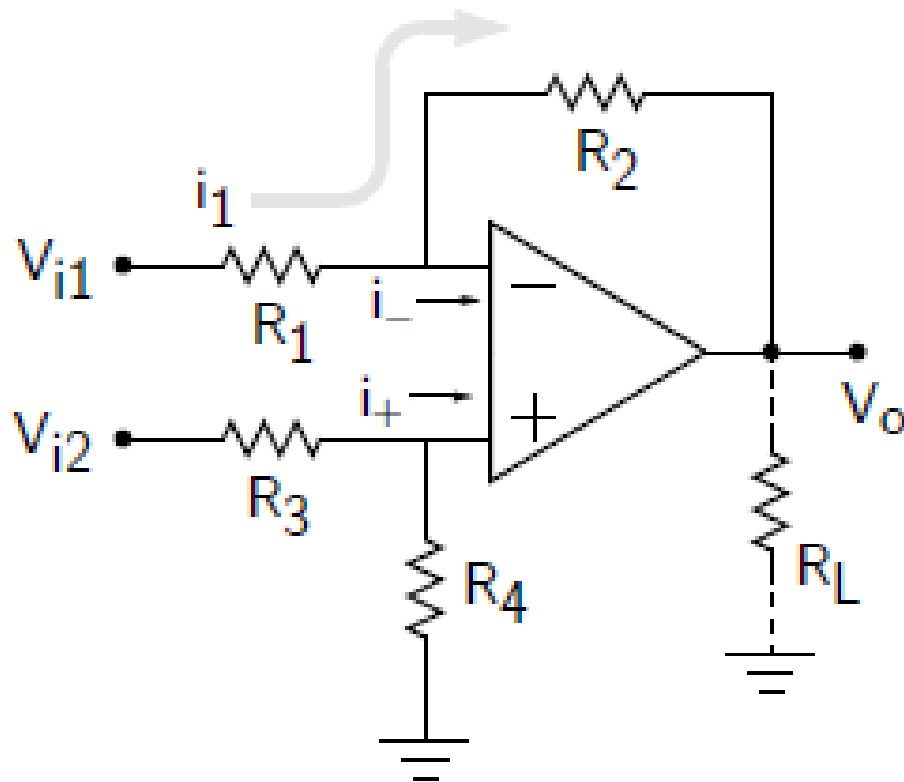Linear Op-Amps: Example 5 (Difference Amplifier)



$$i_+ = 0, V_+ = \frac{R_4}{R_3 + R_4} V_{i2}$$

$$i_1 = \frac{1}{R_1} (V_{i1} - V_+)$$



$$i_+ = 0 \Rightarrow V_o = V_+ - i_1 R_2 = V_+ - \frac{R_2}{R_1} (V_{i1} - V_+)$$

$$\frac{R_3}{R_4} = \frac{R_1}{R_2}$$


$$V_o = \frac{R_2}{R_1} (V_{i2} - V_{i1})$$

Difference Amplifier

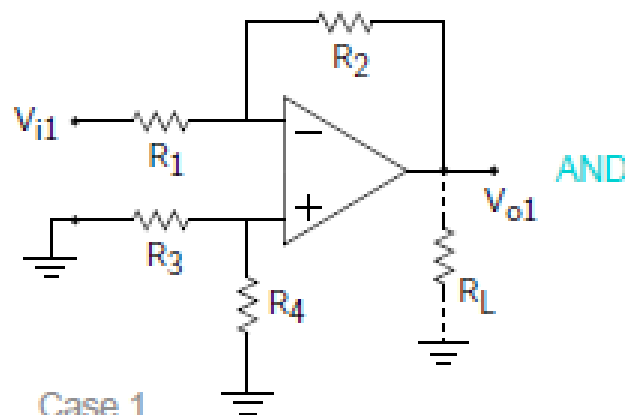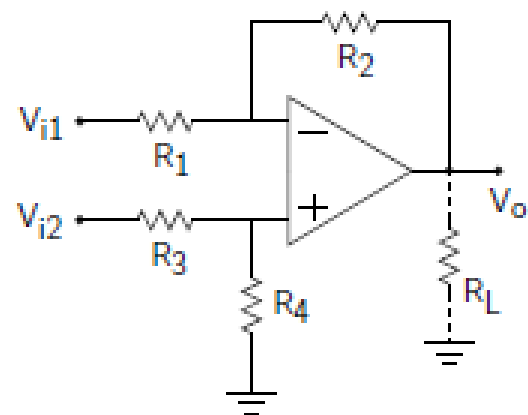Linear Op-Amps: Example 5 (Difference Amplifier)



AND

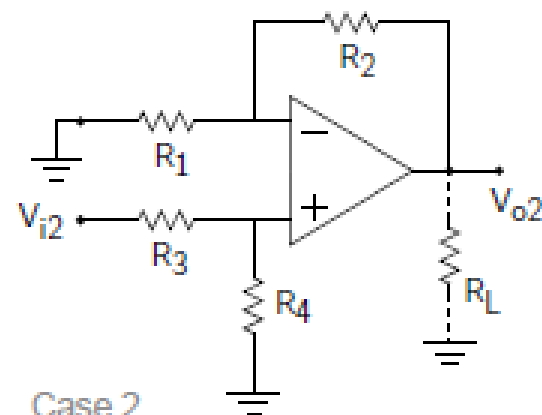

Case 1 (Inverting Amp)

Case 2 (Non-inverting amp)


$$V_{o1} = -\frac{R_2}{R_1} V_{i1}$$

$$V_{o2} = \left(1 + \frac{R_2}{R_1}\right) V_+ = \frac{R_4}{R_3 + R_4} \left(1 + \frac{R_2}{R_1}\right) V_{i2}$$

$$V_o = V_{o1} + V_{o2} = -\frac{R_2}{R_1} V_{i1} + \frac{R_4}{R_3 + R_4} \left(1 + \frac{R_2}{R_1}\right) V_{i2} = \frac{R_2}{R_1} (V_{i2} - V_{i1}) \text{ for } \frac{R_3}{R_4} = \frac{R_1}{R_2}$$

Difference Amplifier

Difference Amplifier: Problem 1

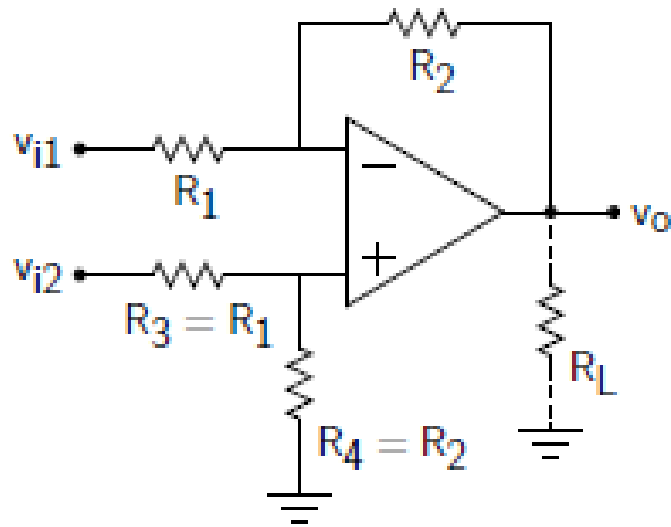

$$v_{i1} = v_c - v_d/2$$

$$v_{i2} = v_c + v_d/2$$

$$v_o = \frac{R_2}{R_1} (v_{i2} - v_{i1}) = A_d v_d$$

Common-mode gain $A_c = 0$

If $R_3 = R_1 + \Delta R$


$$v_o = -\frac{R_2}{R_1} v_{i1} + \frac{R_2}{R_1 + \Delta R + R_2} \left(1 + \frac{R_2}{R_1}\right) v_{i2}$$

$$v_o \cong \frac{R_2}{R_1} (v_d - x v_c) \rightarrow x = \frac{\Delta R}{R_1 + R_2}$$

$$|A_c| = x \frac{R_2}{R_1} \ll |A_d| = \frac{R_2}{R_1}$$

Even though A_c is small w.r.t A_d ($x \sim 0.01$), $v_c \gg v_d$ and hence common-mode amplification cannot be ignored

Difference Amplifier: Problem 1

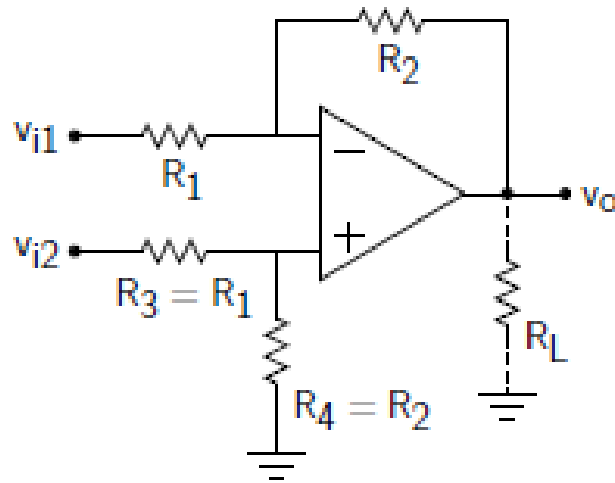

$$v_{i1} = v_c - v_d/2$$

$$v_{i2} = v_c + v_d/2$$

$$\text{If } R_3 = R_1 + \Delta R$$

$$v_o \cong \frac{R_2}{R_1} (v_d - x v_c)$$

$$|A_c| = x \frac{R_2}{R_1}, |A_d| = \frac{R_2}{R_1}, x = \frac{\Delta R}{R_1 + R_2}$$

$$v_d = 0.0375V, v_c = 7.5V$$


$$R_1 = 1k, R_2 = 10k, x = 0.01$$

$$|A_c v_c| = x \frac{R_2}{R_1} v_c = 0.75V$$

$$|A_d v_d| = \frac{R_2}{R_1} v_d = 0.375V$$


Substantial common-mode contribution at the output

Difference Amplifier: Problem 2

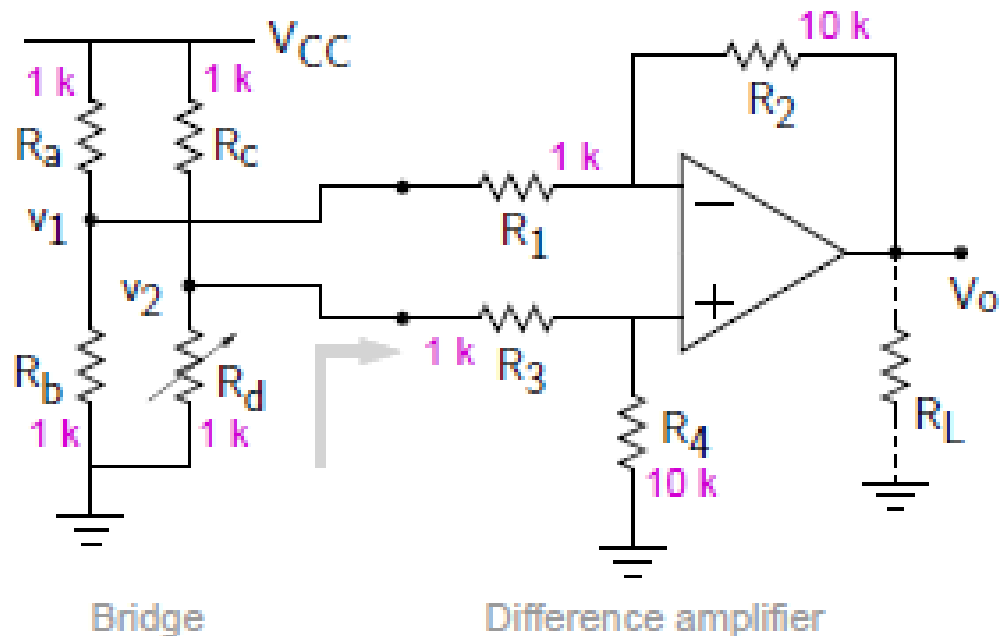

- Resistance seen from v_2 is $R_3 + R_4 \rightarrow$ small enough to cause v_2 to change
- Need higher input resistance

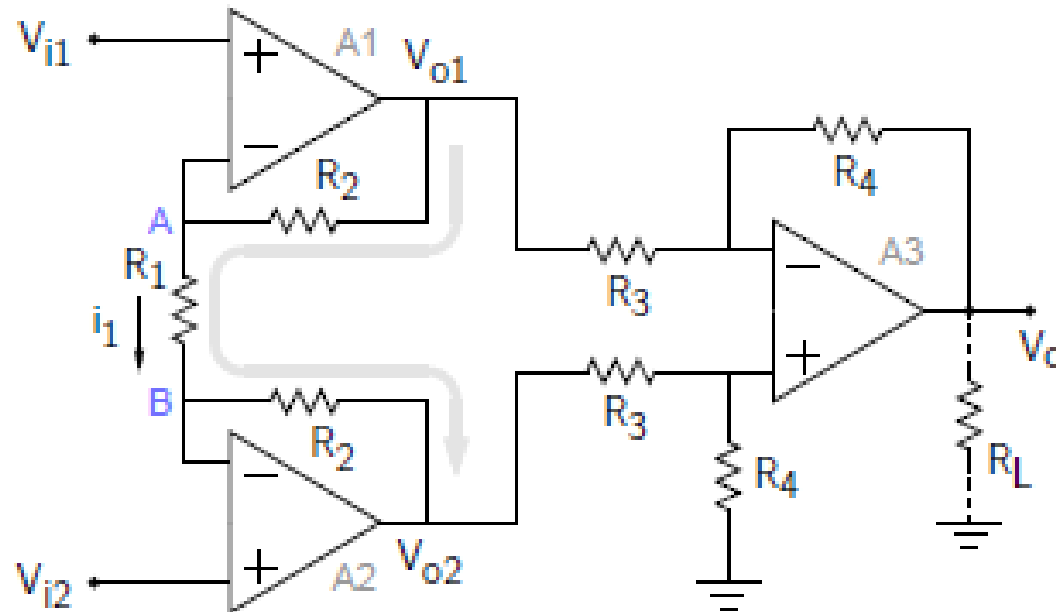Improved Difference Amplifier: Instrumentation Amplifier




$$V_A = V_{i1}, V_B = V_{i2} \Rightarrow i_1 = \frac{V_{i1} - V_{i2}}{R_1}$$

$$V_{o1} - V_{o2} = i_1 (R_1 + 2R_2) = \frac{V_{i1} - V_{i2}}{R_1} (R_1 + 2R_2) = (V_{i1} - V_{i2}) \left(1 + \frac{2R_2}{R_1}\right)$$


$$V_o = \frac{R_4}{R_3} (V_{o2} - V_{o1}) = \frac{R_4}{R_3} \left(1 + \frac{2R_2}{R_1}\right) (V_{i2} - V_{i1})$$

Input Resistance?

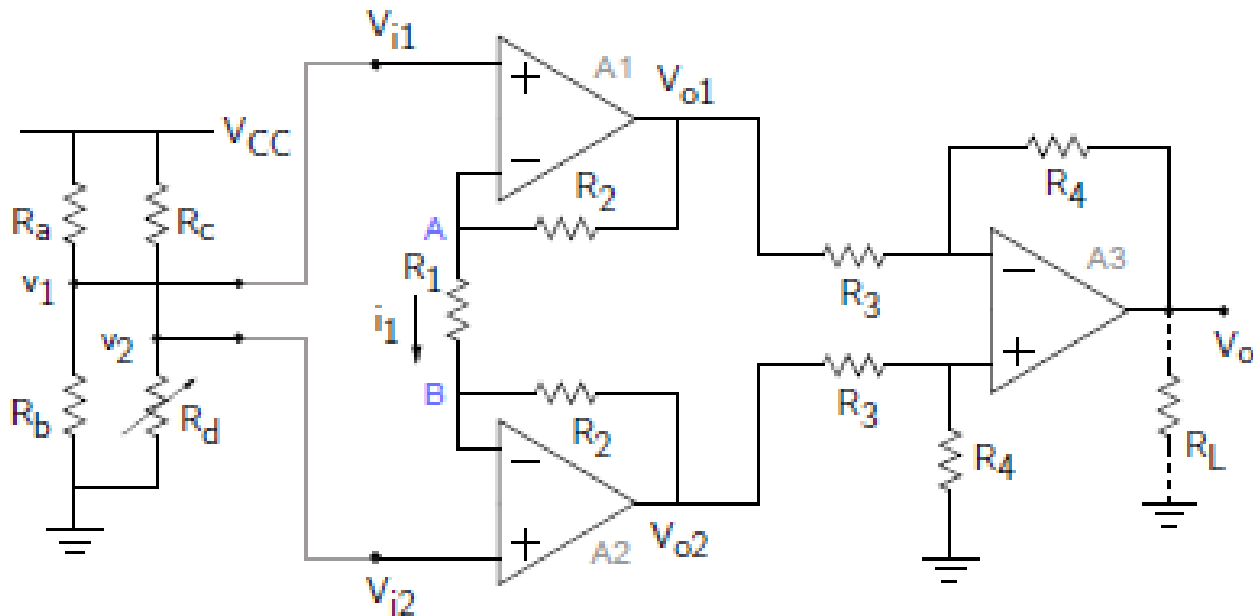

- Input resistance seen from V_{i1} and V_{i2} is large
- Does not “load” the bridge circuit
 - v_2 does not change


Common mode contribution?

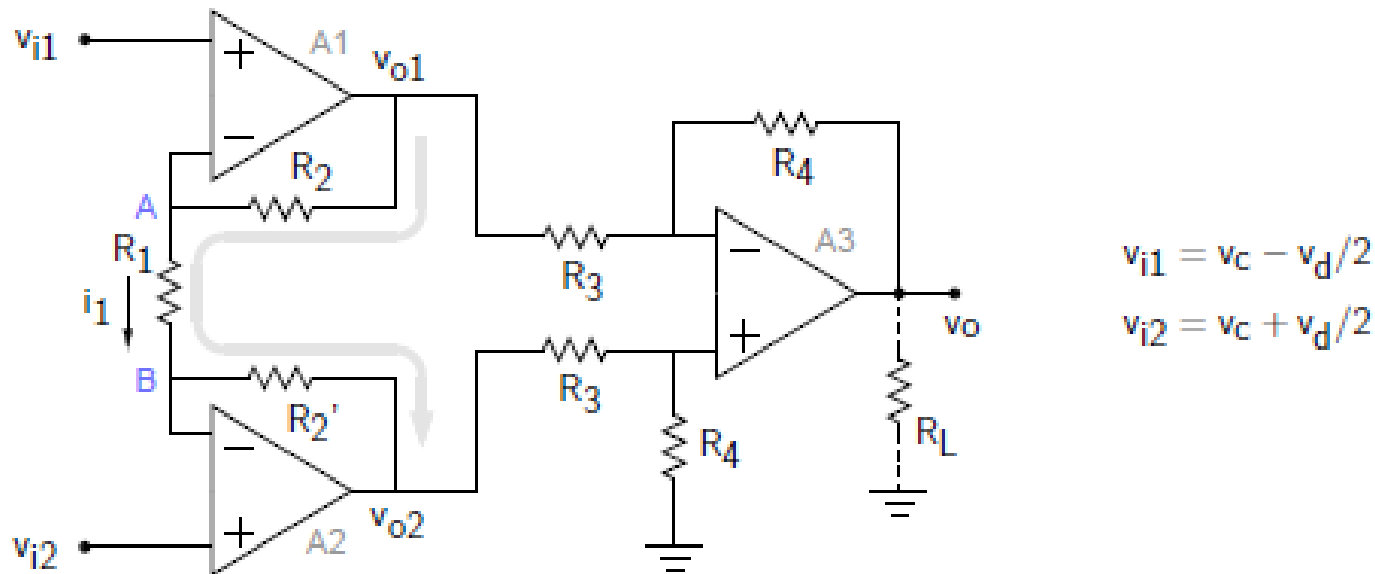

$$v_A = v_c - \frac{v_d}{2}, v_B = v_c + \frac{v_d}{2} \Rightarrow i_1 = \frac{v_A - v_B}{R_1} = -\frac{v_d}{R_1}$$

- What happens to the large common-mode component v_c ?
- Gets cancelled (even if R_2 and R_2' are not matched)

Current \rightarrow Voltage Conversion

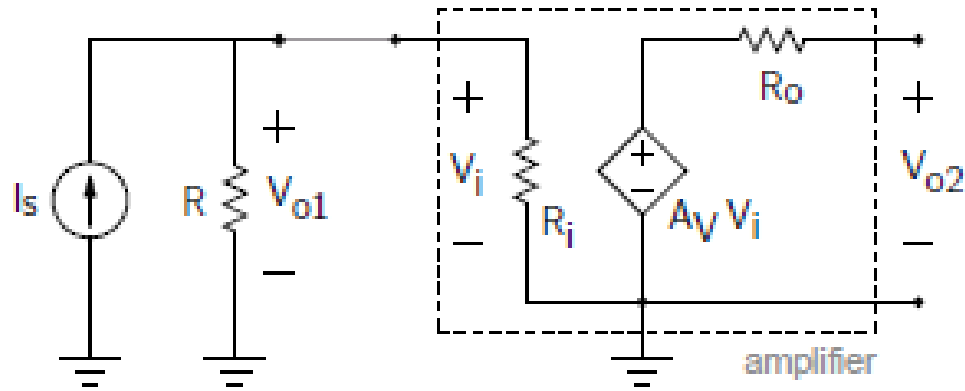


$$V_{o1} = I_s R \quad \text{Ideally}$$

$$V_{o1} = I_s (R_i \parallel R) \quad \text{In reality, } R_i \text{ affects } V_{o1}$$


Some circuits produce current output that needs to be converted to voltage to simplify further processing

If next stage is an amplifier, it can modify $V_{o1} \rightarrow$ not desirable.

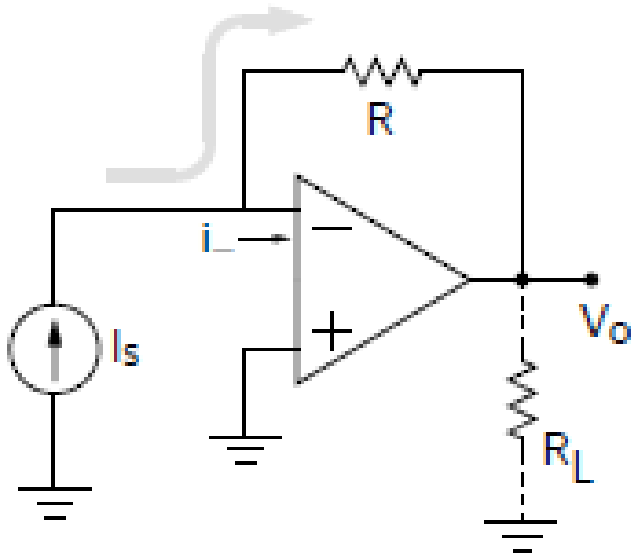Linear Op-Amps: Example 6 Current \rightarrow Voltage Conversion




$$V_o = -I_s R$$

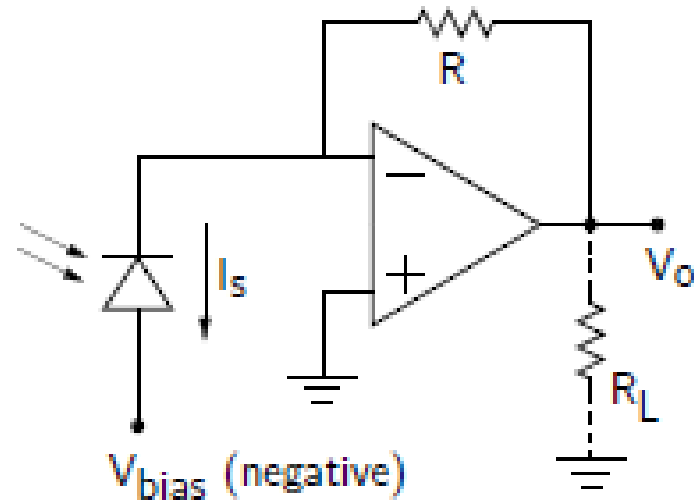

$$V_o = I_s R$$

- Output voltage is $-I_s R$ irrespective of R_L , i.e. irrespective of the next stage
- Practical Example \rightarrow Photocurrent detector ($V_o = I_s R$)



Linear Op-Amps: Example 7 Integrator

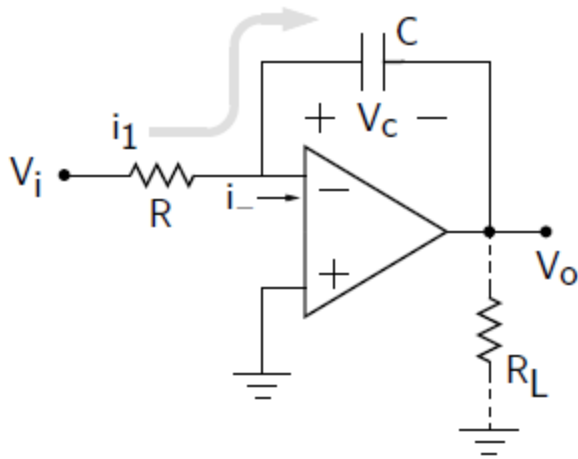

$$i_1 = \frac{V_i}{R} = C \frac{dV_c}{dt} = C \frac{d(0 - V_o)}{dt} = -C \frac{dV_o}{dt}$$


$$\Rightarrow V_o = -\frac{1}{RC} \int V_i dt$$

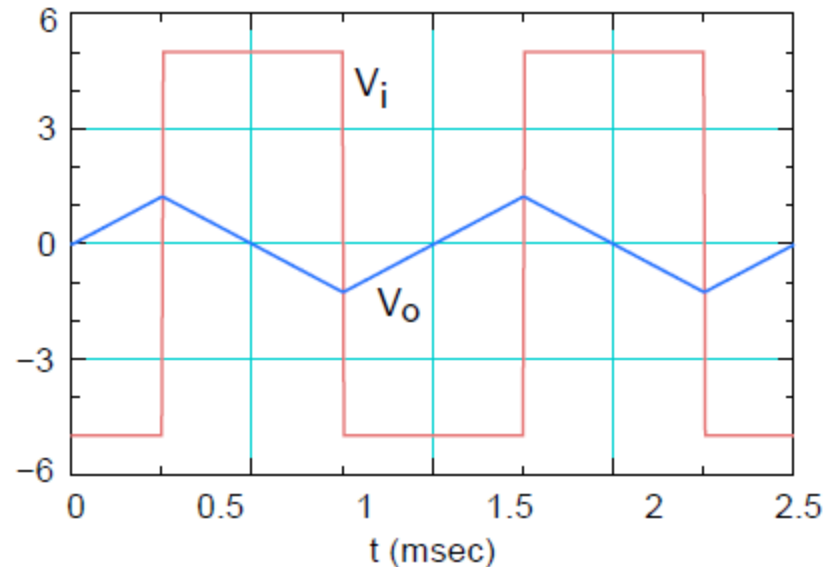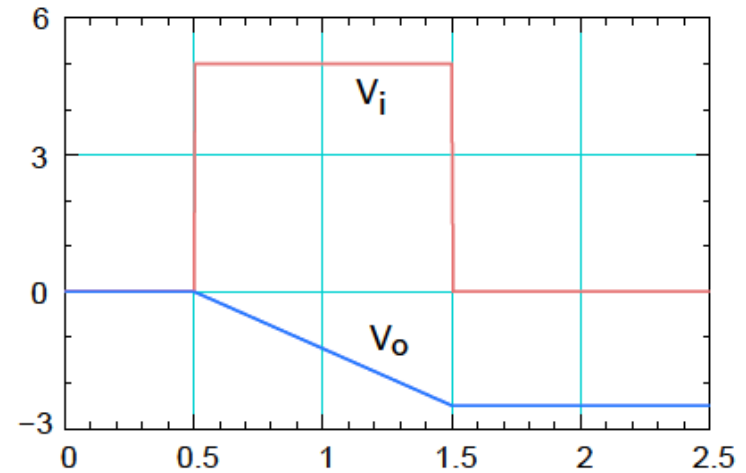If $R=1 \text{ k}\Omega$ and $C=0.2 \text{ }\mu\text{F}$



Linear Op-Amps: Example 8

Differentiator

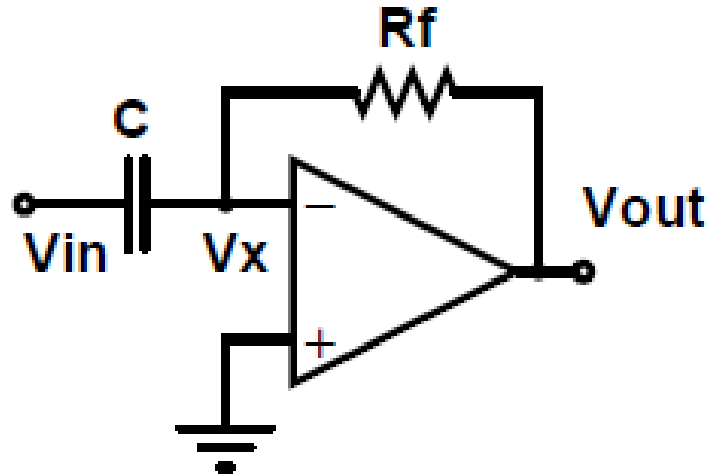


$$-\frac{V_{out}}{R_f} = C \frac{dV_{in}}{dt}$$

$$\Rightarrow V_{out} = -R_f C \frac{dV_{in}}{dt}$$

Linear Op-Amps: Example 9

Logarithmic Amplifier

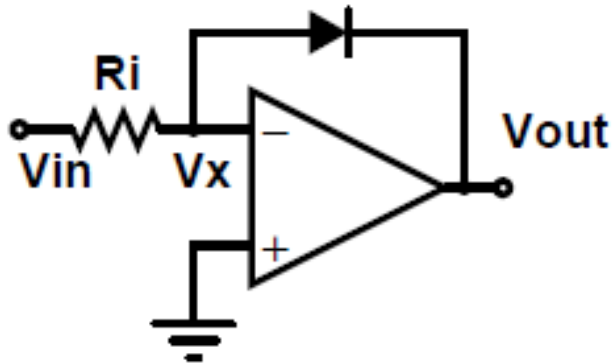





Assume V_{in} is always positive $\rightarrow V_{out}$ will be negative and diode will be forward biased

$$-\frac{V_{in}}{R} = I_o e^{-\frac{qV_{out}}{kT}}$$












$$\Rightarrow V_{out} = -\frac{kT}{q} \ln\left(\frac{V_{in}}{RI_o}\right)$$

Filters using Op-Amps


Ideal Filters

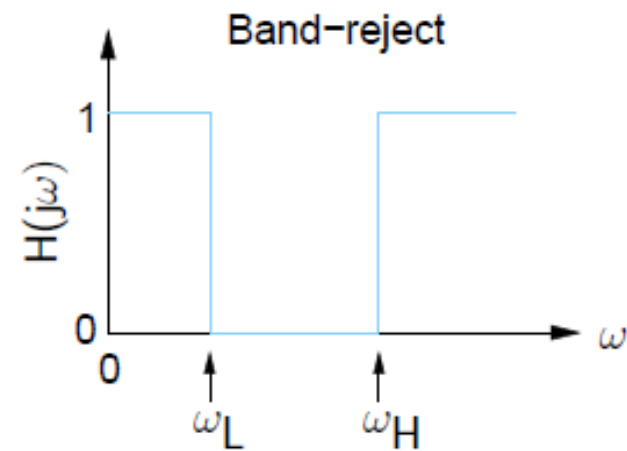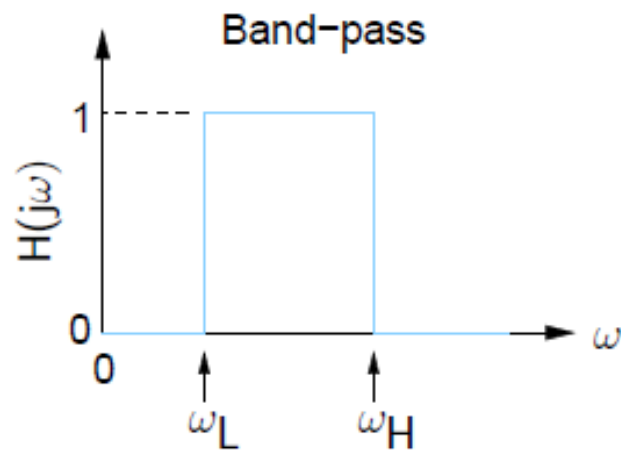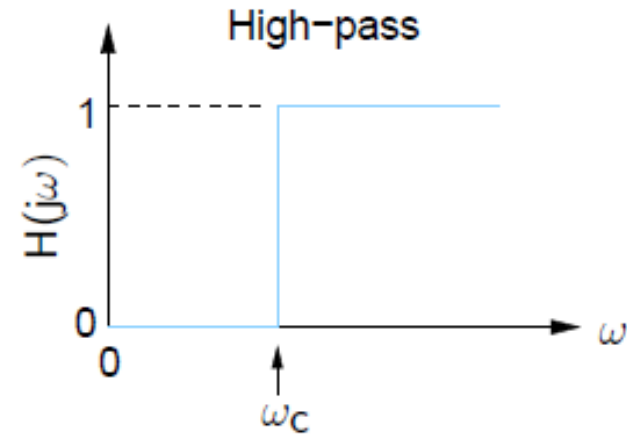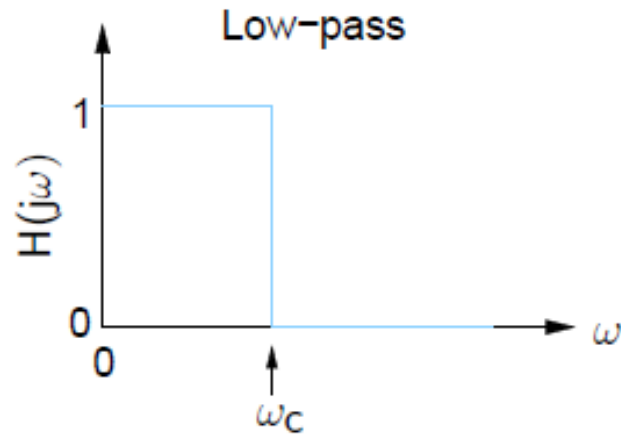

Ideal Filters

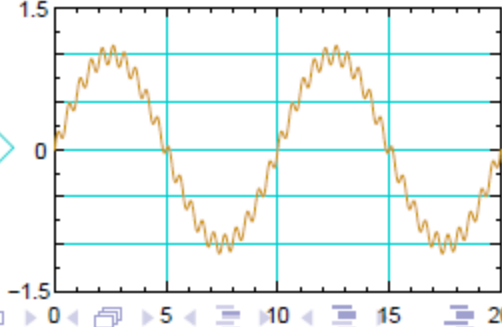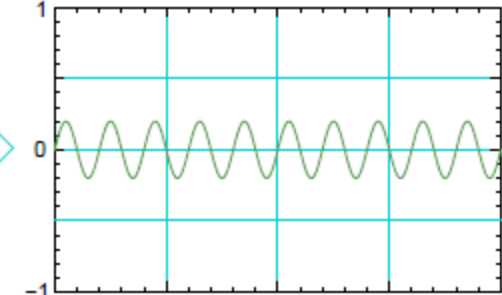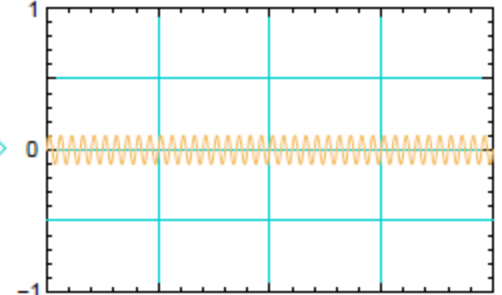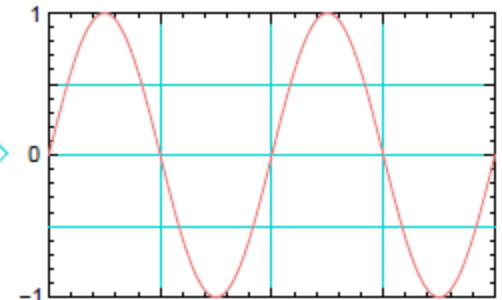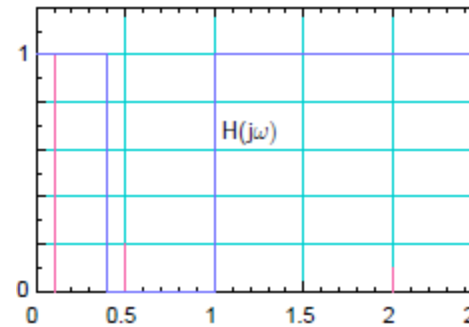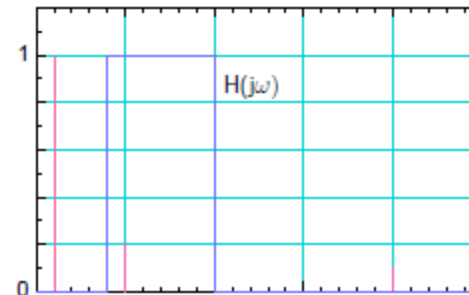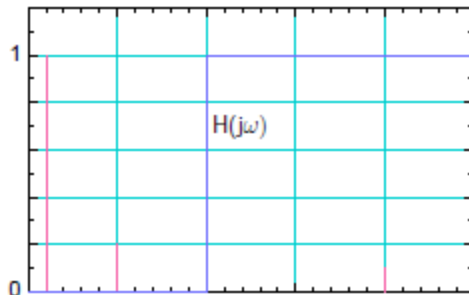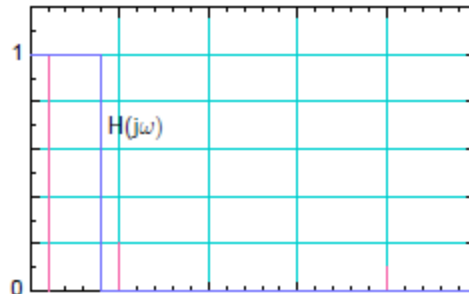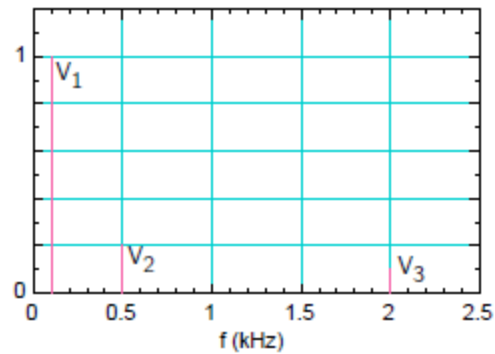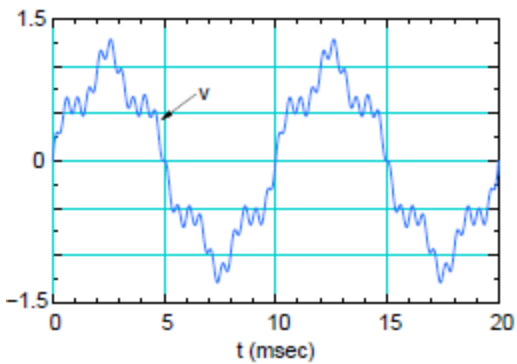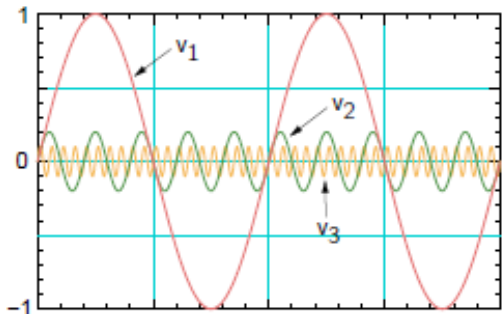

Practical filters

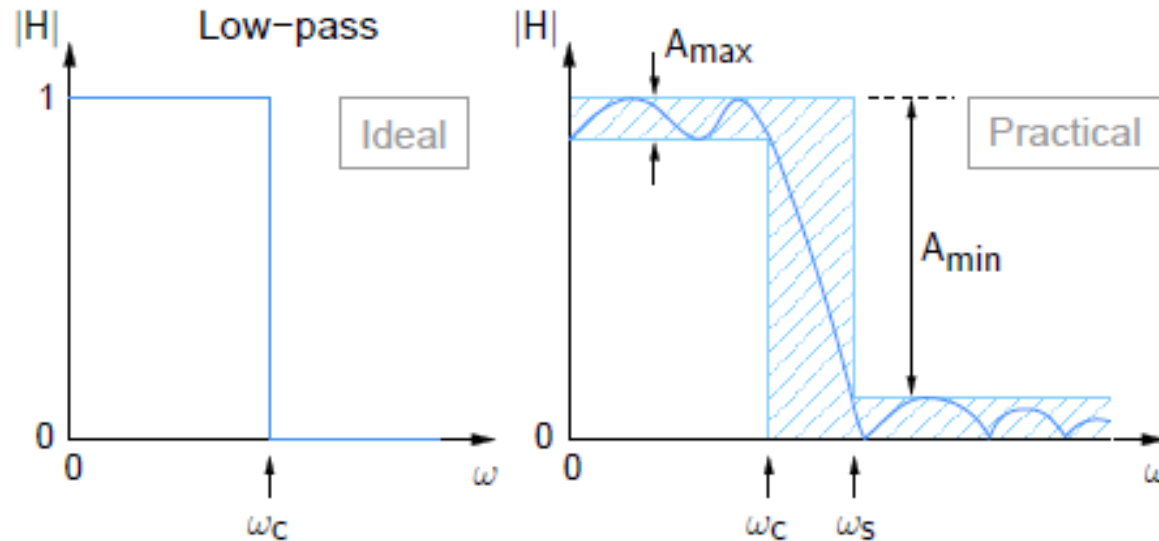

- A_{\max} is called the maximum pass band ripple, e.g. $A_{\max}=1\text{dB}$
- A_{\min} is the minimum attenuation provided by the filter, e.g. $A_{\min}=60\text{dB}$
- $\omega_s \rightarrow$ edge of stop band
- $\omega_s/\omega_c \rightarrow$ selectivity/sharpness of the filter
- $\omega_c < \omega < \omega_s \rightarrow$ transition band of the filter

Practical filters

- A low pass filter $H(s) = \frac{1}{\sum_{i=0}^n a_i (s/\omega_c)^i}$
- E.g. 5th order low pass filter $H(s) = \frac{1}{a_5 s^5 + a_4 s^4 + a_3 s^3 + a_2 s^2 + a_1 s + a_0}$
- Commonly used approximations (polynomials) are:
 - Butterworth, Chebyshev, Bessel and elliptic functions
- Butterworth filters: $|H(j\omega)| = \frac{1}{\sqrt{1 + \varepsilon^2 (\omega/\omega_c)^{2n}}}$
- Chebyshev filters:



$$|H(j\omega)| = \frac{1}{\sqrt{1 + \varepsilon^2 C_n^2(\omega/\omega_c)^{2n}}}$$

$$C_n = \cos[n \cos^{-1}(x)], x \leq 1$$



$$C_n = \cos[n \cosh^{-1}(x)], x \geq 1$$
- High pass filter can be obtained from low pass filter by replacing s/ω_c with ω_c/s

Practical low-pass filters

Butterworth filters:

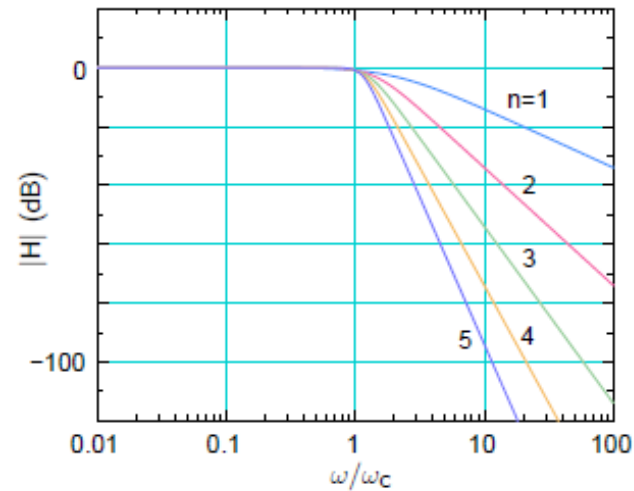
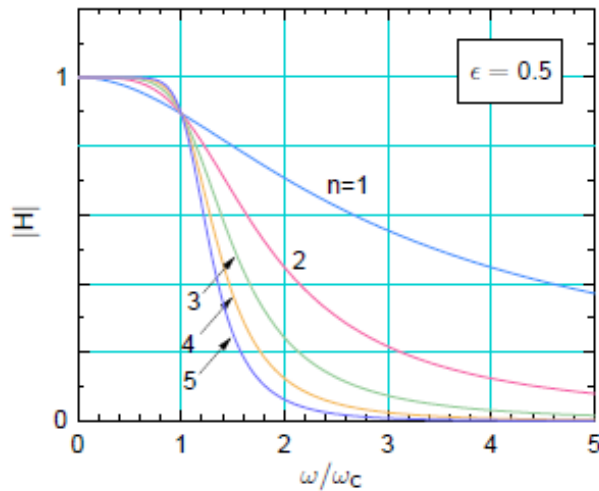


Chebyshev filters:

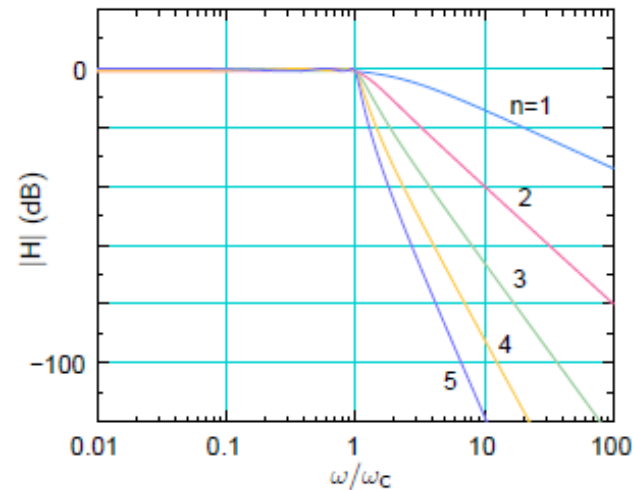
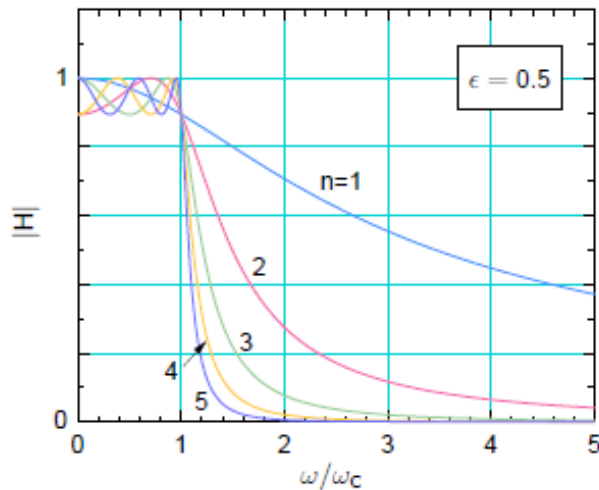


Practical high-pass filters


Butterworth filters:

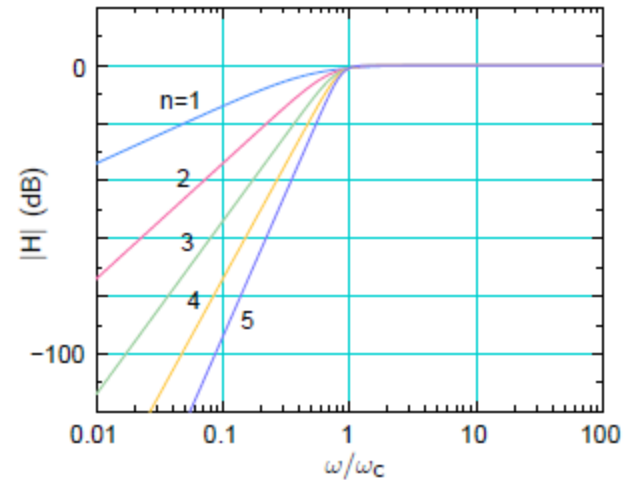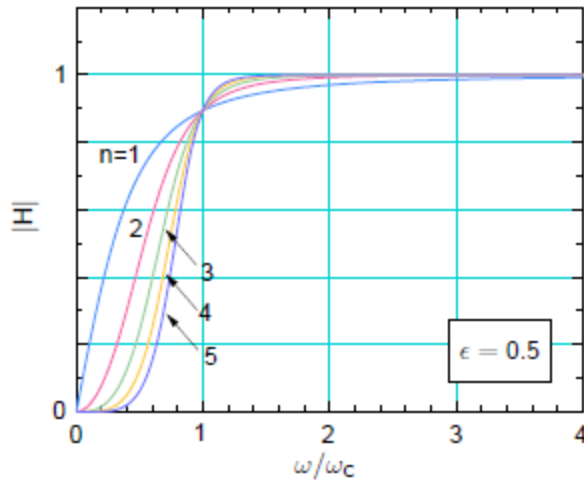

Chebyshev filters:

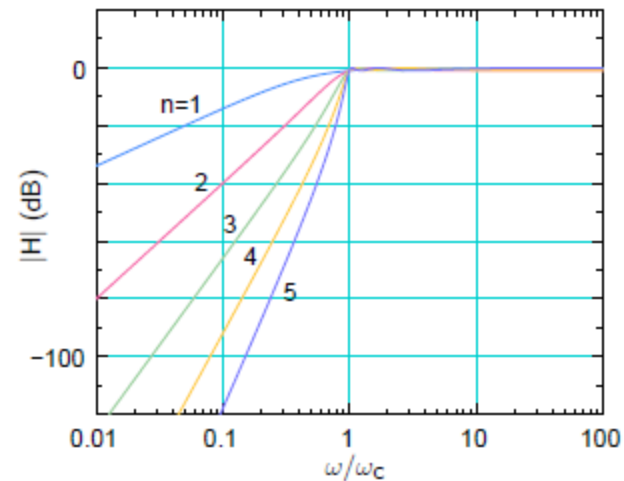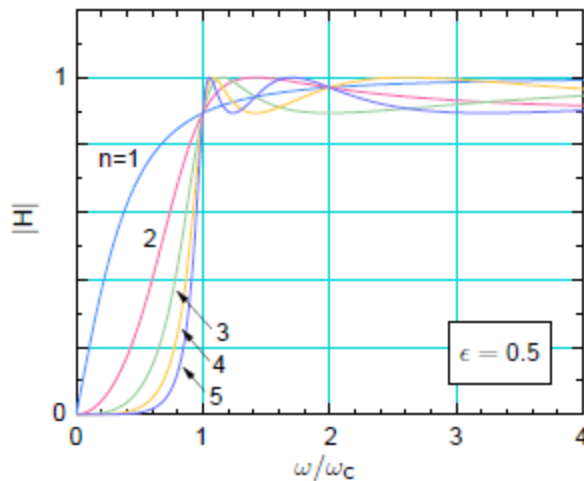


Passive low pass filter

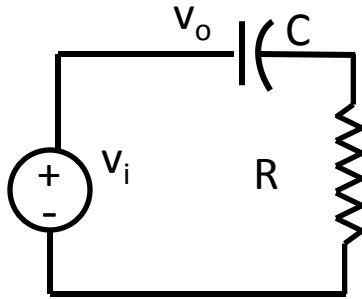


$$H(s) = \frac{1}{1 + s/RC} = \frac{1}{1 + s/\omega_o}$$

$$\omega_o = RC$$

$R=100\ \Omega$, $C=5\ \mu\text{F}$

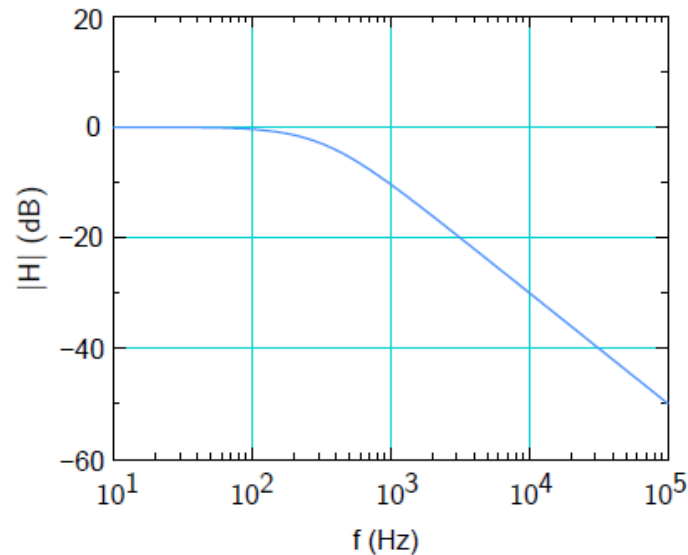


Passive band pass filter

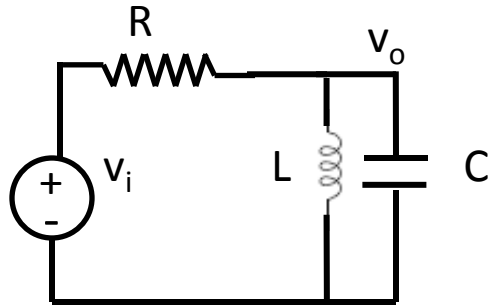

$$H(s) = \frac{s(L/R)}{1 + s(L/R) + s^2 LC}$$

$$\omega_o = 1/\sqrt{LC}$$


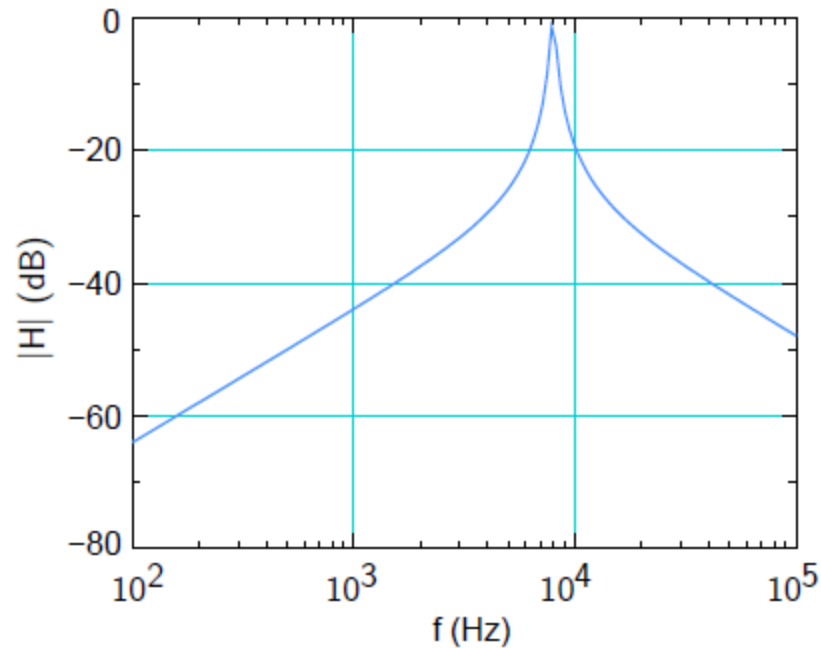
$R=100\ \Omega$, $C=4\ \mu\text{F}$, $L=0.1\ \text{mH}$



Op-Amp “Active” Filters

- Advantages
 - No inductors (bulky, expensive, non-linear)
 - “Gain” in pass-band
 - Easy to integrate in ICs
 - High input impedance and low output impedance
- Limitations
 - No gain at High frequencies (MHz)
 - Not good for high power requirement

Op-Amp Active Low Pass Filter

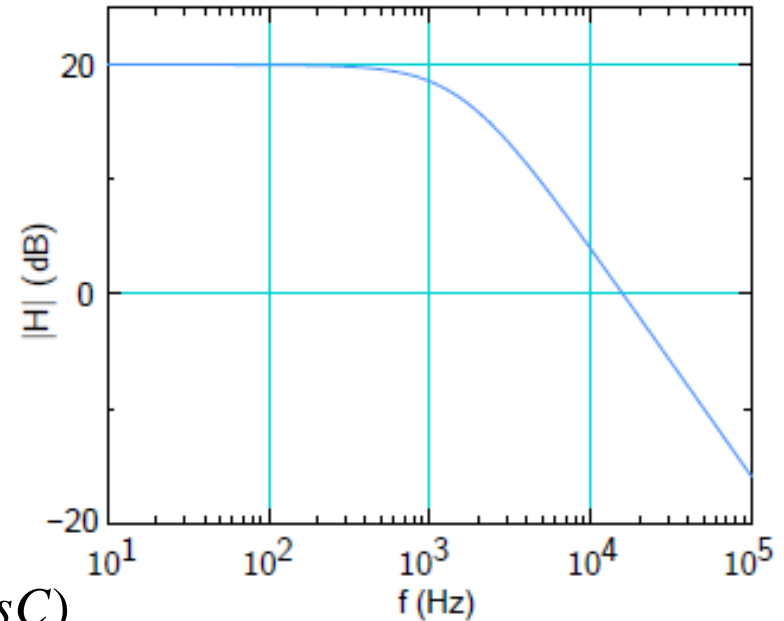
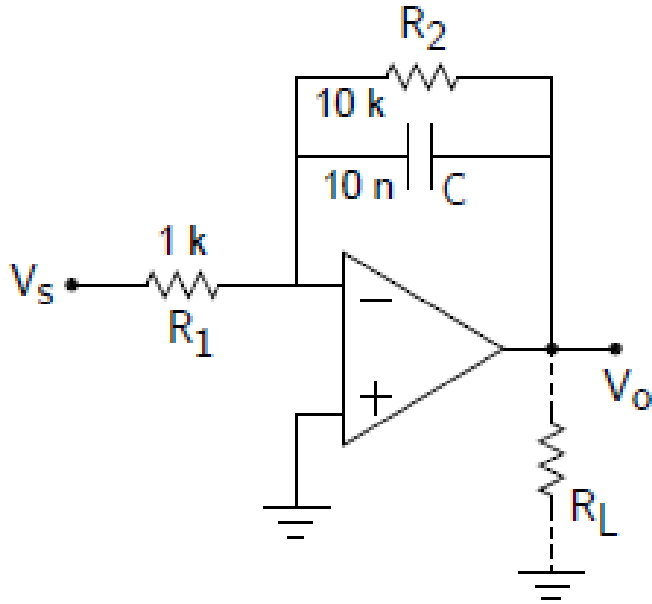


$$V_o = -\frac{R_2 \parallel (1/sC)}{R_1} V_s$$

$$H(s) = -\frac{R_2}{R_1} \frac{1}{1 + sR_2C}$$

$$\omega_o = 1/R_2C$$



Op-Amp Active High Pass Filter

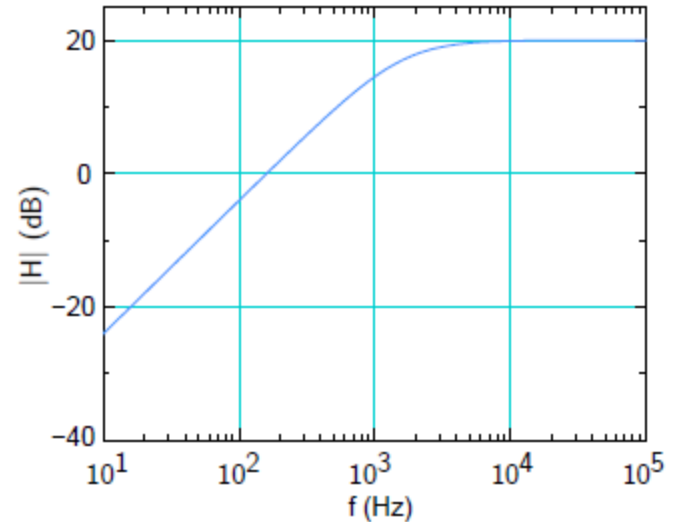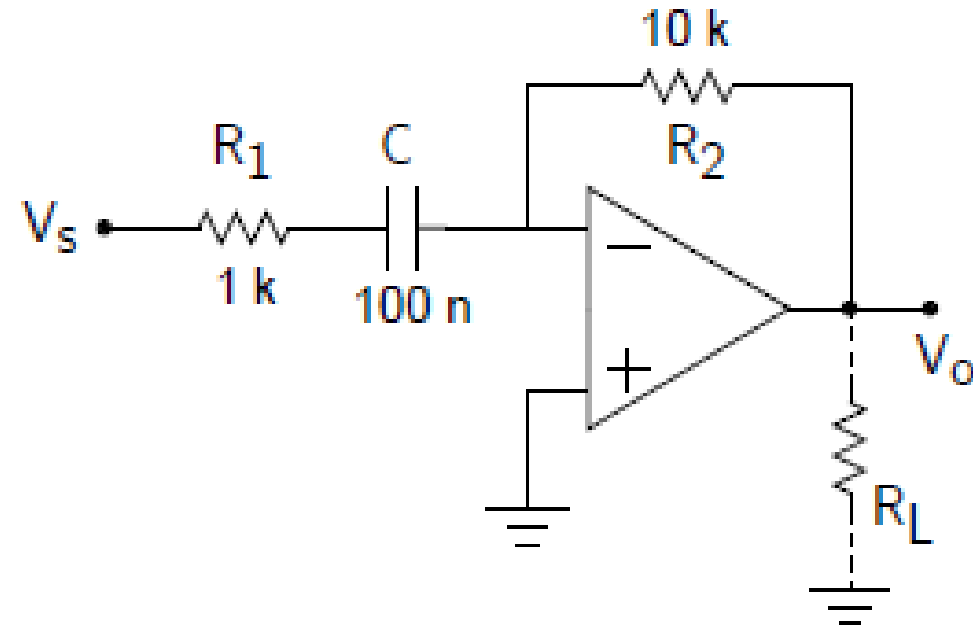

$$H(s) = -\frac{sR_2C}{1 + sR_1C}$$

$$\omega_o = 1/R_1C$$



Op-Amp Active Band Pass Filter

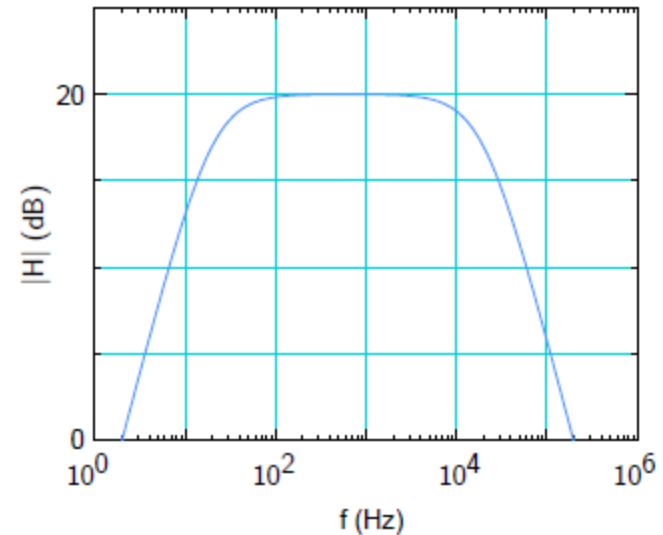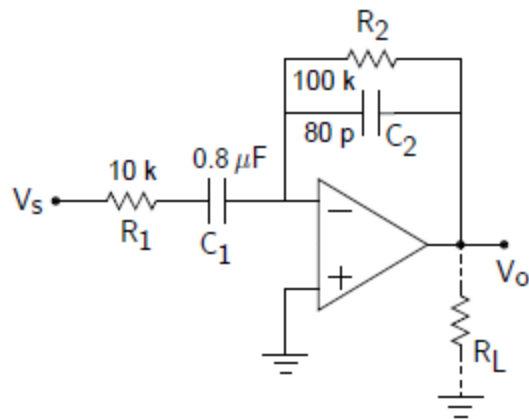

$$H(s) = -\frac{R_2 \parallel (1/sC_2)}{R_1 + (1/sC_1)} = -\frac{R_2}{R_1} \frac{sR_1C_1}{(1+sR_1C_1)(1+sR_2C_2)}$$

$$\omega_L = 1/R_1C_1, \omega_H = 1/R_2C_2$$

Example of a Graphic Equalizer

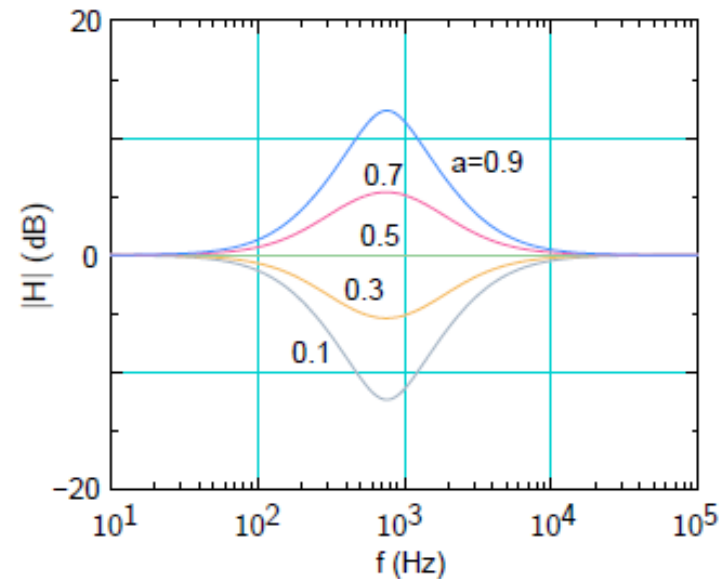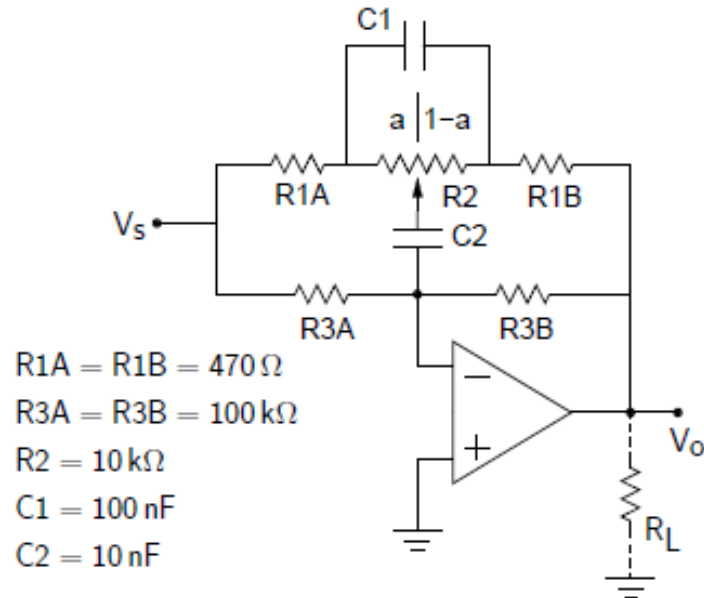

(Ref.: S. Franco, "Design with Op Amps and analog ICs")

- Adjustable gain around a center frequency
- Array of such narrow-band filters

Example of a Notch Filter

