

# Introduction to Semiconductors


## P-N Junction Diode

S. Lodha

EE 101

Autumn 2015

# Conductivity of metals

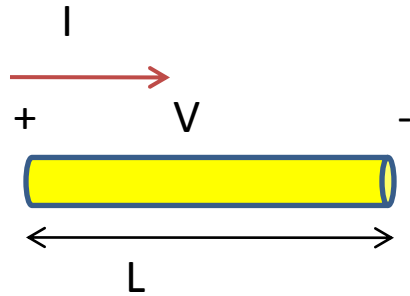

$$I = \frac{Nq}{T} = \frac{Nqv}{L}$$

$$J = \frac{Nqv}{AL} = nqv = nq\mu E$$

$$J = \sigma E \Rightarrow \sigma = nq\mu$$

Ohm's Law


$$J = \sigma E \Rightarrow I = \frac{\sigma A}{L} V$$

$$R = \frac{\sigma A}{L}$$

- Metal  $\rightarrow$  free valence electrons
- Without applied voltage  $\rightarrow$  random thermal motion, avg current=0
- With applied voltage  $\rightarrow$  electrons go from high to low potential
- $v$ =drift velocity= $\mu E$
- $\mu$  is mobility in  $\text{cm}^2/\text{Vs}$
- Typically for metals
  - Cu,  $n \sim 10^{28}$ - $10^{29} \text{ e/m}^3$
  - High conductivity ( $\sigma$ )
- For insulators,  $n \sim 10^7 \text{ e/m}^3$
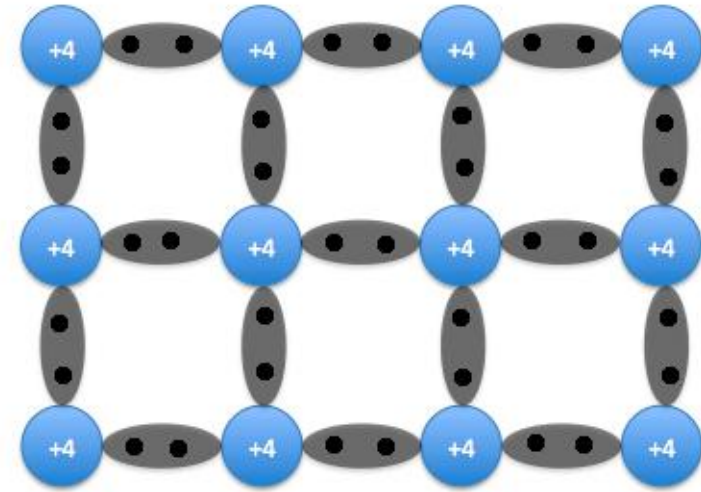
# Semiconductors

- $n \sim 10^{16} - 10^{19} \text{ e/m}^3$
- For example,
  - Si,  $n = 1.5 \times 10^{16} \text{ m}^{-3}$
  - Ge,  $n = 2.6 \times 10^{19} \text{ m}^{-3}$
- Two types of mobile charge carriers
  - Electrons and holes
  - In Si, 4 valence electrons, covalent bond
  - Thermal energy at room T excites electrons to break away
  - Vacated state  $\rightarrow$  hole,  $+q$
  - In pure intrinsic semiconductors,  $n = p = n_i$
- In Si, 1.1 eV to form an electron – hole pair,  $E_g = \text{bandgap} = 1.1 \text{ eV}$
- In Ge,  $E_g = 0.67 \text{ eV}$



$E_g = 1.1 \text{ eV}$  for Si  
 $E_g = 0.67 \text{ eV}$  for Ge

# Semiconductor conductivity

- Metals → unipolar (only electrons)
- Semiconductor → bipolar conductivity (electrons and holes)

$$J = nq\mu_n E + nq\mu_p E$$

$$J = \sigma E \Rightarrow \sigma = nq\mu_n + nq\mu_p$$

In Si, at RT,  $\mu_n = 0.13, \mu_p = 0.05 \text{ cm}^2/\text{Vs}$

$$n_i = 1.5 \times 10^{16} \text{ m}^{-3}$$



$$\Rightarrow \sigma = nq\mu_n + nq\mu_p = n_i q (\mu_n + \mu_p) = 4.32 \times 10^{-4} \text{ mho/m}$$

$$\text{Cu at RT, } \sigma = 5.8 \times 10^{+7} \text{ mho/m}$$

# Other semiconductors

- Elemental (Group IV): Si, Ge
- Compound
  - IV-IV: SiC
  - III-V: GaAs, GaN, GaP, In P, AlAs
  - II-VI: ZnO, ZnS, CdSe, CdTe
- Alloyed:  $\text{Si}_{1-x}\text{Ge}_x$ ,  $\text{Al}_x\text{Ga}_{1-x}\text{As}$ ,  $\text{Ga}_x\text{In}_{1-x}\text{As}_{1-y}\text{P}_y$
- Used for high speed, optoelectronic, high power and high temperature devices

# Doping of semiconductors

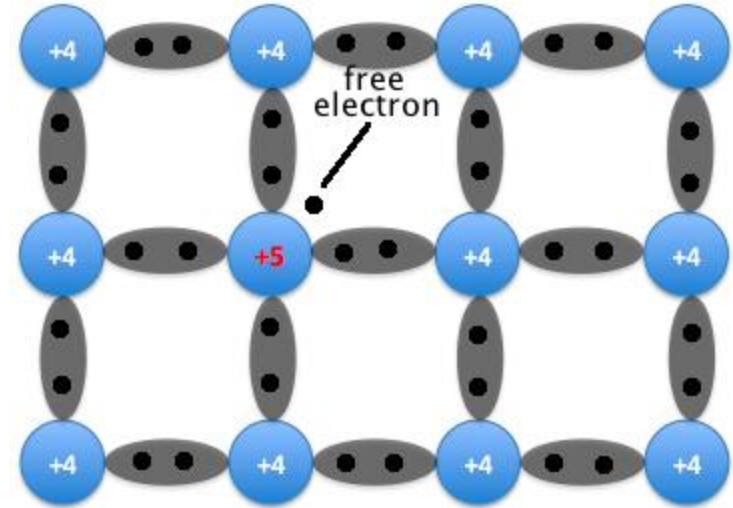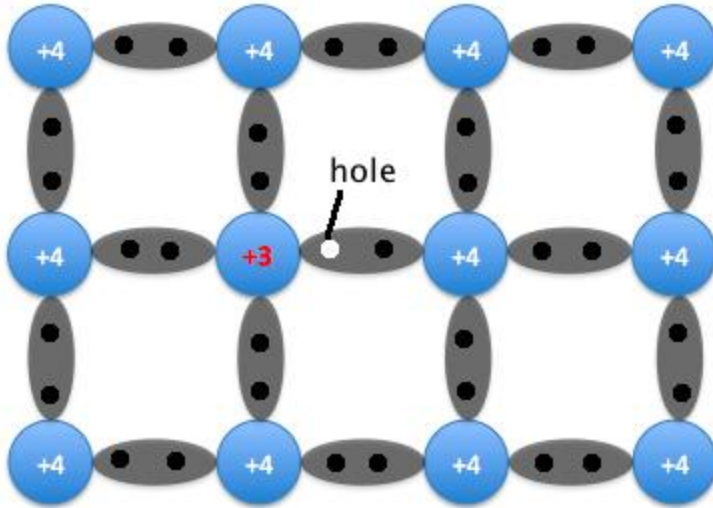

Group III impurity  $\rightarrow$  B, Ga (3 valence  $e^-$ )  
Holes that can “accept” electrons  
Acceptor impurity  
Positively charged  $h^+ \rightarrow$  p-type semiconductor

Group V impurity  $\rightarrow$  P, As, Sb (5 valence  $e^-$ )  
“Donate” electrons  
Donor impurity  
Negatively charged  $e^- \rightarrow$  n-type semiconductor

- Doping  $\rightarrow$  modulate conductivity by introducing impurities

# Doping → concentrations

Under thermal equilibrium,

$$np = n_i^2$$

For pure (intrinsic) semiconductor

$$n = p = n_i$$

## N-type Doped

Charge neutrality implies

$$N_D + p = N_A + n$$

For n - type,  $N_A = 0$

$$N_D + p = n$$

$$n \gg p, n \approx N_D, p = \frac{n_i^2}{n} = \frac{n_i^2}{N_D}$$

## P-type Doped

Charge neutrality implies

$$N_D + p = N_A + n$$

For p - type,  $N_D = 0$

$$N_A + n = p$$

$$p \gg n, p \approx N_A, n = \frac{n_i^2}{p} = \frac{n_i^2}{N_A}$$

# Doping → conductivity

In Si, at RT,  $\mu_n = 0.13$ ,  $\mu_p = 0.05 \text{ cm}^2/\text{Vs}$

$$n_i = 1.5 \times 10^{16} \text{ m}^{-3}$$

2 parts per  $10^8$  of donor impurity

$$N_D = (5 \times 10^{28}) \left( \frac{2}{10^8} \right) = 10^{21} \text{ m}^{-3}$$

$$n \sim 10^{21} \text{ m}^{-3} \text{ and } p = \frac{n_i^2}{n} = 2.25 \times 10^{11} \text{ m}^{-3}$$


$$\Rightarrow \sigma = nq\mu_n + p q \mu_p = q(n\mu_n + p\mu_p) = 20.8 \text{ mho/m}$$

A factor of 50000 increase w.r.t undoped ( $4.3 \times 10^{-4}$ ) case

- Small percentage of impurity can drastically alter conductivity



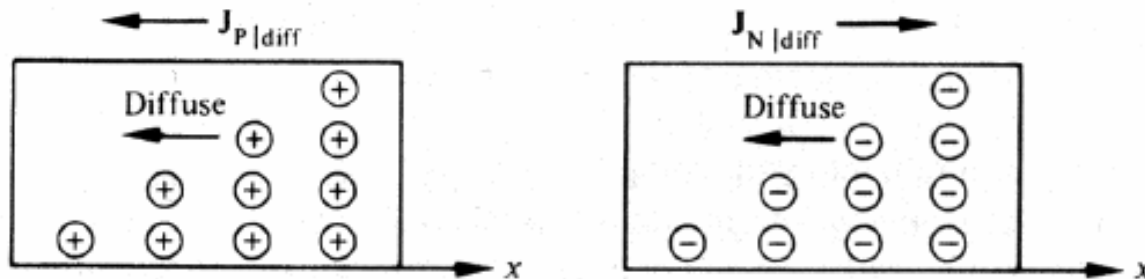
# How does current flow in semiconductors? – Diffusion Current



$$J_p |_{Diffusion} = -qD_p \nabla p \quad \text{or} \quad J_n |_{Diffusion} = qD_n \nabla n$$

- Diffusion current: “flow of carriers” from one region of higher concentration to lower concentration results in a “diffusion current”.
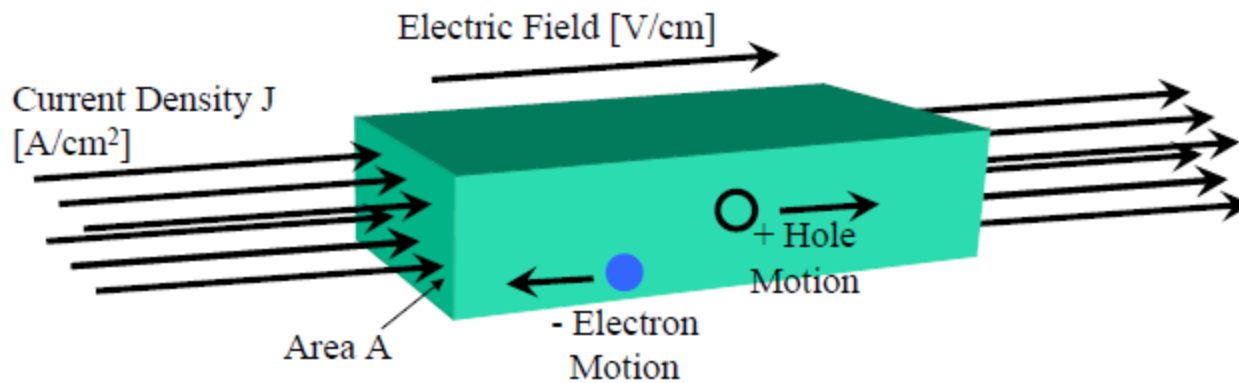
# How does current flow in semiconductors? – Drift Current



$$J_{p|_{\text{Drift}}} = q p v_d \quad \text{and} \quad J_{n|_{\text{Drift}}} = q n v_d$$

Hole Drift current density

Electron Drift current density

Under low electric field,

$$J_p = q p \mu_p E \quad \text{and} \quad J_n = q n \mu_n E$$

- Current due to motion of carrier under the influence of an electric field

# Total current

$$J_p = J_p|_{\text{Drift}} + J_p|_{\text{Diffusion}} = q\mu_p pE - qD_p \nabla p$$

and

$$J_n = J_n|_{\text{Drift}} + J_n|_{\text{Diffusion}} = q\mu_n nE + qD_n \nabla n$$

and

$$J = J_p + J_n$$


$$\frac{D_n}{\mu_n} = \frac{D_p}{\mu_p} = \frac{kT}{q}$$

Einstein's relationship

- Summation of drift and diffusion currents of both holes and electrons

# Graded Semiconductor

In general,

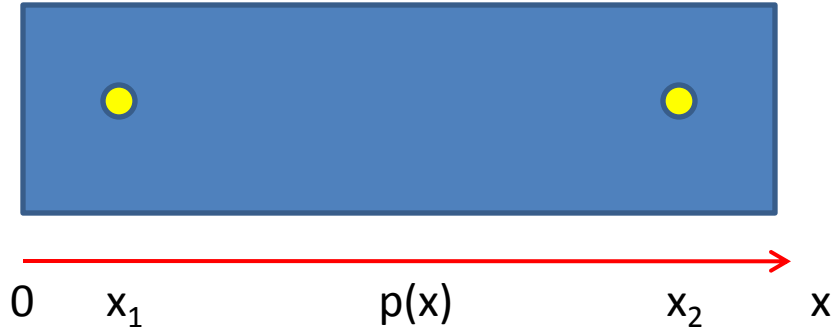

$$J = J_p(x) = J_{pdrift}(x) + J_{pdiff}(x)$$

$$J = qp\mu_p E - qD_p \frac{dp}{dx} = 0$$

$$\Rightarrow E(x) = \frac{D_p}{\mu_p} \frac{1}{p} \frac{dp}{dx} = \frac{kT}{q} \frac{1}{p} \frac{dp}{dx}$$


$$\int_{V_1}^{V_2} dV = -\frac{kT}{q} \int_{p_1}^{p_2} \frac{dp}{p}$$

$$V_{21} = \frac{kT}{q} \ln \frac{p_1}{p_2}$$

$$\Rightarrow p_1 = p_2 e^{\frac{qV_{21}}{kT}} \text{ and } n_1 = n_2 e^{-\frac{qV_{21}}{kT}}$$

$$\Rightarrow p_1 n_1 = p_2 n_2 = n_i^2$$

# The p-n junction diode

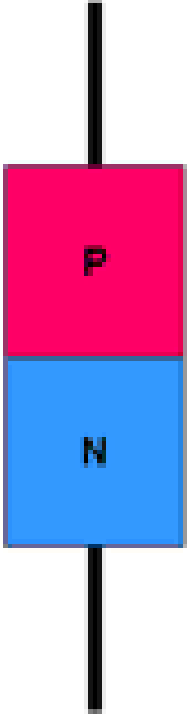

$$p_p = N_A$$

$$n_n = N_D$$

$$n_p = \frac{n_i^2}{N_A}$$



$$p_n = \frac{n_i^2}{N_D}$$

Barrier potential or built-in voltage

$$V_o = \frac{kT}{q} \ln \frac{p_p}{p_n} = \frac{kT}{q} \ln \frac{n_n}{n_p} = \frac{kT}{q} \ln \frac{N_A N_D}{n_i^2}$$

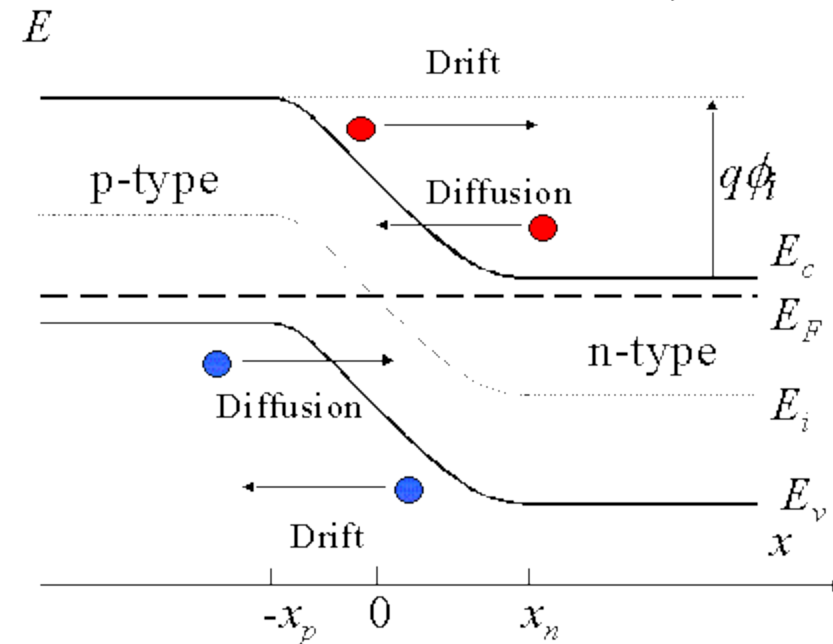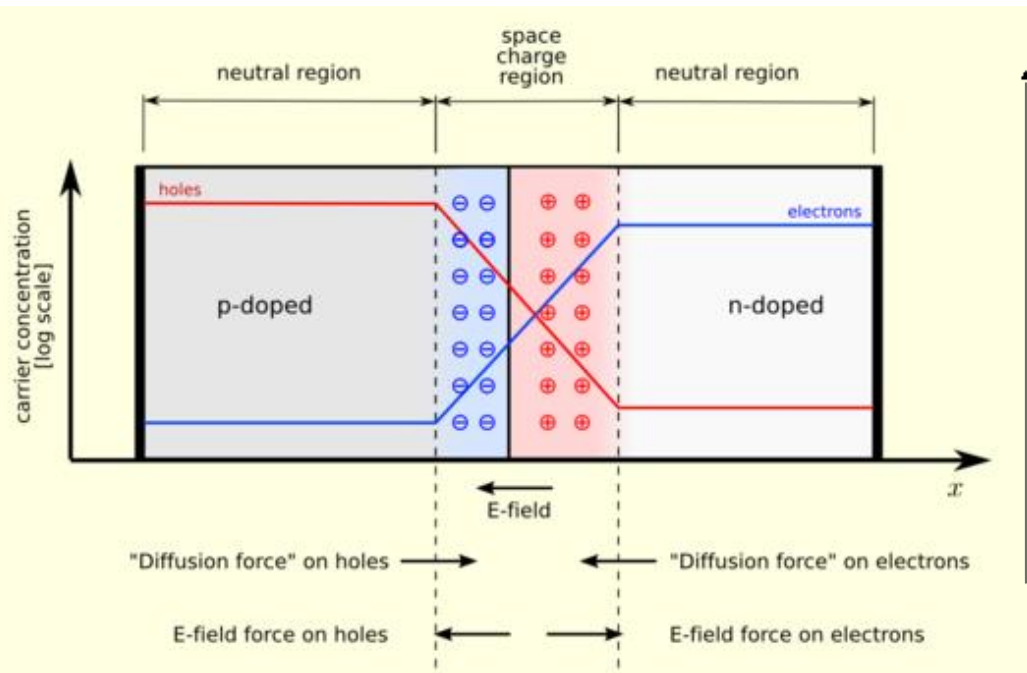
# Equilibrium picture (no voltage applied)

$$\phi_i = \frac{kT}{q} \ln \frac{N_A N_D}{n_i^2}$$




- $J_{\text{drift}}$  and  $J_{\text{diff}}$  for each carrier type cancel out
- Net current is zero

# The Biased Diode

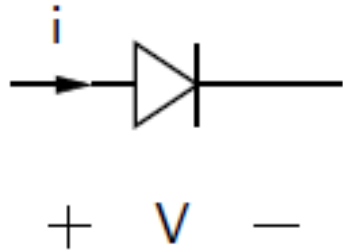


- Low resistance state in forward bias
- High resistance state in reverse bias
- Check Valve  $\rightarrow$  diode

**A**




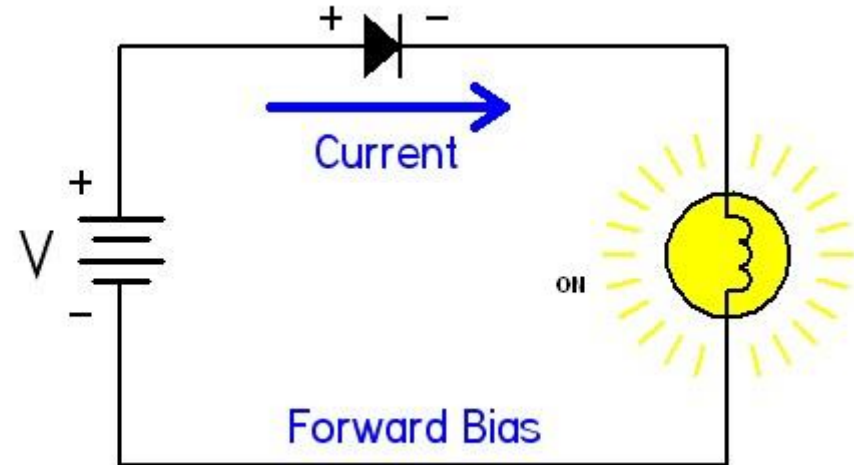


**B**

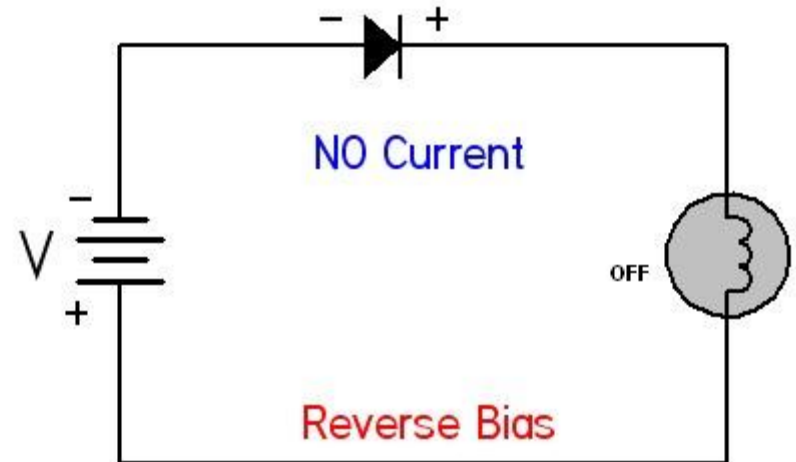


[www.electrapk.com](http://www.electrapk.com)

# Current flow (Band diagrams)

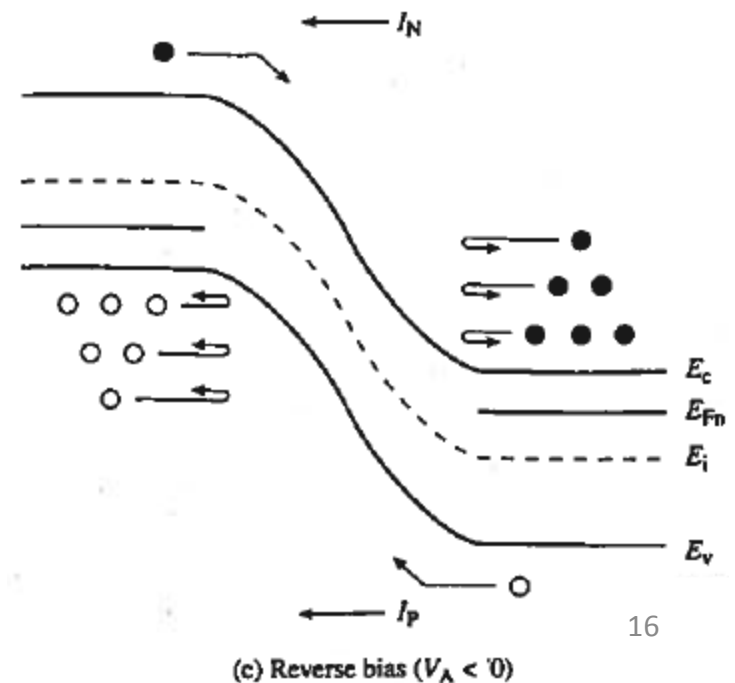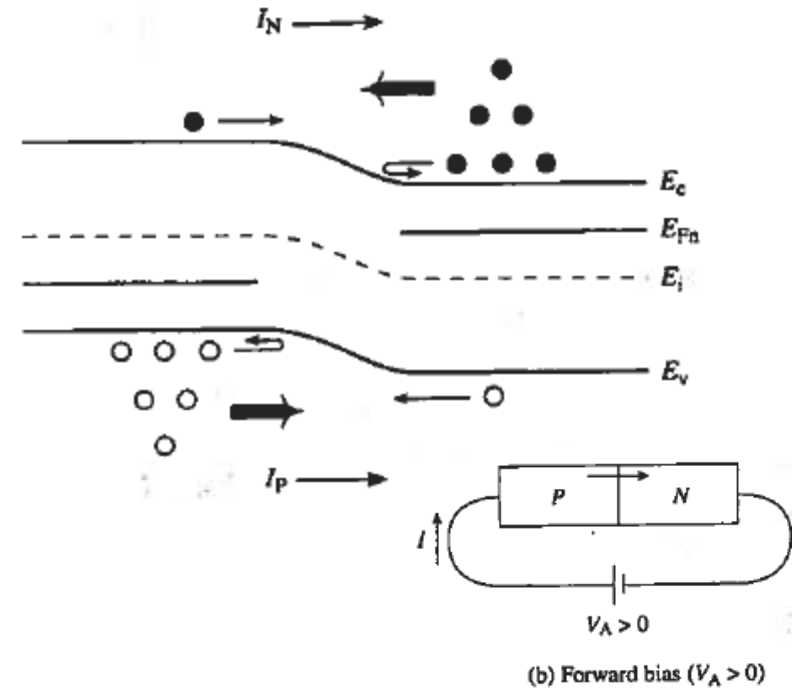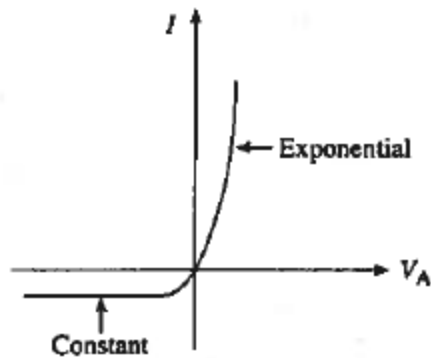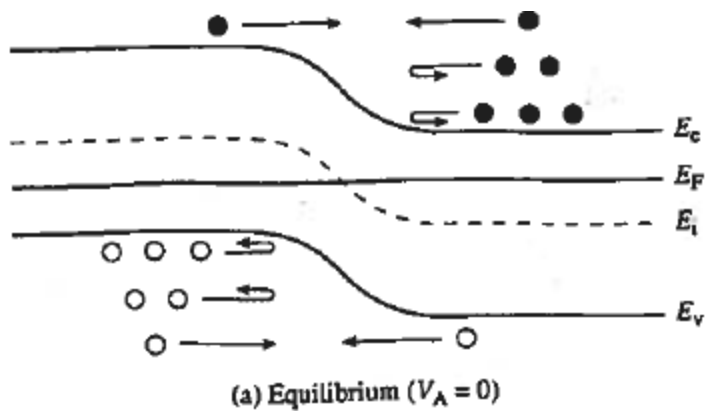




# Forward Bias Diode I-V

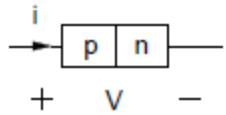


$$i = I_s \left[ \exp \left( \frac{V}{V_T} \right) - 1 \right] \quad I_s = 10^{-13} \text{ A}, V_T = 25 \text{ mV}$$

V	$x = V/V_T$	$e^x$	$i$ (Amp)
0.1	3.87	$0.479 \times 10^2$	$0.469 \times 10^{-11}$
0.2	7.74	$0.229 \times 10^4$	$0.229 \times 10^{-9}$
0.3	11.6	$0.110 \times 10^6$	$0.110 \times 10^{-7}$
0.4	15.5	$0.525 \times 10^7$	$0.525 \times 10^{-6}$
0.5	19.3	$0.251 \times 10^9$	$0.251 \times 10^{-4}$
0.6	23.2	$0.120 \times 10^{11}$	$0.120 \times 10^{-2}$
0.62	24.0	$0.260 \times 10^{11}$	$0.260 \times 10^{-2}$
0.64	24.8	$0.565 \times 10^{11}$	$0.565 \times 10^{-2}$
0.66	25.5	$0.122 \times 10^{12}$	$0.122 \times 10^{-1}$
0.68	26.3	$0.265 \times 10^{12}$	$0.265 \times 10^{-1}$
0.70	27.1	$0.575 \times 10^{12}$	$0.575 \times 10^{-1}$
0.72	27.8	$0.125 \times 10^{13}$	0.125

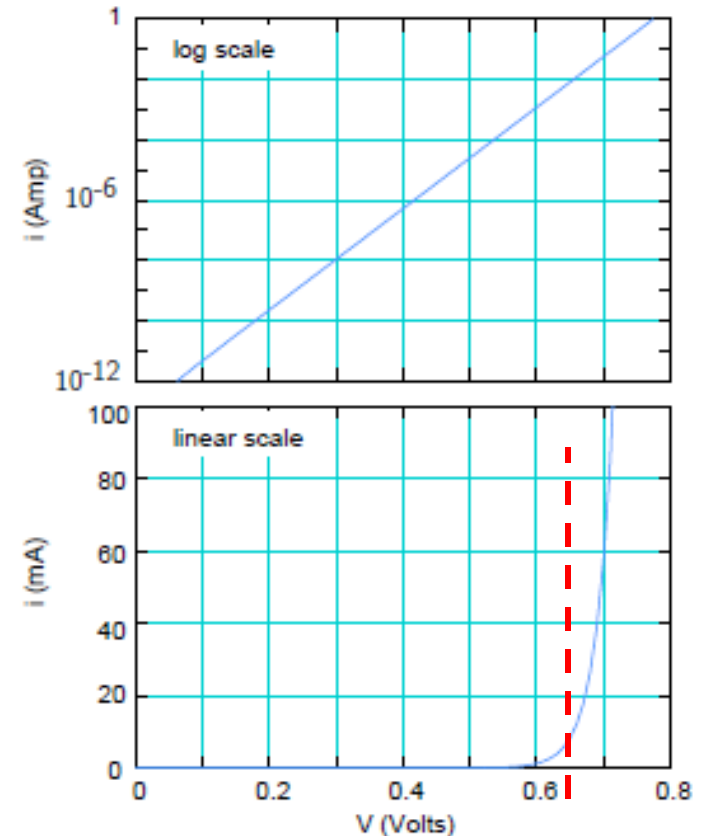

- Note that  $I$  increases significantly beyond 0.65 V  $\rightarrow$  10's of mA
- 0.65 is the "cut-in" voltage of the diode  $\rightarrow I_s$  dependent
- For Si, typically, cut-in voltage  $\rightarrow$  0.6 – 0.7 V, Ge  $\rightarrow$  0.2 – 0.3 V, GaAs  $\rightarrow$  1.1 V

# Types and Applications of Diodes

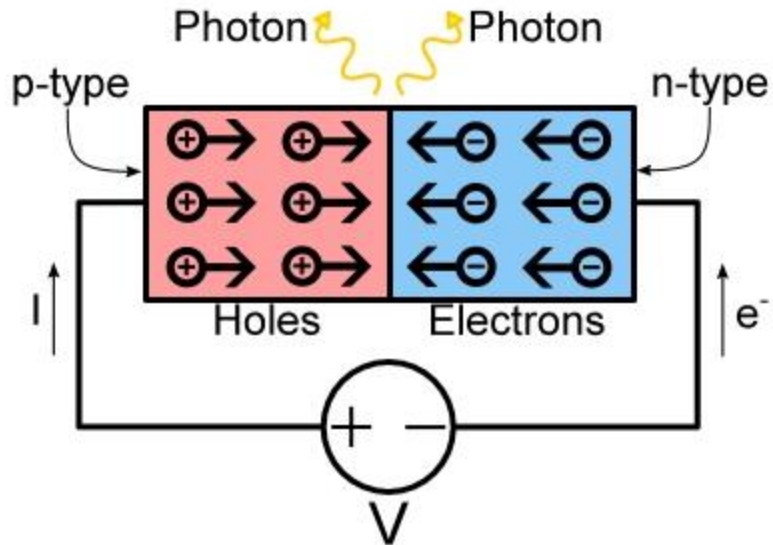

(source: wikipedia)



- Light-emitting diodes (LEDs)
  - Electrical  $\rightarrow$  Optical conversion
  - Made of III-V semiconductors
  - Light of specific wavelength (red, blue, green, yellow)
  - Semiconductor lasers  $\rightarrow$  Coherent light

25/08/2015

Parameter	Type of Light Bulb			
	Incandescent	Fluorescent	White LED	
			Circa 2010	Circa 2025
Luminous Efficiency (Lumens/W)	~12	~40	~70	~150
Useful Lifetime (hours)	~1000	~20,000	~60,000	~100,000
Purchase Price	~\$1.50	~\$5	~\$10	~\$5
Estimated Cost over 10 Years	~\$410	~\$110	~\$100	~\$40
Courtesy of: "Fundamentals of Applied Electromagnetics" by Fawwaz T. Ulaby, Eric Michielssen, Umberto Ravaioli. Page 33, Figure TF1-7				
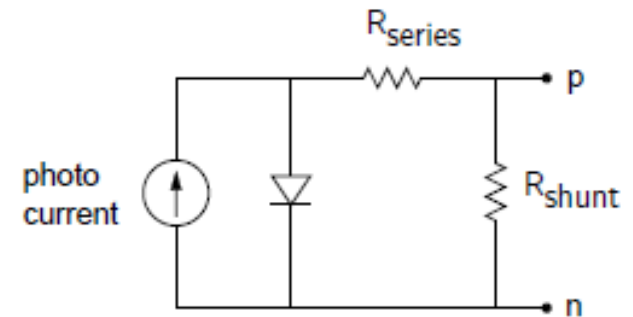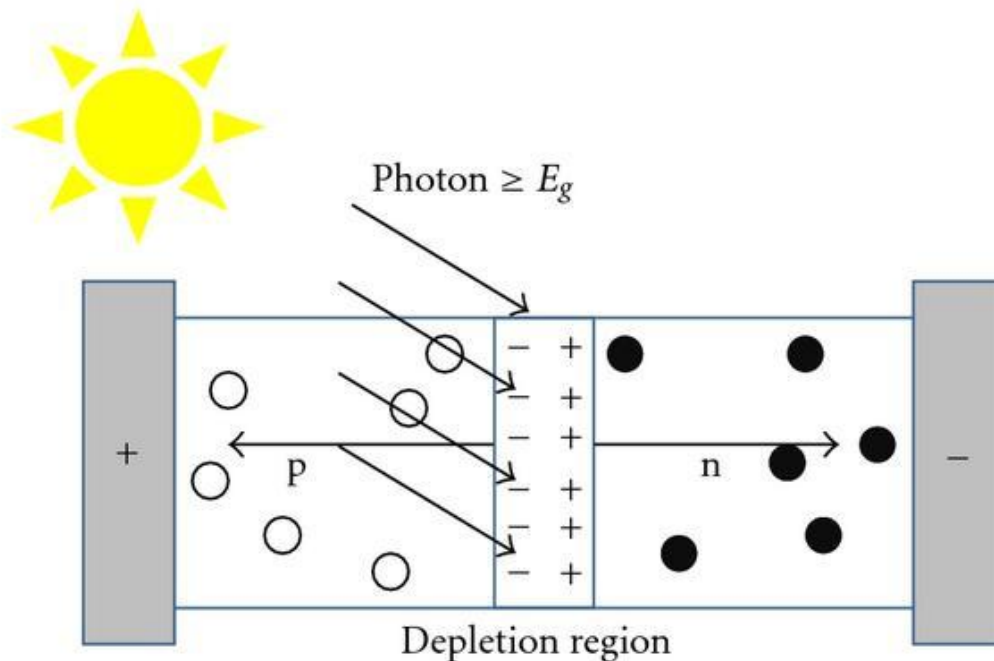
# Types and Applications of Diodes


- Solar cells
  - Optical  $\rightarrow$  Energy
  - Solar panel  $\rightarrow$  Multiple solar cells in series/parallel



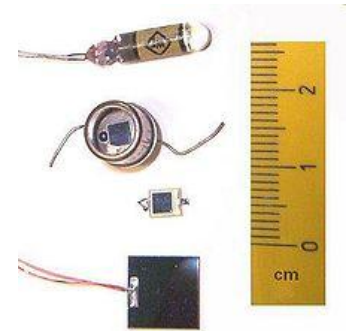
# Types and Applications of Diodes

- Photodiodes

- Detect optical signals (DC or time-varying) → Electrical signal
- Similar to solar cell → Optimized for high sensitivity, low noise and high frequency applications
- Consumer electronics
  - CD players, infrared remote control receivers, cameras
- Fibre-optic communications → high frequency application
- Spectroscopy, night vision, astronomy → high sensitivity app



Discrete

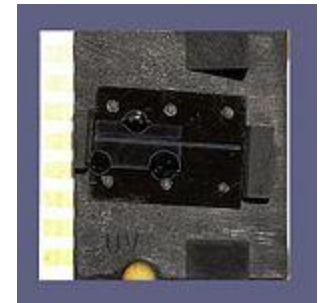


Chip




Material	<a href="#">Electromagnetic spectrum wavelength</a> range (nm)
<a href="#">Silicon</a>	190–1100
<a href="#">Germanium</a>	400–1700
<a href="#">Indium gallium arsenide</a>	800–2600
<a href="#">Lead(II) sulfide</a>	<1000–3500

# Diode circuits

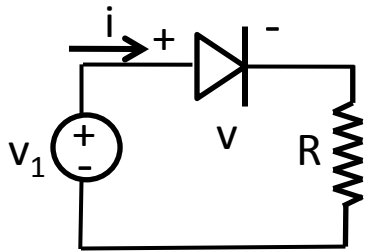

$$i = I_S \left( e^{\frac{v}{\eta V_T}} - 1 \right)$$
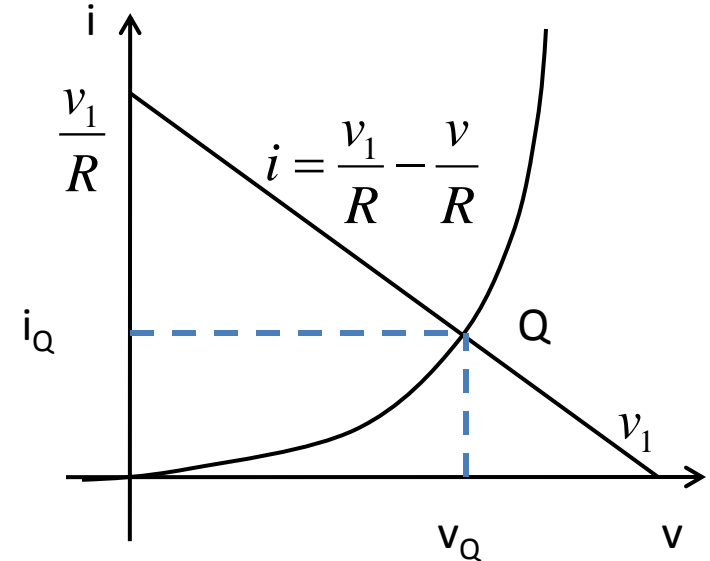
$$v_1 = v + Ri \Rightarrow i = \frac{v_1}{R} - \frac{v}{R}$$



Transcendental equation -> no analytical equation


Graphical solution

$i = (v_1 - v)/R$  is called the load line  $\rightarrow$  external constraint on the diode

Q  $\rightarrow$  Quiescent operating point, or Q point or operating point
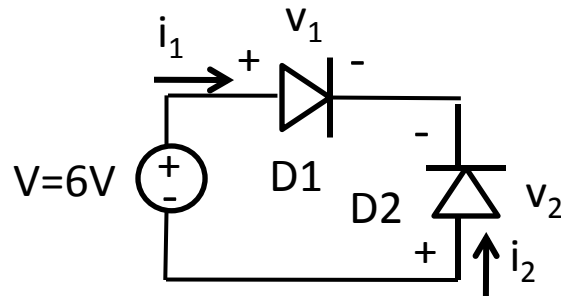
# Diode circuits

The battery will forward bias D1 and reverse bias D2



Hence  $i_2 = -I_S = -i_1$

$$i_1 = I_S (e^{\frac{v_1}{\eta V_T}} - 1) \Rightarrow v_1 = \eta V_T \ln \left( \frac{i_1}{I_S} + 1 \right)$$



$$v_1 = \eta V_T \ln \left( \frac{I_S}{I_S} + 1 \right) = 0.036V$$

$$v_2 = -6 + v_1 = -5.964V$$



- Assume both diodes have the same saturation current  $I_S$  and  $\eta$

# DC Diode Models

(i) Ideal diode

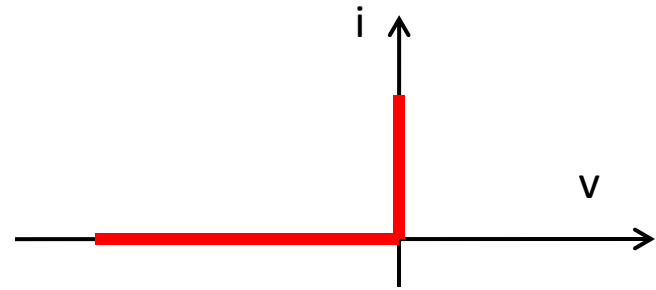
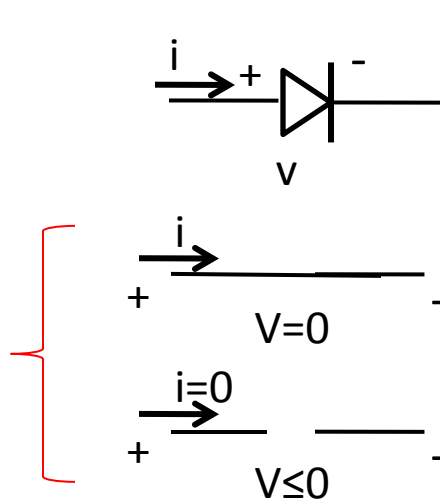


(ii) Non-ideal diode Model 1

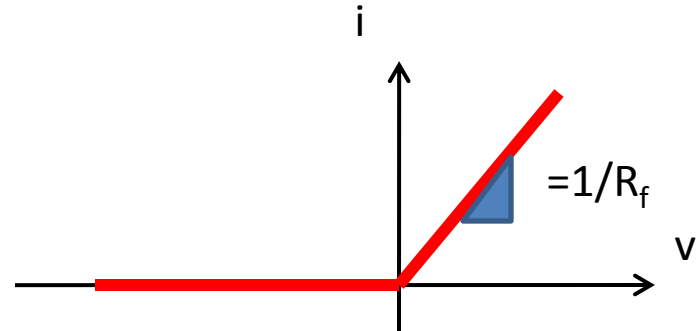
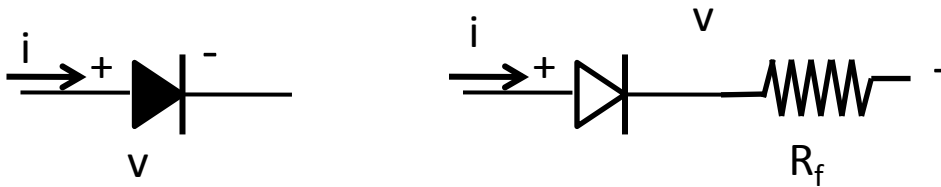


# DC Diode Models

## (iii) Non-ideal diode Model 2

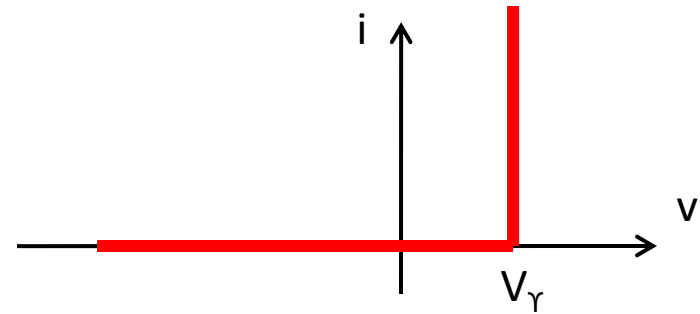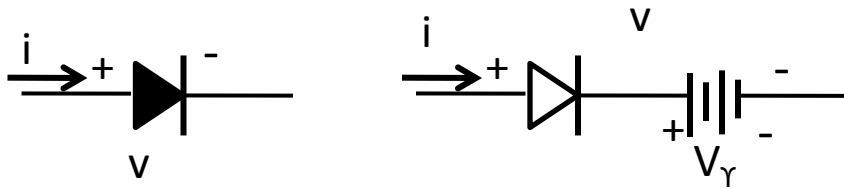

## (iv) Non-ideal diode Model 3

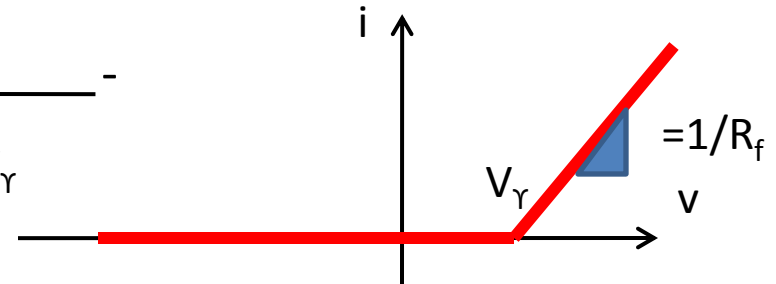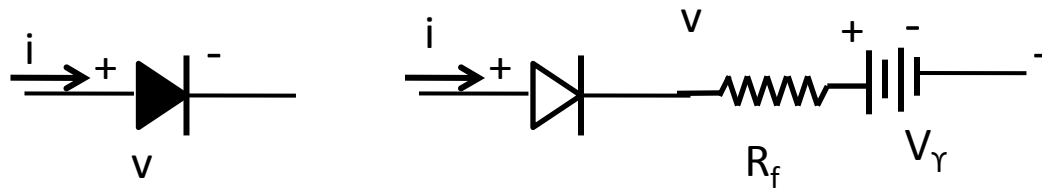




# Algorithm for diode circuits (Ideal diode model)

- Assume forward bias (ON) or reverse bias (OFF)
- Replace the diode by a short circuit or open circuit
- Solve the circuit using known techniques
- If inconsistent, e.g.  $I < 0$  for forward bias, then change assumption and resolve


# Example: Half-wave rectifier

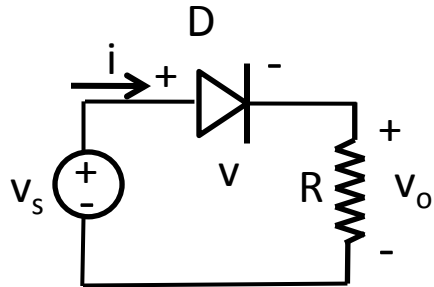

For  $v_s > 0$ , assume D is ON

$$v_o = v_s$$

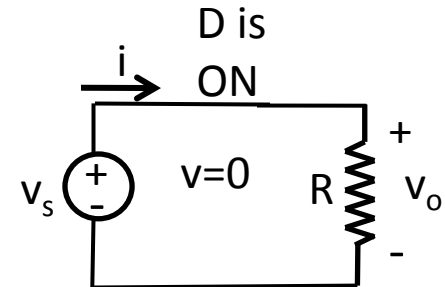
$$i = v_s / R > 0 \rightarrow \text{D is ON is correct}$$




For  $v_s \leq 0$ , assume D is OFF

$$i = 0$$
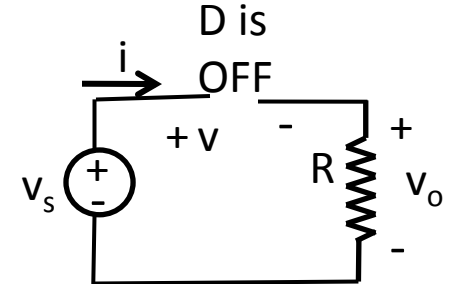
$$v = v_s - Ri = v_s \leq 0 \rightarrow \text{D is OFF is correct}$$




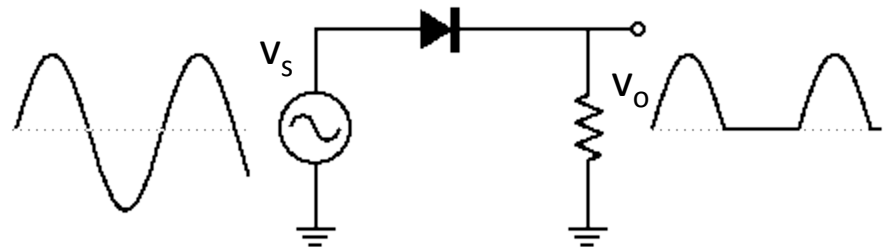
$$v_o = \begin{cases} 0 \text{ V} & \text{for } v_s \leq 0 \\ v_s & \text{for } v_s > 0 \end{cases}$$



# Example: Diode clipper circuit

For  $v_s > 0$  assume that D is ON

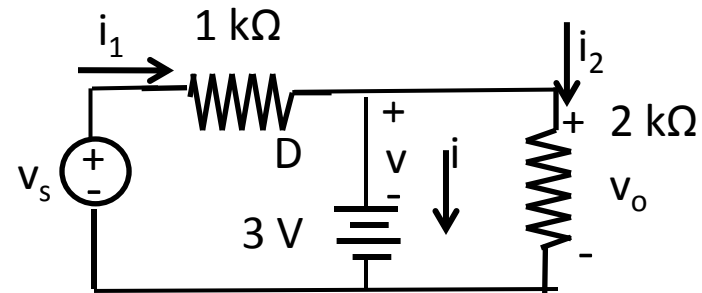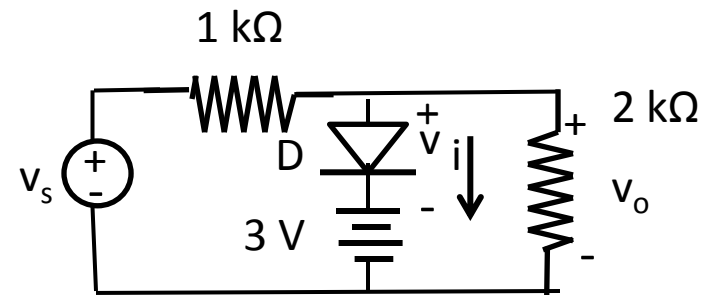

$$i_1 = \frac{v_s - 3}{1000}, i_2 = \frac{3}{2000} = 1.5 \text{ mA}$$



$$i = i_1 - i_2 = \frac{v_s}{1000} - 3 \times 10^{-3} - 1.5 \times 10^{-3}$$

$$i > 0 \Rightarrow v_s > 4.5 \text{ V}$$

$$v_o = 2000 \times 1.5 \times 10^{-3} = 3 \text{ V}$$
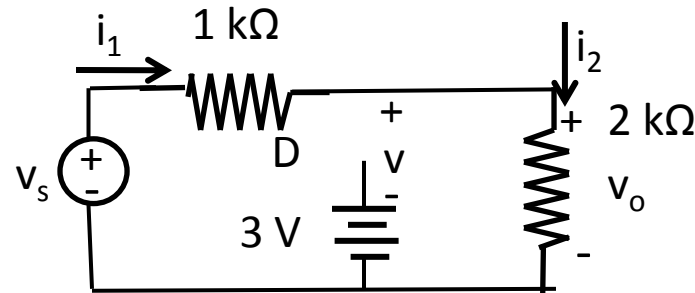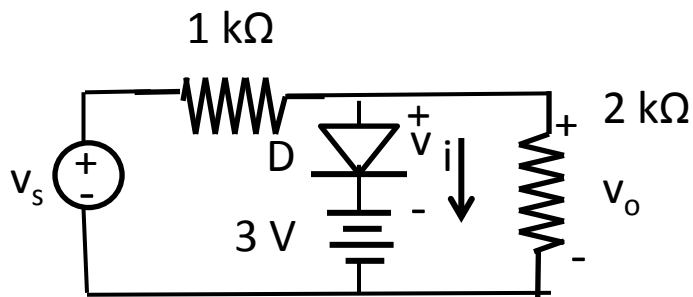
# Example: Diode clipper circuit

For  $v_s \leq 4.5$  0 assume that D is OFF




$$v_o = \frac{2}{1+2} \times v_s = \frac{2}{3} v_s$$



$$v = v_o - 3 = \frac{2}{3} v_s - 3 \leq 0$$

Hence assumption that D is OFF is correct



# Example: Diode clipper circuit

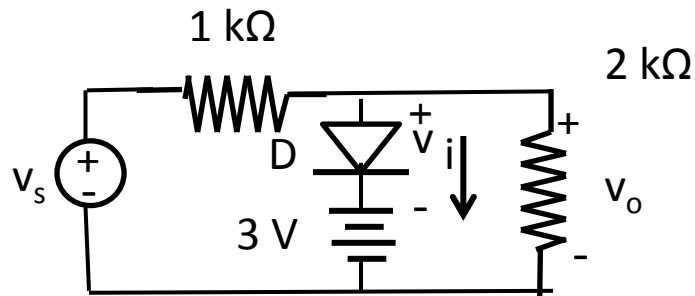

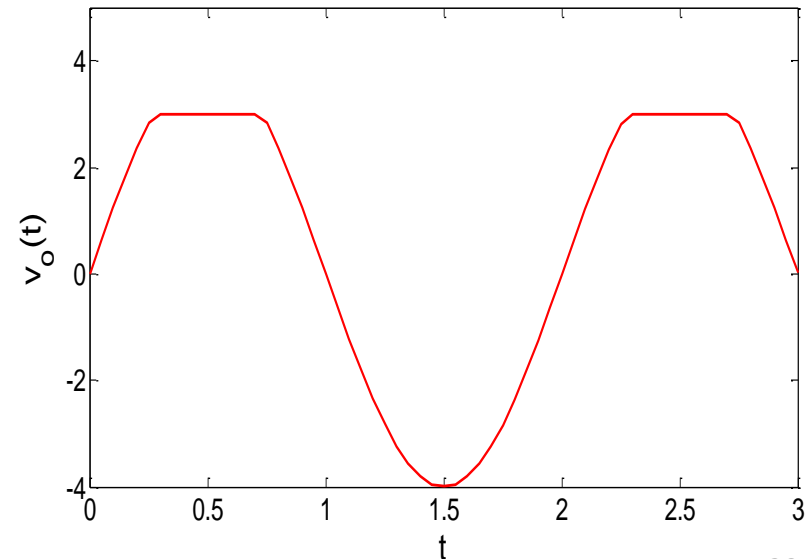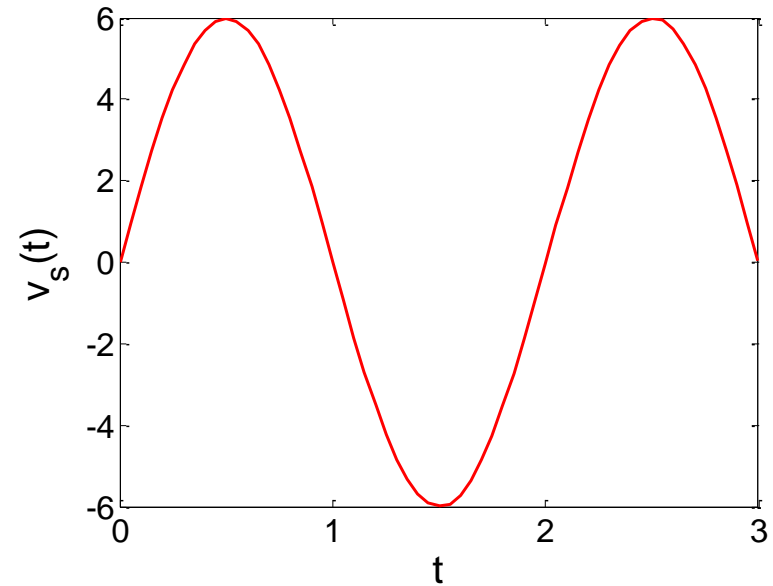
$$v_o = \begin{cases} \frac{2}{3} v_s & \text{for } v_s \leq 4.5\text{V} \\ 3\text{V} & \text{for } v_s > 4.5\text{V} \end{cases}$$



# Example

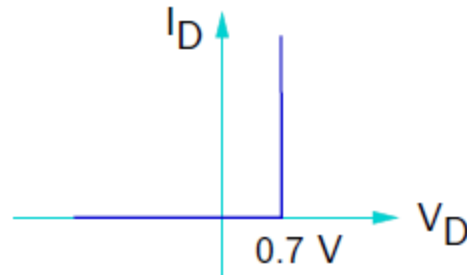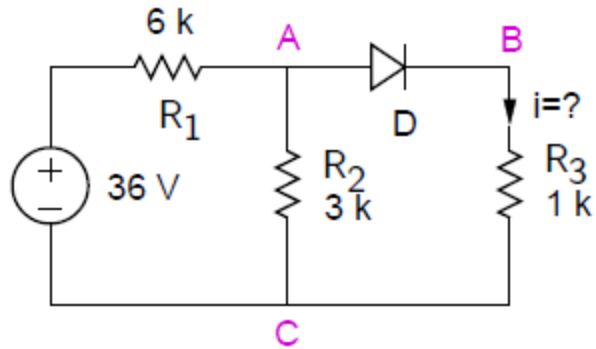


Case 1: D is off.

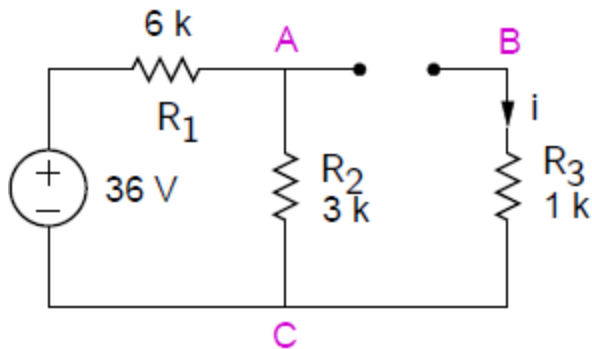

$V_{AB} = V_{AC} = (3 \times 36) / 9 = 12 \text{ V}$   
 which is not consistent with our  
 assumption of D being off.  
 $\rightarrow$  D must be on.

Case 2: D is on.

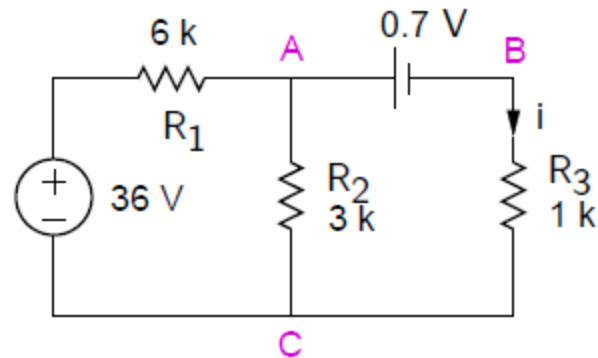


Taking  $V_C = 0 \text{ V}$ ,

$$\frac{V_A - 36}{6 \text{ k}} + \frac{V_A}{3 \text{ k}} + \frac{V_A - 0.7}{1 \text{ k}} = 0,$$

$$\rightarrow V_A = 4.47 \text{ V}, i = 3.77 \text{ mA}.$$

# Application to Digital Logic

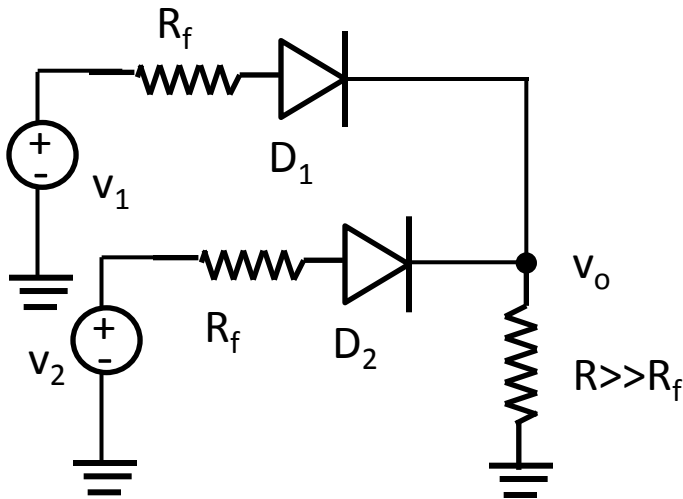



$V_1$	$V_2$	$D_1$	$D_2$	$V_o$
0	0	OFF	OFF	0
0	$V_H$	OFF	ON	$(R/R_f + R)V_H \sim V_H$
$V_H$	0	ON	OFF	$(R/R_f + R)V_H \sim V_H$
$V_H$	$V_H$	ON	ON	$(2R/R_f + 2R)V_H \sim V_H$

- Assume high voltage= $V_H > 0$  represents “1”
- Assume low voltage= $0V$  represents “0”
- Assume ideal diodes

$V_1$	$V_2$	$V_o$
0	0	0
0	1	1
1	0	1
1	1	1

OR Gate

# Zener Diodes

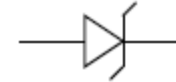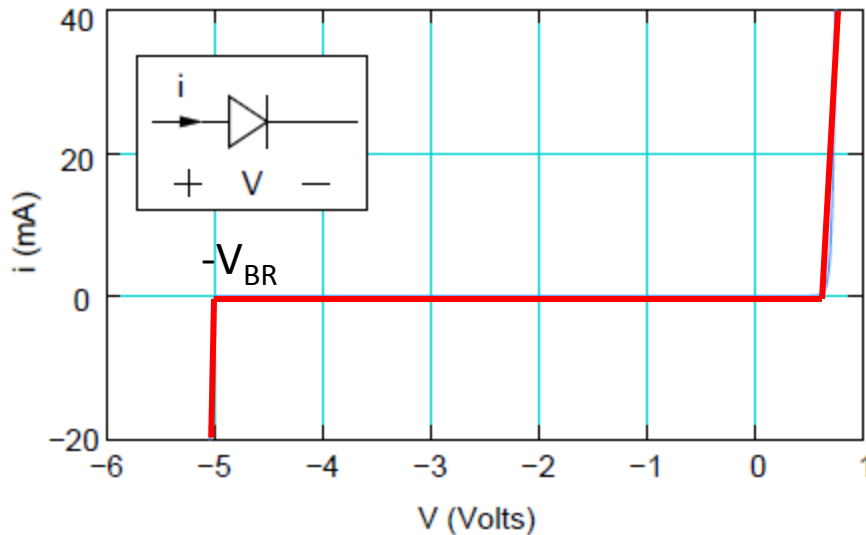


Symbol for a Zener diode

- At high reverse biases, diodes “break down”
  - Large current flow, voltage “clamped” at  $-V_{BR}$
- Breakdown occurs due to
  - (i) Avalanche of carriers generated by collisions  $\rightarrow$  typically in lightly doped diodes, large  $|V_{BR}| \rightarrow$  tens to hundreds of V
  - (ii) Zener tunneling of carriers  $\rightarrow$  typically in heavily doped diodes, small  $|V_{BR}| = V_Z \rightarrow 5-6$  V in Si
- Zener diodes are used to limit voltage swing in electronic circuits




# Example

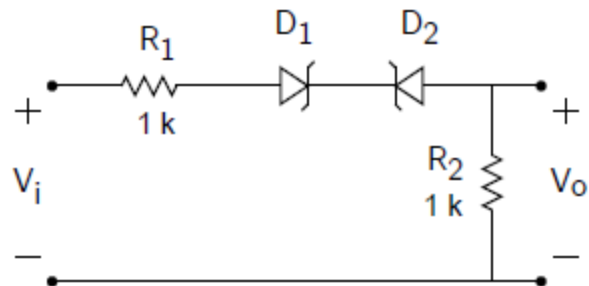


$V_{on} = 0.7 \text{ V}$ ,  $V_Z = 5 \text{ V}$ .

Plot  $V_o$  versus  $V_i$ .

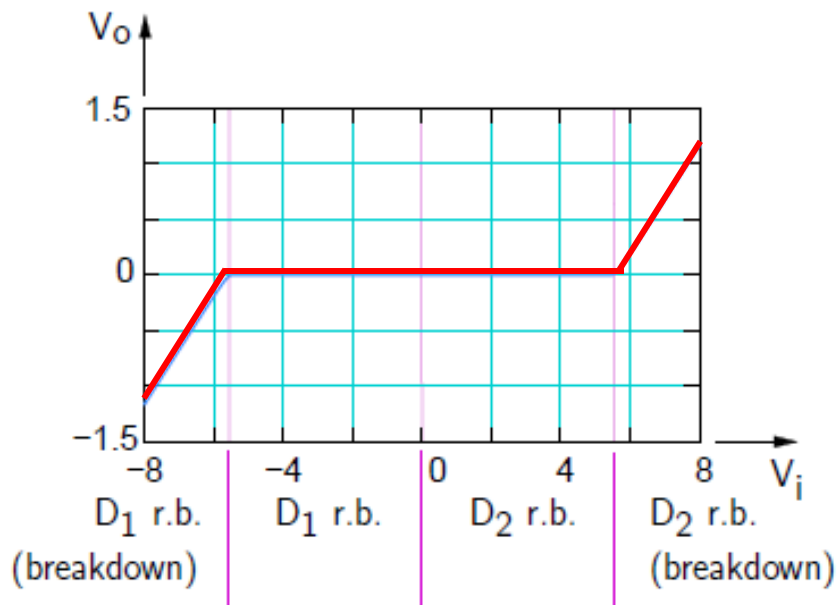

For a current to flow, we have two possibilities:

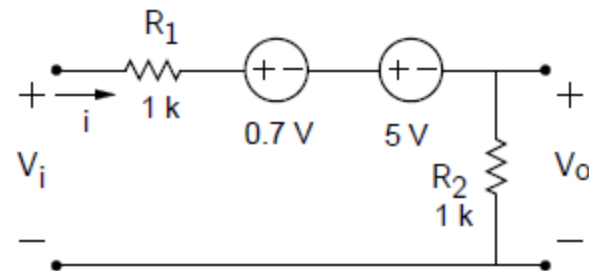
$D_1$  on (forward),  $D_2$  in reverse breakdown



$$V_o = iR_2 = \frac{V_i - 5.7}{R_1 + R_2} R_2$$

Since  $i > 0$ , this can happen only when  $V_i > 5.7 \text{ V}$ .

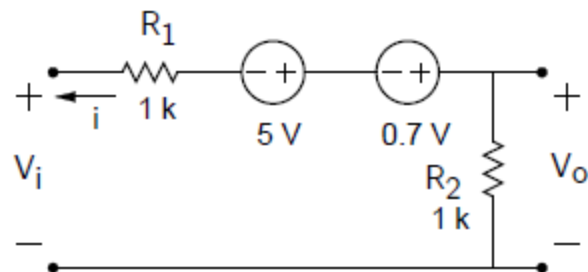
$D_2$  on (forward),  $D_1$  in reverse breakdown



$$V_o = -iR_2 = \frac{V_i + 5.7}{R_1 + R_2} R_2$$


Since  $i > 0$ , this can happen only when  $V_i < -5.7 \text{ V}$ .

# Example: Voltage Limiter

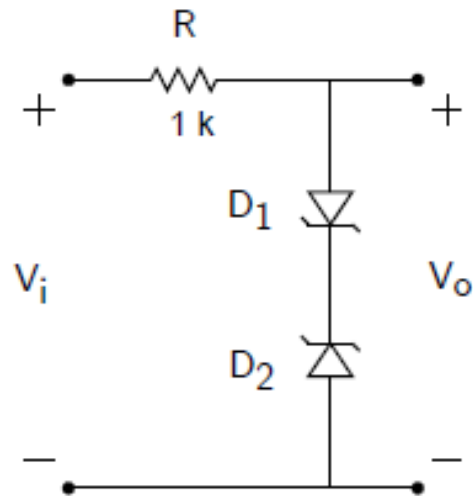


$V_{on} = 0.7\text{ V}$ ,  $V_Z = 5\text{ V}$ .

Plot  $V_o$  versus  $V_i$ .

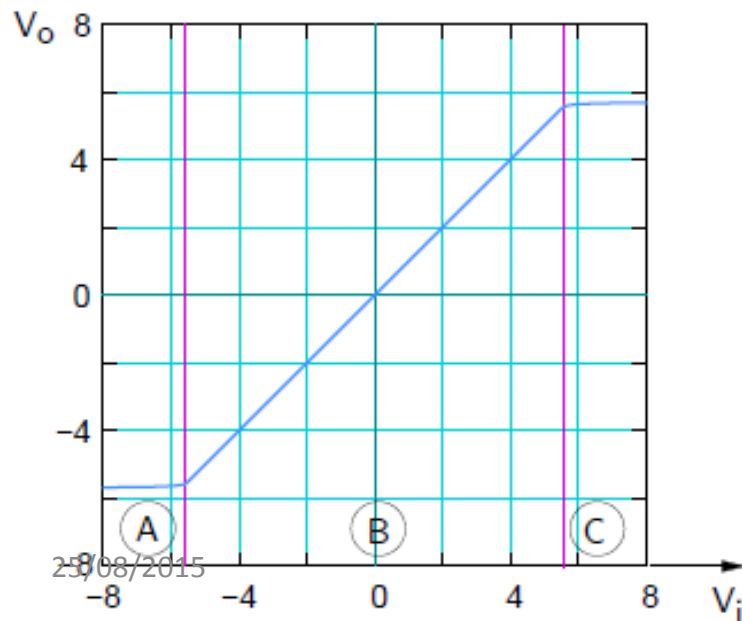


For a current to flow, we have two possibilities:

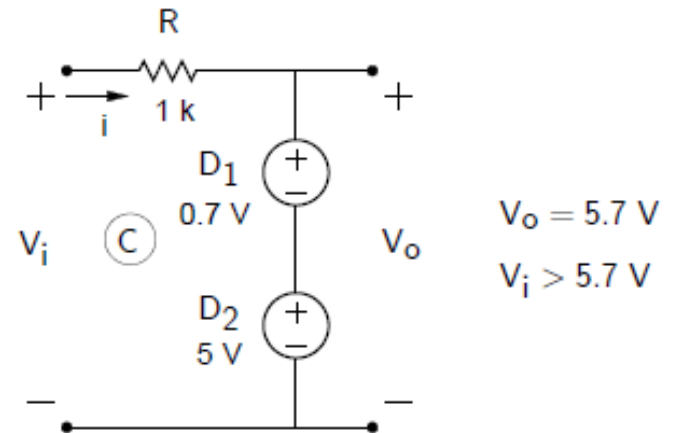$D_1$  on (forward),  $D_2$  in reverse breakdown





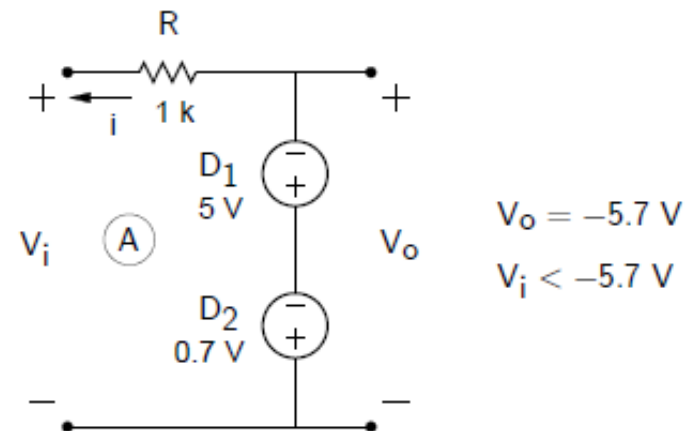$D_2$  on (forward),  $D_1$  in reverse breakdown





In the range,  $-5.7\text{ V} < V_i < 5.7\text{ V}$ , no current flows, and  $V_o = V_i$ . (B)

# Peak Detector

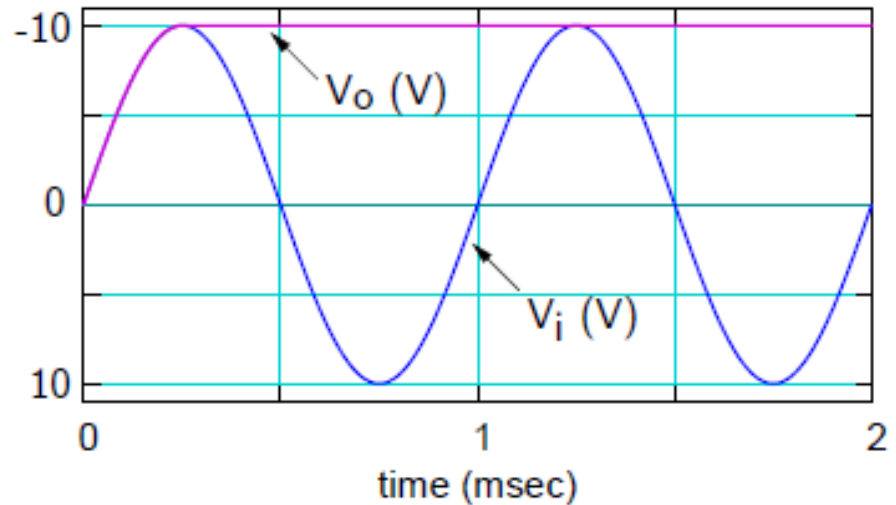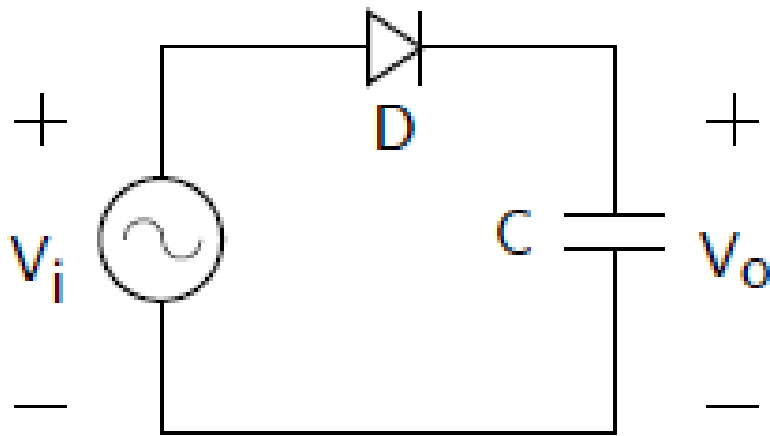



- Let  $V_o(t)=0$  V at  $t = 0$ , and assume the diode to be ideal, with  $V_{on}=0$  V.
- For  $0 < t < T/4$ ,  $V_i$  rises from 0 to  $V_m$ . As a result, the capacitor charges.
- Since the on resistance of the diode is small, time constant  $\tau \ll T/4$ ; therefore the charging process is instantaneous  $\rightarrow V_o(t) = V_i(t)$ .
- For  $t > T/4$ ,  $V_i$  starts falling. The capacitor holds the charge it had at  $t=T/4$  since the diode prevents discharging.

# Peak Detector (Contd.)

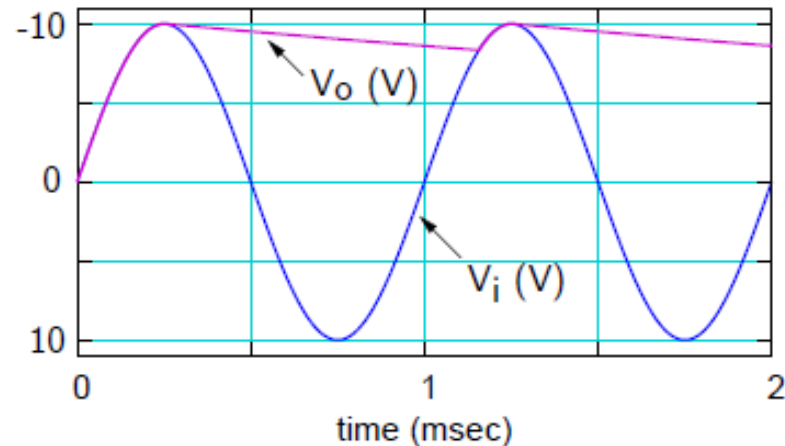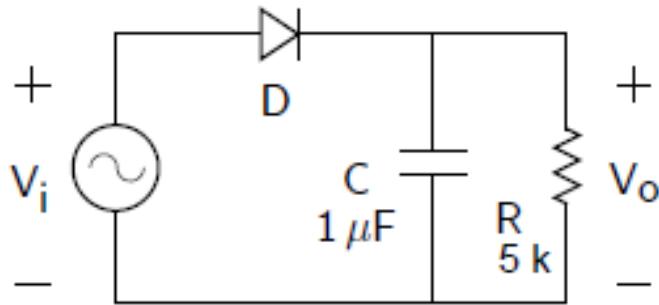



- Capacitor can discharge through  $R$  when diode is off
- When  $V_i > V_o$ , the capacitor charges again.
- The time constant for the charging process is  $\tau = R_{Th}C$ , where  $R_{Th} = R \parallel R_{on}$  is the Thevenin resistance seen by the capacitor,  $R_{on}$  being the on resistance of the diode.
- Since  $\tau \ll T$ , the charging process is instantaneous.
- Used to demodulate AM signals  $\rightarrow$  envelope detector

# Clamping Circuit (DC restorer)

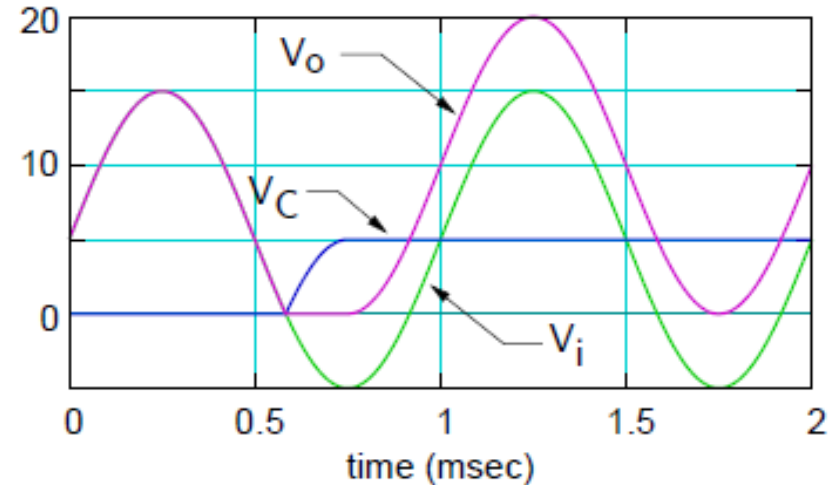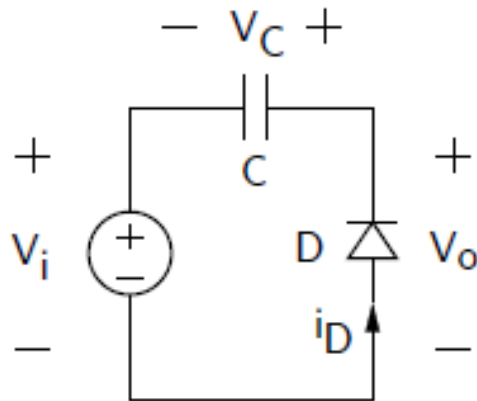

- Assume  $V_{on} = 0$  V for the diode.
- When  $D$  conducts,  $V_D = -V_o = 0 \rightarrow V_C + V_i = 0$ , i.e.,  $V_C = -V_i$ .
- $V_C$  can only increase with time (or remain constant) since  $i_D$  can only be positive.
- The net result is that the capacitor gets charged to a voltage  $V_C = -V_i$  corresponding to the maximum negative value of  $V_i$ , and holds that voltage thereafter. Let us call this voltage  $V_C^0$  (a constant).
- $V_o(t) = V_C(t) + V_i(t) = V_C^0 + V_i(t)$ , which is a “level-shifted” version of  $V_i$ .

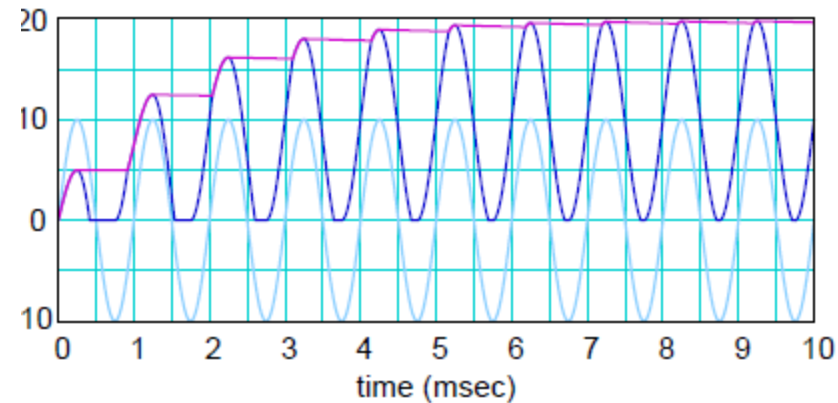
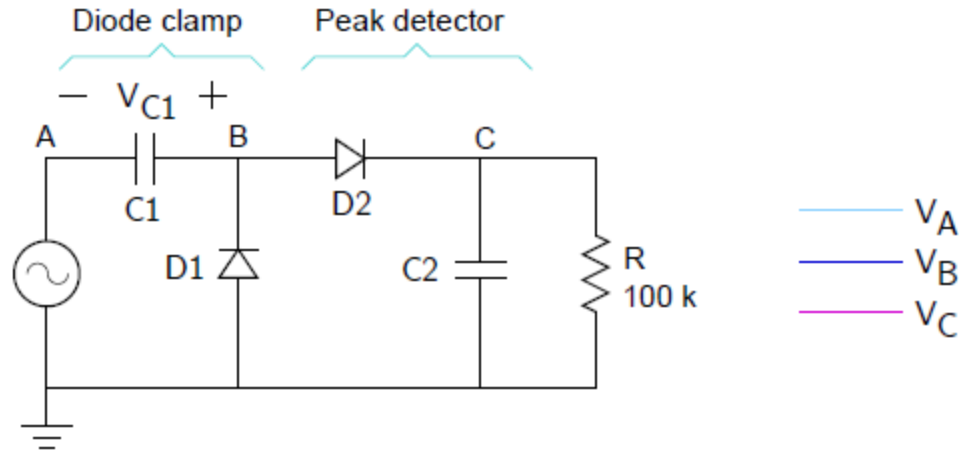
# Voltage doubler (Peak-to-peak detector)



- The diode clamp shifts  $V_A$  up by  $V_m$  (the amplitude of the AC source), making  $V_B$  go from 0 to  $2V_m$ .
- The peak detector detects the peak of  $V_B$  ( $2V_m$  w.r.t. ground), and holds it constant.
- Note that it takes a few cycles to reach steady state.

# Backup

# Example

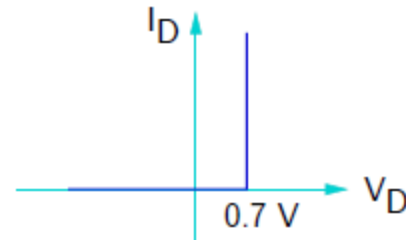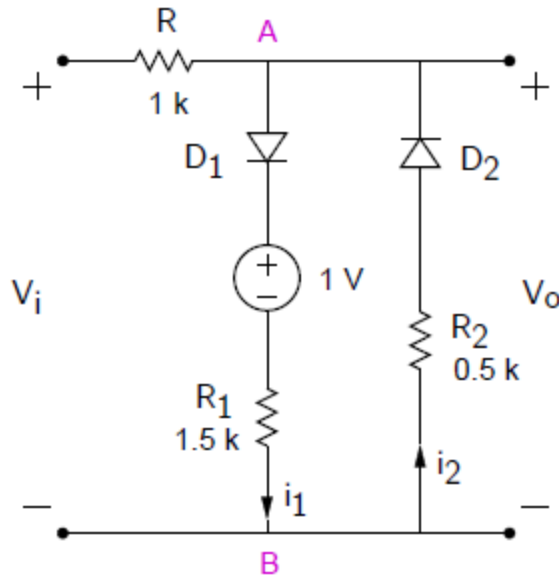

(a) Plot  $V_o$  versus  $V_i$  for  $-5 \text{ V} < V_i < 5 \text{ V}$ .

- First, let us show that  $D_1$  on  $\rightarrow D_2$  off, and  $D_2$  on  $\rightarrow D_1$  off.
- Consider  $D_1$  to be on  $\rightarrow V_{AB} = 0.7 + 1 + i_1 R_1$ .
  - Note that  $i_1 > 0$ , since  $D_1$  can only conduct in the forward direction.
  - $V_{AB} > 1.7 \text{ V} \rightarrow D_2$  cannot conduct.
- Similarly, if  $D_2$  is on,  $V_{BA} > 0.7 \text{ V}$ , i.e.,  $V_{AB} < -0.7 \text{ V} \rightarrow D_1$  cannot conduct.
- Clearly,  $D_1$  on  $\Rightarrow D_2$  off, and  $D_2$  on  $\Rightarrow D_1$  off.



# Example

- For  $-0.7 \text{ V} < V_i < 1.7 \text{ V}$ , both  $D_1$  and  $D_2$  are off.
  - no drop across  $R$ , and  $V_o = V_i$ .
- For  $V_i < -0.7 \text{ V}$ ,  $D_2$  conducts  $\rightarrow V_o = -0.7 - i_2 R_2$

Use KVL to get  $i_2$ :  $V_i + i_2 R_2 + 0.7 + R i_2 = 0$ .

$$\rightarrow i_2 = -\frac{V_i + 0.7}{R + R_2}, \text{ and}$$



$$V_o = -0.7 - R_2 i_2 = \frac{R_2}{R + R_2} V_i - 0.7 \frac{R}{R + R_2}.$$

- For  $V_i > 1.7 \text{ V}$ ,  $D_1$  conducts  $\rightarrow V_o = 0.7 + 1 + i_1 R_1$


Use KVL to get  $i_1$ :  $-V_i + i_1 R + 0.7 + 1 + i_1 R_1 = 0$ .

$$\rightarrow i_1 = \frac{V_i - 1.7}{R + R_1}, \text{ and}$$

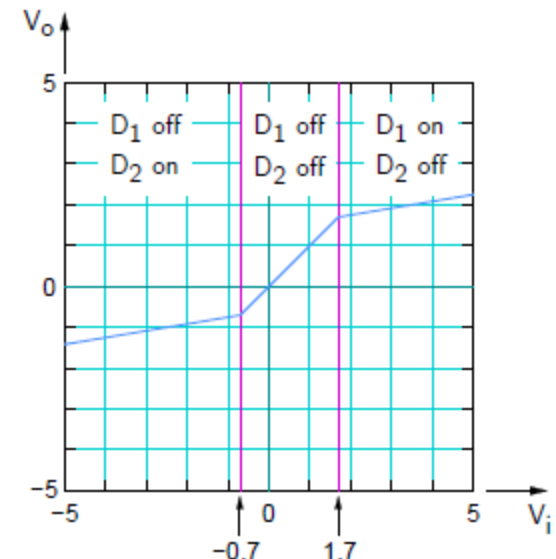
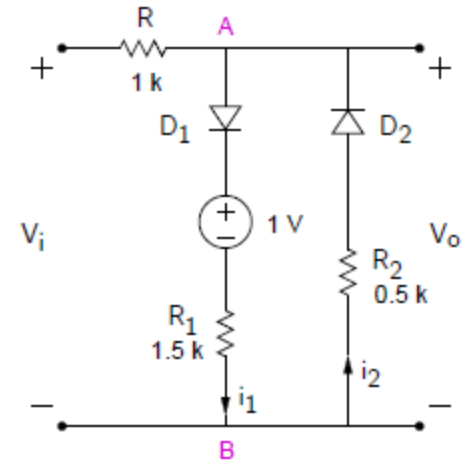
$$V_o = 1.7 + R_1 i_1 = \frac{R_1}{R + R_1} V_i + 1.7 \frac{R}{R + R_1}.$$



# Example

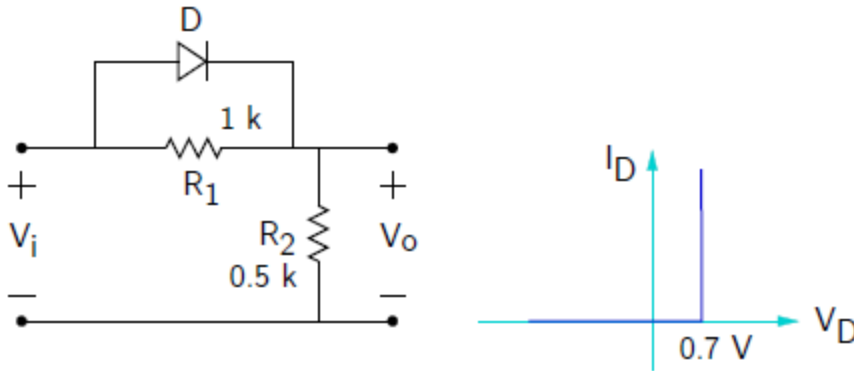

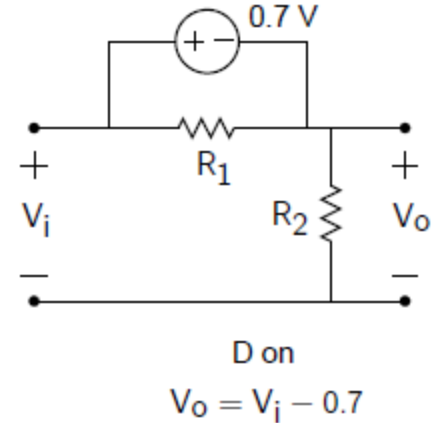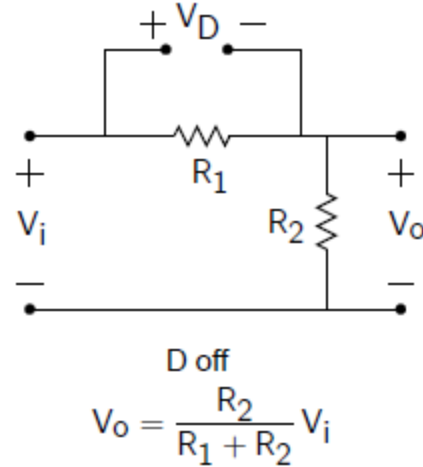Plot  $V_o$  versus  $V_i$  for  $-5 \text{ V} < V_i < 5 \text{ V}$ .



- At what value of  $V_i$  will the diode turn on?

In the off state,  $V_D = \frac{R_1}{R_1 + R_2} V_i$ .

For  $D$  to change to the on state,  $V_D = 0.7 \text{ V}$ .

i.e.,  $V_i = \frac{R_1 + R_2}{R_1} \times 0.7 = 1.05 \text{ V}$ .

