

Sinusoidal steady state analysis (Phasors)



S. Lodha

Reference: L. Bobrow

Sinusoidal signals (AC signals)

- Response to repetitive, sinusoidal (AC) signal
 - Ubiquitous
 - Ordinary household voltage
 - Radio (AM/FM)
 - Television etc.
- In a lot of circuit applications
 - Power consumed/supplied is of importance
 - Instantaneous power (ratings in circuits)

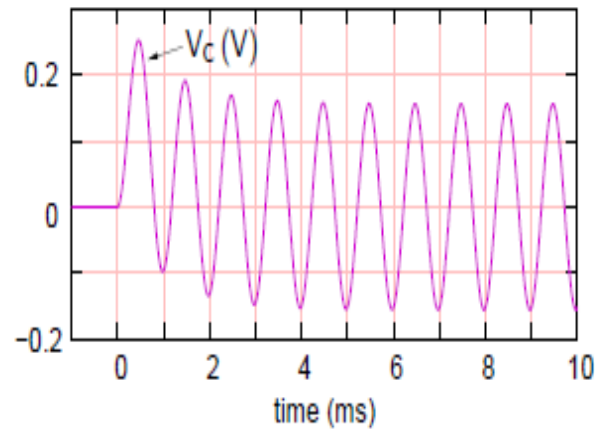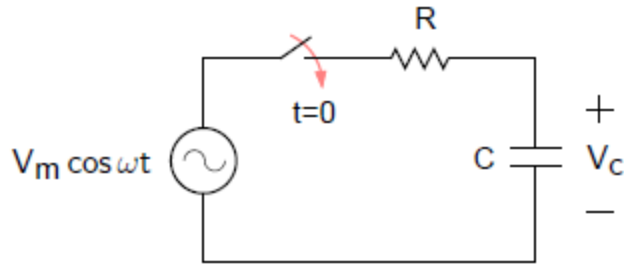Sinusoidal analysis (time-domain, steady state)



$$RCV'_c + V_c = V_m \cos \omega t$$

$$V_c(t) = V_f(t) + V_n(t)$$

$$V_n(t) = Ae^{-\frac{t}{RC}}$$

$$V_f(t) = C_1 \cos \omega t + C_2 \sin \omega t$$

Substituting

$$\omega RC(-C_1 \sin \omega t + C_2 \cos \omega t) + C_1 \cos \omega t + C_2 \sin \omega t = V_m \cos \omega t$$

C_1 and C_2 can be found by equating coefficients on both sides

$$V_c(t) = Ae^{-\frac{t}{RC}} + C_1 \cos \omega t + C_2 \sin \omega t$$

$t \rightarrow \infty$

$$V_c(t) = C_1 \cos \omega t + C_2 \sin \omega t$$

Sinusoidal steady-state response



- We assume the forced response of RLC ckts to a sinusoidal input to be a sinusoid
 - Each of the elements – R, L, C will respond with a sinusoid to a sinusoidal input; no change in frequency ω
 - Sum of sinusoidal outputs is also a sinusoid
- Any circuit containing resistors, capacitors, inductors, sinusoidal voltage and current sources (of the same frequency), dependent (linear) sources behaves in a similar manner, viz., each current and voltage in the circuit becomes purely sinusoidal as $t \rightarrow \infty$

Real sinusoid \rightarrow Complex Sinusoid

RLC ckt

Input

Output

$$A \cos(\omega t + \theta)$$

$$B \cos(\omega t + \phi)$$

Shift by 90deg

$$A \sin(\omega t + \theta)$$

$$B \sin(\omega t + \phi)$$

Scale by K, linearity

$$KA \sin(\omega t + \theta)$$

$$KB \sin(\omega t + \phi)$$

Superposition

$$A \cos(\omega t + \theta) + KA \sin(\omega t + \theta)$$

$$B \cos(\omega t + \phi) + KB \sin(\omega t + \phi)$$

K=j

$$A \cos(\omega t + \theta) + jA \sin(\omega t + \theta)$$

$$B \cos(\omega t + \phi) + jB \sin(\omega t + \phi)$$

Euler's formula

$$Ae^{j(\omega t + \theta)}$$

$$Be^{j(\omega t + \phi)}$$


- Finding soln (B, ϕ) to real sinusoid is equivalent to finding the soln (B, ϕ) to the complex sinusoid (B, ϕ)
- Using complex numbers makes differential eqn soln easier

Phasors: Definition

$$\mathbf{X} = X_m e^{j\theta} = X_m \angle \theta$$

$$x(t) = \text{Re}[\mathbf{X}e^{j\omega t}] = \text{Re}[X_m e^{j\theta} e^{j\omega t}] = X_m \cos(\omega t + \theta)$$
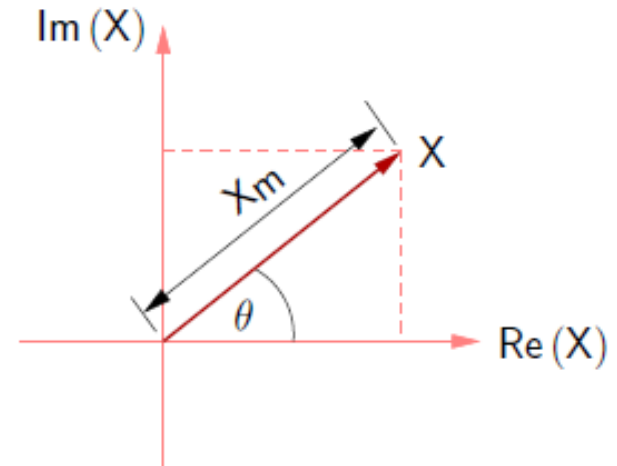
$$X_m \angle \theta = X_m \cos \theta + X_m j \sin \theta$$




- Phasor is a complex number
- The term ωt is implicit
- Can also be written in the polar or rectangular form
- Also called frequency domain representation
- Significant simplification of sinusoidal steady state analysis

Phasor: Examples


| Time domain | Frequency domain |
|--|--|
| $v_1(t) = 3.2 \cos(\omega t + 30^\circ) \text{ V}$ | $V_1 = 3.2 \angle 30^\circ = 3.2 \exp(j\pi/6) \text{ V}$ |
| $i(t) = -1.5 \cos(\omega t + 60^\circ) \text{ A}$ $= 1.5 \cos(\omega t + \pi/3 - \pi) \text{ A}$ $= 1.5 \cos(\omega t - 2\pi/3) \text{ A}$ | $I = 1.5 \angle (-2\pi/3) \text{ A}$ |
| $v_2(t) = -0.1 \cos(\omega t) \text{ V}$ $= 0.1 \cos(\omega t + \pi) \text{ V}$ | $V_2 = 0.1 \angle \pi \text{ V}$ |
| $i_2(t) = 0.18 \sin(\omega t) \text{ A}$ $= 0.18 \cos(\omega t - \pi/2) \text{ A}$ | $I_2 = 0.18 \angle (-\pi/2) \text{ A}$ |
| $i_3(t) = \sqrt{2} \cos(\omega t + 45^\circ) \text{ A}$ | $I_3 = 1 + j1 \text{ A}$ $= \sqrt{2} \angle 45^\circ \text{ A}$ |

Phasor representation/Impedance of resistor

Time domain

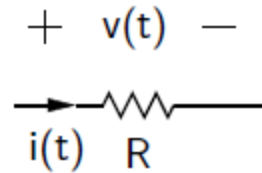

Phasor

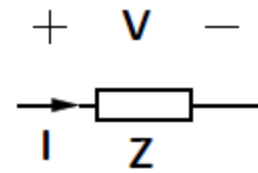

$$i(t) = I_m \cos(\omega t + \theta)$$

$$v(t) = Ri(t) = RI_m \cos(\omega t + \theta) = V_m \cos(\omega t + \theta)$$

$$\text{Re}[V_m e^{j(\omega t + \theta)}] = \text{Re}[RI_m e^{j(\omega t + \theta)}]$$

$$\mathbf{V} = R\mathbf{I}$$


$$\mathbf{Z} = \mathbf{V}/\mathbf{I} = R + j0$$

Phasor representation


Z is the impedance of the resistor

Phasor representation/Impedance of capacitor

Time domain

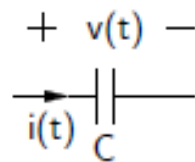

Phasor

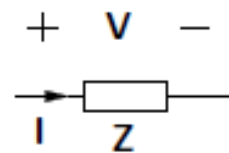

$$v(t) = V_m \cos(\omega t + \theta)$$

$$i(t) = C \frac{dv(t)}{dt} = -C\omega V_m \sin(\omega t + \theta) = C\omega V_m \cos(\omega t + \theta + \frac{\pi}{2})$$

$$\mathbf{V} = V_m \angle \theta$$

$$\mathbf{I} = C\omega V_m \angle(\theta + \frac{\pi}{2}) = \omega C V_m e^{j\theta} e^{j\frac{\pi}{2}} = j\omega C \mathbf{V}$$

Phasor representation

$$\mathbf{Z} = \mathbf{V}/\mathbf{I} = 0 + \frac{1}{j\omega C}$$


$$\mathbf{Y} = \mathbf{I}/\mathbf{V} = 0 + j\omega C$$

Z is the impedance of the capacitor


Y is the admittance of the capacitor

Phasor representation/Impedance of inductor

Time domain

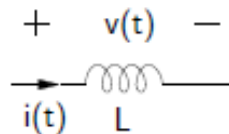

Phasor

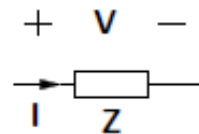

$$i(t) = I_m \cos(\omega t + \theta)$$

$$v(t) = L \frac{di(t)}{dt} = -L\omega I_m \sin(\omega t + \theta) = L\omega I_m \cos(\omega t + \theta + \frac{\pi}{2})$$

$$\mathbf{I} = I_m \angle \theta$$

$$\mathbf{V} = L\omega I_m \angle(\theta + \frac{\pi}{2}) = \omega L I_m e^{j\theta} e^{j\frac{\pi}{2}} = j\omega L \mathbf{I}$$

Phasor representation

$$\mathbf{Z} = \mathbf{V}/\mathbf{I} = 0 + j\omega L$$

$$\mathbf{Y} = \mathbf{I}/\mathbf{V} = 0 + \frac{1}{j\omega L}$$

Z is the impedance of the capacitor

Y is the admittance of the capacitor




Lead and Lag

$$\mathbf{V} = R\mathbf{I}$$

$$\mathbf{I} = C\omega V_m \angle(\theta + \frac{\pi}{2}) = \omega C V_m e^{j\theta} e^{j\frac{\pi}{2}} = j\omega C \mathbf{V}$$

$$\mathbf{V} = L\omega I_m \angle(\theta + \frac{\pi}{2}) = \omega L I_m e^{j\theta} e^{j\frac{\pi}{2}} = j\omega L \mathbf{I}$$

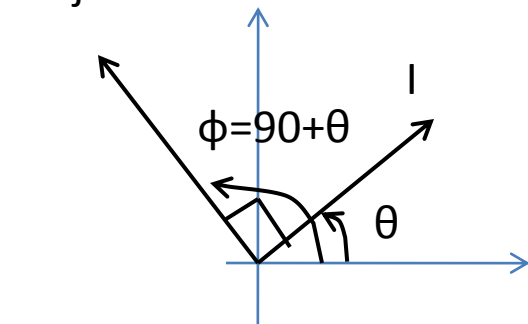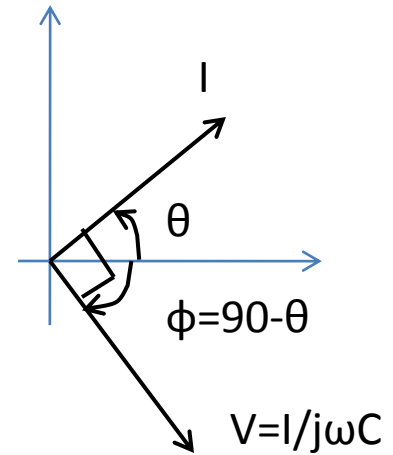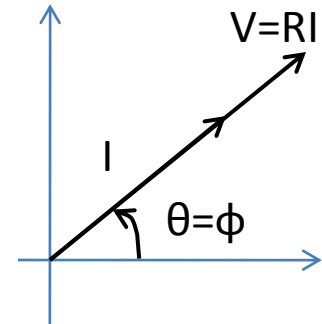
- Resistor \rightarrow in phase
- Capacitor \rightarrow current **leads** \mathbf{V} by 90deg
- Inductor \rightarrow voltage **leads** \mathbf{I} by 90deg



Sources


Time domain

Phasor

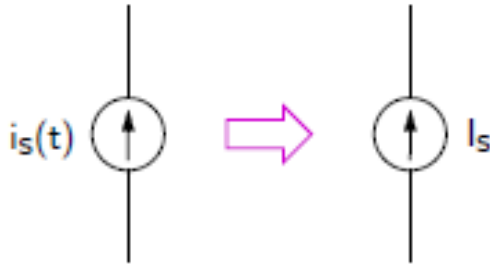

Time domain

Phasor

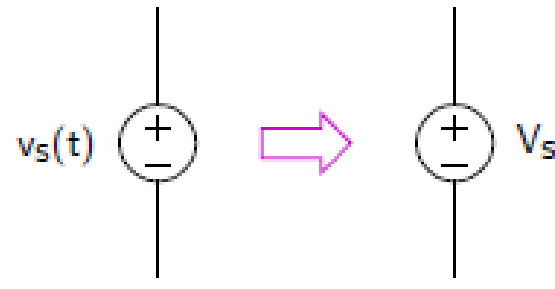

- An independent sinusoidal current source, $i_s(t) = I_m \cos(\omega t + \theta)$, can be represented by the phasor $I_m \angle \theta$ (i.e., a constant complex number)
- An independent sinusoidal voltage source, $v_s(t) = V_m \cos(\omega t + \theta)$, can be represented by the phasor $V_m \angle \theta$ (i.e., a constant complex number)
- Dependent (linear) sources can be treated in the sinusoidal steady state in the same manner as a resistor, i.e., by the corresponding phasor relationship. For example, for a CCVS, we have,
 - $v(t) = r i_c(t)$ in the time domain
 - $\mathbf{V} = r \mathbf{I}_c$ in the frequency domain


Phasor addition

$$v(t) = v_1(t) + v_2(t) = V_{m1} \cos(\omega t + \theta_1) + V_{m2} \cos(\omega t + \theta_2)$$

$$\mathbf{V} = \mathbf{V}_1 + \mathbf{V}_2 = V_{m1} e^{j\theta_1} + V_{m2} e^{j\theta_2}$$

$$\tilde{v}(t) = \text{Re}[(V_{m1} e^{j\theta_1} + V_{m2} e^{j\theta_2}) e^{j\omega t}] = V_{m1} \cos(\omega t + \theta_1) + V_{m2} \cos(\omega t + \theta_2) = v(t)$$



- Addition of sinusoidal quantities in the time domain can be replaced by addition of the corresponding phasors in the sinusoidal steady state.
- KCL and KVL in time domain hold for phasors also
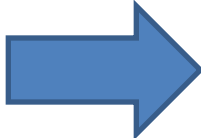
| | | | |
|------------|-------------------|--|-------------------------|
| For meshes | $\sum v_k(t) = 0$ |  | $\sum \mathbf{V}_k = 0$ |
| For nodes | $\sum i_k(t) = 0$ | | $\sum \mathbf{I}_k = 0$ |

Sinusoidal Steady State Analysis

- Resistors, capacitors, and inductors can be described by $\mathbf{V} = \mathbf{Z} \mathbf{I}$ in the frequency domain, which is similar to $V = R I$ in DC conditions (except that we are dealing with complex numbers in the frequency domain)
- An independent sinusoidal source in the frequency domain behaves like a DC source, e.g., $V_s = \text{constant}$ (a complex number)
- For dependent sources, a time-domain relationship such as $i(t) = \beta i_c(t)$ translates to $I = \beta I_c$ in the frequency domain
- **Circuit analysis in the sinusoidal steady state using phasors is therefore very similar to DC circuits with independent and dependent sources, and resistors**
- **Series/parallel formulas for resistors, nodal analysis, mesh analysis, Thevenin's and Norton's theorems can be directly applied**
- No differential equations!
- This is called the **frequency domain approach**

Example: RL circuit

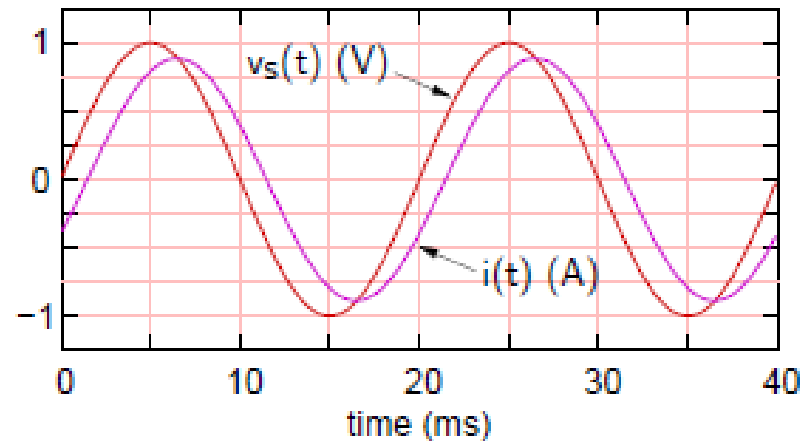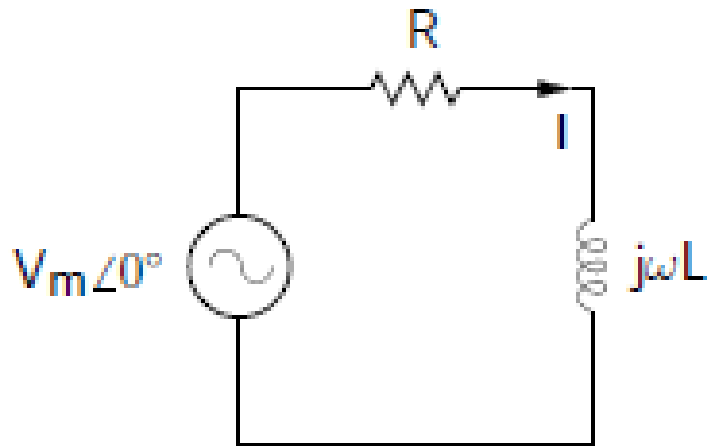


$$R = 1 \Omega$$
$$L = 1.6 \text{ mH}$$

$$I = \frac{V_m \angle 0}{R + j\omega L} \equiv I_m \angle (-\theta),$$

$$\text{where } I_m = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}}, \text{ and } \theta = \tan^{-1}(\omega L / R).$$

- In the time domain, $i(t) = I_m \cos(\omega t - \theta)$, which lags the source voltage since the peak (or zero) of $i(t)$ occurs $t = \theta / \omega$ seconds after that of the source voltage.
- For $R = 1 \Omega$, $L = 1.6 \text{ mH}$, $f = 50 \text{ Hz}$, $\theta = 26.6^\circ$, $t_{\text{lag}} = 1.48 \text{ ms}$.

Example: RL Circuit (contd)

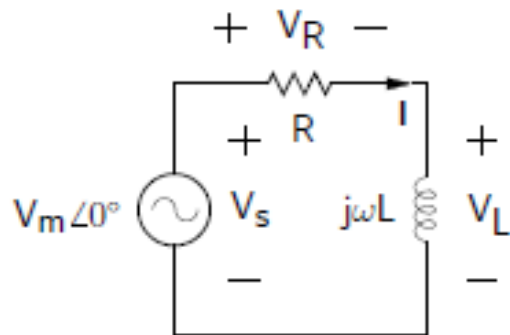


$$I = \frac{V_m \angle 0}{R + j\omega L} \equiv I_m \angle (-\theta),$$

$$\text{where } I_m = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}}, \text{ and } \theta = \tan^{-1}(\omega L / R).$$

$$V_R = I \times R = R I_m \angle (-\theta),$$
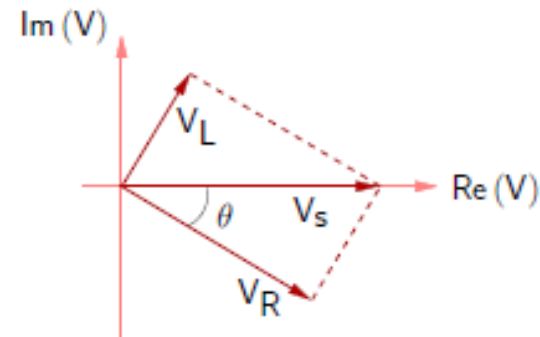
$$V_L = I \times j\omega L = \omega I_m L \angle (-\theta + \pi/2),$$



$$\text{KVL: } V_s = V_R + V_L$$

- If $R \gg j\omega L$, $\theta \rightarrow 0$, $|V_R| \approx |V_s| = V_m$.
- If $R \ll j\omega L$, $\theta \rightarrow \pi/2$, $|V_L| \approx |V_s| = V_m$.