
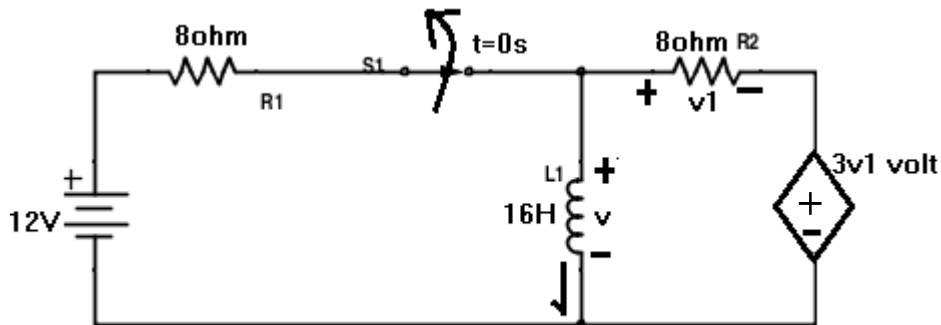


TUTORIAL 2

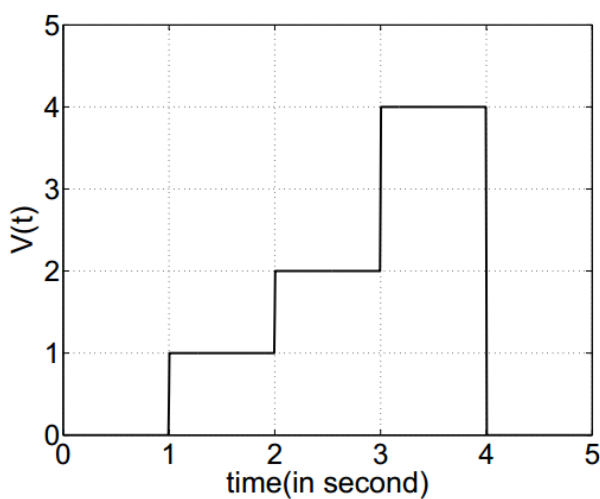
Q1) For the circuit shown in Figure below the switch opens at time $t = 0$ s. Write a differential equation in $i(t)$ for $t \geq 0$ s. Find $i(t)$ and $V(t)$ for all time .




2) The staircase input voltage wave form shown in Fig. (a) is applied across a series LR circuit consisting of $R=1\Omega$ and $L=1$ H. Find the current through the circuit.



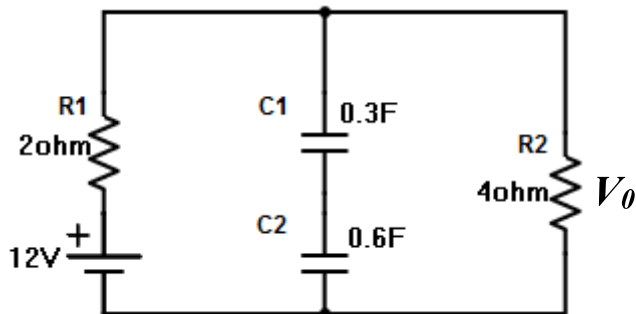
Q3) Given $V_{C1}(0^-) = 6$ and $V_{C2}(0^-) = 24$, Find V_o :



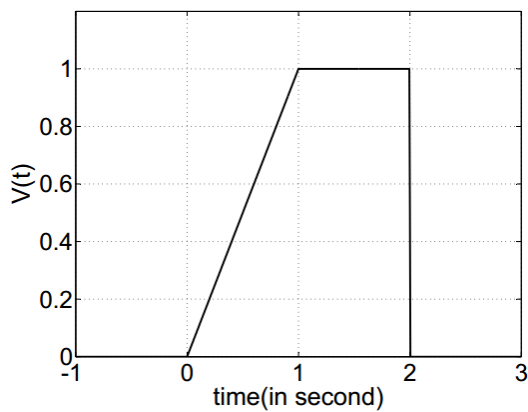4) The input voltage wave form shown in Fig. (a) is applied across a RC circuit shown in Fig. (b). Find the output voltage across the capacitor C. Plot $i_c(t)$, $v_c(t)$.




(a)

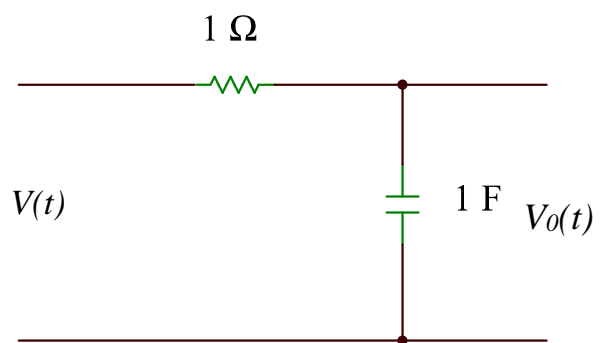


(b)

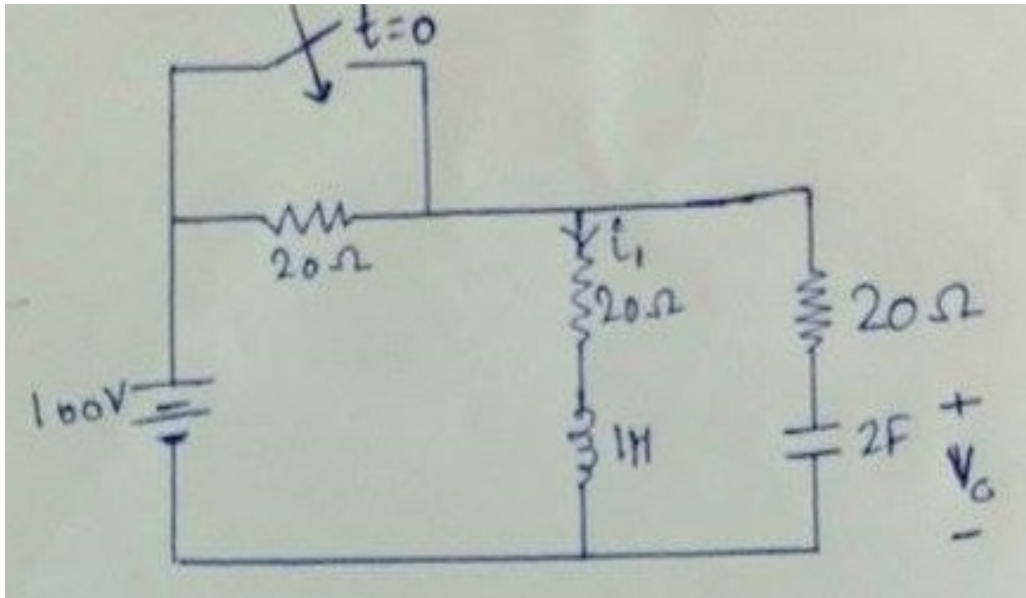
Q5) FIND $\frac{di_1}{dt}(0^+)$, $\frac{dv_c}{dt}(0^+)$, $i_1(0^+)$, $v_c(\infty)$ in the below figure



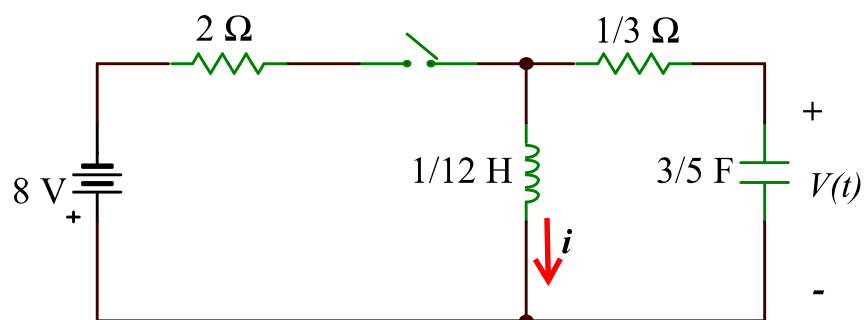6) For the circuit shown in the Fig.6 , the switch opens at time $t = 0$. Find $V(t)$ and $i(t)$ for all time.



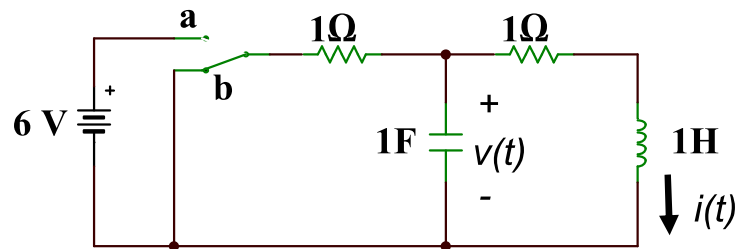7) For the circuit shown in fig. switch was moved from position *a* to position *b* at time $t=0$; Find $i(t)$ and $v(t)$ for $t>0$.



8) For the circuit shown in fig. switch was moved from position *a* to position *b* at time $t=0$; Find $i(t)$ for $t>0$.

